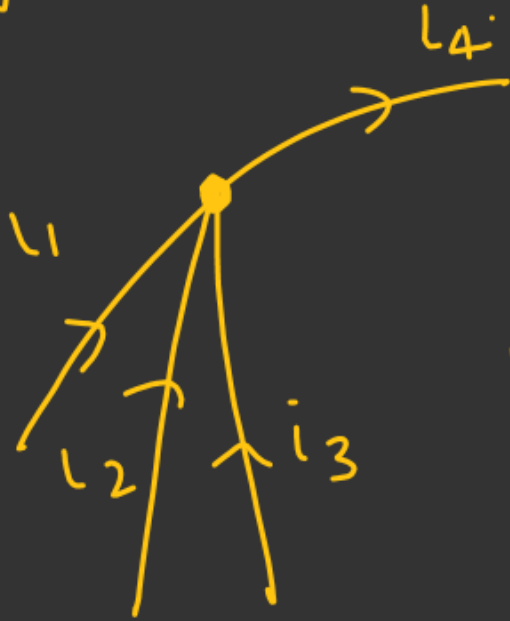


Nodal Analysis

→ Assume any node as reference potential.

→ Mark the potential of other node w.r.t assumed zero potential



$$l_1 + l_2 + l_3 = l_4$$

$$l_1 + l_2 + l_3 - l_4 = 0$$

→ Apply K-C.L at node.


Q.1 A constant voltage $V = 25\text{ V}$ is maintained between points A and B of the circuit as shown in figure. Find the magnitude and direction current flowing through the wire CD if the resistances are equal to $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$ and $R_4 = 4\Omega$.

M-1. Nodal analysis Method
 For Node D.
 $\frac{25-18}{1} = i_{AC}$
 $i_{AC} = 7\text{ Amp.}$
 $i_{CB} = \frac{18-0}{3} = 6\text{ Amp.}$
 $i_{CD} = 1\text{ Amp.}$

$$\left(\frac{x-0}{4}\right) + \left(\frac{x-25}{2}\right) + \left(\frac{x-0}{3}\right) + \left(\frac{x-25}{1}\right) = 0.$$

$$\left[\frac{x}{4} + \frac{x}{2} + \frac{x}{3} + x\right] - \frac{25}{2} - 25 = 0.$$
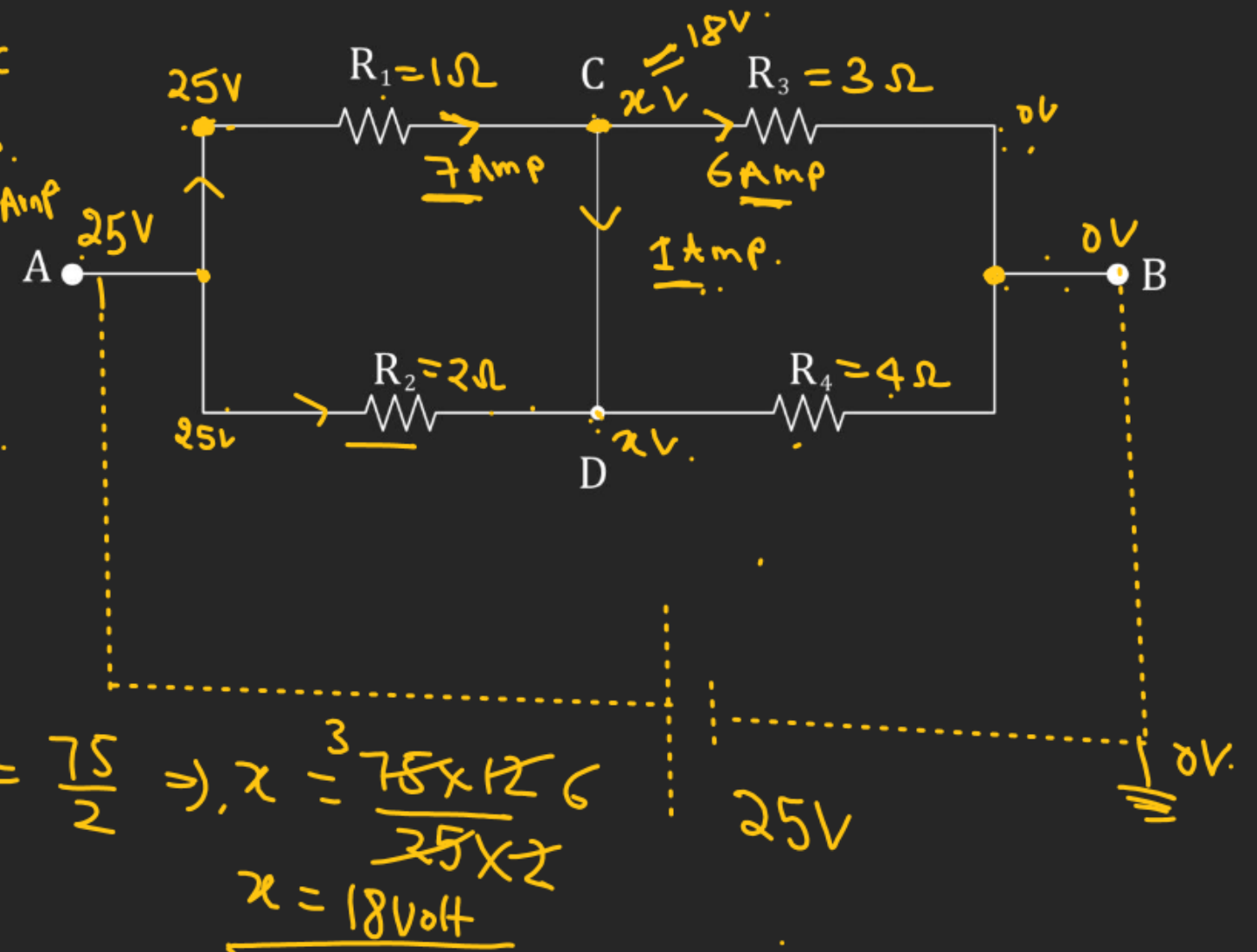
$$\frac{3x+6x+4x+12x}{12} = \left(\frac{75}{2}\right) \Rightarrow \frac{25x}{12} = \frac{75}{2} \Rightarrow x = \frac{75 \times 12}{25 \times 2} = 18\text{ Volt}$$



Find $(R_{eq})_{A-B}$.

Nodal Analysis

$$\frac{x-100}{5} + \frac{x-0}{2} +$$

$$\frac{x-100}{5} + \left(\frac{x-0}{2}\right) + \frac{x-(100-x)}{10} = 0$$

$$\left(\frac{x}{5} + \frac{x}{2} + \frac{x}{5}\right) - 20 - 10 = 0.$$

$$\frac{2x+2x+5x}{10} = 30.$$

$$9x = 300 \Rightarrow x = \frac{300}{9} = \frac{100}{3} \text{ volt}$$



$$V = I R_{eq}$$



A+B

$$i_1 + i_2 = i$$

$$\frac{x-0}{2} + \frac{100-x}{5} = i$$

$$\frac{100}{3 \times 2} + \frac{100}{5} - \frac{100}{5} \times \frac{1}{3} = i$$

$$V = I R_{eq}$$

$$\frac{100}{I} = R_{eq}$$

$$\frac{V_{12} = V_{1'2'}}{(100-x)/2}$$

$$R_{eq} = \left(\frac{100}{I} \right)$$

$$\frac{100}{3 \times 2} + \frac{100}{5} - \frac{100 \times 1}{5 \times 3} = I.$$

$$100 \left[\frac{1}{6} + \frac{1}{5} - \frac{1}{15} \right] = I.$$


$$\left(\frac{100}{I} \right) =$$

$$R_{eq} =$$


$$\frac{1}{\left[\frac{1}{6} + \frac{1}{5} - \frac{1}{15} \right]}$$

$$= \frac{1}{\frac{15+18-6}{90}} = \left(\frac{90}{27} \right) = \left(\frac{10}{3} \right) \Omega.$$

H.W.

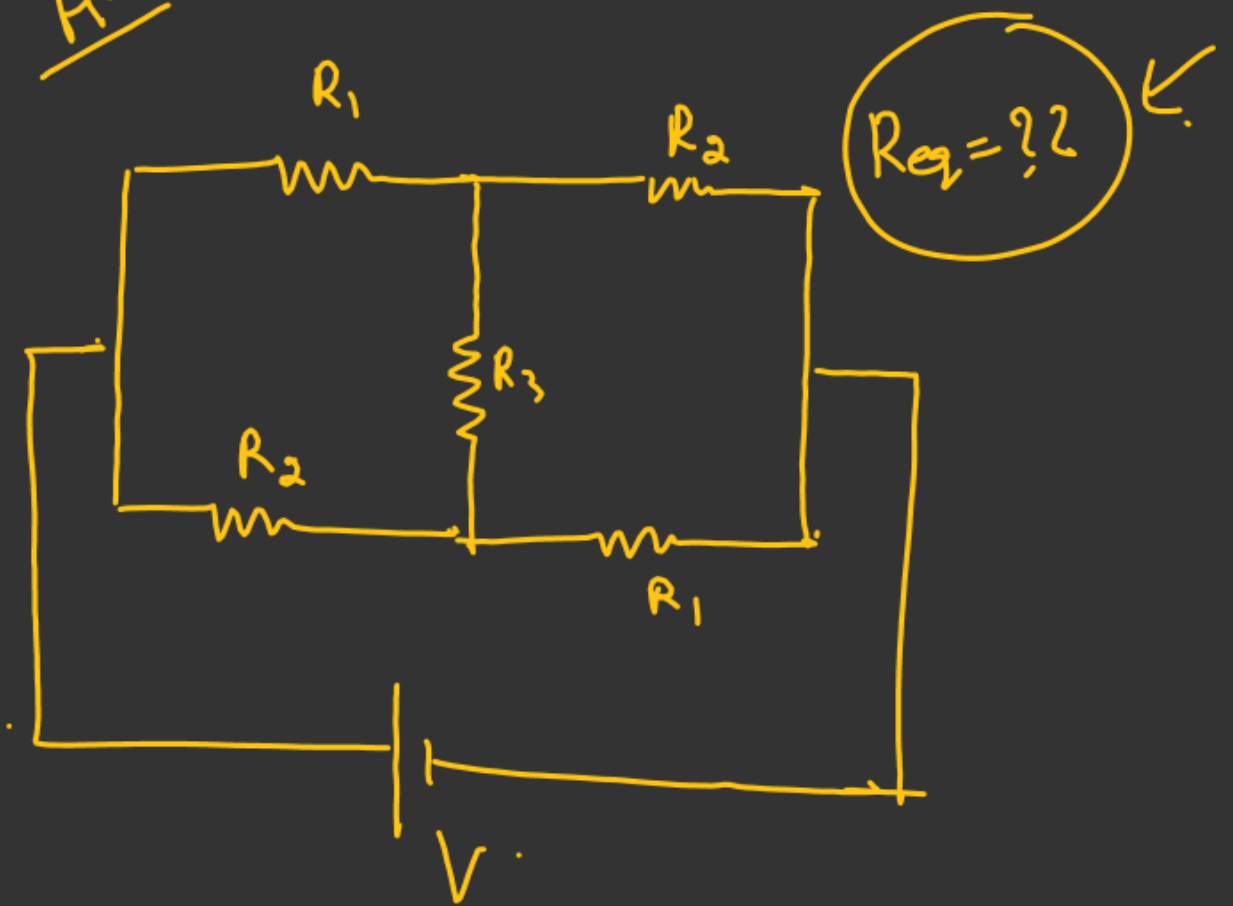

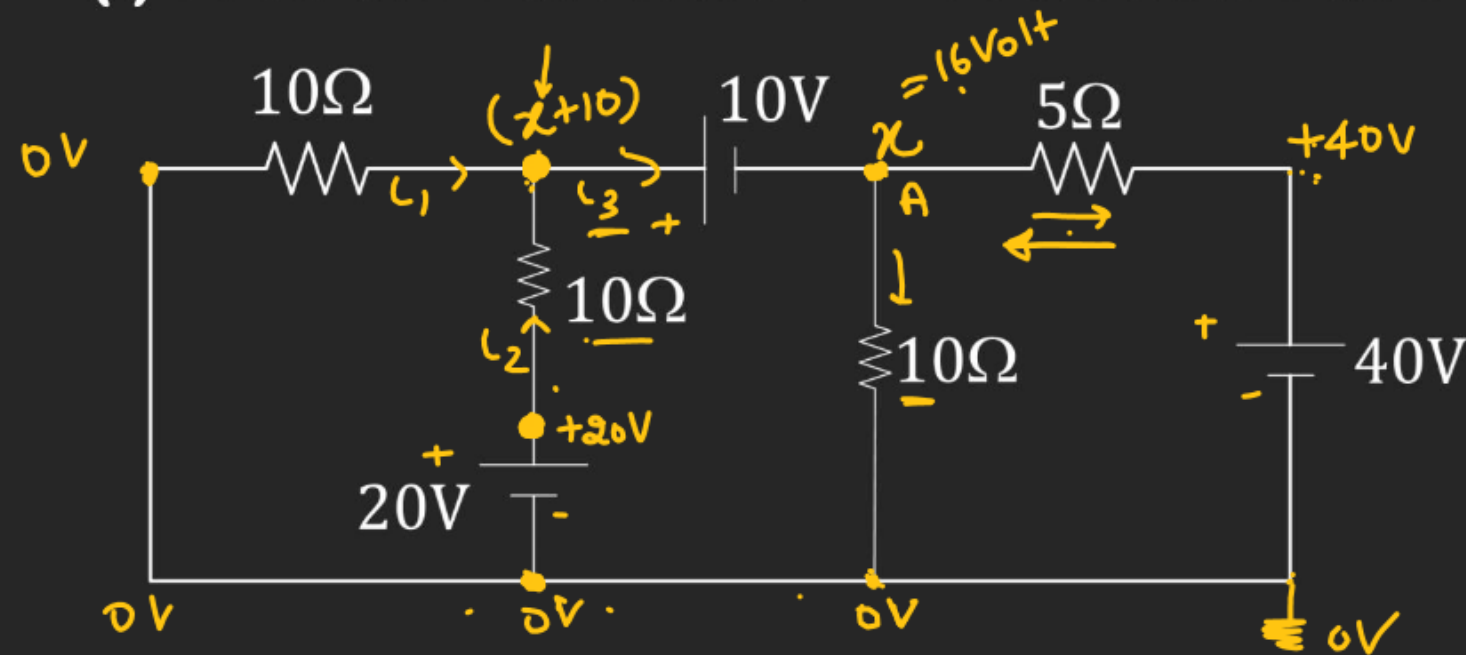Q.2 (i) Find the current in 5Ω resistance in circuit shown in figure



$$(i_3 = i_2 + i_1)$$

$$i_3 = \left[\frac{x+10}{10} + \frac{(x+10)-20}{10} \right]$$

K.C.L at node A

$$\frac{x-40}{5} + \left(\frac{x-0}{10} \right) + \left(\frac{x+10}{10} \right) + \left(\frac{x-10}{10} \right) = 0$$

$$\left[\frac{x}{5} + \frac{x}{10} + \frac{x}{10} + \frac{x}{10} \right] - 8 + 1 - 1 = 0$$

$$\frac{2x+3x}{10} = 8$$

$$5x = 80$$

$$x = 16 \text{ Volt}$$

Current in 5Ω

$$= \frac{40-16}{5}$$

$$= \frac{24}{5} \text{ Amp}$$

$$= \underline{4.8 \text{ Amp}}$$

Q.3 In the circuit shown in figure, find:

(a) The current in the 3Ω resistor = (8Amp) ✓

(b) The unknown emfs E_1 and E_2

(c) The resistance R = ?

K-V.L in loop
ABCDHA :-

$$-2R - E_1 + E_2 = 0$$

$$2R = (E_2 - E_1)$$


$$R = \frac{E_2 - E_1}{2} = \frac{54 - 36}{2} = \frac{18}{2} = \boxed{9\Omega}$$

K-V.L in loop DCHGD

$$E_1 - (3 \times 4) - (3 \times 8) = 0$$

$$E_1 = (12 + 24)$$
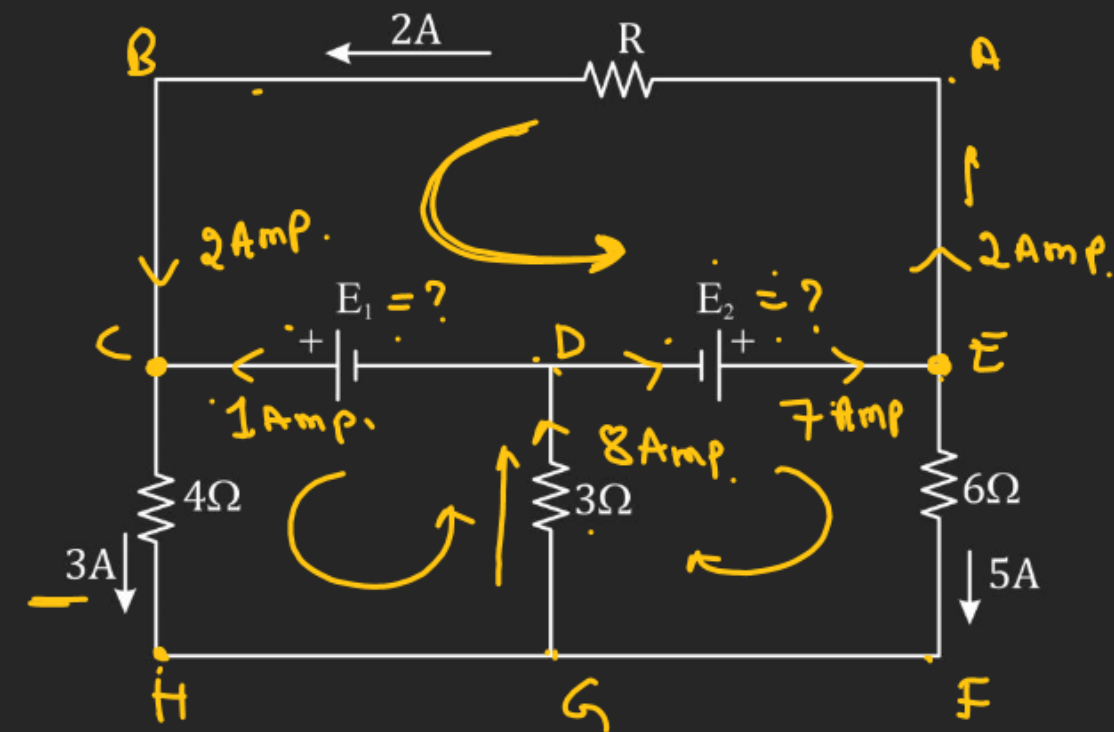
$$E_1 = \underline{36 \text{ Volt}} \checkmark$$



K-V.L in loop DEFGD

$$E_2 - (6 \times 5) - (8 \times 3) = 0$$

$$E_2 = 30 + 24 = \underline{54 \text{ Volt}}$$

Q.4 In the circuit shown in figure find potential difference between the point A and B and the currents through each branch.


M-1:-

$$|V_A - V_B| = ??$$

$$\frac{x-1}{1} + \frac{x-2}{1} + \frac{x-3}{1} = 0$$

$$3x - 6 = 0$$

$$(x = 2 \text{ volt})$$

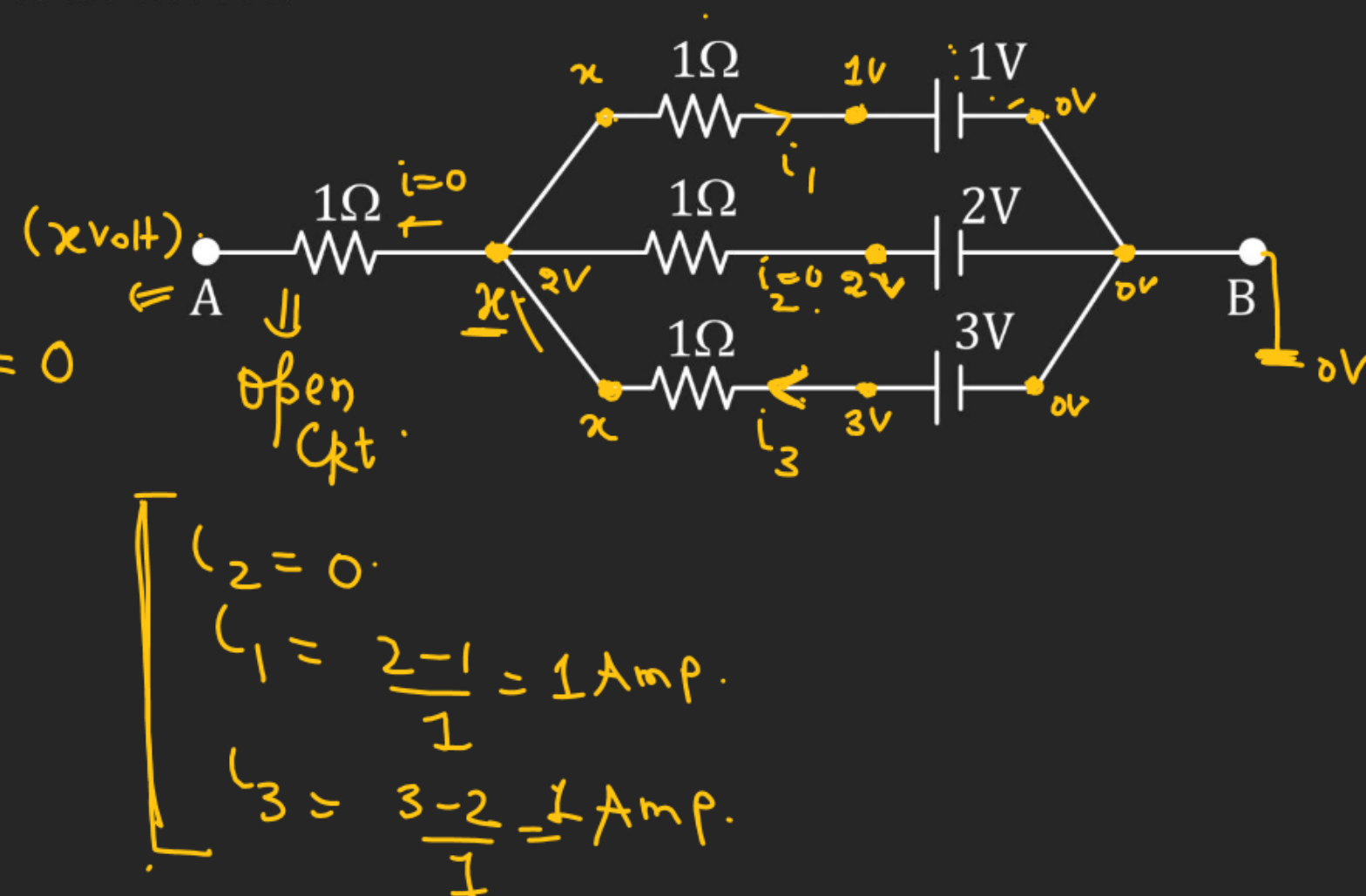

H.W.

CURRENT ELECTRICITY

Q.5 Find out the value of current through 2Ω resistance for the given circuit.


(2005)

(A) Zero

(B) 2 A

(C) 5 A

(D) 4 A.

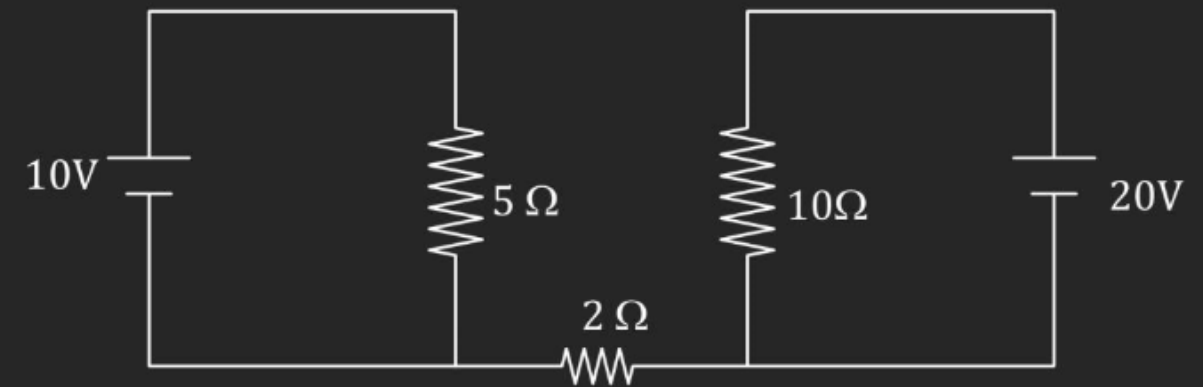

Q.6 In the circuit shown in figure the current through


(1998)

(A) the 3Ω resistor is 0.50 A .

(B) the 3Ω resistor is 0.25 A .

(C) the 4Ω resistor is 0.50 A .

(D) the 4Ω resistor is 0.25 A .

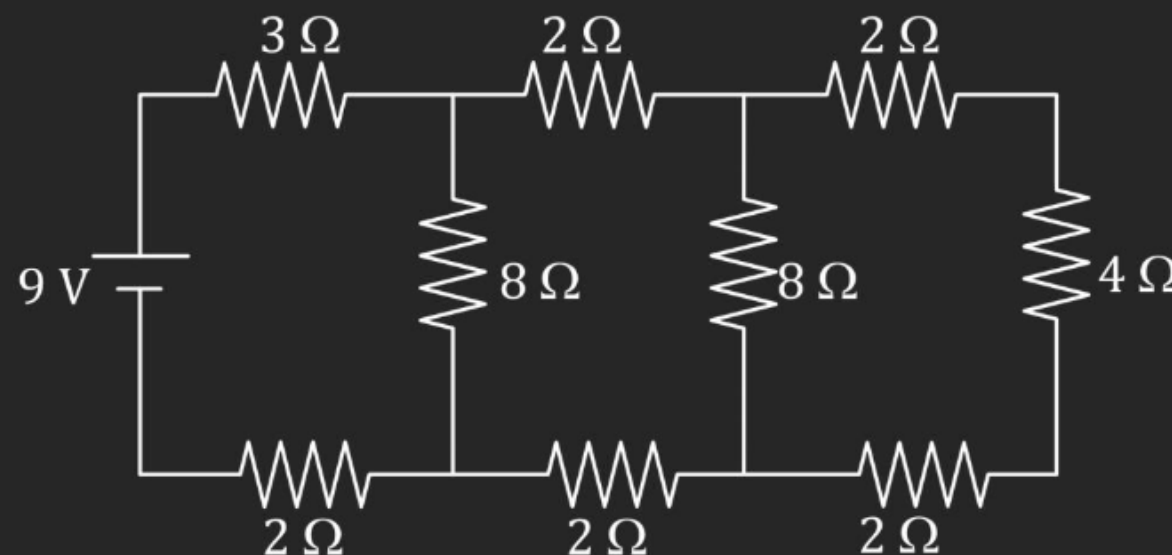

Q.7 For the circuit shown in the figure

(2009)

(A) the current I through the battery is 7.5 mA

(B) the potential difference across R_L is 18 V

(C) ratio of powers dissipated in R_1 and R_2 is 3


(D) if R_1 and R_2 are interchanged, magnitude of the power dissipated in R_L will decrease by a factor of 9 .



Q.8 For the resistance network shown in the figure, choose the correct option(s).


(2012)

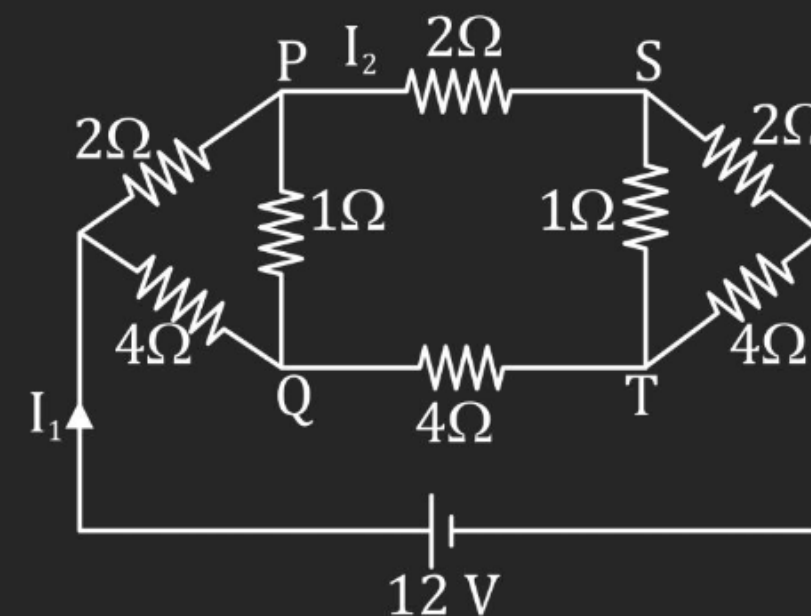- (A) The current through PQ is zero.
- (B) $I_1 = 3 \text{ A}$.
- (C) The potential at S is less than that at Q.
- (D) $I_2 = 2 \text{ A}$



Q.10 Two ideal batteries of emf V_1 and V_2 and three resistances R_1 , R_2 and R_3 are connected as shown in the figure. The current in resistance R_2 would be zero if **(2014)**

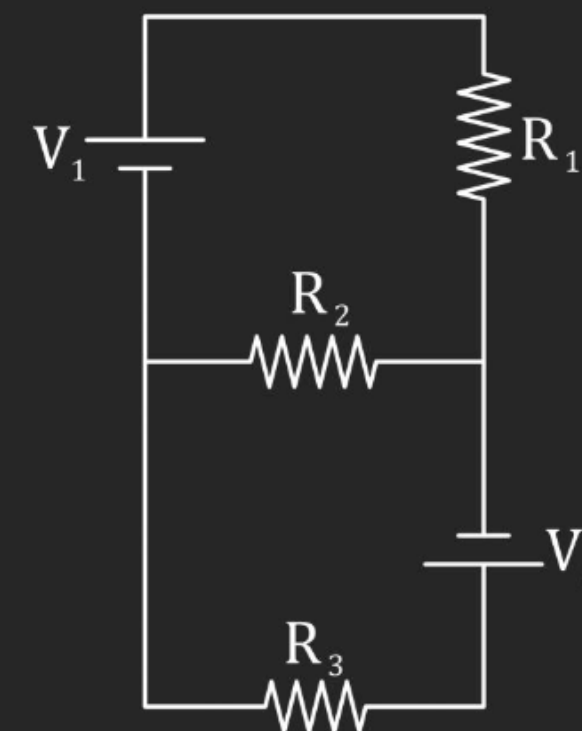
- (A) $V_1 = V_2$ and $R_1 = R_2 = R_3$
- (B) $V_1 = V_2$ and $R_1 = 2R_2 = R_3$
- (C) $V_1 = 2V_2$ and $2R_1 = 2R_2 = R_3$
- (D) $2V_1 = V_2$ and $2R_1 = R_2 = R_3$



Q.11 The figure shows a circuit having eight resistances of 1Ω each, labelled R_1 to R_8 , and two ideal batteries with voltages $\varepsilon_1 = 12\text{ V}$ and $\varepsilon_2 = 6\text{ V}$. Which of the following statement(s) is (are) correct?

(2022)

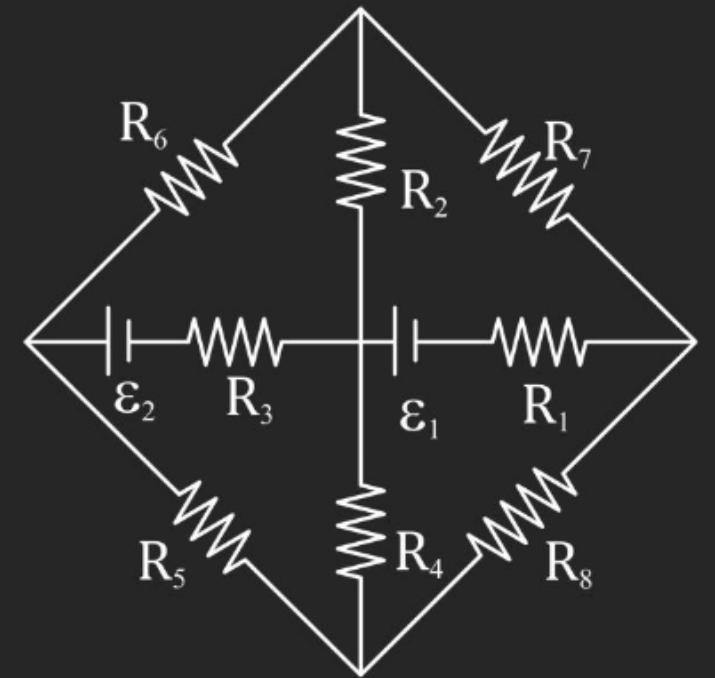- (A) The magnitude of current flowing through R_1 is 7.2 A .
- (B) The magnitude of current flowing through R_2 is 1.2 A .
- (C) The magnitude of current flowing through R_3 is 4.8 A .
- (D) The magnitude of current flowing through R_5 is 2.4 A .



Q.12 An electrical circuit is shown in the figure. Calculate the potential difference across the resistor of 400Ω , as will be measured by the voltmeter V of resistance 400Ω , either by applying Kirchhoff's rules or otherwise. **(1996)**

