
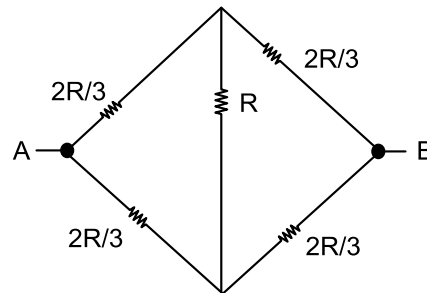


DPP-5

SOLUTION


Link to View Video Solution: [Click Here](#)

1. Requivalebt b/w A and B

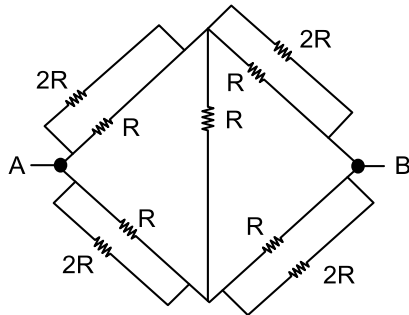

It is balanced wheat stone bridge

So current is  $R = 0$

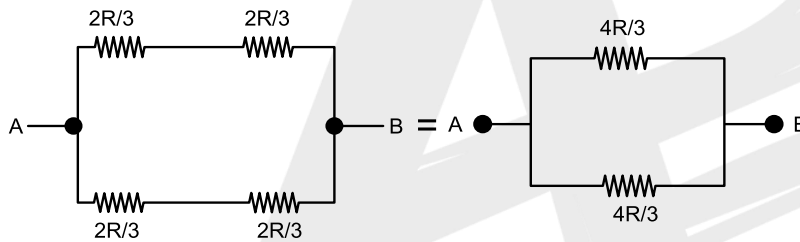

$$R_{AB} = \frac{4R}{6} = \frac{2R}{3}$$

2. In circuit

$$V_B = V_D$$

that's mean


$$(15 + 3) \left( \frac{8x}{8 + x} + 3 \right) = (21 \times 6)$$

$$\frac{18}{3} \left( \frac{8x + 24 + 3x}{8 + x} \right) = 21 \times 6 \Rightarrow 11x + 24 = 56 + 7x$$


$$4x = 56 - 24 \Rightarrow x = \frac{32}{4}$$

$$x = 8\Omega$$

3. Each resistance =  $r_0$

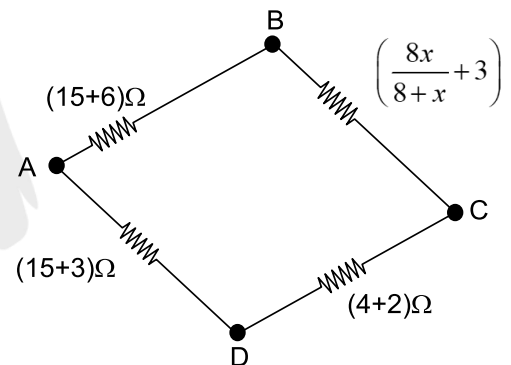

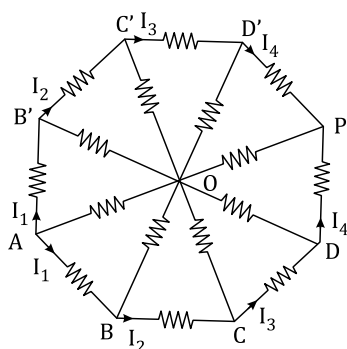Link to View Video Solution: [Click Here](#)




Potential of  $B = B'$

$$C = C'$$



$$D = D'$$

This circuit symmetry about AOP

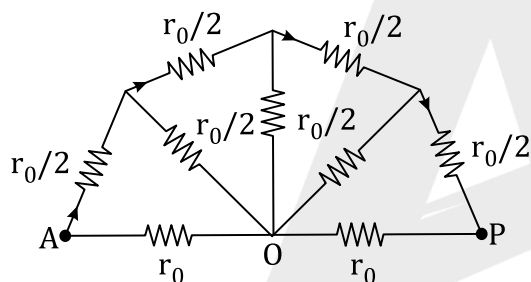

After solving  $R_{AO} = \frac{69r_0}{149}$


4. Circuit is symmetrical about line AB

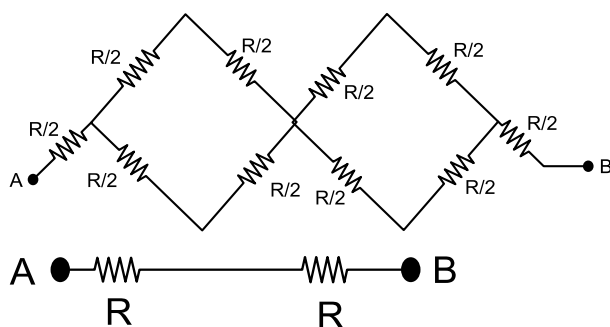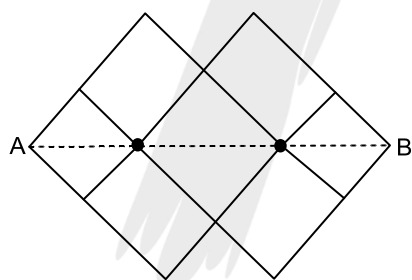

$$R_{AB} = 2R$$

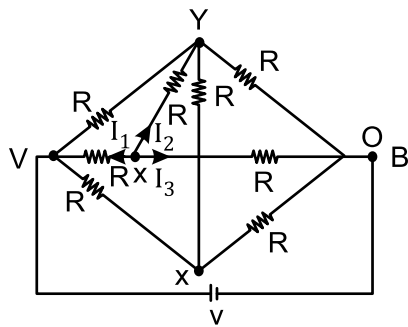5. Method of solving this question. one of the best approach is node analysis with battery connection

Link to View Video Solution: [Click Here](#)



step-: Attach a V-Volt battery and assign potential at each node

By symmetry

$$V - Y = Y - 0$$

$$Y = V/2$$

Using KCL is at point p


$$\frac{X - V}{R} + \frac{X - Y}{R} + \frac{X - 0}{R} = 0$$

$$3X = V + Y$$

$$x = \frac{V}{2} \quad [Y = V/2]$$

$$\Rightarrow V_x = V_y$$

final circuit

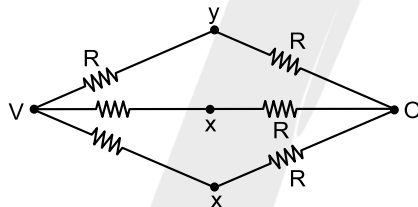

$$R_{eq} = \frac{2R}{3}$$

6. Equivalent resistance can be obtained by.


$$R_{AB} = \frac{100}{\frac{2x}{R} + \frac{50}{R}}$$

$$\frac{x}{R} + \frac{x-50}{R} + \frac{x(100-x)}{R} = 0$$



$$x = \frac{75}{R}$$

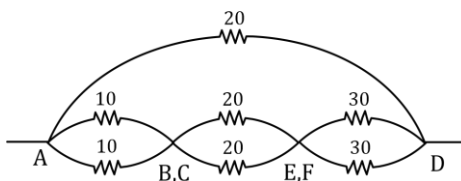7. Points B and C, and E and F are at the same potential, so the circuit can be redrawn as shown in figure. Thus, the equivalent resistance is  $1\Omega$ . There exists parallel axis of symmetry. The points across the parallel axis of symmetry can be treated as equipotential points.

Link to View Video Solution: [Click Here](#)



8.

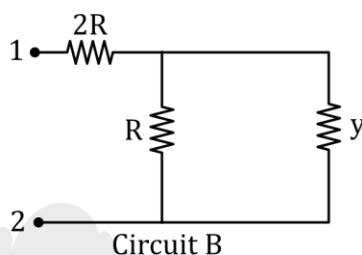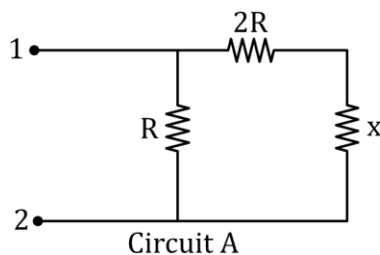

$$x = \frac{R(2R+x)}{3R+x}$$

$$\Rightarrow 3Rx + x^2 = 2R^2 + Rx$$

$$\Rightarrow x^2 + 2Rx - 2R^2 = 0$$


$$\Rightarrow x = \frac{-2R \pm \sqrt{4R^2 + 8R^2}}{2}$$

$$\Rightarrow x = \frac{-2R + 2\sqrt{3}R}{2}$$


$$\Rightarrow x = (\sqrt{3} - 1)R$$

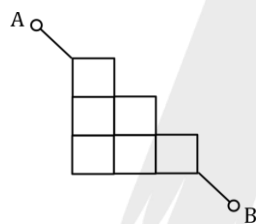9. First fold the circuit about diagonal AB.s


Find  $R_{AB}$  given resistance of each branch is R.




Resistance is now  $\frac{R}{2}$ .

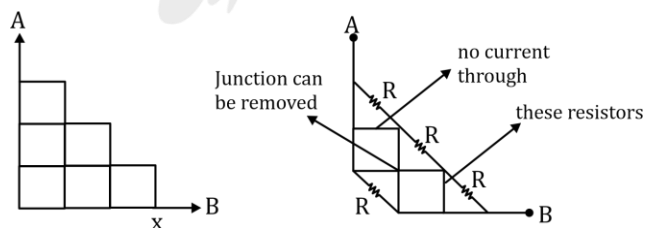

\*\*For folding the potentials of points must be same.

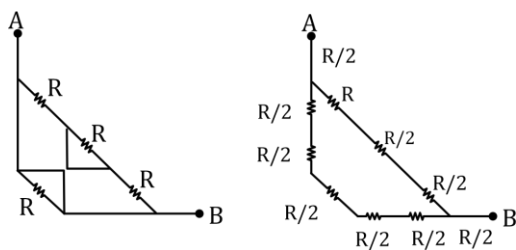Link to View Video Solution:  [Click Here](#)



Now equivalent is  $\frac{9R}{4}$