

DPP - 10

SOLUTION

Link to View Video Solution: [Click Here](#)

1. Current in circuit $i = \frac{4}{R+20}$

$$V_{AB} = i R_{AB} = \frac{4}{(R+20)} \times 20 = \frac{80}{(R+20)}$$

$$V_{AN} = \left(\frac{V_{AB}}{300} \right) \times 60$$


→ Potential gradient

$$= \frac{(80)}{(R+20) \times 5} = \frac{16}{(R+20)}$$

$$V_{AN} = 20 \times 10^{-3} \text{ V} = 2 \times 10^{-2}$$

$$\frac{16}{R+20} = 2 \times 10^{-2} \Rightarrow \frac{8}{10^{-2}} = R+20$$
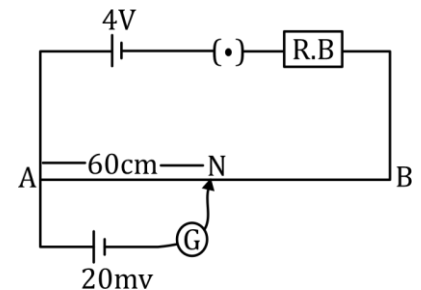
$$800 = R+20 \Rightarrow R = 780 \Omega$$




2. $E_1 \propto 380$

$$E_2 \propto 760$$

$$\frac{E_1}{E_2} = \frac{1}{2} = \frac{a}{b}$$

$$a = 1$$

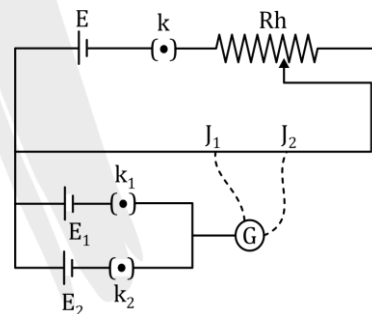


3. When key is plugged b/w 2 & 1

$$V_1 = iR_1 = xl_1$$

when key is plugged b/w 3 & 1

$$V_2 = i(R_1 + R_2) = xl_2$$

$$\frac{R_1}{R_1 + R_2} = \frac{l_1}{l_2}$$

Link to View Video Solution:  [Click Here](#)

$$\frac{R_1}{R_2} = \frac{l_1}{l_2 - 1}$$

4. $R_{\text{wire}} = 40\Omega$


$$l = 10 \text{ m}$$

$$I = \frac{2}{760+40} = \frac{2}{800} = \frac{1}{400}$$

$$I = \frac{1}{400} \text{ Amp.}$$

$$V_{AB} = I \cdot R_L = \frac{1}{400} \times 40 = \frac{1}{10} \text{ volt}$$
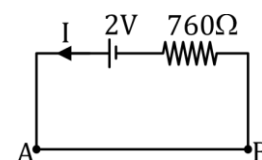
$$X = \frac{V_{AB}}{l} = \frac{1}{10 \times 10} = 10^{-2} \text{ V/m}$$



5. $l = 4\text{m}$

$$R_l = 8\Omega$$

$$I = \frac{2}{8+R}$$


$$V_{AB} = \left(\frac{2}{8+R} \right) \cdot 8 = \frac{16}{8+R}$$

$$V_{AB} = \frac{16}{8+R}$$

$$X = \frac{V_{AB}}{l} = \frac{16}{(8+R)4} = \frac{1 \times 10^{-3}}{10^{-2}} \text{ V/m}$$

$$\frac{4}{8+R} = 0.1 \Rightarrow 4 = 0.8 + 0.1R$$

$$0.1R = 3.2 \Rightarrow R = 32\Omega$$

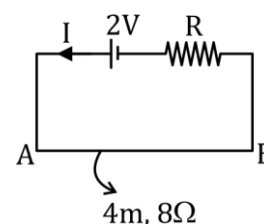


6. $E = \left(\frac{V_{AB}}{L} \right) l$

$$I = \frac{E_0}{r+r_1} \Rightarrow V_{AB} = \left(\frac{E_0}{r+r_1} \right) \times r$$

Link to View Video Solution: [Click Here](#)
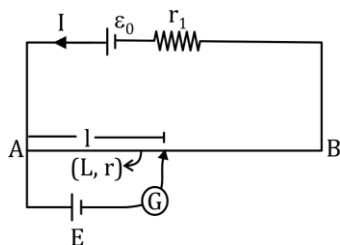
$$x = \frac{V_{AB}}{L} = \frac{E_0 r}{(r + r_1)L}$$



$$E = xl = \frac{E_0 r \cdot l}{(r + r_1)L} \Rightarrow \left[E = \frac{E_0 r l}{(r + r_1)L} \right]$$

7. $l = 100 \text{ cm}$

$$E_1 + E_2 = x \cdot 50 \quad \text{--- (i)}$$

$x \rightarrow$ Potential gradient


when connect opposite to each other

$$E_1 - E_2 = x \cdot 10 \quad \text{--- (ii)}$$

$$\frac{E_1 + E_2}{E_1 - E_2} = 5$$

$$E_1 + E_2 = 5E_1 - 5E_2$$
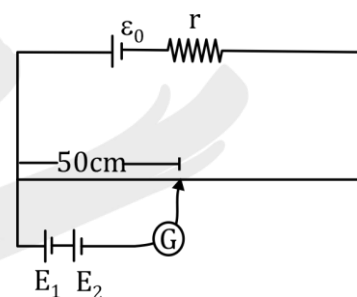
$$4E_1 = 6E_2 \Rightarrow \frac{E_1}{E_2} = \frac{3}{2}$$




8. Initial Condition

$$\varepsilon = x \cdot 55 \quad \text{--- (i)}$$

$x \rightarrow$ Potential gradient.


Final case.

$$i = \frac{\varepsilon}{10 + r}$$

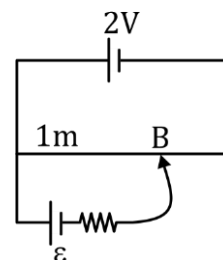

Link to View Video Solution: [Click Here](#)

$$V_{PQ} = \varepsilon - ir$$

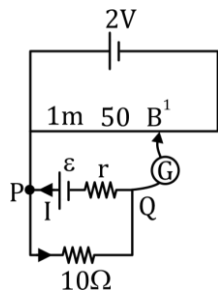

$$= \varepsilon - \frac{\varepsilon}{(10 + r)} \cdot r$$

$$= \varepsilon \left(1 - \frac{r}{10 + r} \right) = \frac{10\varepsilon}{10 + r}$$

$$V_{PQ} = x \cdot 50$$

$$\frac{10\varepsilon}{10 + r} = 50x \quad \text{--- (ii)}$$

$$\frac{(i)}{(ii)} \Rightarrow \frac{\varepsilon}{\frac{10\varepsilon}{10 + r}} = \frac{11}{10} \Rightarrow \frac{10 + r}{10} = \frac{11}{10}$$

$$100 + 10r = 110$$

$$10r = 10$$

$$r = 10\Omega$$

9. $I = \frac{12}{8 + R_{\text{wire}}} \quad R_{\text{wire}} = 4 \times 4 = 16\Omega$


$$I = \frac{12}{8 + 16} = \frac{12}{24} = \frac{1}{2} \text{ Amp.}$$


Using KVL

$$4 - 2 - 2i - 6i = 0$$

$$8i = 2 \Rightarrow i = \frac{1}{4}$$

$$V_p - 4 + 6 \times \frac{1}{4} = V_Q$$

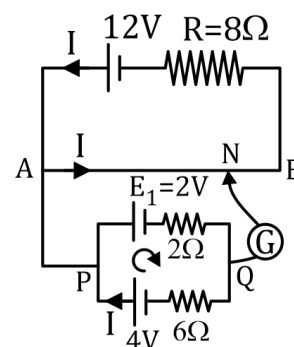


Link to View Video Solution:  [Click Here](#)

$$V_P - V_Q = 4 - \frac{3}{2} = \frac{5}{2}$$

$$\frac{5}{2} = 2 \times L_{AN}$$

$$L_{AN} = \frac{5}{4} = 1.25 \Rightarrow 125\text{cm.}$$

10.

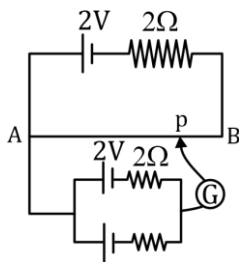

A & P have same potential.

Ans. 0

11. ϵ must be greater than ϵ'

→ Either the +ive terminal of C & D or -ive terminal of both C & D must be joined to A

→ b cz this device based on null deflection.

12. $\pi > R_0$

13. $E_2 = xI$

$$x = \frac{V_1}{I_{\text{wire}}}$$


→ If I_2 shifted towards right current in primary circuit decreases Potential across wire decrease
So Potential gradient also decreases

↓ due to this J_1 shifter right & l increase.

→ If E_1 increase

Potential gradient also increase l decrease. (C)

(A, B, C)

Link to View Video Solution:  [Click Here](#)

14. If E_1 is increased

Potential gradient across wire also increase, l decrease.

→ R shift towards Left

(a) → p.

(b) If resistance of rheostatic is increased, Potential gradient across wire also decrease R shift towards right.

(b) → q

& similar $c \rightarrow q \Rightarrow d \rightarrow r$