

metry

the direction  
flow.

axis Symmetry

flow and ckt  
age.are Symmetrically  
at same potentialare at same  
can overlap.Perpendicular  
axis Symmetry

→ It is perpendicular  
to the direction  
of current flow

→ In perpendicular axis Symmetry  
Current is not the mirror image

→ Points which lie on the perpendicular  
axis Symmetry are at same  
potential

→ In perpendicular axis Symmetry, Symmetrically located  
resistances have same current but in opposite

Path Symm

→ Resistances  
are Symmet  
located  
battery  
Same cur




# CURRENT ELECTRICITY

Perpendicular axis of Symmetry

Parallel axis of Symmetry

Points (b) and (d) are at same potential

$V_b = V_d$   
Folding of ckt about AB

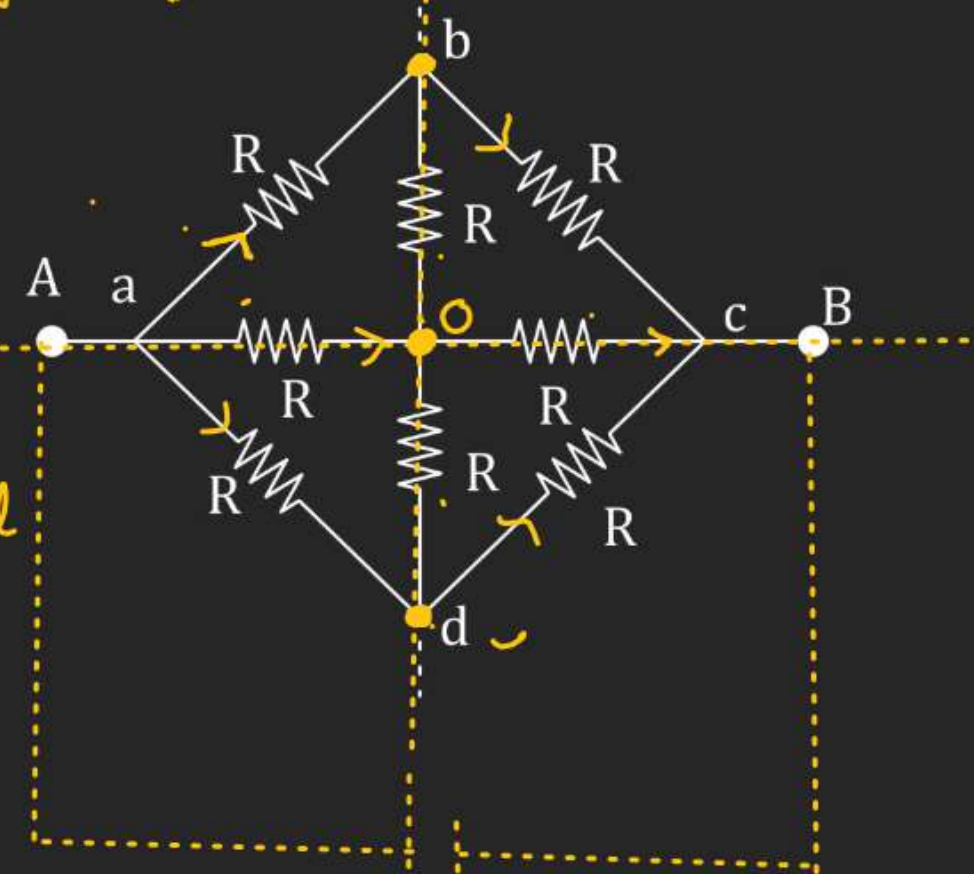



#.  $(R_{eq})_{A-B}$

M-1:- Balance wheat stone bridge.

M-2:- By Symmetry

By perpendicular axis of Symmetry:

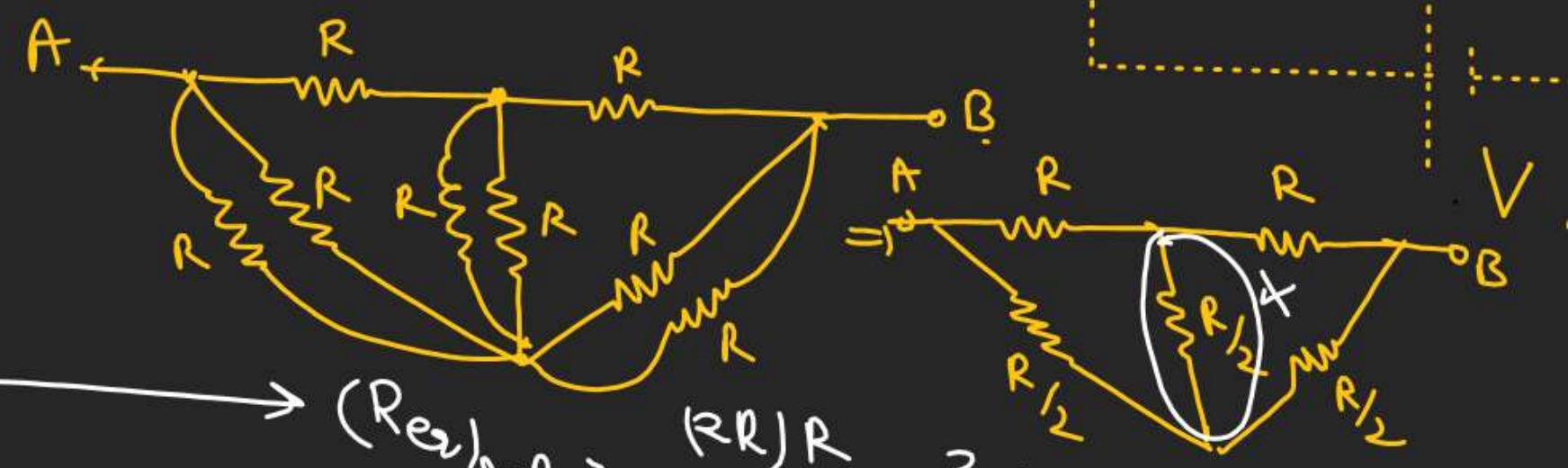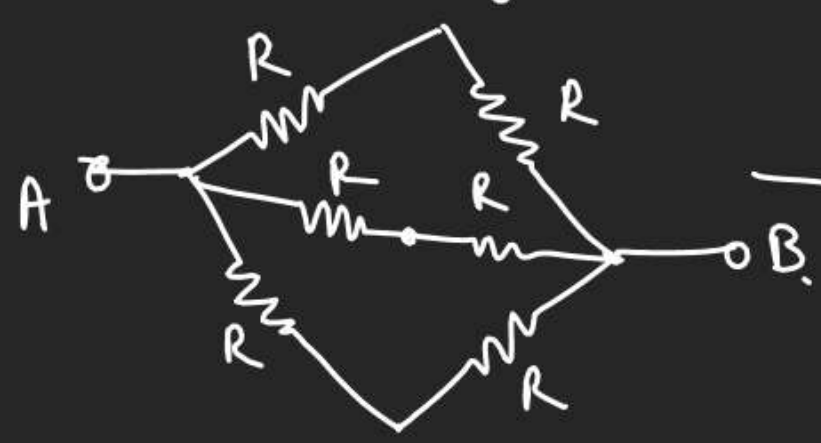Points b, o & d are at same potential  
 $V_b = V_o = V_d$



$$(R_{eq})_{A-B} = \frac{(R \parallel R) R}{2R + R} = \frac{2}{3} R$$



# CURRENT ELECTRICITY

## Equivalent resistance by symmetry

$$(R_{eq})_{A-B} = ??$$

By parallel axis of Symmetry  
 $(V_1 = V_1'), (V_2 = V_2')$

By perpendicular axis of Symmetry.





$$I_{10} = I_{02}$$



Equal and opposite


$$I_{1'0} = I_{02'}$$

Parallel axis of Symmetry.

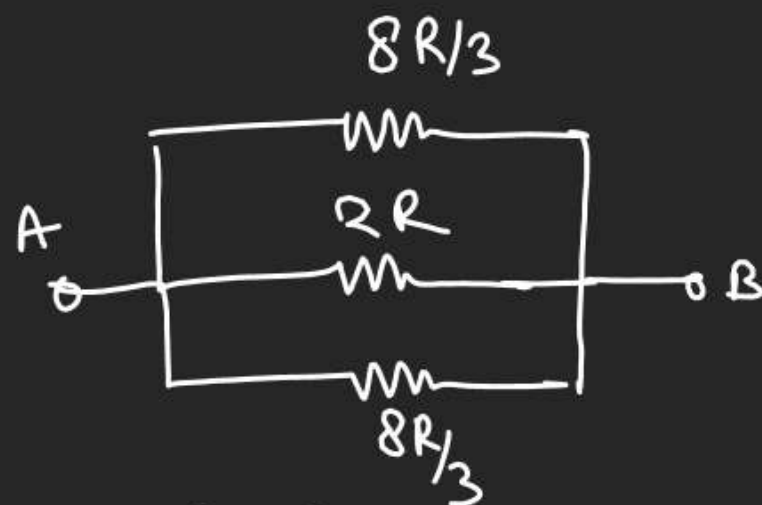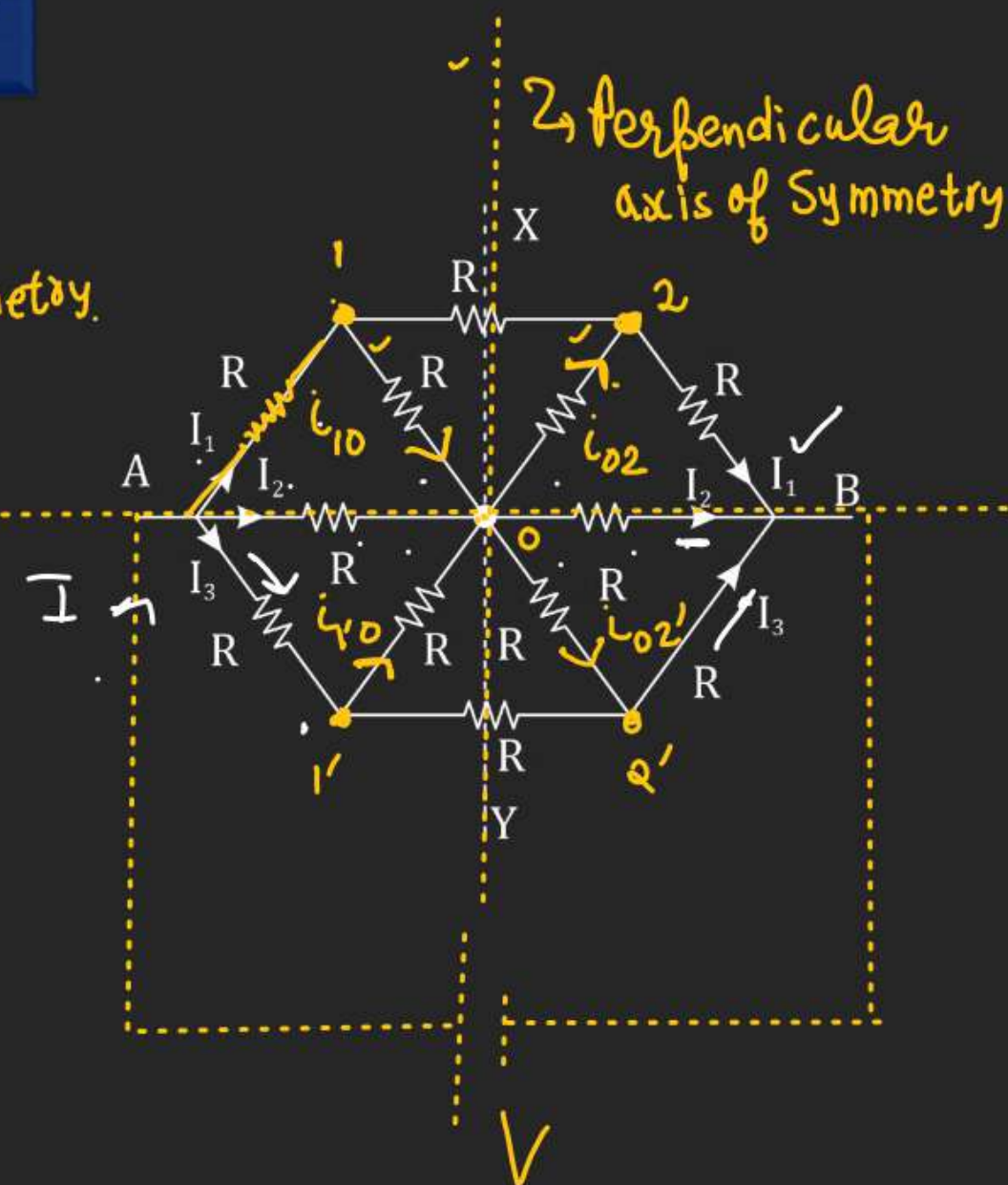

$$R_{eq} = \frac{\frac{4R}{3} \times 2R}{\frac{4R}{3} + 2R} = \frac{8R/3}{10R/3}$$
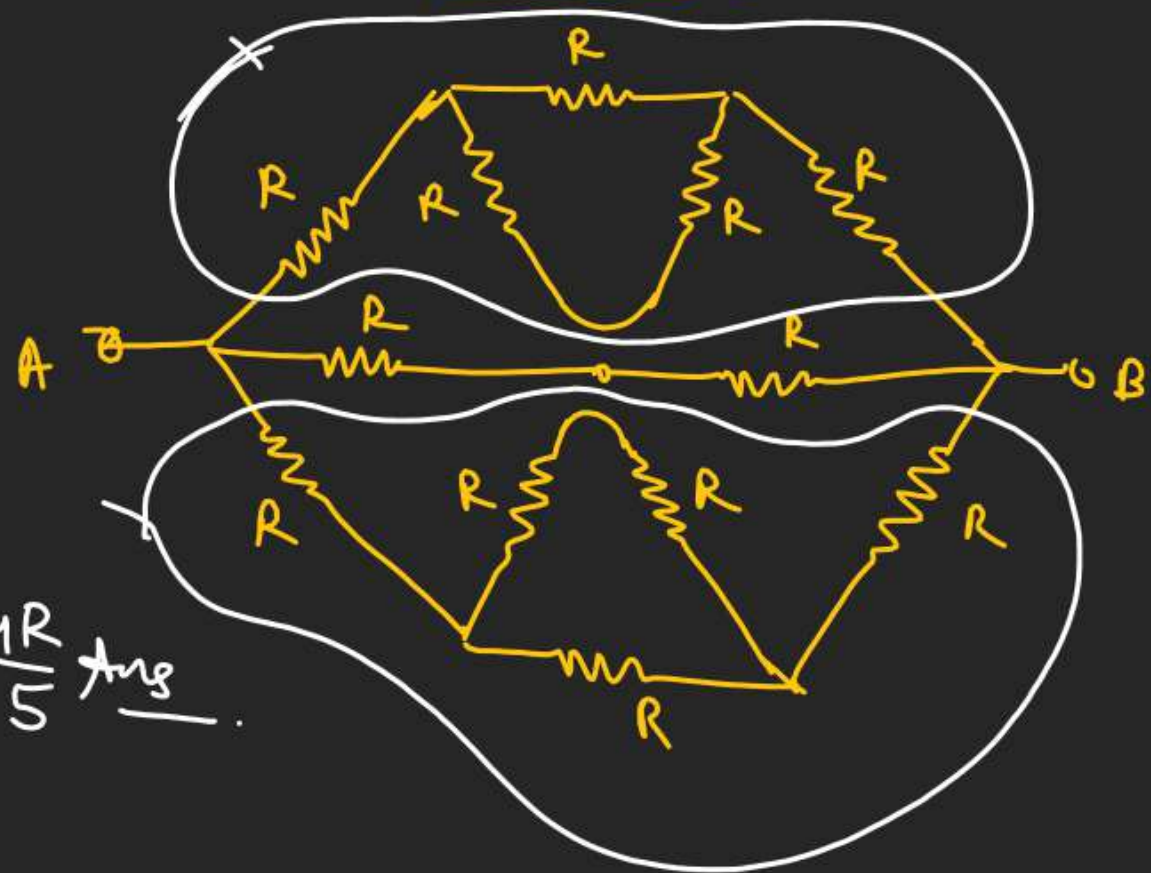
$$R_{eq} = \frac{8R}{10} = \frac{4R}{5} \text{ Ans}$$






# CURRENT ELECTRICITY

## Equivalent resistance by symmetry

Q.4:  $(R_{eq})_{A-B} = ??$


Parallel axis Symmetry

$$V_3 = V_5$$

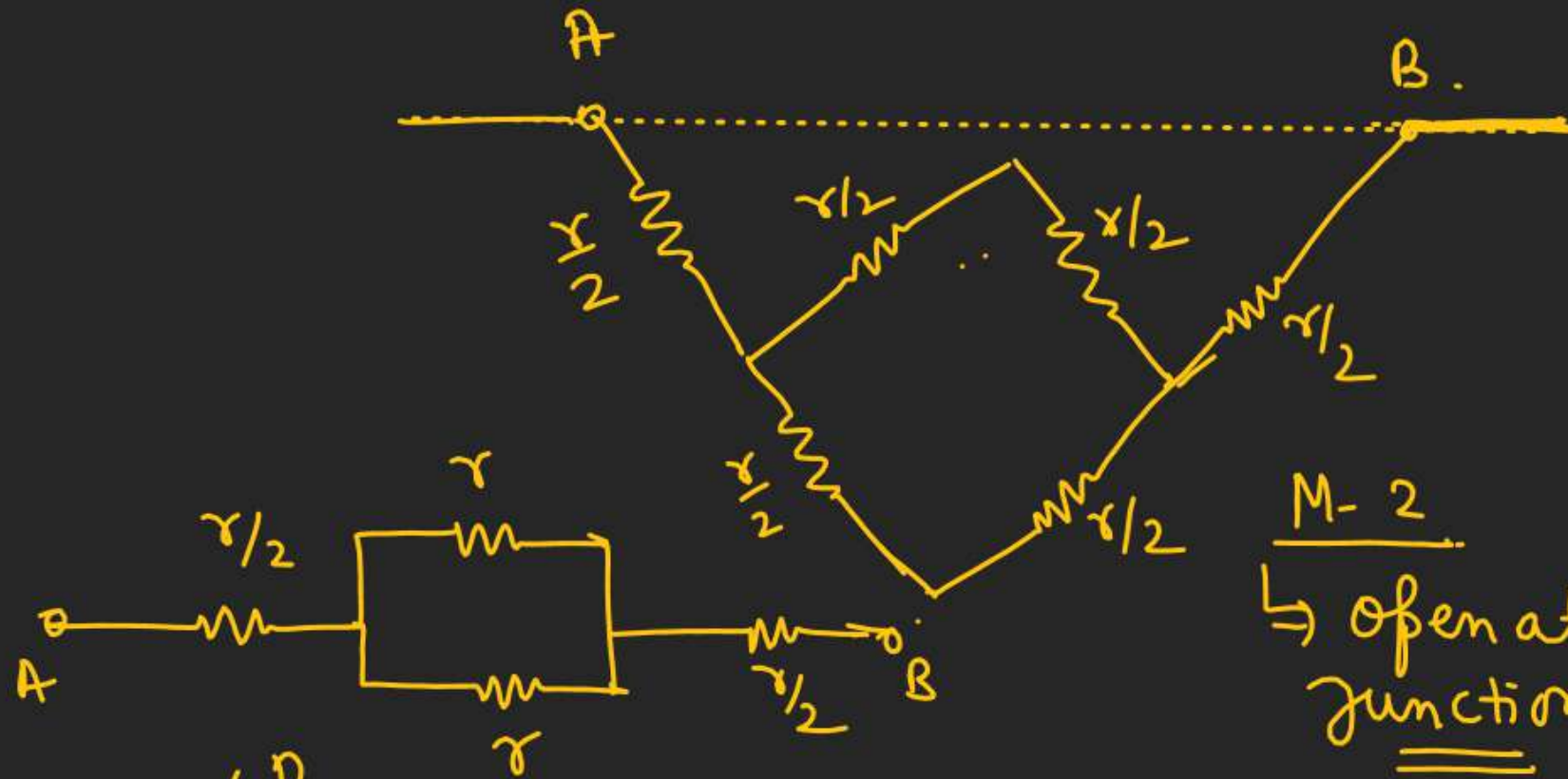

$$(R_{eq})_{A-B} = \left[ \frac{3r}{2} \right] A.$$

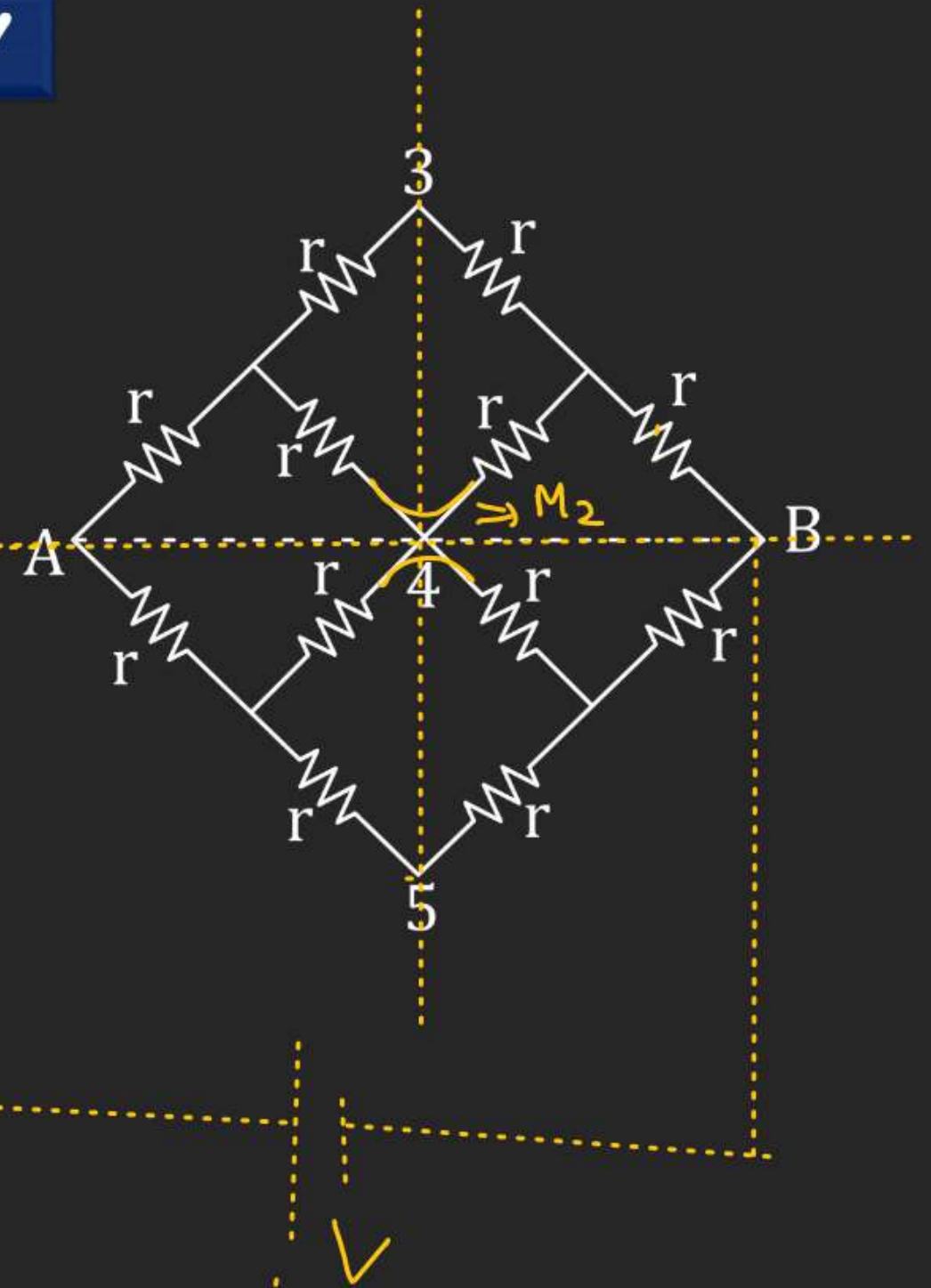M-2  
 $\Rightarrow$  Open at junction  
✓




# CURRENT ELECTRICITY

## Equivalent resistance by symmetry



Perpendicular axis of Symmetry.

$$V_B = V_F = V_H = V_D$$

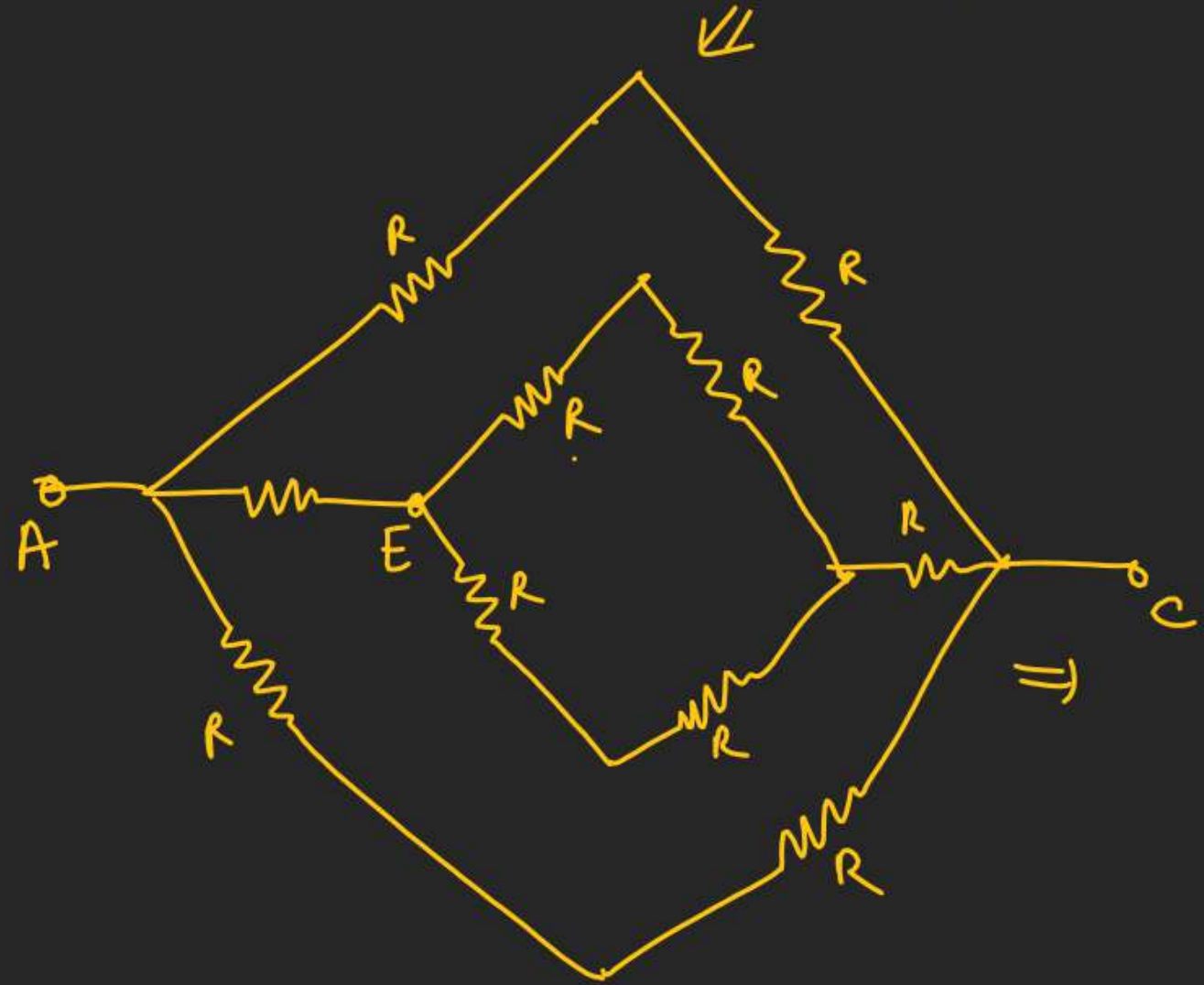

Parallel axis Symmetry
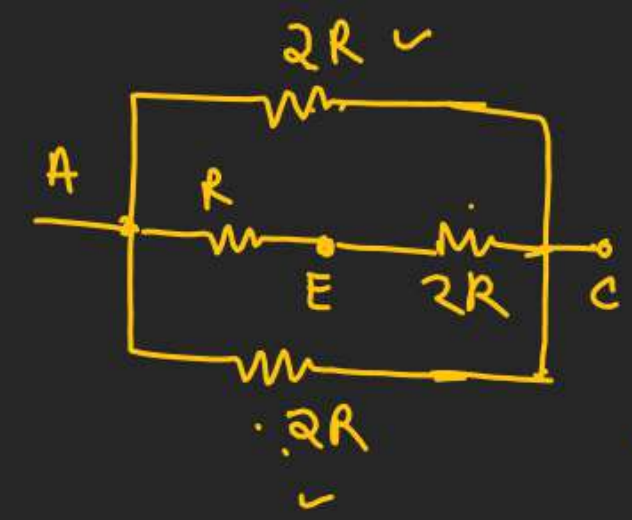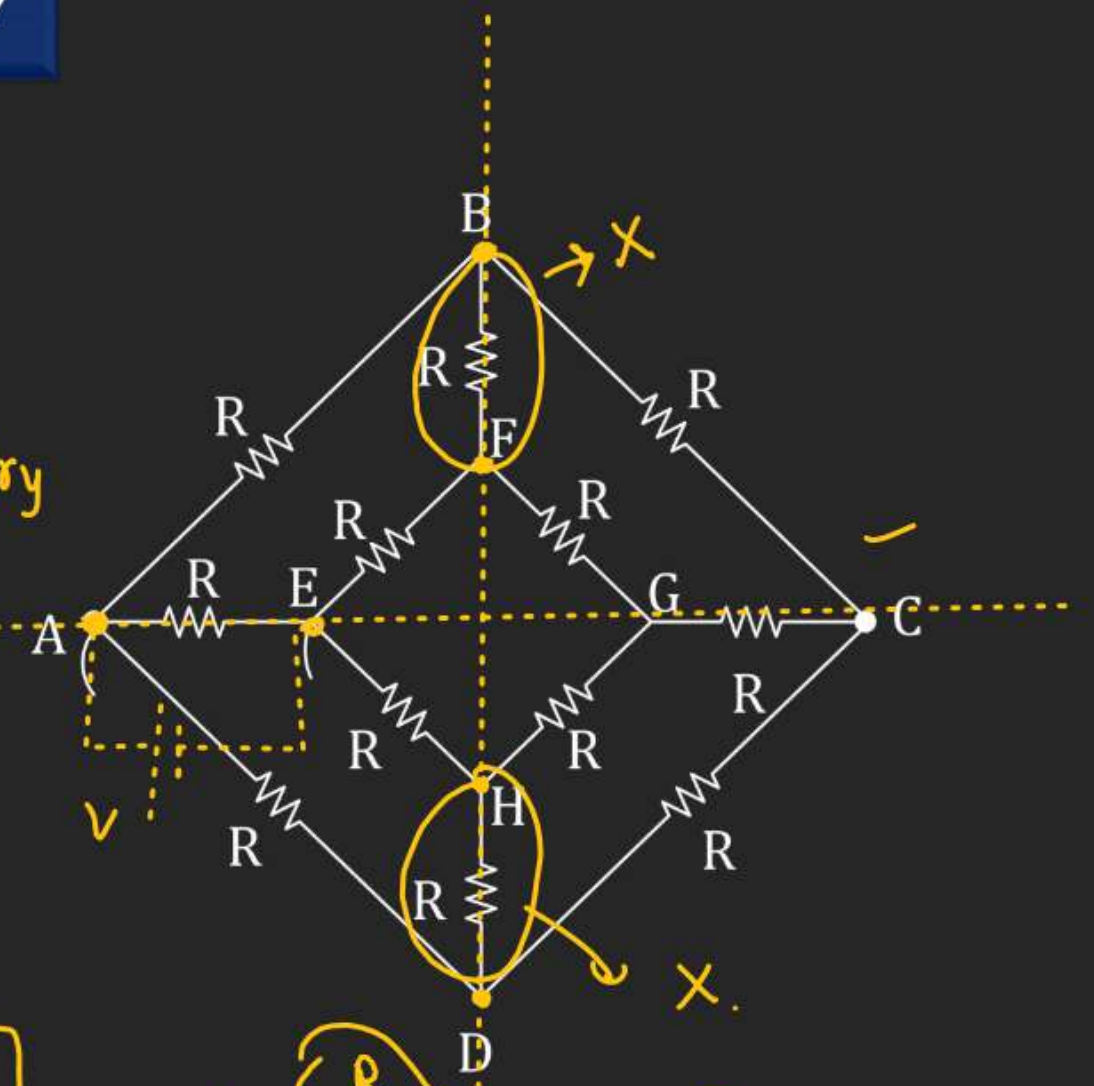
$$\begin{cases} V_B = V_D \\ V_F = V_H \end{cases}$$



Series.

$$R_{AE} = \frac{3R \cdot R}{3R + R} = \frac{3R}{4}$$



## Equivalent resistance by symmetry

**Q.1** Each branch in the following circuit has a resistance  $R$ . The equivalent resistance of the circuit between the points A and B is:

(A)  $R$

(B)  $2R$  ✓


(C)  $4R$

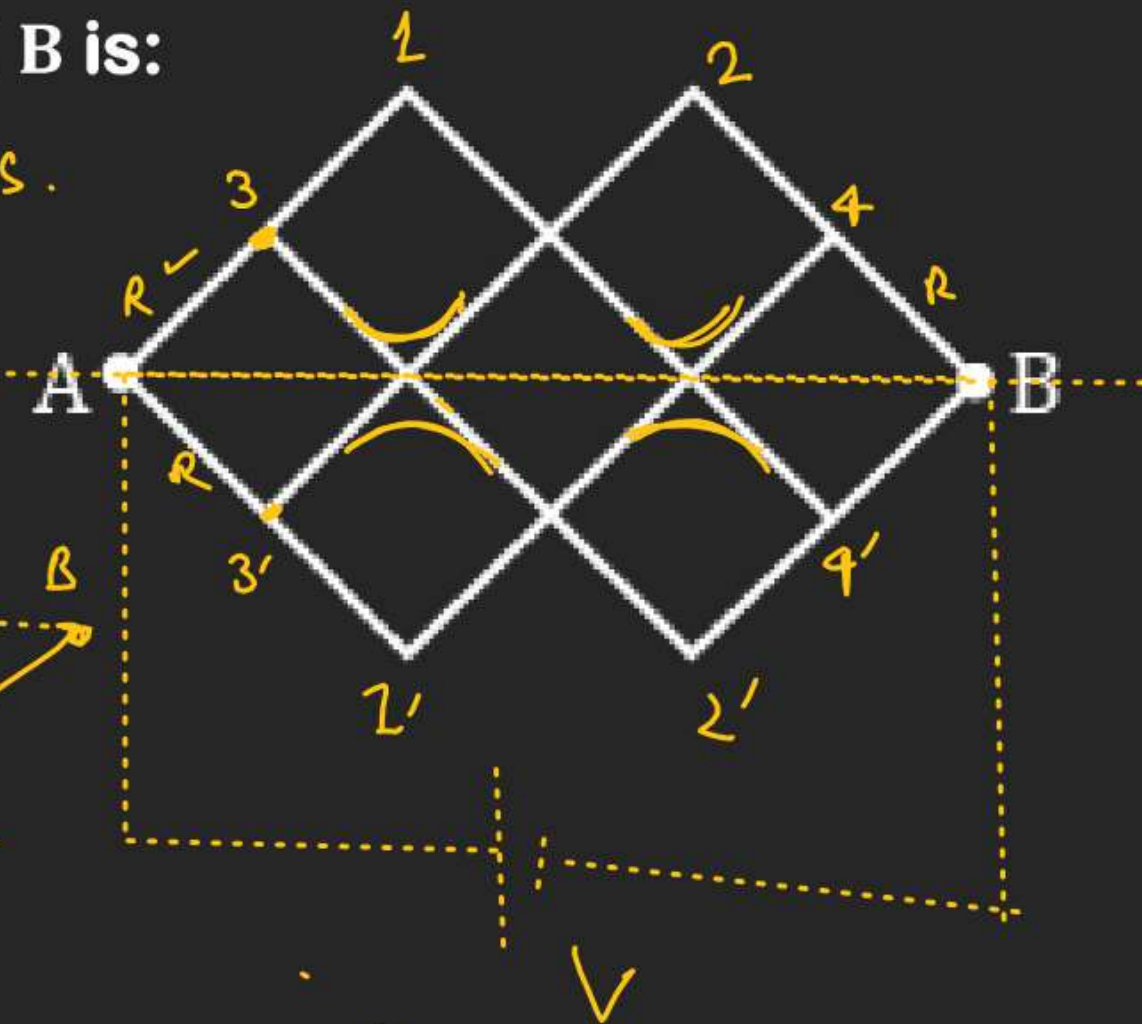
(D)  $8R$

$\left[ \begin{array}{l} V_3 = V_{3'} \\ V_4 = V_{4'} \end{array} \right]$ 
 $\left[ \begin{array}{l} V_1 = V_{1'} \\ V_2 = V_{2'} \end{array} \right]$ 
 Parallel axis of Symmetry



$$\begin{aligned}
 (R_{eq})_{AB} &= 4(R/2) \\
 &= 2R
 \end{aligned}$$



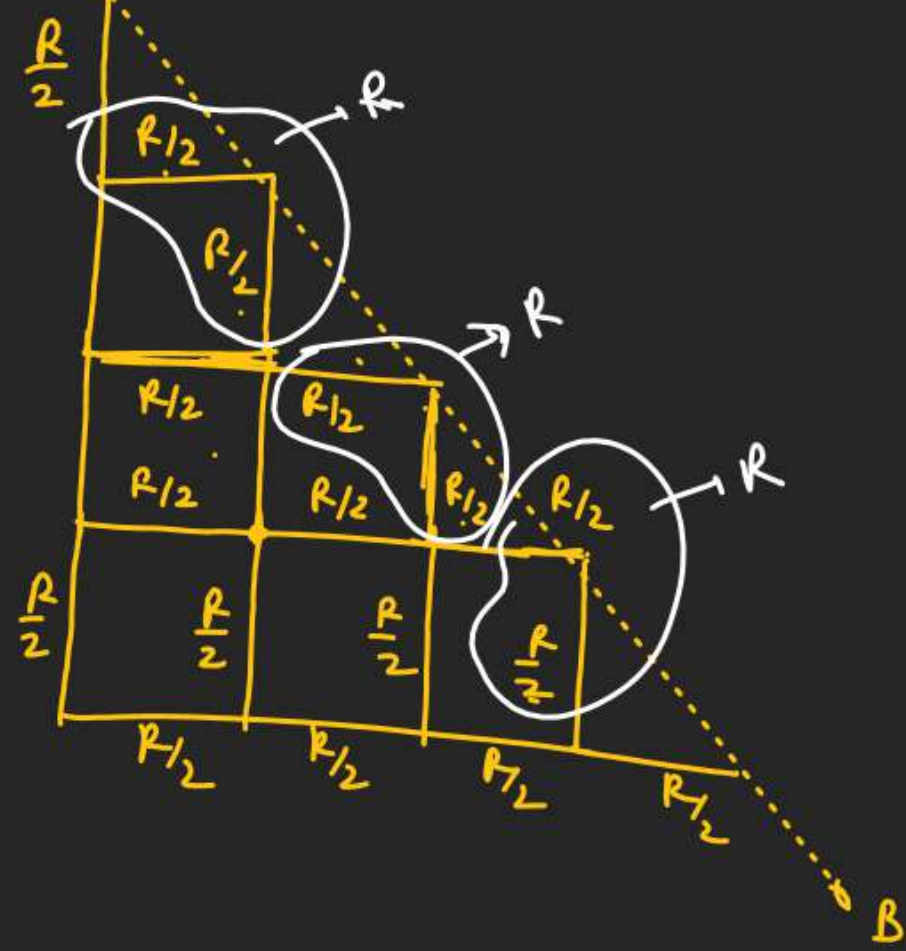


$$\begin{bmatrix} V_1 = V_1' \\ V_2 = V_2' \\ V_3 = V_3' \end{bmatrix}$$



**Q.3** In the circuit shown in Fig.  $abcd$  is a square. All the wires forming the square and its diagonals are homogeneous and have same cross-section. Find the ratio of power dissipated in resistors  $ab$  and  $cd$ .


*18-12*

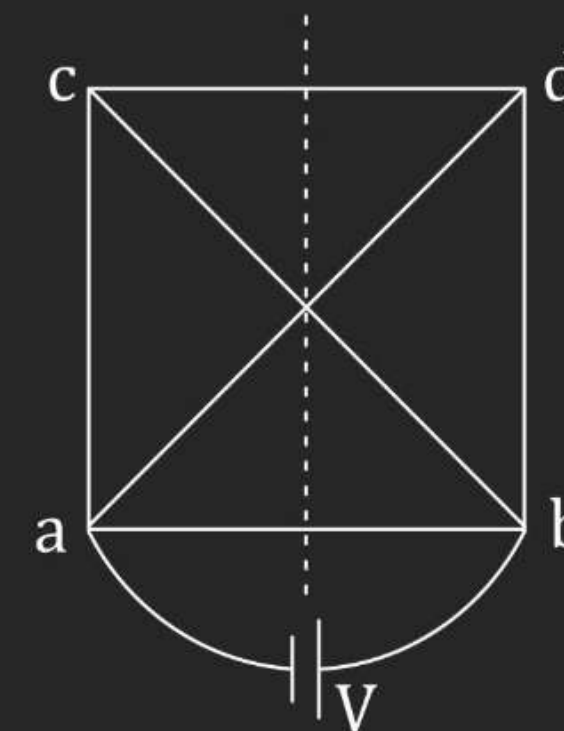



**Q.4** In the network shown in figure find the equivalent resistance across the points M and M'.

*H.W*

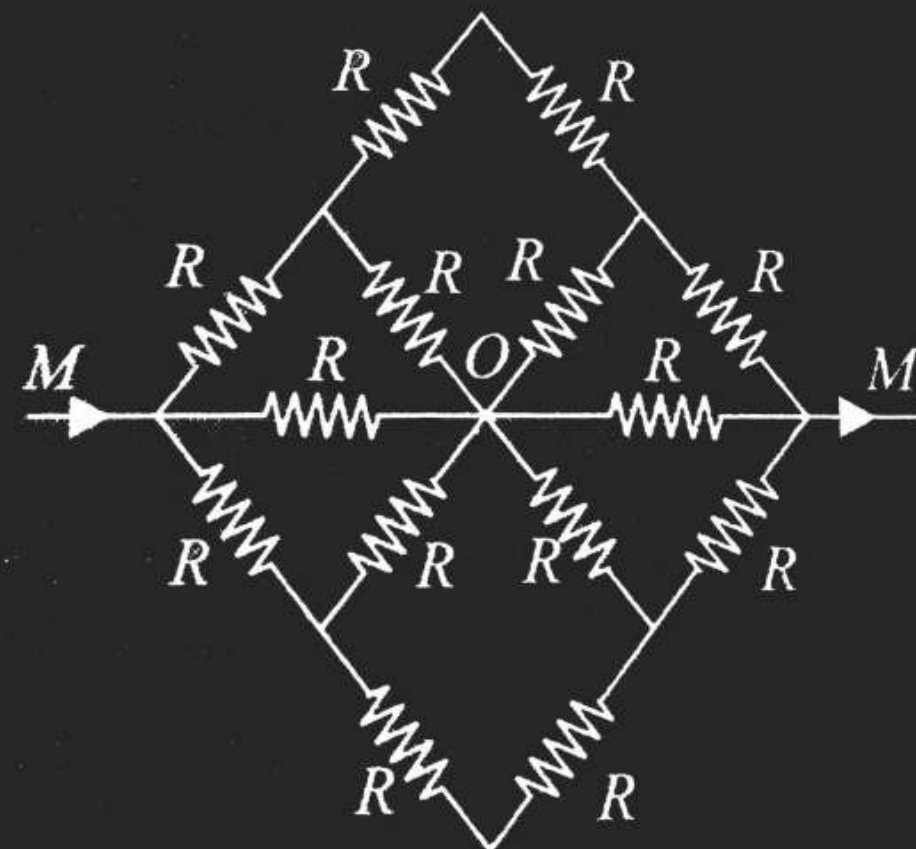

**Q.6** ABCD is square see Fig where each side is a uniform wire of resistance  $1\Omega$ . A point E lies on CD such that if a uniform wire of resistance  $1\Omega$  is connected across AE and constant potential difference is applied across A and C then B and E are equipotential.


*H.W*

(A)  $\frac{CE}{ED} = 1$

(B)  $\frac{CE}{ED} = 2$


(C)  $\frac{CE}{ED} = \frac{1}{\sqrt{2}}$

(D)  $\frac{CE}{ED} = \sqrt{2}$

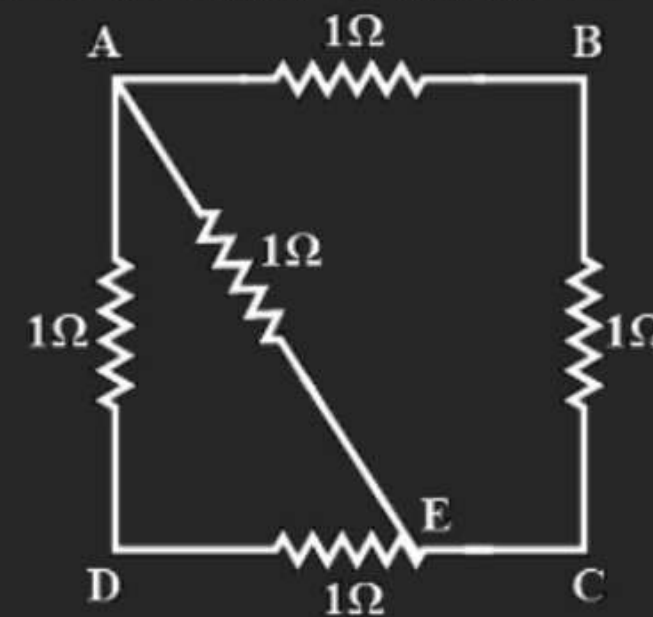




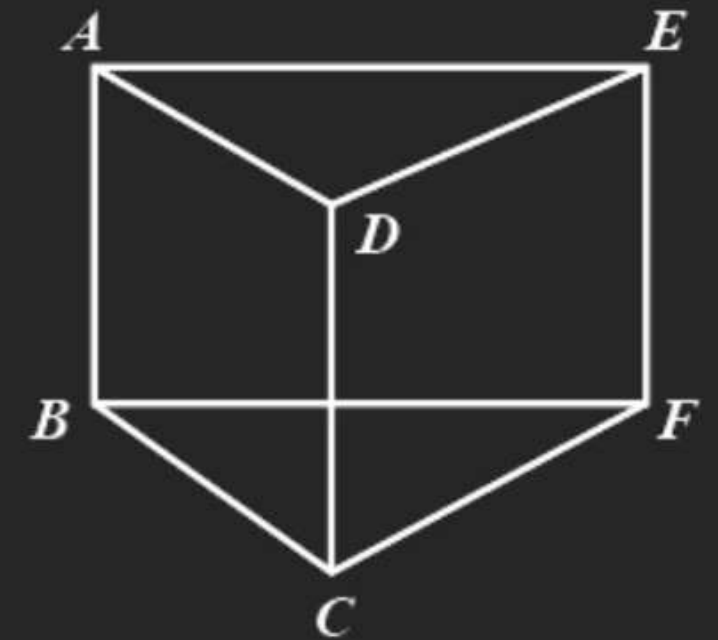**Q.3** Nine wires each of resistance  $r$  are connected to make a prism as shown in figure. Find the equivalent resistance of the arrangement across terminals (a) *H.W.* A and D (b) A and B



**Q.4** Find the equivalent resistance of the circuit between points A and B shown in figure is: (each branch is of resistance =  $1\Omega$ )

H.W.

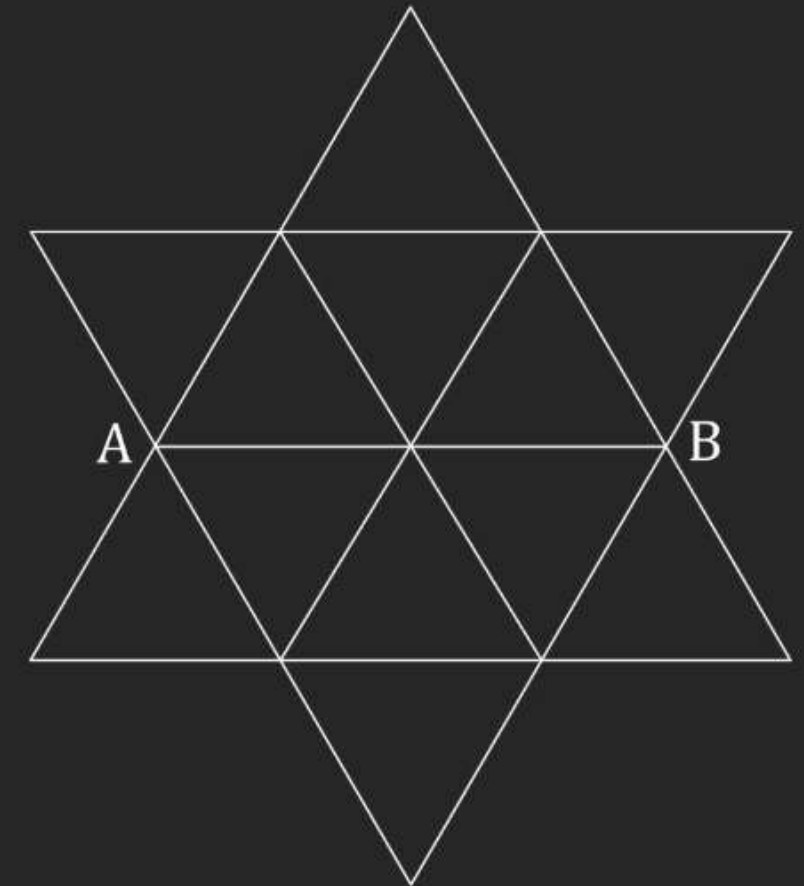



**Q.5** Figure shows five identical wires connected in symmetrical zig-zag fashion between points A and F. What will be the change in the resistance of the circuit between A and F if two similar identical wires are added as shown by the dashed line in figure.

