

★★★

L-R Ckt

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$


$$I = \underline{I_0} \sin(\omega t - \phi)$$

$$I_0 = \frac{\mathcal{E}_0}{|Z|}$$

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{R^2 + \omega^2 L^2}$$

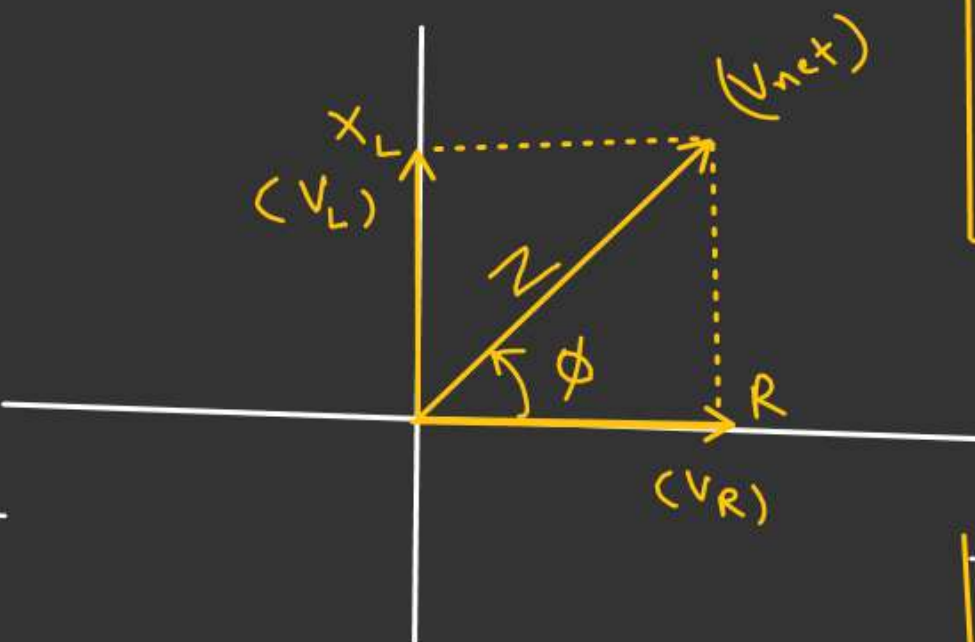
$$I_0 = \frac{\mathcal{E}}{\sqrt{R^2 + \omega^2 L^2}}$$



$$\tan \phi = \left(\frac{X_L}{R} \right) = \frac{\omega L}{R}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

Initial phase constant.

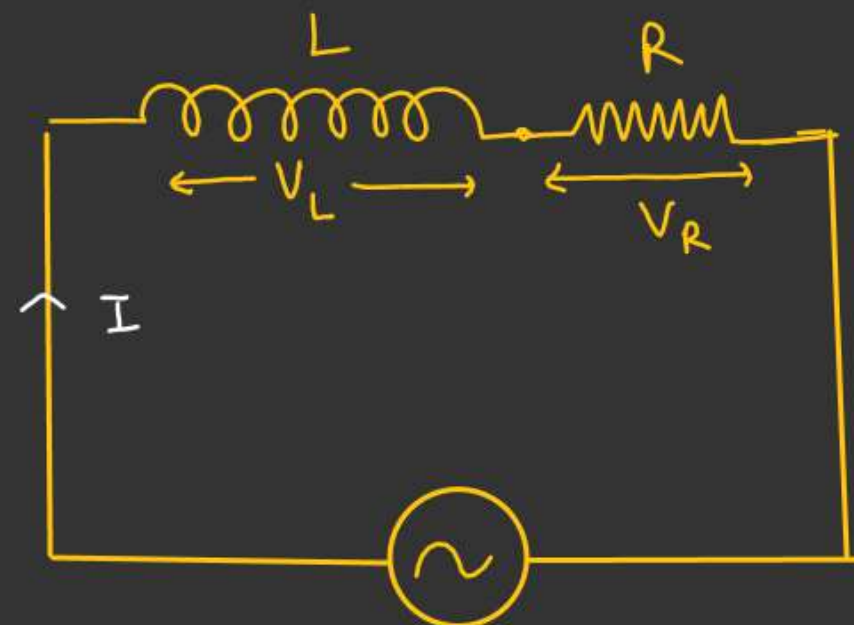

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

In L-R ckt current is lagging by an angle of ϕ with voltage.

$$V_L = I X_L$$

$$V_R = I R$$

$$V = \sqrt{V_L^2 + V_R^2}$$

$$V = I \sqrt{X_L^2 + R^2}$$

$$V = I Z$$

✱✱

L-C-R Series Ckt


$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$I = \underline{\underline{I_0}} \sin(\omega t + \underline{\underline{\phi}})$$

$$I_0 = \frac{\mathcal{E}_0}{|Z|}$$

Case-1

$$\underline{\underline{X_L > X_C}}$$

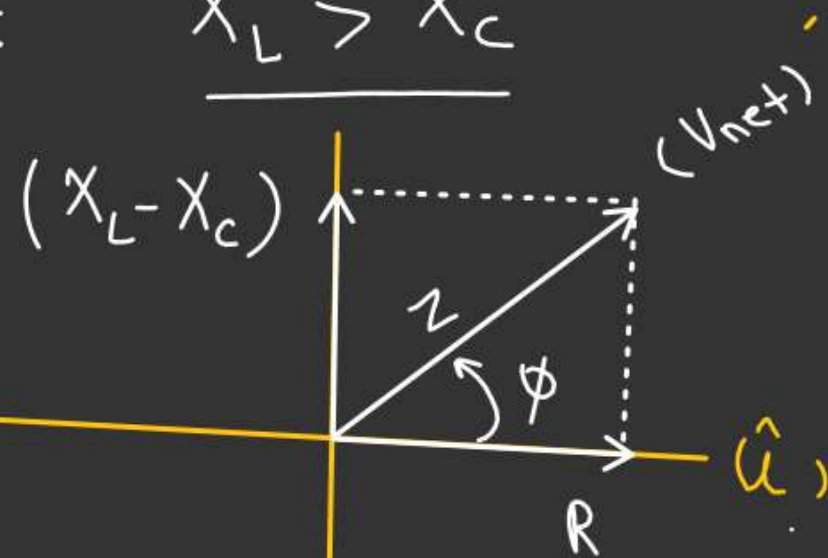



$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (X_L - X_C)^2}} \sin(\omega t - \phi)$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2} \quad \omega L = X_L$$

$$\tan \phi = \frac{|X_L - X_C|}{R}$$

$$\phi = \tan^{-1} \left(\frac{|X_L - X_C|}{R} \right)$$

$$\frac{1}{\omega C} = X_C$$

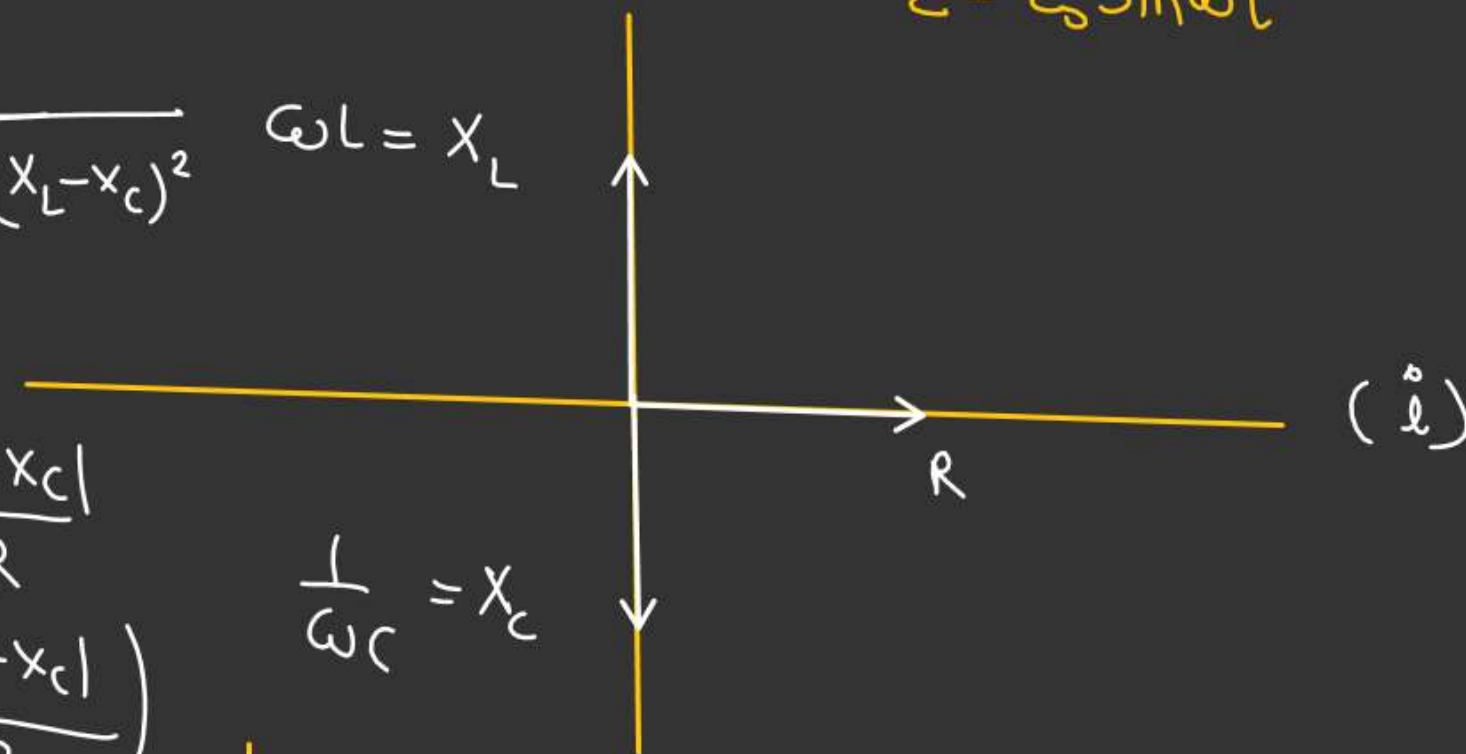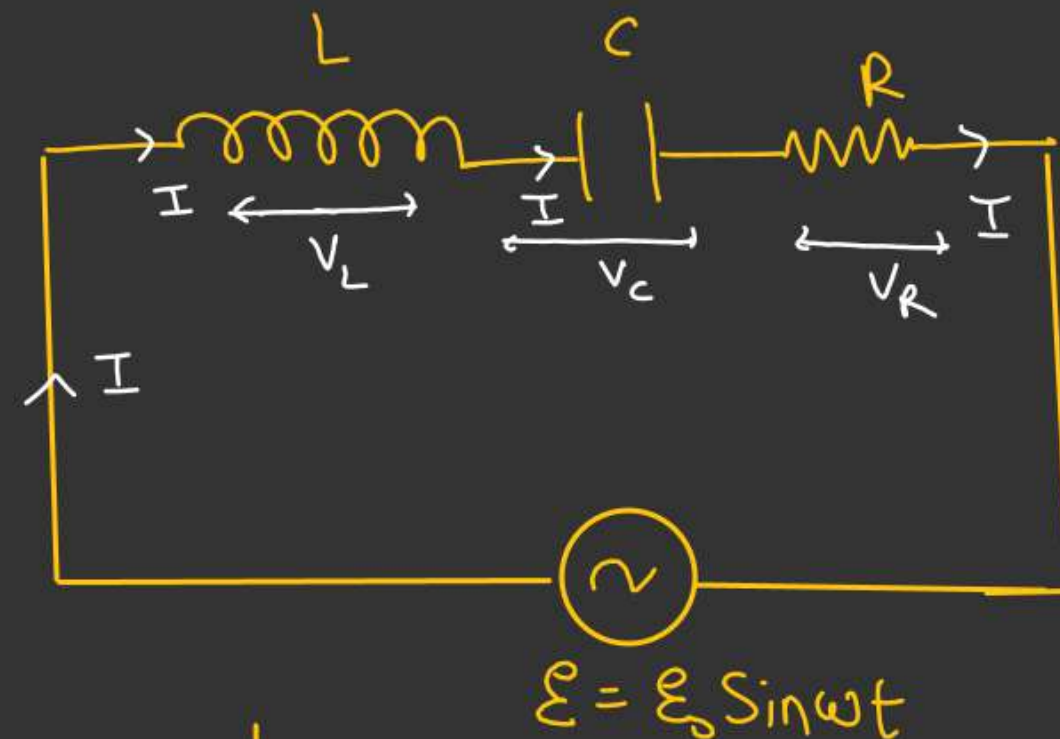


Case-2 $X_C > X_L \Rightarrow$ Current leading the voltage.

$$|Z| = \sqrt{R^2 + (X_C - X_L)^2}$$

$$I_0 = \frac{\mathcal{E}_0}{|Z|} = \frac{\mathcal{E}_0}{\sqrt{R^2 + (X_C - X_L)^2}}$$
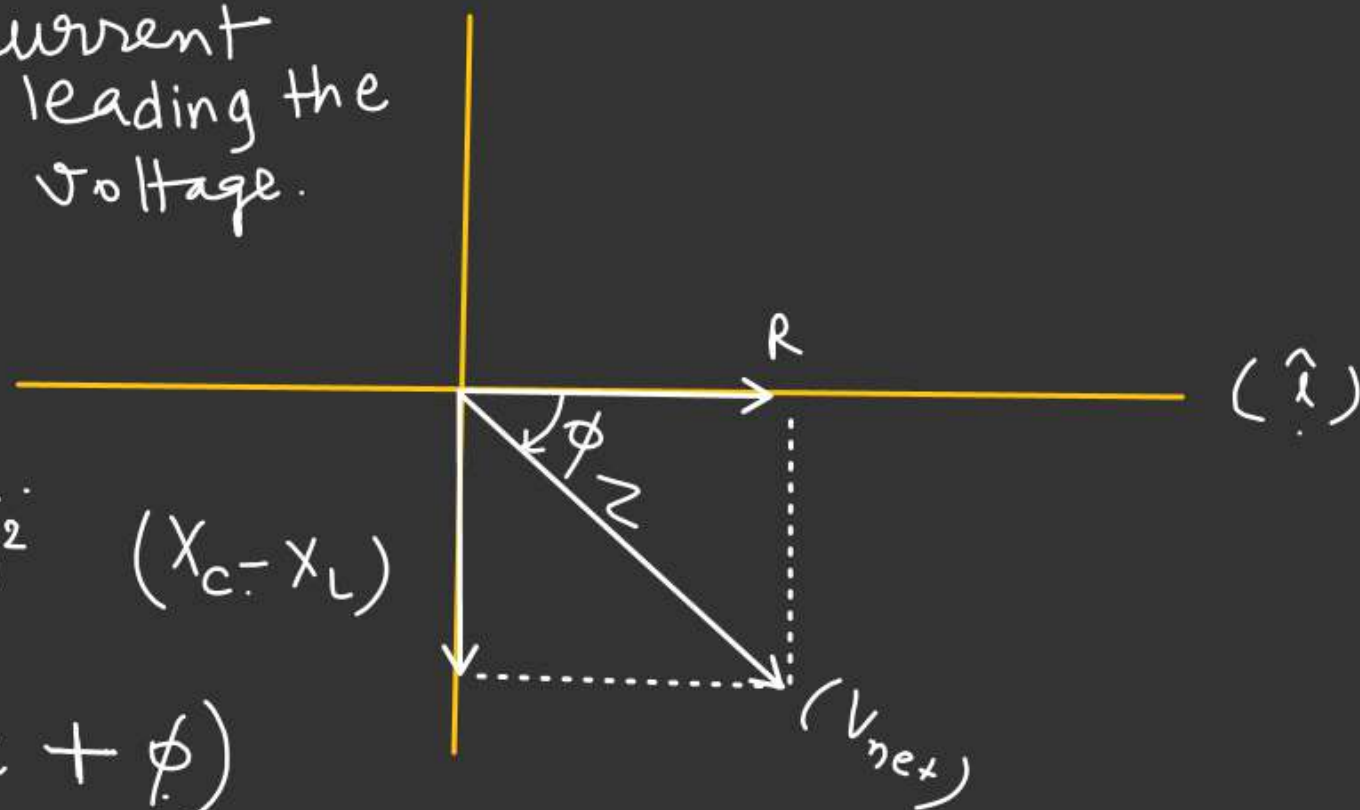
$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (X_C - X_L)^2}} \sin(\omega t + \phi)$$



$$\tan \phi = \left(\frac{|X_C - X_L|}{R} \right)$$

$$\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

Case-3 :-

$$X_L = X_C$$

 \Rightarrow Condition of Resonance in L-C-R Series Ckt.

$$|Z| = R$$

$$I_0 = \frac{E_0}{|Z|} = \frac{E_0}{R}$$

$$E = E_0 \sin \omega t$$

$$\phi = 0$$

$$I = I_0 \sin \omega t$$

Condition of Resonance

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$


$$\omega^2 = \frac{1}{LC}$$

Angular frequency $\leftarrow \omega = \frac{1}{\sqrt{LC}}$


$$\omega = \frac{2\pi}{T} = 2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

Resonating frequency.

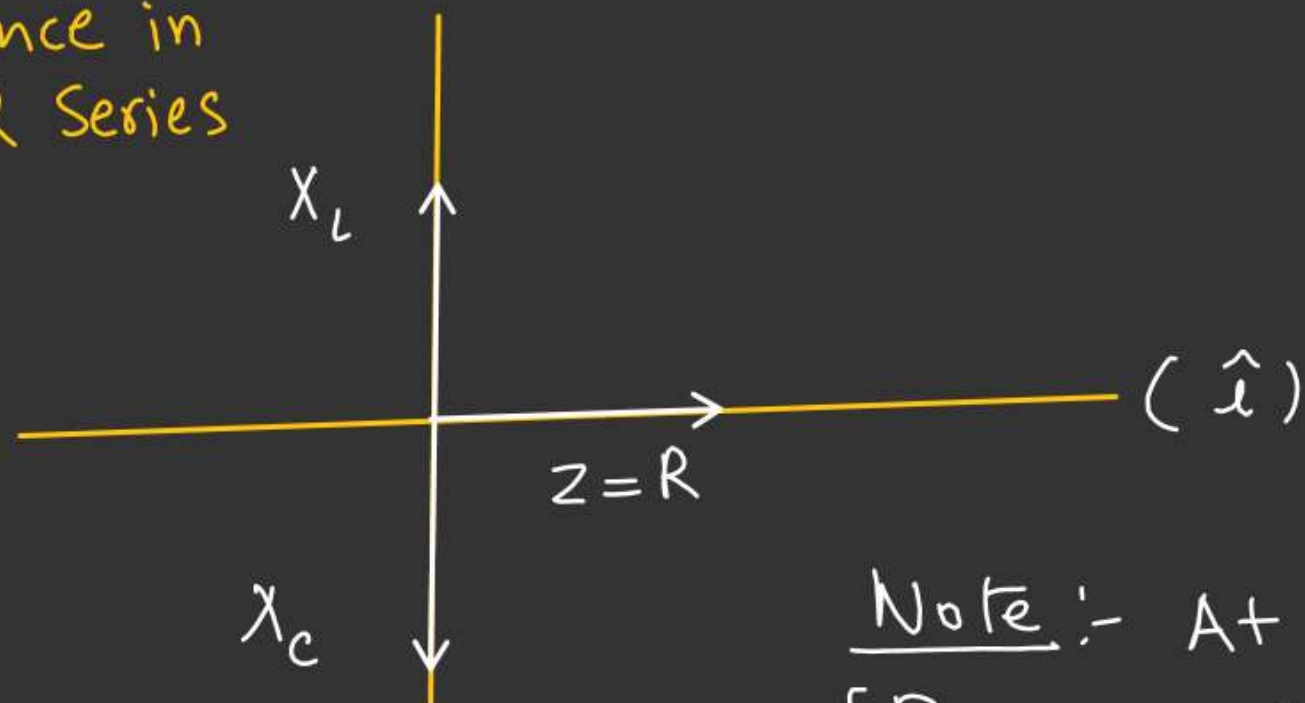

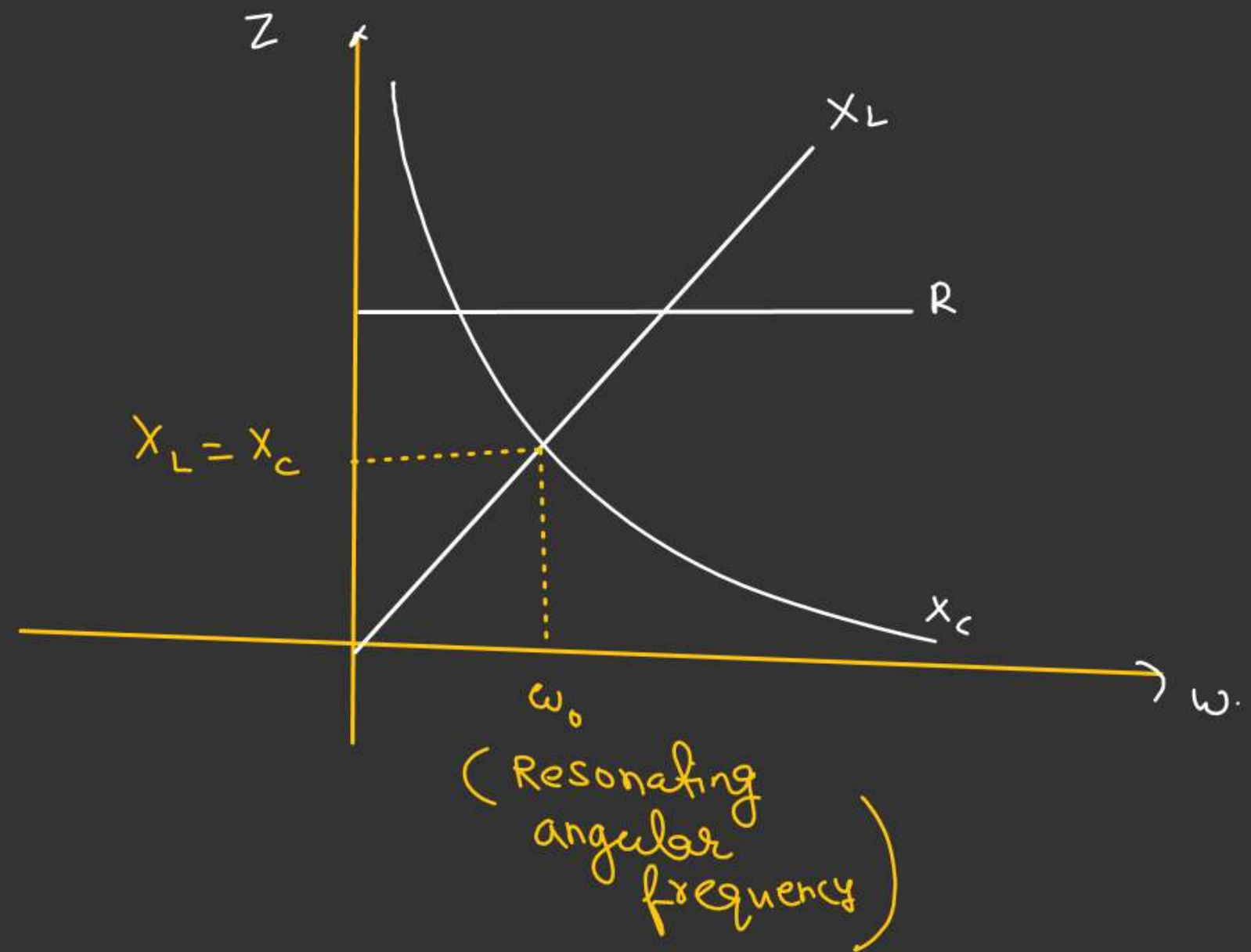
Note :- At Resonance L-C-R Series behave as purely Resistive Ckt





General A.C Ckt


$$\hat{v} \rightarrow \hat{i}$$

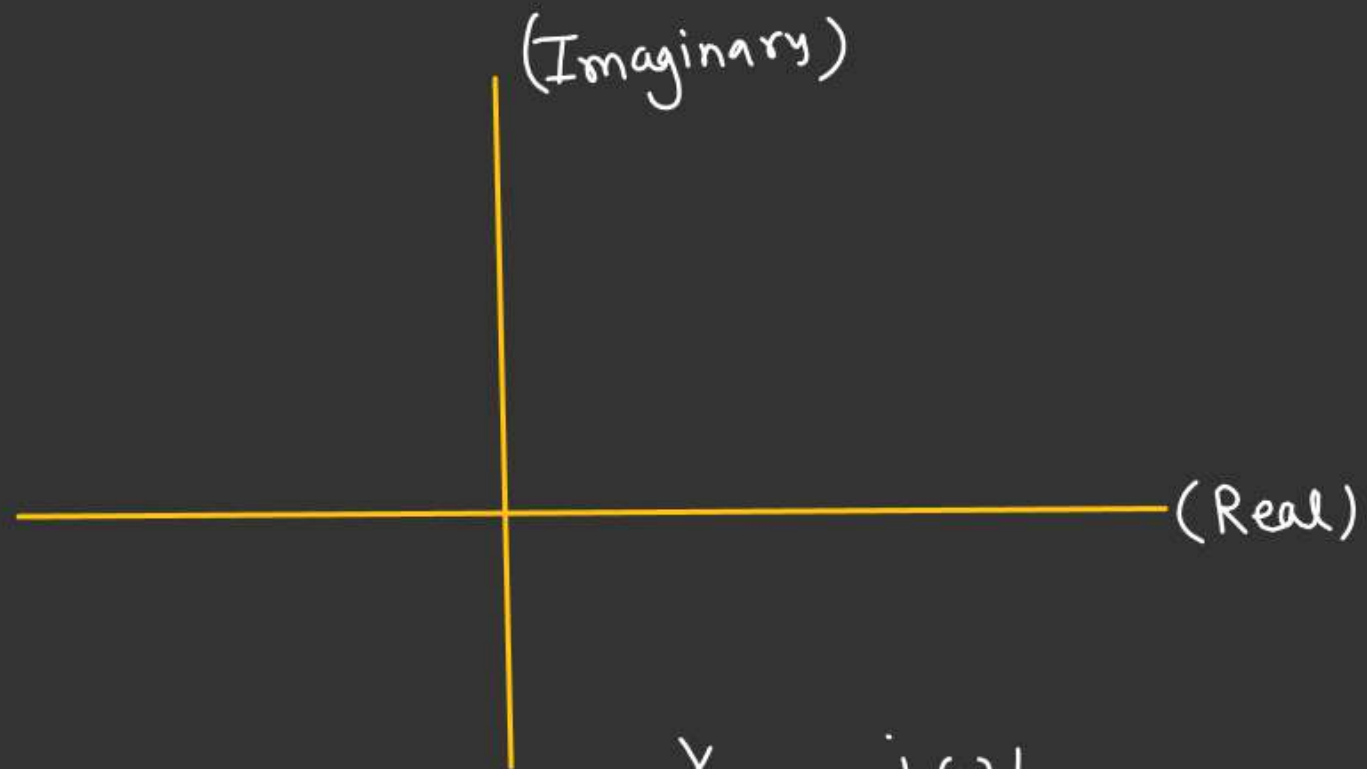

$$X_L = j\omega L$$

$$X_C = \frac{1}{j\omega C}$$
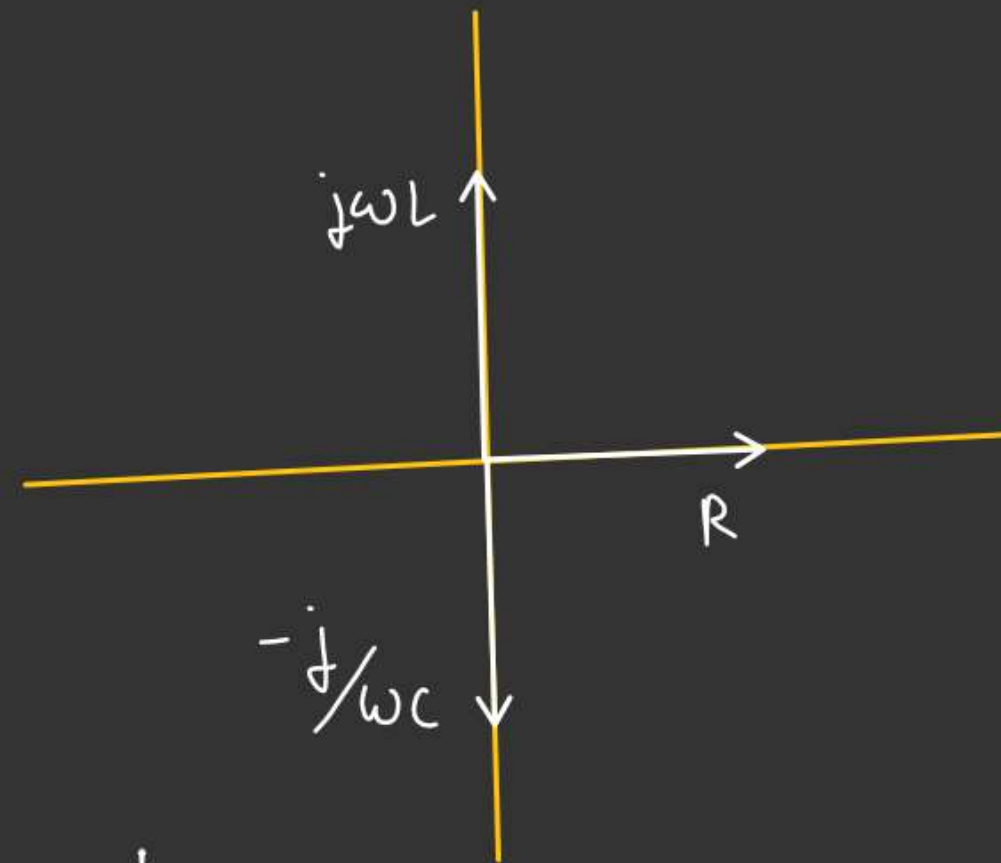
$$X_C = \frac{1}{j\omega C} \times \frac{j}{j} = \frac{-j}{\omega C}$$



Condition of Resonance

⇒ For Resonance imaginary part of impedance will be zero.


$$X_C = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$

$$X_L = j\omega L$$

$$\frac{1}{Z} = \frac{1}{X_L + R} + \frac{1}{X_C}$$

$$\frac{1}{Z} = \frac{1}{R + j\omega L} + j\omega C$$
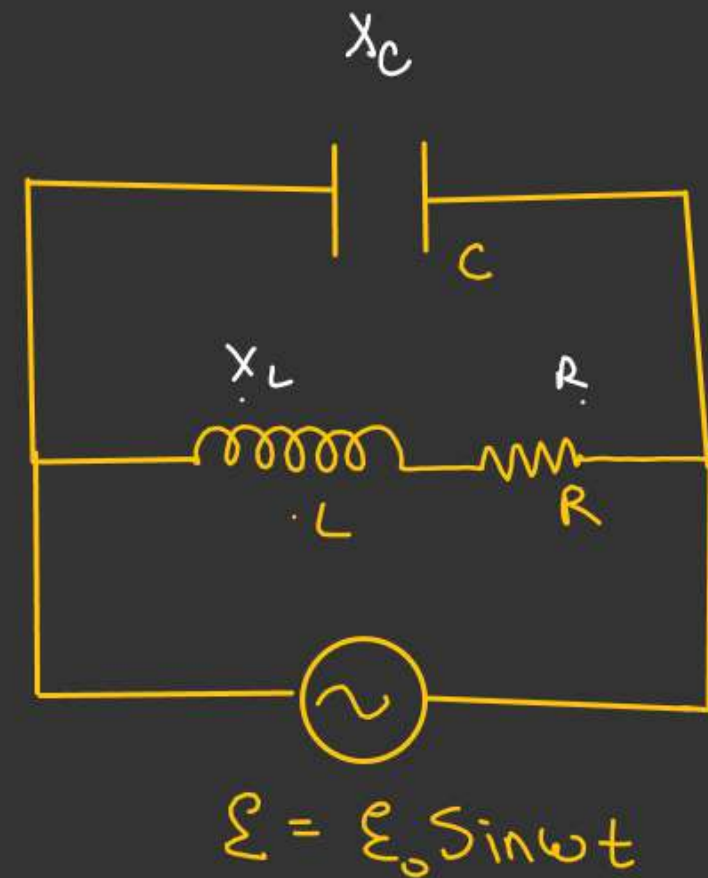
$$\frac{1}{Z} = \frac{1}{R^2 + \omega^2 L^2} (R - j\omega L) + j\omega C$$



$$\frac{1}{Z} = \frac{1}{R^2 + \omega^2 L^2} (R - j\omega L) + j\omega C$$

$$\frac{1}{Z} = \frac{R}{R^2 + \omega^2 L^2} + j \left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2} \right)$$

\Downarrow
 Imaginary part.

For Resonance.

$$\text{Im}(Z) = 0$$

$$\omega C - \frac{\omega L}{R^2 + \omega^2 L^2} = 0$$

$$C = \frac{L}{R^2 + \omega^2 L^2}$$

$$R^2 + \omega^2 L^2 = \frac{L}{C}$$

$$\omega^2 L^2 = \frac{L}{C} - R^2$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Resonating frequency.

ALTERNATING CURRENT

HW


Q.1 Determine the rms value of a semi-circular current wave which has a maximum value of a .

(A) $(1/\sqrt{2})a$

(B) $\sqrt{(3/2)}a$

(C) $\sqrt{(2/3)}a$

(D) $(1/\sqrt{3})a$

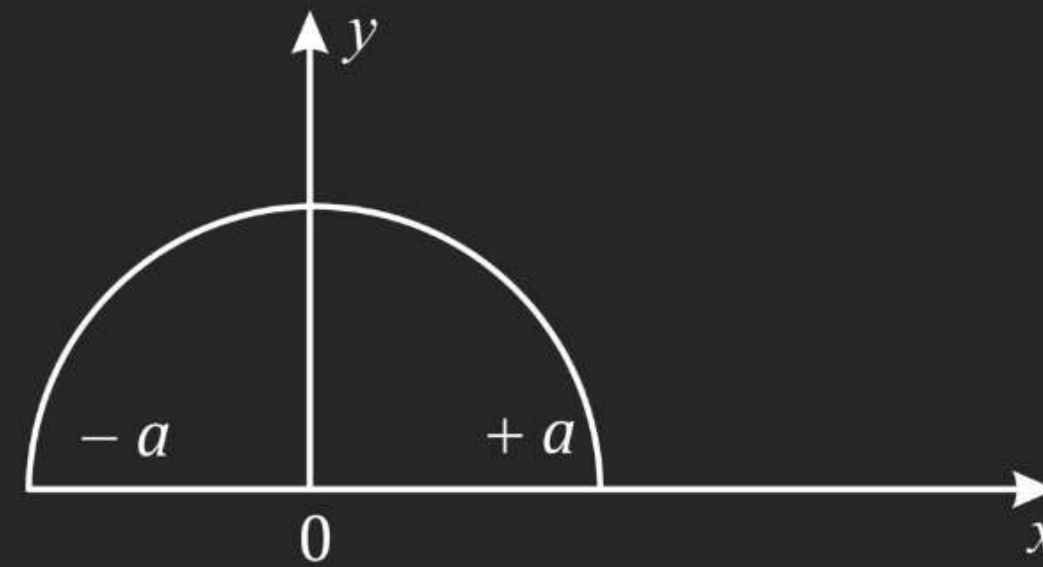

ALTERNATING CURRENT

H.W.


Q.2 If a direct current of value a ampere is superimposed on an alternative current $I = b \sin \omega t$ flowing through a wire, what is the effective value of the resulting current in the circuit?

(A) $\left[a^2 - \frac{1}{2}b^2\right]^{1/2}$

(B) $\left[a^2 + b^2\right]^{1/2}$

(C) $\left[\frac{a^2}{2} + b^2\right]^{1/2}$

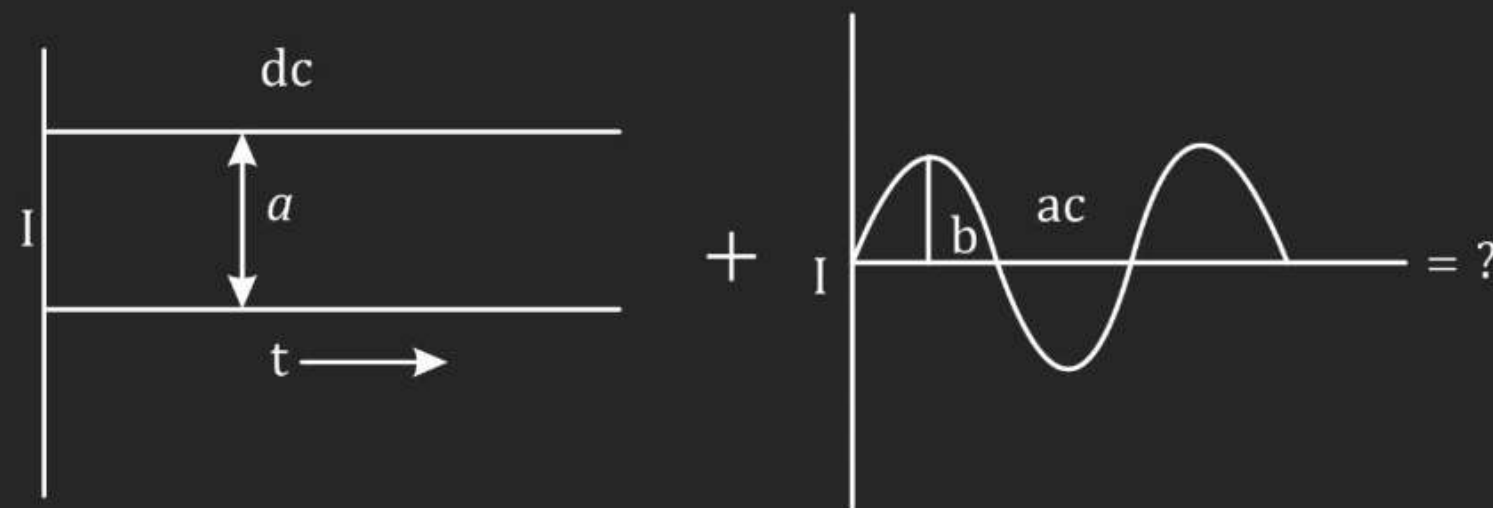
(D) $\left[a^2 + \frac{1}{2}b^2\right]^{1/2}$



ALTERNATING CURRENT

H.W.

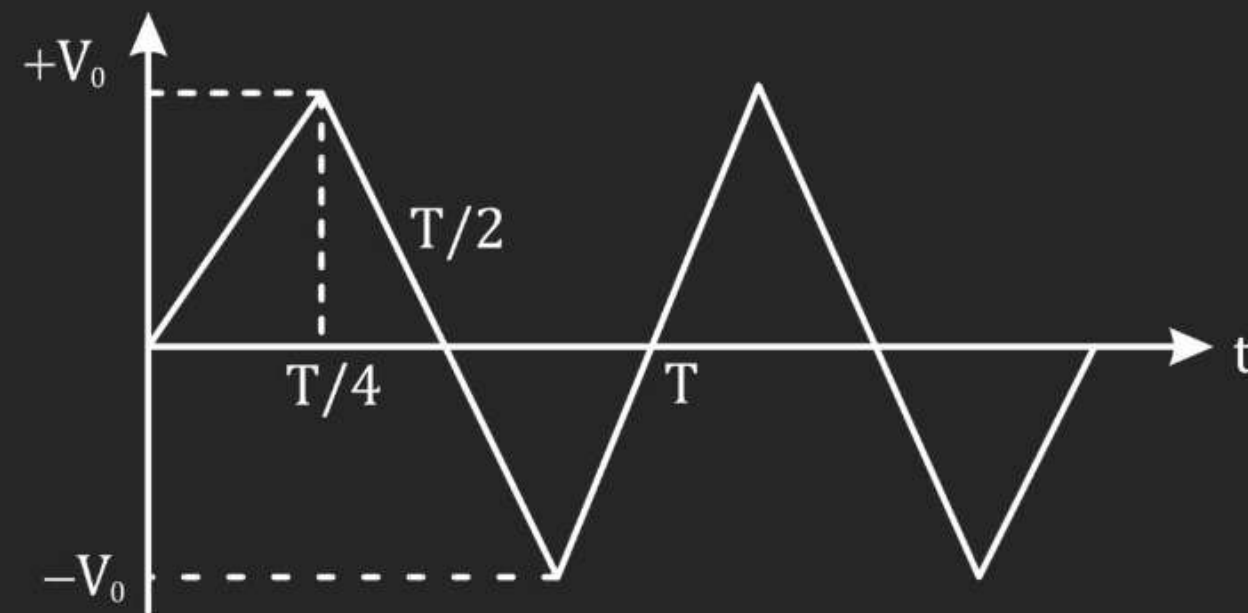Q.3 The voltage time ($V - t$) graph for triangular wave having peak value V_0 is as shown in



H.W. Fig in Q-3.

ALTERNATING CURRENT

Q.4 The rms value of V in time interval from $t = 0$ to $T/4$ is

(A) $\frac{V_0}{\sqrt{3}}$

(B) $\frac{V_0}{2}$

(C) $\frac{V_0}{\sqrt{2}}$

(D) None of these

H-W Fig in Q. No-3

ALTERNATING CURRENT

Q.5 In the above question, the average value of voltage (V) in one time period will be

(A) $\frac{V_0}{\sqrt{3}}$

(B) $\frac{V_0}{2}$

(C) $\frac{V_0}{\sqrt{2}}$

(D) 0

ALTERNATING CURRENT

H.W.

For problems 6 – 8

A series LCR circuit containing a resistance of 120Ω has angular resonance frequency $4 \times 10^5 \text{rads}^{-1}$. At resonance the voltages across resistance and inductance are 60 V and 40 V. respectively.

6. The value of inductance L is

- (A) 0.1mH (B) 0.2mH (C) 0.35mH (D) 0.4mH

7. The value of capacitance C is

- (A) $\frac{1}{32} \mu\text{F}$ (B) $\frac{1}{16} \mu\text{F}$ (C) $32 \mu\text{F}$ (D) $16 \mu\text{F}$

8. At what frequency, the current in the circuit lags the voltage by 45° ?


- (A) $4 \times 10^5 \text{rads}^{-1}$ (B) $3 \times 10^5 \text{rad}$
(C) $8 \times 10^5 \text{rads}^{-1}$ (D) $2 \times 10^5 \text{rads}^{-1}$

ALTERNATING CURRENT

H.W.

Q.9 In the series LCR circuit (Fig), the voltmeter and ammeter readings are:

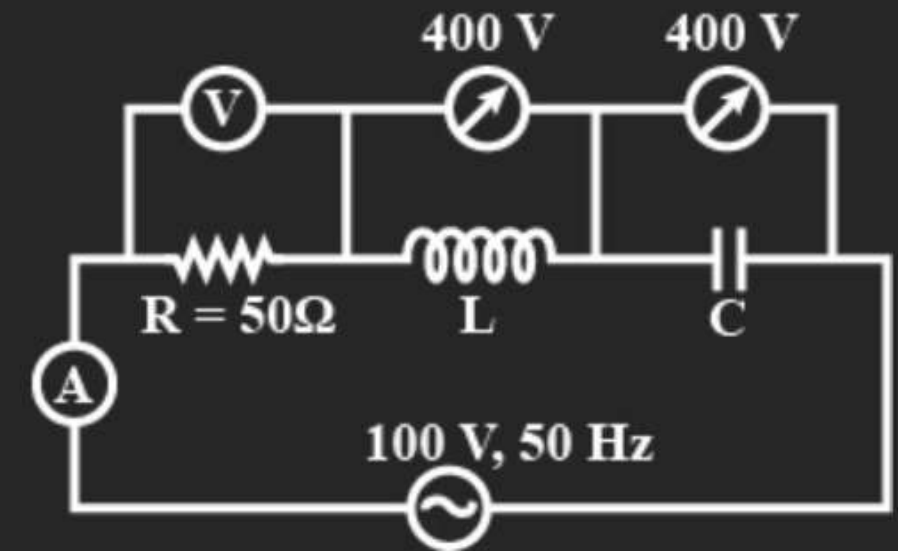- (A) $V = 100 \text{ V}, I = 2 \text{ A}$
- (B) $V = 100 \text{ V}, I = 5 \text{ A}$
- (C) $V = 1000 \text{ V}, I = 2 \text{ A}$
- (D) $V = 300 \text{ V}, I = 1 \text{ A}$




H.W.

ALTERNATING CURRENT

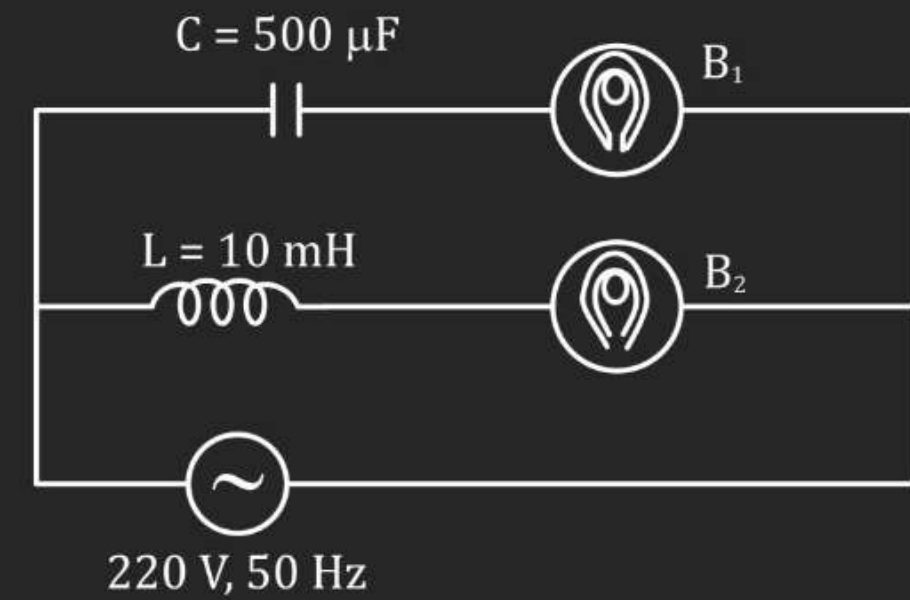Q.10 In the circuit shown in Fig, if both the bulbs B_1 and B_2 are identical,

- (A)** their brightness will be the same
- (B)** B_2 will be brighter than B_1
- (C)** B_1 will be brighter than B_2
- (D)** only B_2 will glow because the capacitor has infinite impedance



ALTERNATING CURRENT

H.W.

Q.10 The circuit given in Fig. has a resistance less choke coil L and a resistance R . The voltages across R and L are also given in the figure. The virtual value of the applied voltage is

(A) 100 V

(B) 200 V

(C) 300 V

(D) 400 V

