
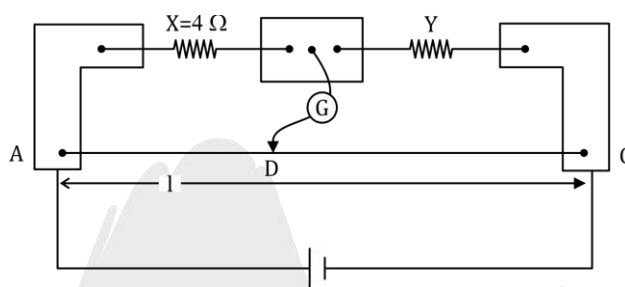


DPP - 9

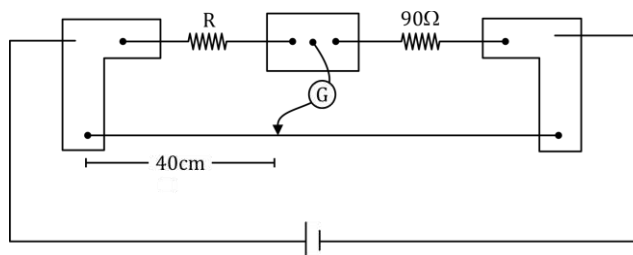- Q.1** In figure a meter bridge, A wire AC has uniform cross-section. length of AC is 100 cm. Y is a coil & x is a standard resistor of 4Ω . When Y is immersed in melting ice the null deflection point is at 40 cm from point A. When the coil Y is heated to 100°C $R\Omega$ resistor has to be connected in parallel with Y in order to keep the bridge balanced at the same point If $[\alpha_{\text{coil}} = 6.3 \times 10^{-4}/\text{K}]$ find value of R _____.



- Q.2** In a meter bridge, null point is found to be at 20 cm, when the unknown resistance R is shunted by 10Ω resistance, null point is found to be shifted by 10 cm. the unknown resistance x, is _____.
- Q.3** Resistance R_1 in resistance box is 100Ω & balanced length 75 cm from end A. The diameter of unknown wire is 1 mm and length of the Unknown wire is 20 cm. the specific resistance of the unknow wire ρ is $N\pi \times 10^{-3}\Omega - \text{m}$, value of N is
- Q.4** Resistance in the two gaps of a meter bridge are 10Ω & 30Ω respectively. If the resistance are interchanged the balance point shifts by.
- (A) 33.3 cm (B) 50 cm (C) 25 cm (D) 66.67 cm
- Q.5** During an experiment with a metre bridge, the galvanometer shows a null point when the jockey is pressed at 40 cm using a standard resistance of 90Ω as shown in the figure. The least count of the scale used in the metre bridge is 1 mm. The unknown resistance is




- (A) $135 \pm 0.23\Omega$ (B) $60 \pm 0.15\Omega$ (C) $60 \pm 0.25\Omega$ (D) $135 \pm 0.56\Omega$

(Physics)

CURRENT ELECTRICITY

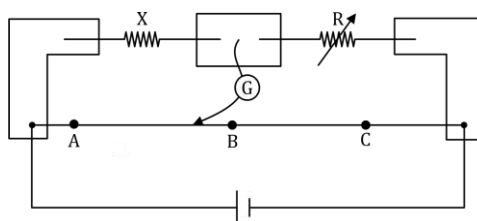
- Q.6** For which resistance, the value of x will be the most accurate, If R_1, R_2, R_3 are different values of R . A, B & C are the respective null points obtained



- (A) R_1 (B) R_2 (C) R_3 (D) For all

[Think about reason]

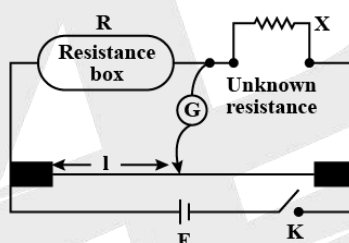- Q.7.** In a meter bridge experiment, the circuit diagram and the corresponding observation table are shown in figure.




S. No.	$R(\Omega)$	$l(\text{cm})$
1.	1000	60
2.	100	13
3.	10	1.5
4.	1	1.0

Which of the readings is inconsistent?


- (A) 1 (B) 2 (C) 3 (D) 4

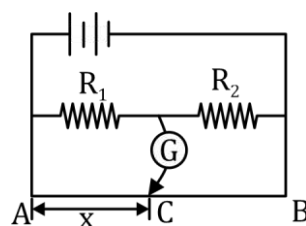- Q.8** In the shown arrangement of the experiment of the meter bridge if AC corresponding to null deflection of galvanometer is x , what would be its value if the radius of the wire AB is doubled?



- (A) x (B) $\frac{x}{4}$ (C) $4x$ (D) $2x$

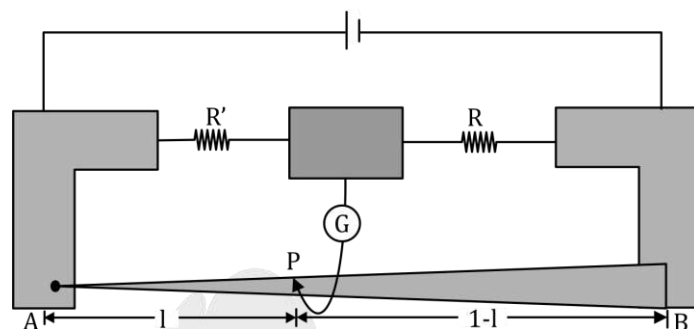- Q.9** In a meter bridge, the wire of length 1 m has a nonuniform cross-section such that, the variation $\frac{dR}{dl}$ of its resistance R with length l is $\frac{dR}{dl} \propto \frac{1}{\sqrt{l}}$. Two equal resistances are connected as shown in the figure. The galvanometer has zero deflection when the jockey is at point P. What is the length AP ?



(A) 0.2 m

(B) 0.35 m

(C) 0.25 m

(D) 0.3 m

ANSWER KEY

1. $R = 101\Omega$ 2. $x = 50\Omega$ 3. $N = 1/6$ 4. (B) 5. (C) 6. (B)
7. (D) 8. (A) 9. (C)

A