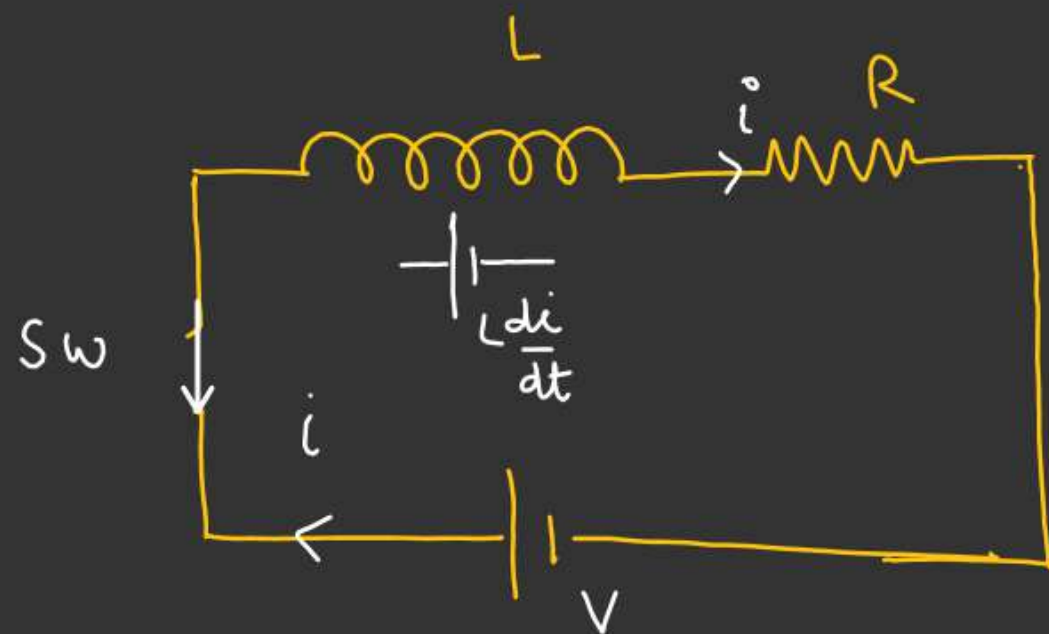


L-C OSCILLATIONAAEnergy Stored in Inductor

$$V - L \frac{di}{dt} - iR = 0$$

$$V = L \frac{di}{dt} + iR$$

$$V i = L i \frac{di}{dt} + i^2 R \quad [\text{Multiplying both side by } i]$$

$$\int_0^i V i dt = L \int_0^i i di + \int_0^i i^2 R dt$$

L-C OSCILLATION

$$\int_0^i V i dt = \underbrace{L \int_0^i i di}_{\text{inductor}} + \int_0^i R i dt$$

$$\frac{dw}{dt} = P = V i$$

$$W_{\text{battery}} = \int_0^i V i dt$$

$$\frac{dH}{dt} = i^2 R$$

$$\int_0^i dH = \int_0^i i^2 R dt$$

Total heat dissipated across resistor.

$$L \int_0^i i di = U_L$$

$$U_L = \frac{1}{2} L i^2$$

$$\text{Energy density} = \frac{U_L}{\text{Volume}} = \frac{B^2}{2\mu_0}$$

Self inductance of an Inductor


$$L = \mu_0 n^2 \frac{\pi R^2 l}{1}$$

$$L = \mu_0 n^2 (A l)$$

$$U_L = \frac{1}{2} \times \mu_0 n^2 (A l) \frac{B^2}{(\mu_0 n^2)} \quad n = \frac{N}{l}$$

$$U_L = \left(\frac{B^2}{2\mu_0} \right) (A l)$$

Volume = A l.

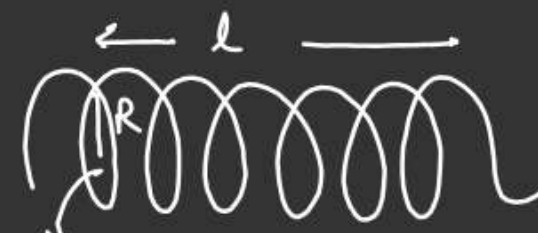


$$A = \pi R^2$$

$$n = \frac{N}{l}$$

$$B = \mu_0 n i$$

$$i = \left(\frac{B}{\mu_0 n} \right)$$

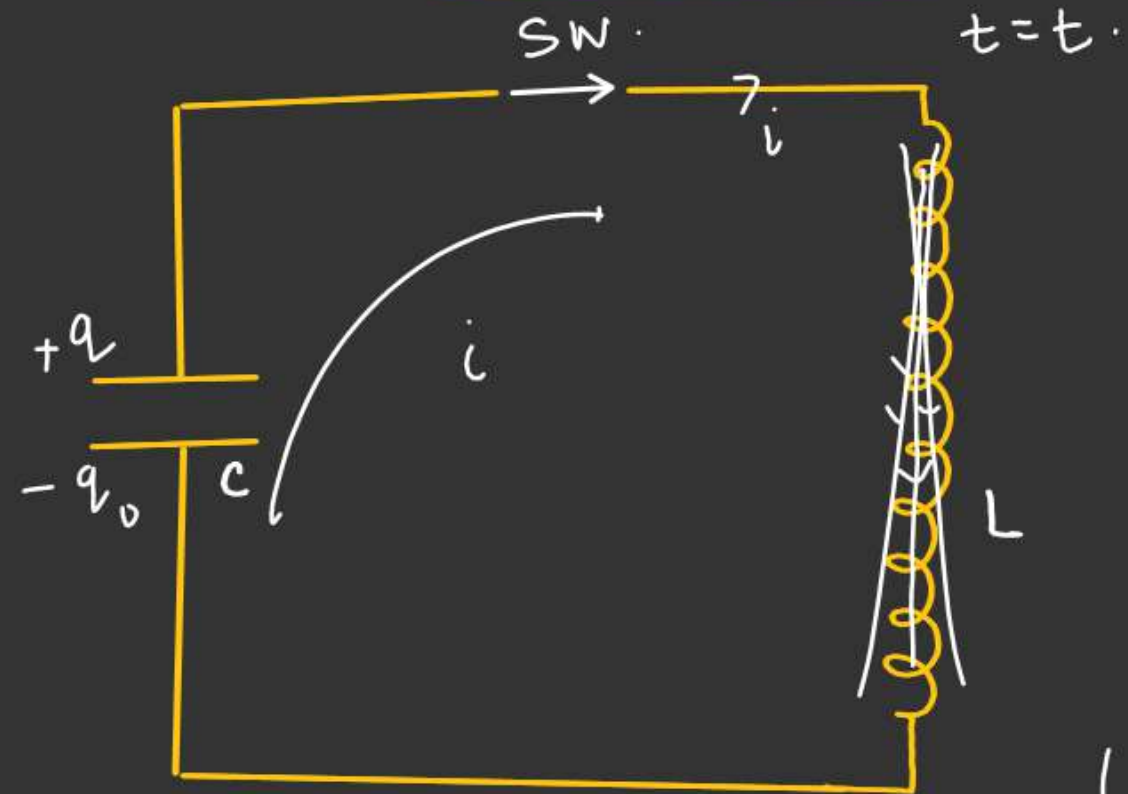L-C Oscillation:-

$$U_T = \frac{q_0^2}{2C} = \text{Constant}$$


$$\text{At } t=t$$

$$U_T = \frac{q^2}{2C} + \frac{1}{2}Li^2$$

$$\left(i = -\frac{dq}{dt} \right)$$

Charge on the Capacitor decreasing w.r.t time.

At $t=0$, SW closed.

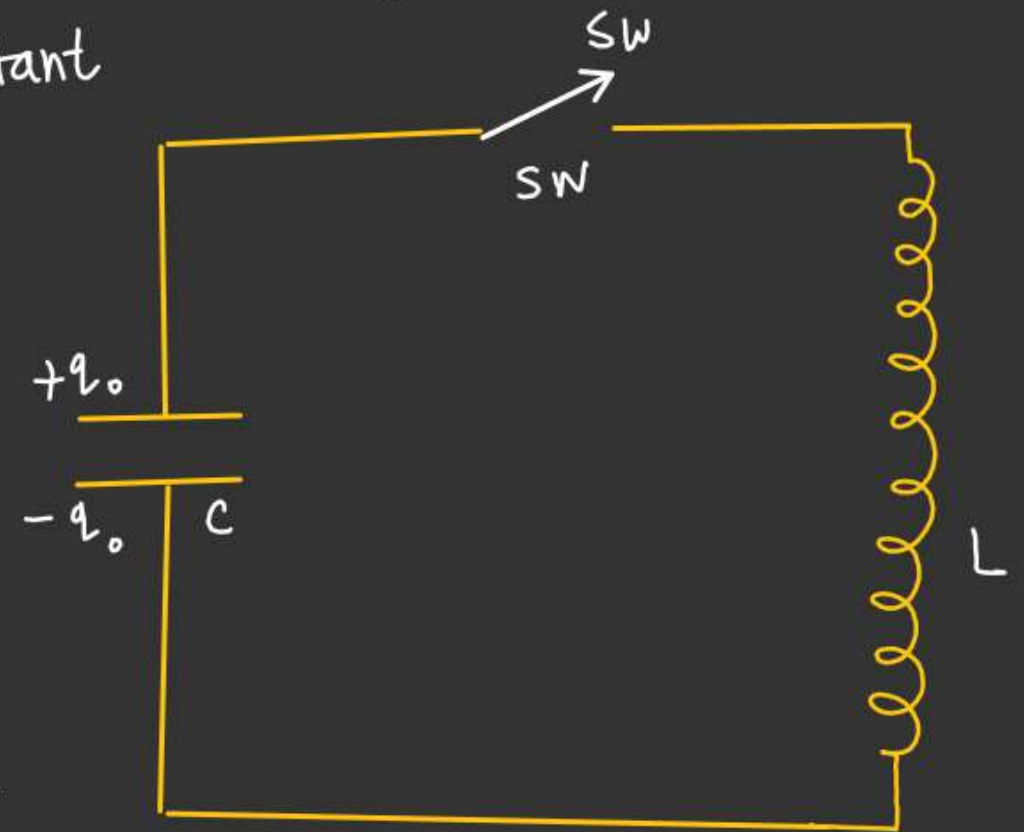

$$U_T = \frac{q^2}{2C} + \frac{1}{2} L i^2$$

$$\frac{dU_T}{dt} = 0 \quad [U_T = \text{Constant}]$$

$$0 = \frac{1}{2C} (2q) \left(\frac{dq}{dt} \right) + \frac{1}{2} L (2i) \left(\frac{di}{dt} \right)$$

$$0 = \frac{q}{C} \left(\frac{dq}{dt} \right) + L i \frac{d}{dt} \left(\frac{dq}{dt} \right)$$

$$-\cancel{\frac{q}{C} \left(\frac{dq}{dt} \right)} = L i \left(\frac{d^2 q}{dt^2} \right)$$

$$\frac{d^2 q}{dt^2} = -\frac{1}{LC} q$$

$$\omega^2$$

$$q = q_0 \sin(\omega t + \phi)$$

$$i = i_0 \sin \omega t$$

$$\text{Maximum current} \leftarrow i_0 = \frac{q_0}{\sqrt{LC}}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

$$\phi = ?$$

$$\text{At } t=0, q = q_0$$

$$q_0 = q_0 \sin \phi$$

$$\sin \phi = 1$$

$$\phi = \pi/2$$

$$q = q_0 \sin(\omega t + \frac{\pi}{2})$$

$$q = q_0 \cos \omega t$$

$$i = -\frac{dq}{dt}$$

$$i = q_0 \omega \sin \omega t$$

$$\leftarrow i = \frac{q_0}{\sqrt{LC}} \sin \omega t$$

Energy in LC oscillation

$$U_L = \frac{1}{2} L i^2$$

$$I_0 = \frac{q_0}{\sqrt{LC}}$$

$$U_L = \frac{1}{2} L I_0^2 \sin^2 \omega t$$

$$U_L = \frac{1}{2} \frac{q_0^2}{C} \sin^2 \omega t$$

$$U_C = \frac{q^2}{2C} = \frac{q_0^2}{2C} \cos^2 \omega t$$

$$U_C = \frac{q_0^2}{2C} \cos^2 \omega t$$

At $t = t$

$$U_L + U_C = \frac{q_0^2}{2C}$$

Minimum time when

$$U_L = U_C$$

$$\frac{q_0^2}{2C} \sin^2 \omega t = \frac{q_0^2}{2C} \cos^2 \omega t$$

$$\omega t = \frac{\pi}{4}$$


$$t = \frac{\pi}{4\omega}$$


$$\Rightarrow t = \frac{\pi}{4} \sqrt{LC}$$

$$T = \frac{2\pi}{\omega}$$

$$t = \frac{T}{4} = \left(\frac{1}{2\omega} \right)$$

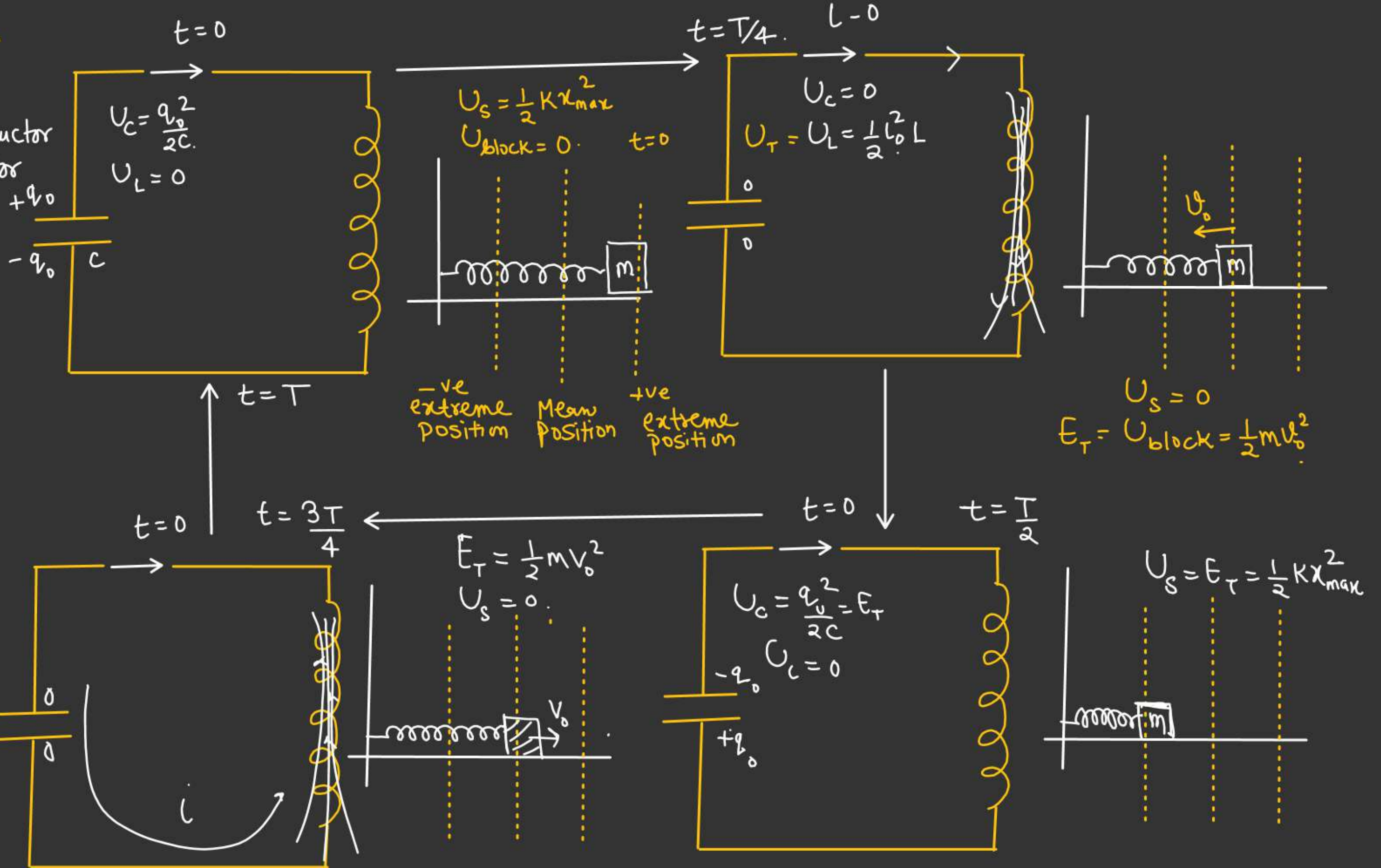Block \rightarrow Inductor
Spring \rightarrow Capacitor



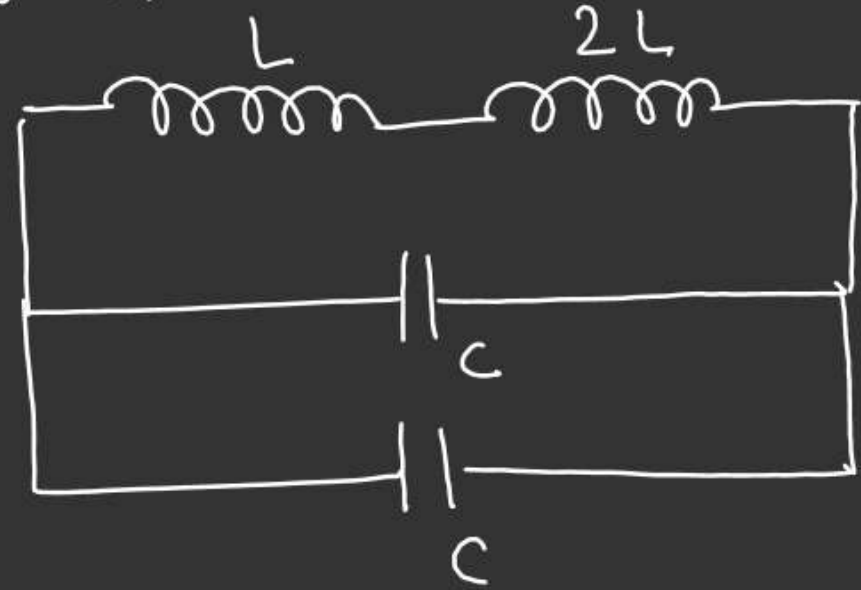$f = ??$ 

$$L_{eq} = 3L$$

$$C_{eq} = 2C$$


$$\omega = \frac{1}{\sqrt{6LC}} \Rightarrow 2\pi f = \frac{1}{\sqrt{6LC}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{6LC}} \checkmark$$

Initially $900\mu\text{F}$ Capacitor charged to 100V battery and $100\mu\text{F}$ is uncharged.

S_2 Closed for t_2 time, after which it is opened at the same time S_1 is closed for t_1 time. & then opened. it is found that voltage across $100\mu\text{F}$ is 300V .

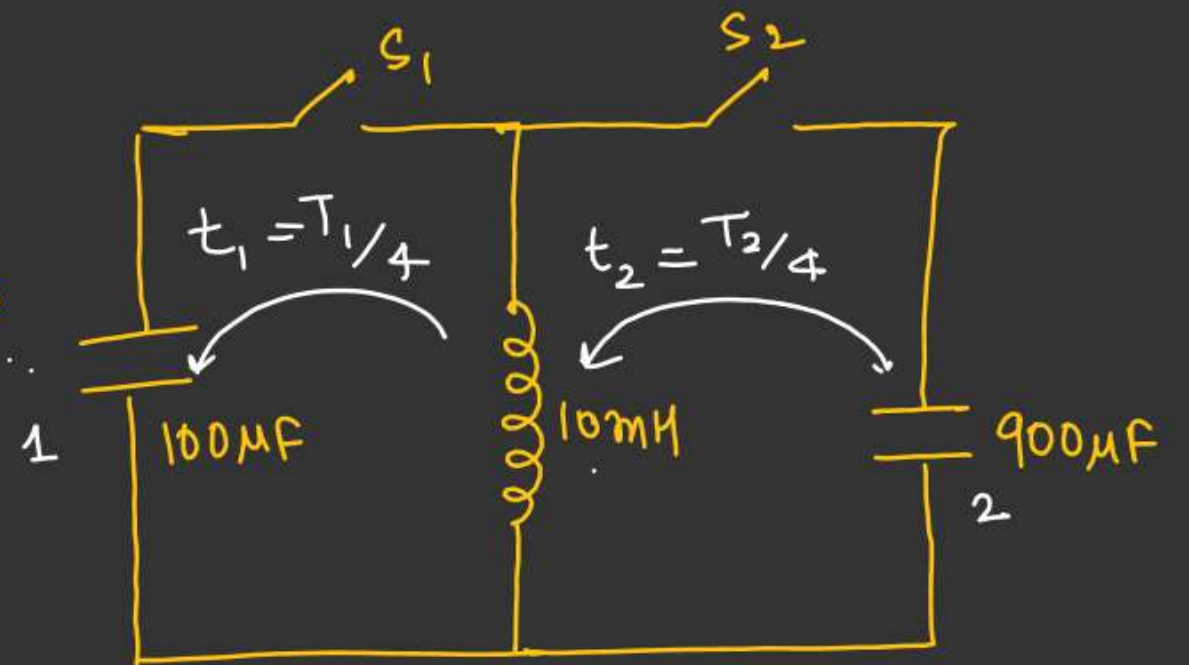
Find min. possible value of t_1 and t_2 .



Q4: Charge on $900\mu\text{F} = 900 \times 10^{-6} \times 100$
 $= 9 \times 10^{-2} \text{C}$

$$T_1 = \frac{2\pi}{\omega}$$

$$T_1 = 2\pi(\sqrt{LC})$$

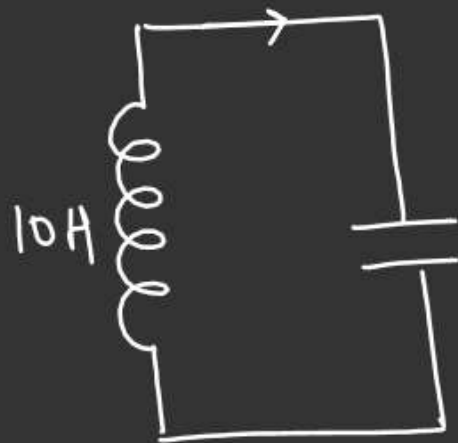

Energy in Capacitor 2

$$= \frac{1}{2} \times 900 \times 10^{-6} \times (100)^2$$

$$= \frac{9}{2} = 4.5 \text{J}$$

$$U_{C_1} = \frac{1}{2} \times 100 \times 10^{-6} \times (300)^2$$

$$U_{C_1} = \frac{9}{2} = 4.5 \text{J}$$

Ckt shown in fig in steady state with S_1 closed.

At $t=0$, S_1 is opened and S_2 is closed.

- Derive charge on Capacitor as a function of time. ✓
- The first instant 't' when energy of inductor become $\frac{1}{3}$ rd of that in the Capacitor. }


When S_1 Closed

$$20 - \frac{q_0}{2} - \frac{q_0}{3} = 0$$

$$20 = \frac{3q_0 + 2q_0}{6}$$

$$120 = 5q_0$$

$$q_0 = 24 \mu C \checkmark$$

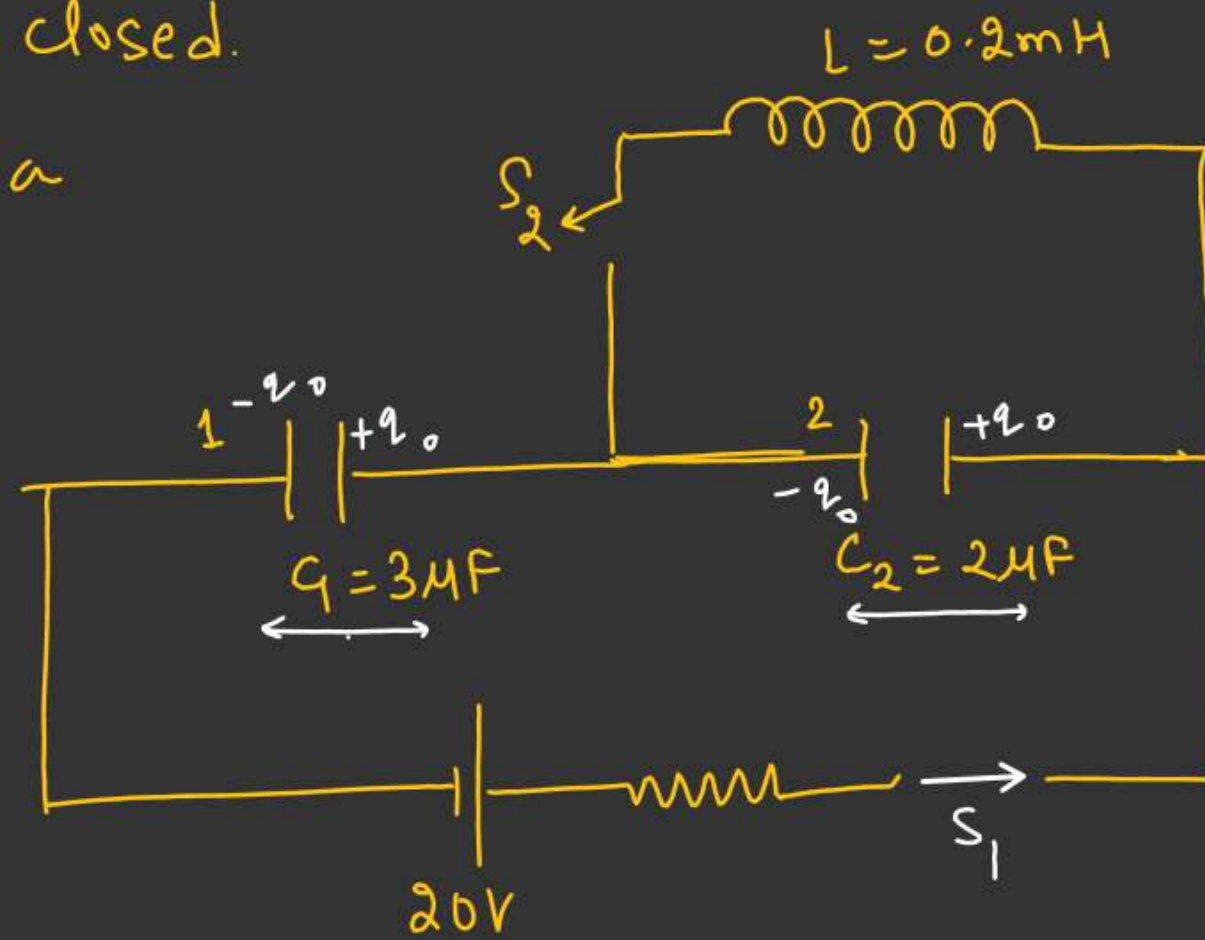

b) The first instant 't' when energy of inductor become $\frac{1}{3}$ rd of that in the Capacitor.

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 10^{-3} \times 2 \times 10^{-6}}}$$

$$\omega = \frac{1}{2 \times 10^{-5}} = 0.5 \times 10^5 = 5 \times 10^4$$


$$q = q_0 \cos \omega t$$

$$q = (24 \times 10^{-6}) \cos[(5 \times 10^4)t]$$

$$U_C = \frac{3}{4} \left(\frac{q_0^2}{2C} \right)$$

$$\frac{q^2}{2C} = \frac{3}{4} \left(\frac{q_0^2}{2C} \right) \Rightarrow t = ??$$

$$10.5 \mu s \text{ Ans}$$

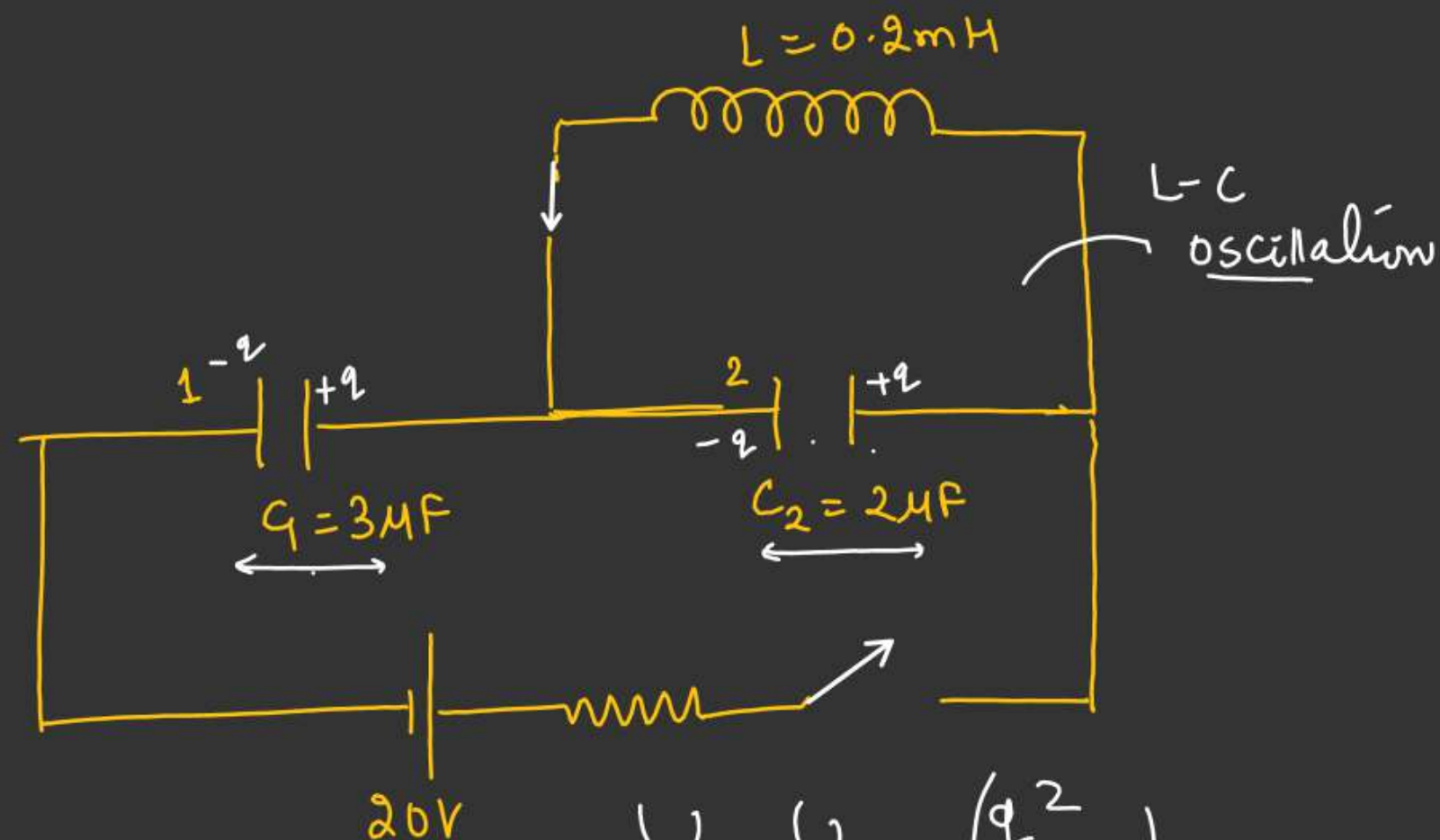

$$U_L + U_C = \frac{q_0^2}{2C} \quad U_C = U_T = \left(\frac{q_0^2}{2C} \right)$$

(According to question)

$$U_L = \left(\frac{U_C}{3} \right)$$

$$\frac{U_C}{3} + U_C = \frac{q_0^2}{2C} \Rightarrow \frac{4U_C}{3} = \frac{q_0^2}{2C}$$