
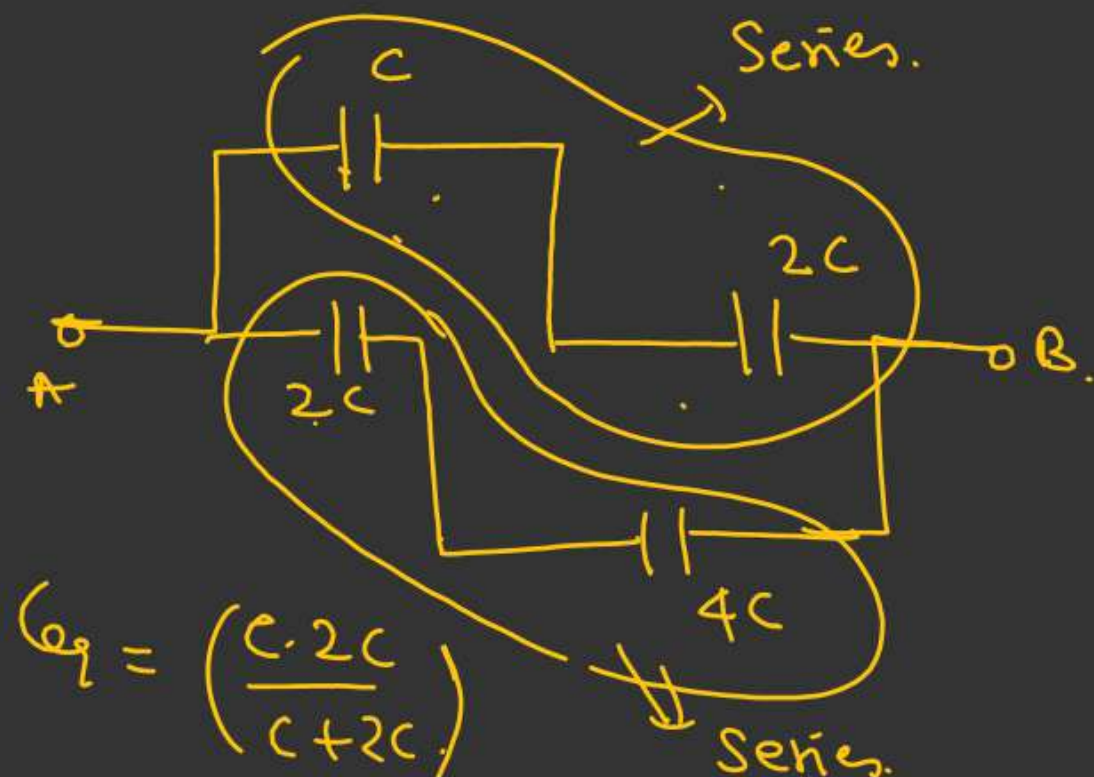
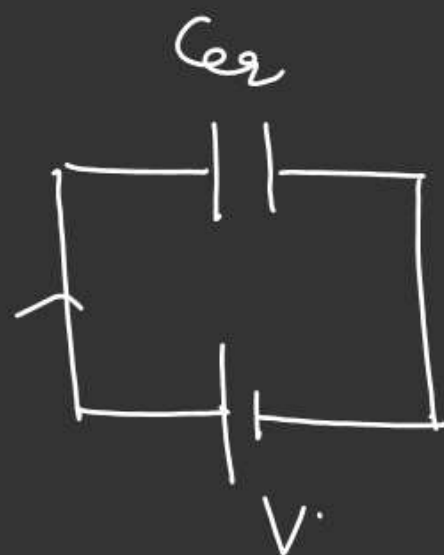


Capacitor

Capacitive ckt

Balance wheat - stone bridge.
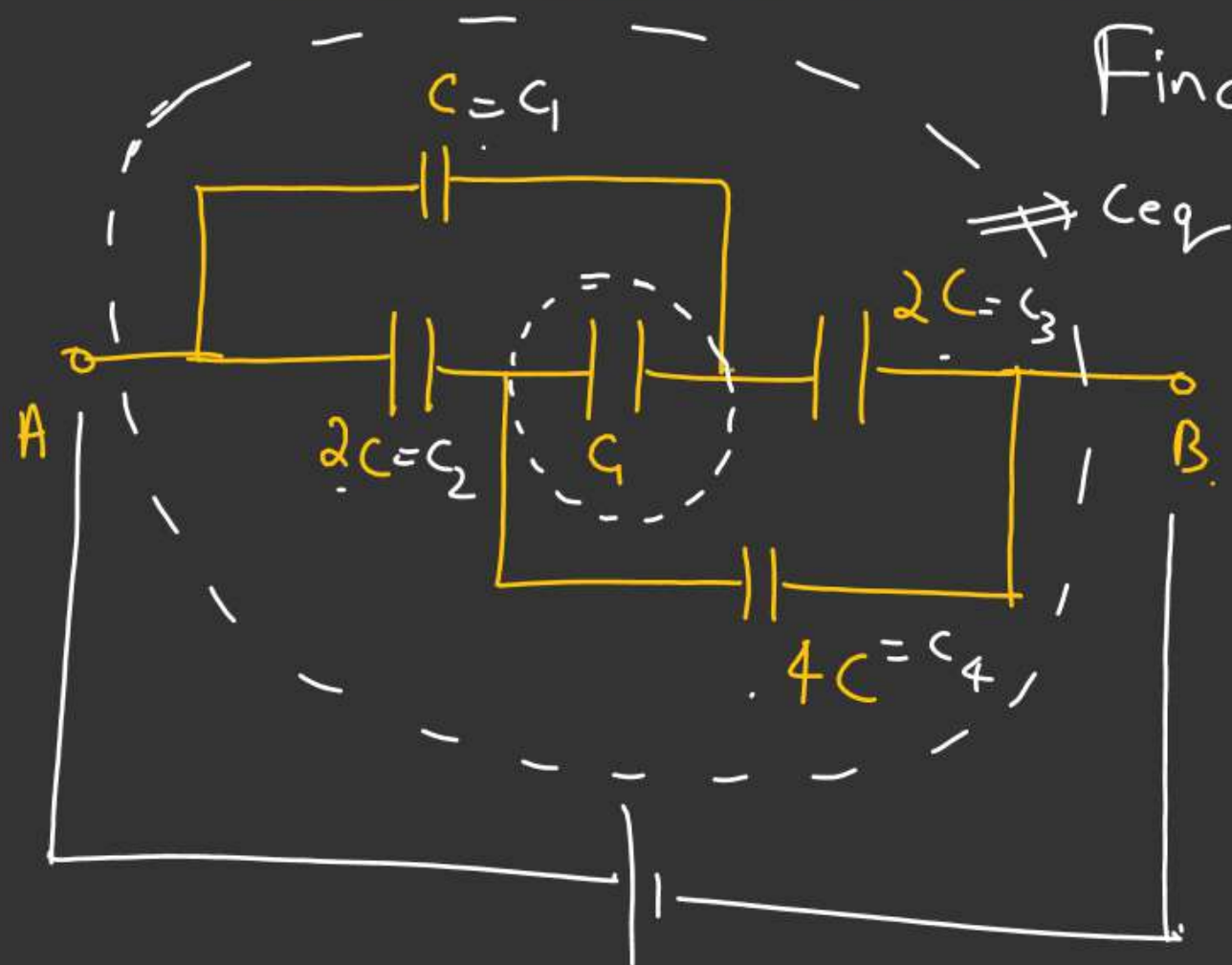
$$\left[\frac{C_1}{C_2} = \frac{C_3}{C_4} \right] = \frac{1}{2}$$




$$C_{eq} = \left(\frac{C \cdot 2C}{C + 2C} \right) + \frac{(2C)(4C)}{(2C + 4C)}$$

$$C_{eq} = \frac{2C^2}{3C} + \frac{8C^2}{6C}$$


$$= \frac{2}{3}C + \frac{4C}{3} = \frac{6C}{3} = 2C$$

Extended Wheat-Stone bridge.


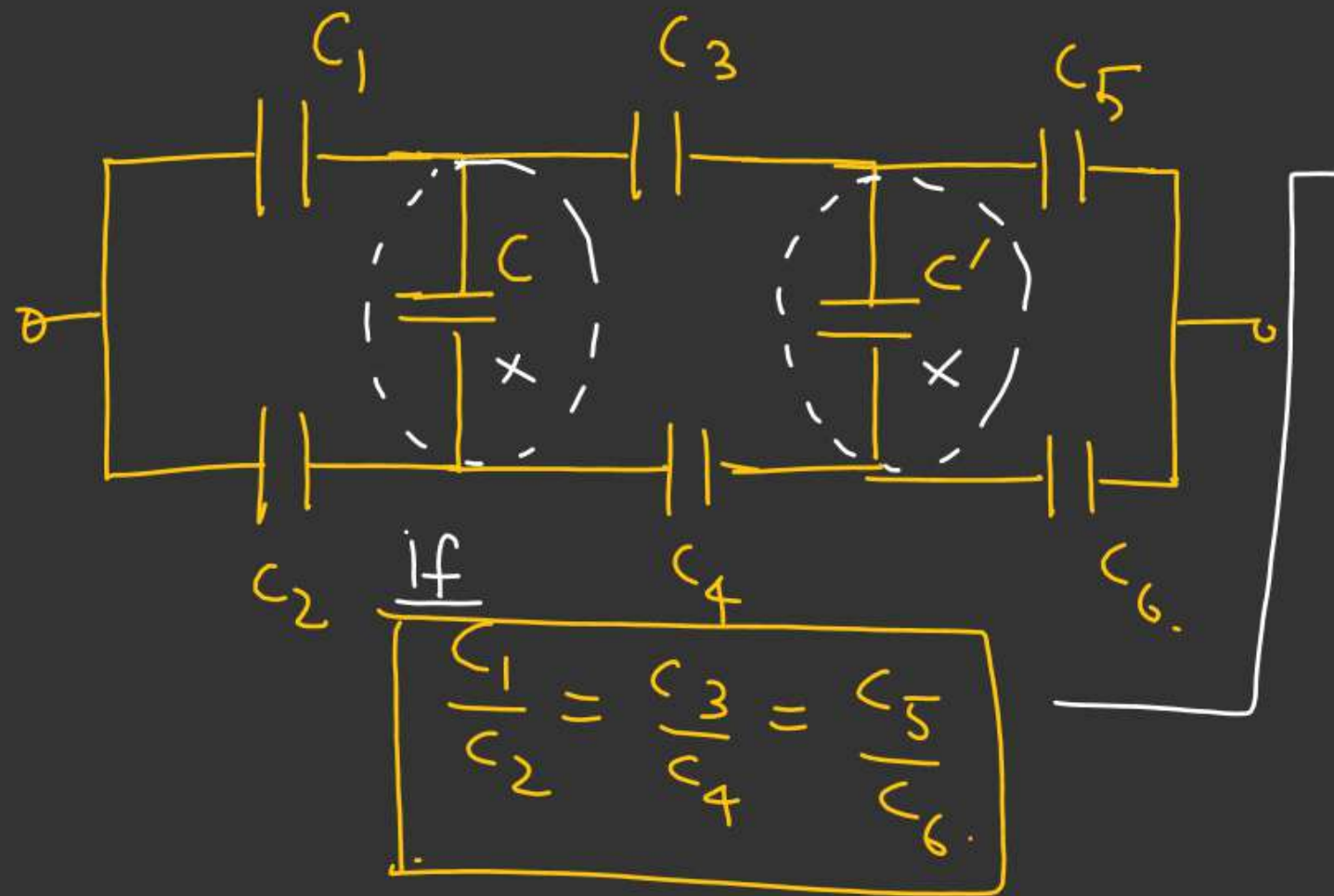
Case-1 :- Horizontal Extended-wheat stone
bridge




Ckt Reduced to

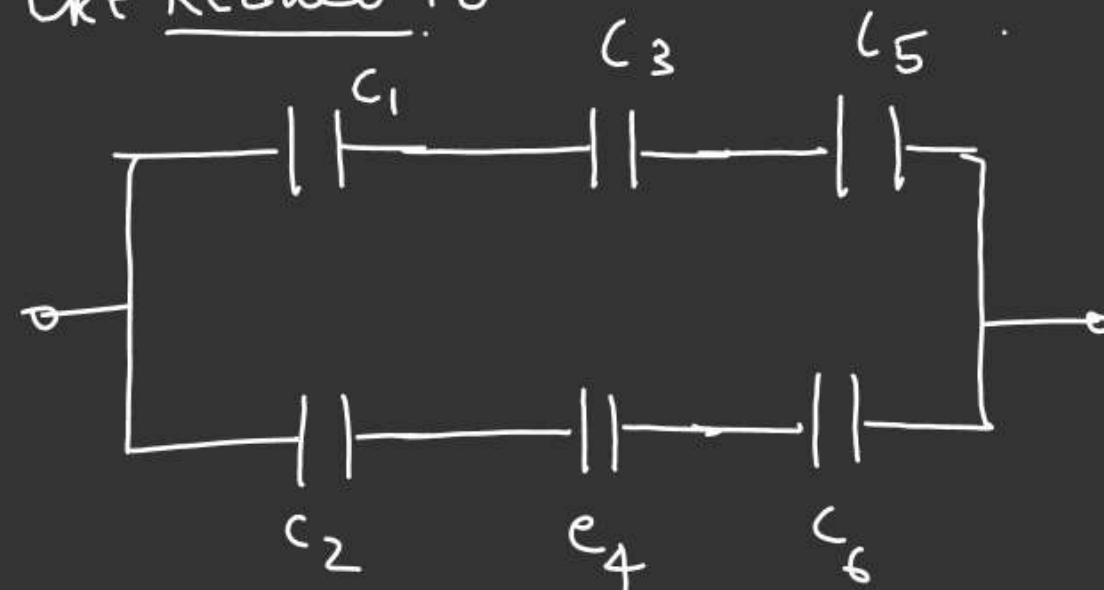

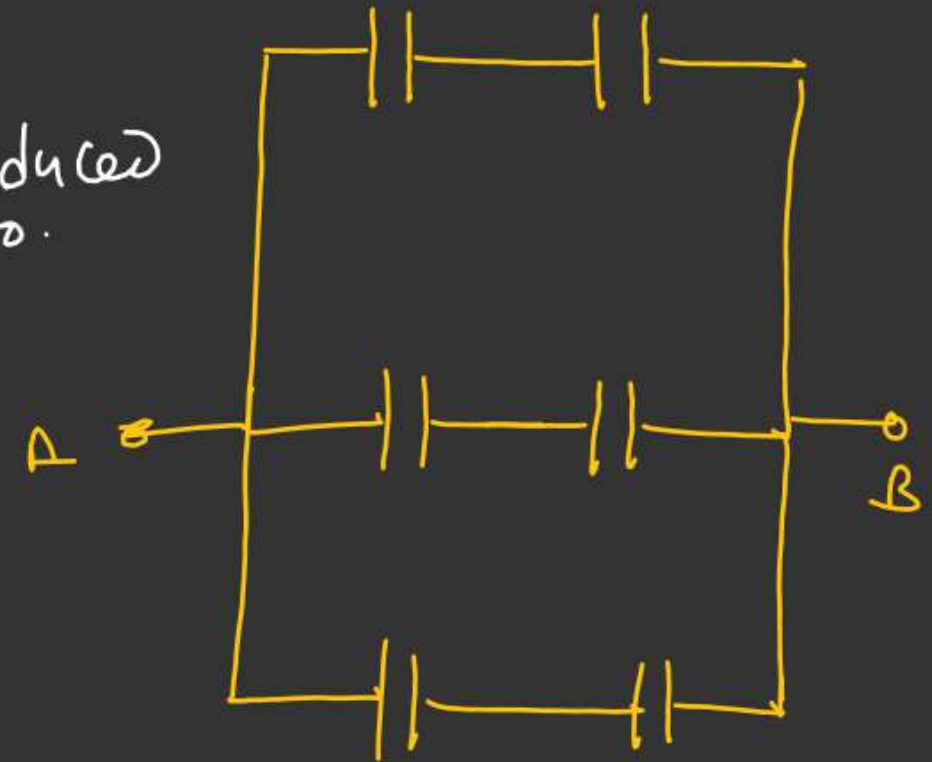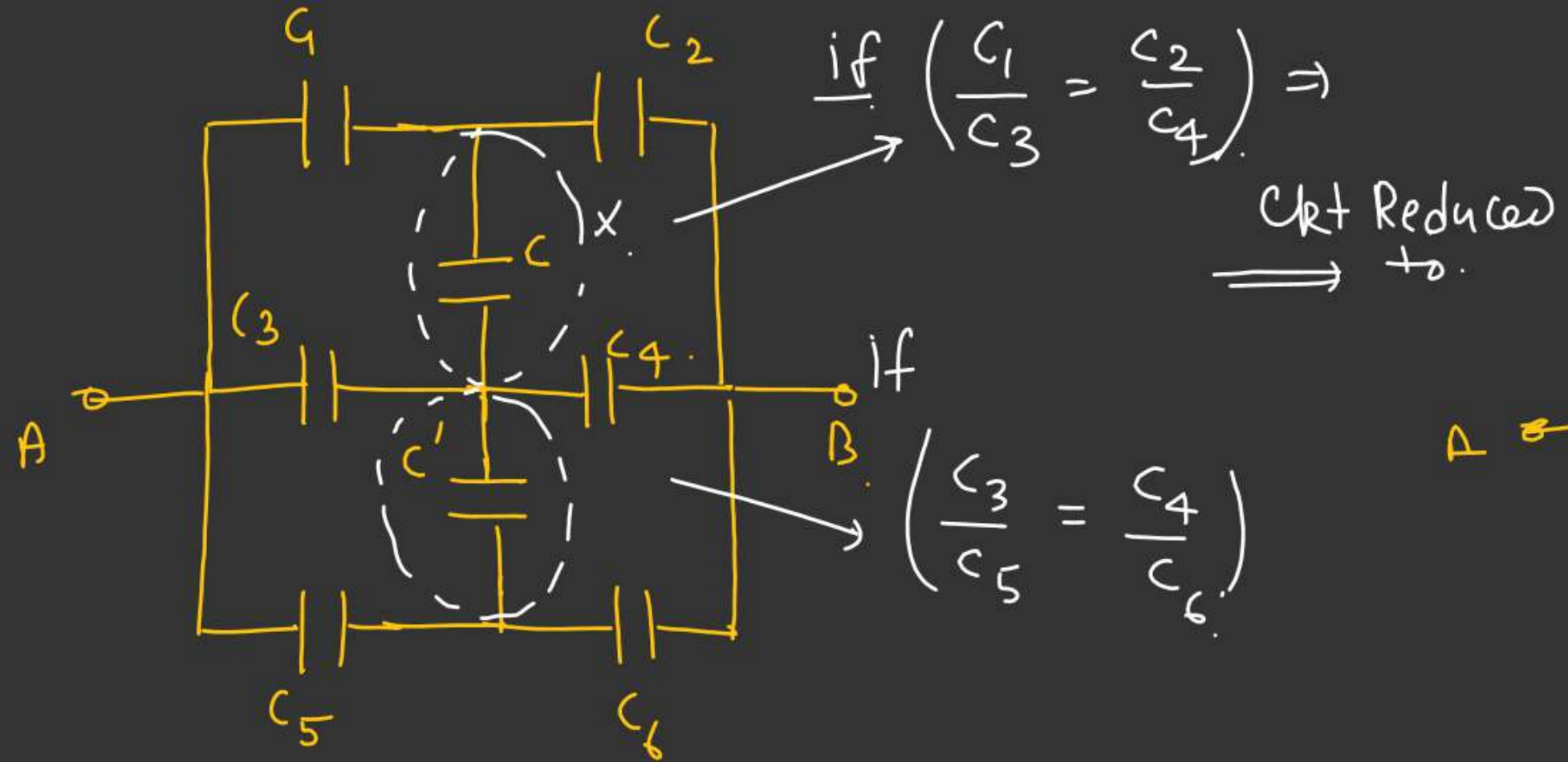Case-2 Vertical Extended Wheatstone bridge:-



Capacitors with diagonal Symmetry! →

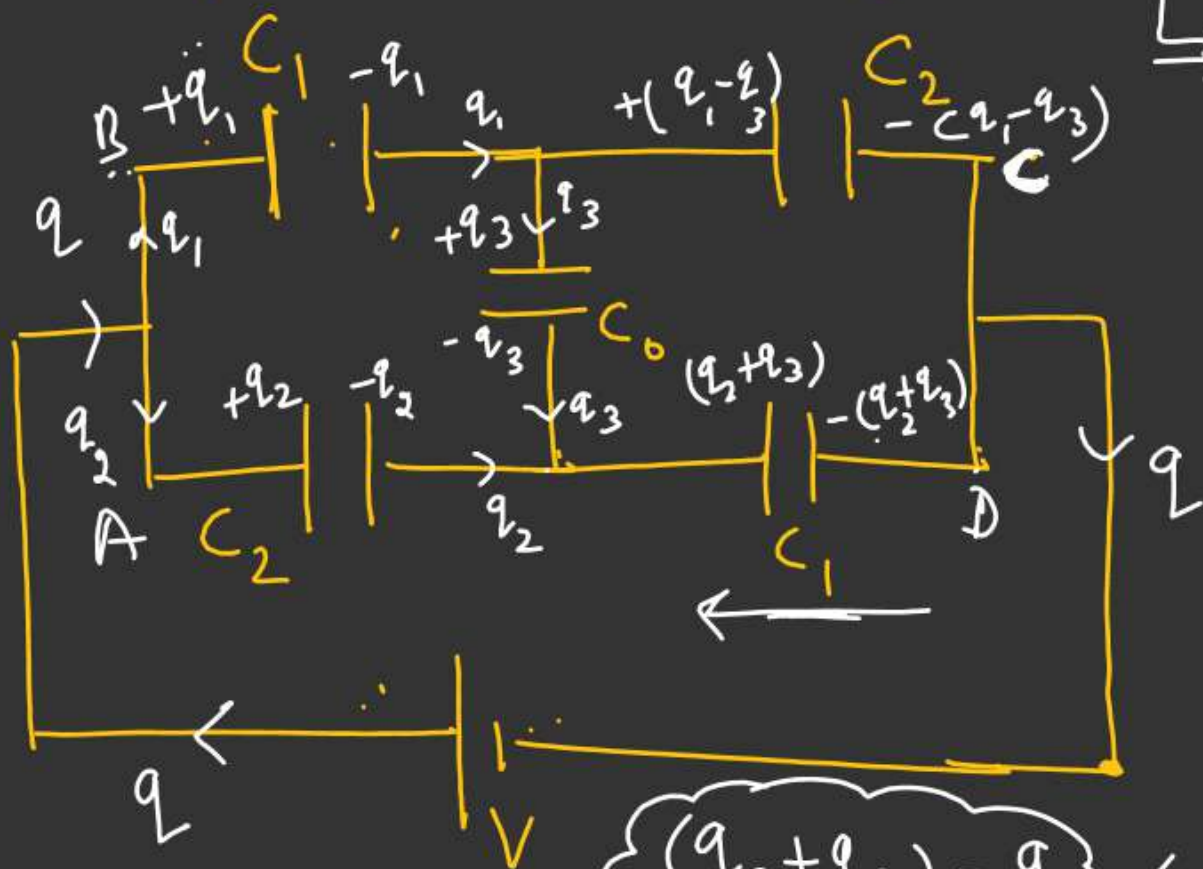

↳ Note! — Capacitors having diagonal Symmetry have Same Charge.

K.V.L in the loop ABCDA:-

$$-\frac{q_1}{C_1} - \frac{(q_1 - q_3)}{C_2} + \frac{(q_2 + q_3)}{C_1} + \frac{q_2}{C_2} = 0$$


$$-\frac{q_1}{C_1} - \frac{q_1}{C_2} + \frac{q_3}{C_2} + \frac{q_2}{C_2} + \frac{q_2 + q_3}{C_1} = 0$$

$$q_1 \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = (q_2 + q_3) \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$


$$q_1 = q_2 + q_3$$

$(q_2 + q_3) = q_1$ ✓✓

#

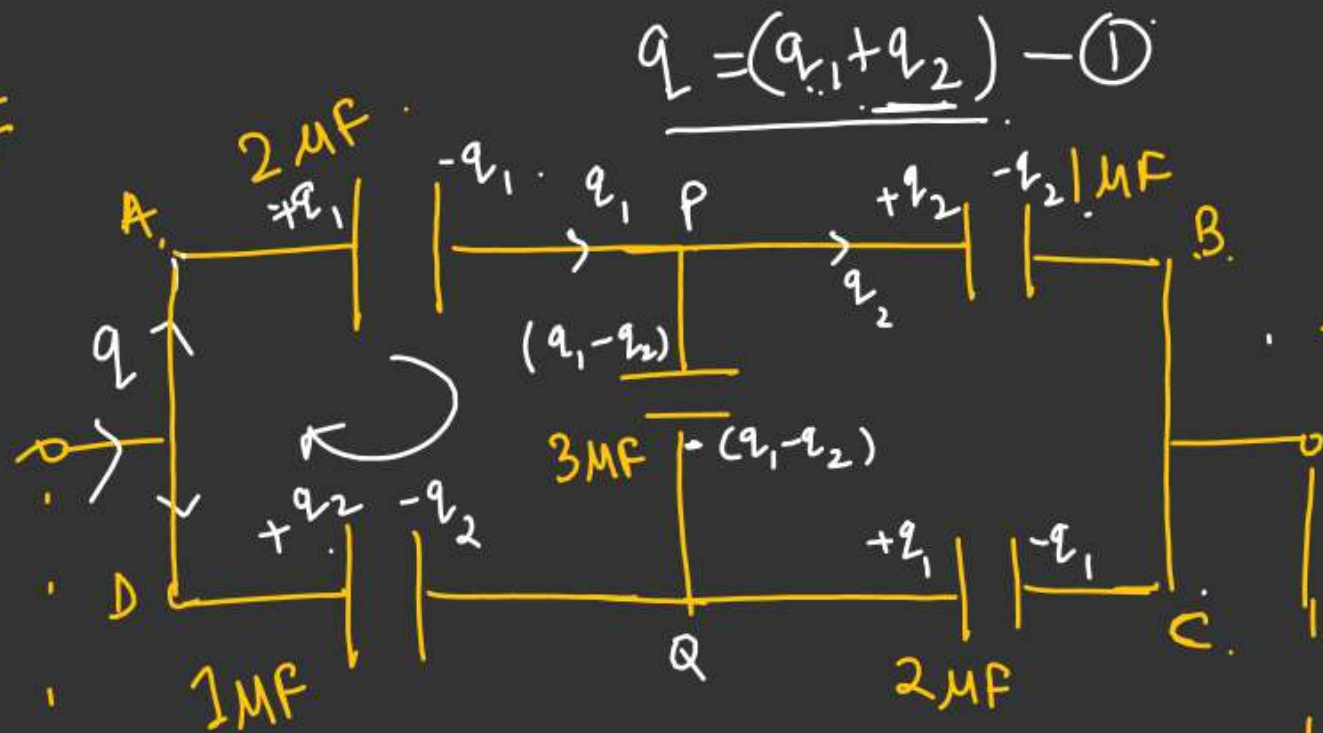

Find $(C_{eq})_{A-B} = ??$

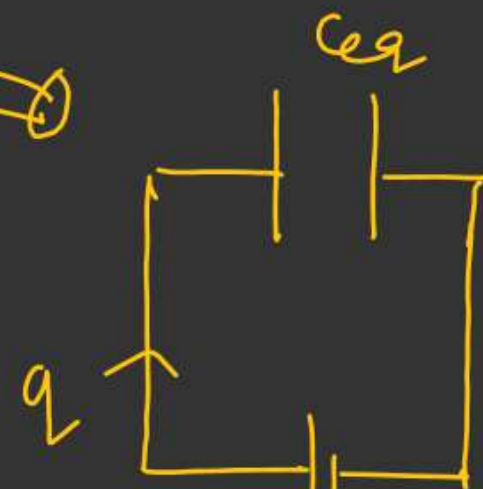

K.V.L in the ABFEA :-

$$-\frac{q_1}{2} - \frac{q_2}{1} + V = 0$$

$$V = \frac{q_1}{2} + \frac{q_2}{1} \quad \text{--- ②}$$

K.V.L in close loop APQDA

$$-\frac{q_1}{2} - \frac{(q_1 - q_2)}{3} + \frac{q_2}{1} = 0$$

$$-\frac{q_1}{2} - \frac{q_1}{3} + \frac{q_2}{3} + q_2 = 0$$

$$\frac{4q_2}{3} = \frac{3q_1 + 2q_1}{6} = \frac{5q_1}{6}$$

$$q_1 = \frac{6}{5} \times \frac{4q_2}{3} = \left(\frac{8q_2}{5}\right) \checkmark$$

$$\boxed{q = C_{eq} \cdot V} \checkmark$$

↑

$$q = \frac{8q_2}{5} + q_2$$

$$q = \frac{13q_2}{5}$$

$$q_2 = \left(\frac{5q}{13}\right), \quad q_1 = \frac{8}{5} \times \frac{5q}{13} = \frac{8q}{13}$$

Put the value of q_1 & q_2 in ①

$$V = \frac{5q}{13} + \frac{1}{2} \left(\frac{8q}{13}\right)$$

$$V = \left(\frac{5q}{13} + \frac{4q}{13}\right) = \frac{9q}{13}$$




$$V = \frac{q}{13}$$

$$q = \frac{13}{9} V$$

$$q = C_{eq} \cdot V$$

$$C_{eq} = \frac{13}{9} \mu F$$

→ (Equivalent Capacitance of the Ckt)

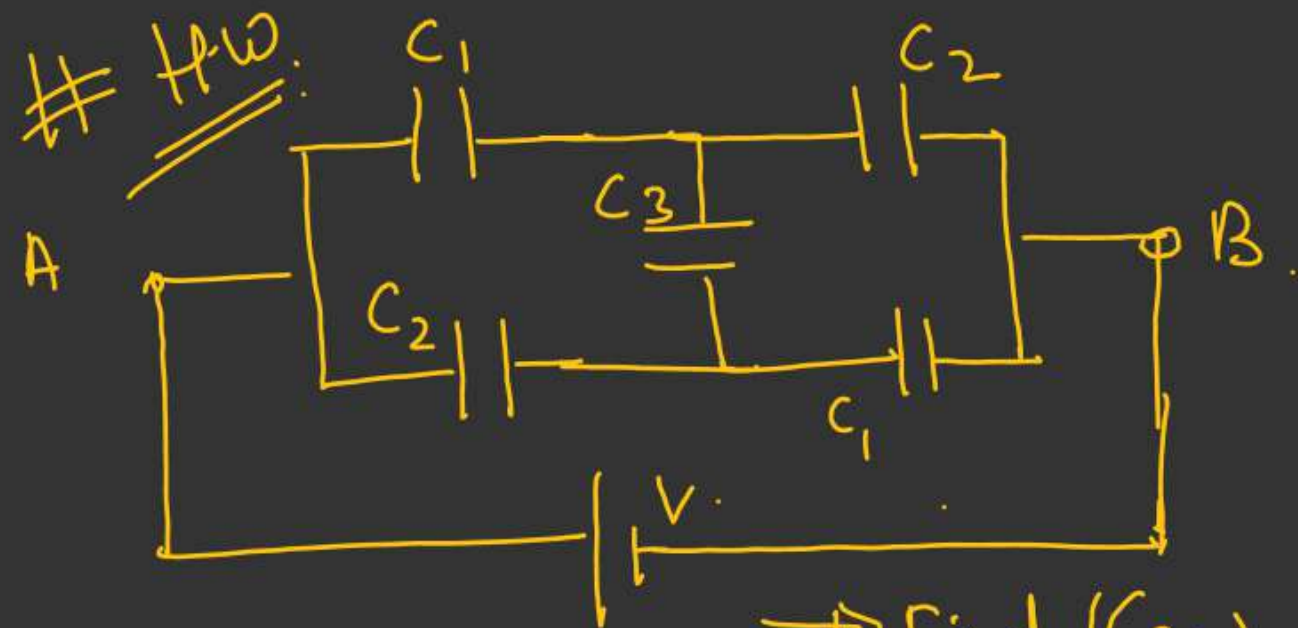

⇒ Find $(C_{eq})_{A-B} = ??$

Nodal method

$$q = CV$$

CAPACITOR

$$(x-20)\text{Volt} \quad | \quad 20\text{V}$$

Q.1 In the circuit shown in Fig. determine charge on each capacitor.

Steps! → ① Assume any node of junction as reference potential i.e. 0.

② Write the potential across the Capacitor w.r.t reference zero potential.

③ Apply (K.C.L.) By junction law at c:


$$-8x = 20$$

$$x = -\frac{20}{8}$$

$$x = \left(-\frac{5}{2}\right) = -2.5\text{Volt}$$

$$-2(x+20) - 4x = (x-10)2$$

$$q_1 + q_2 = q_3$$

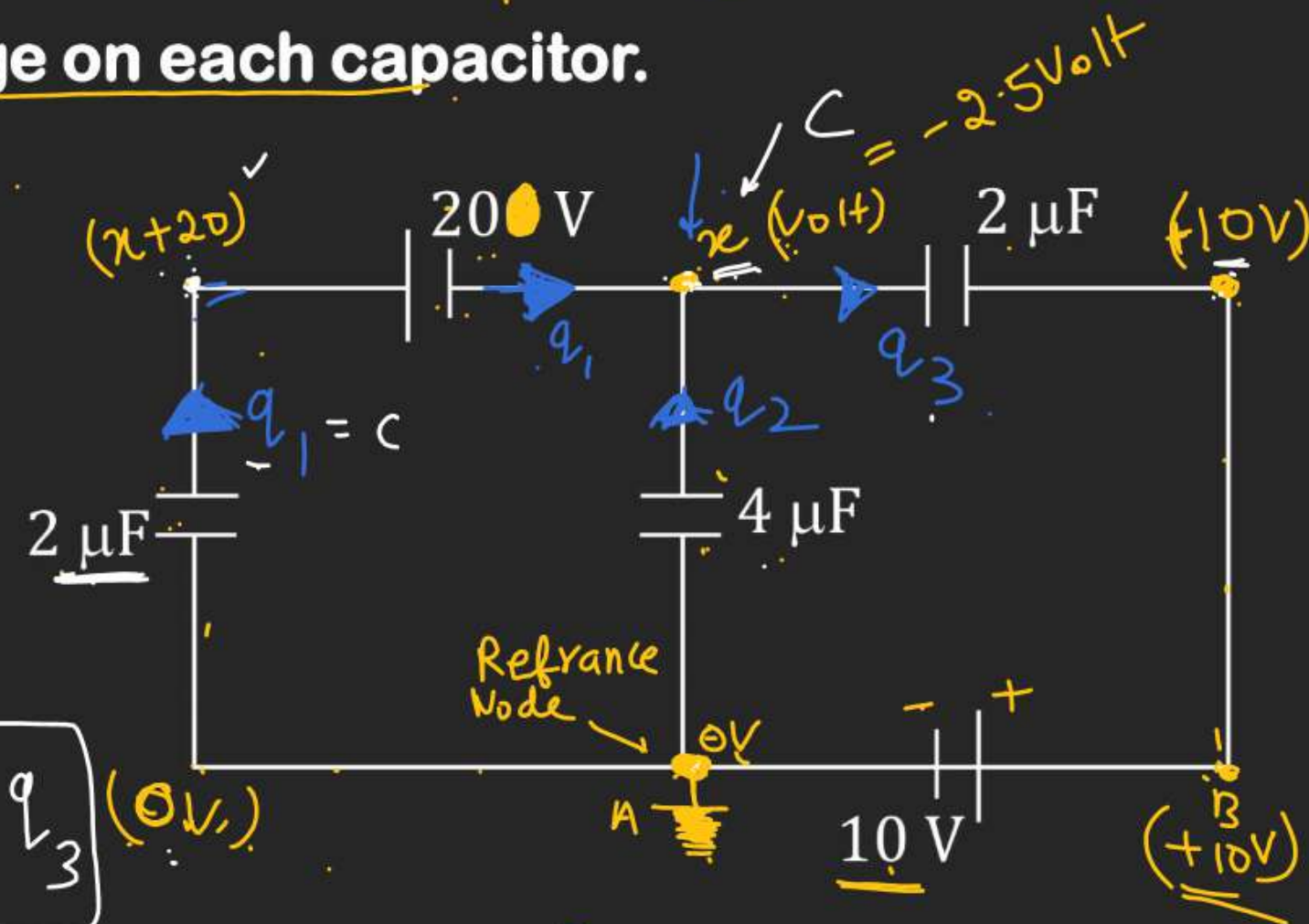

$$\begin{cases} V_A + 10 = V_B \\ V_B = V_A + 10 \\ = 0 + 10 \end{cases}$$