

$$\# \quad y_1 = \underline{A_1} \sin \omega t$$

$$y_2 = \underline{A_2} \sin(\omega t + \phi)$$

[Take reference vector
whose $\phi = 0$.

[Assume amplitudes as
vector]


By Superposition

$$y_R = y_1 + y_2$$

$$= A_1 \sin \omega t + A_2 \sin(\omega t + \phi)$$

$$y_R = \underline{A_R} \sin(\omega t + \phi')$$

Phasor! \rightarrow

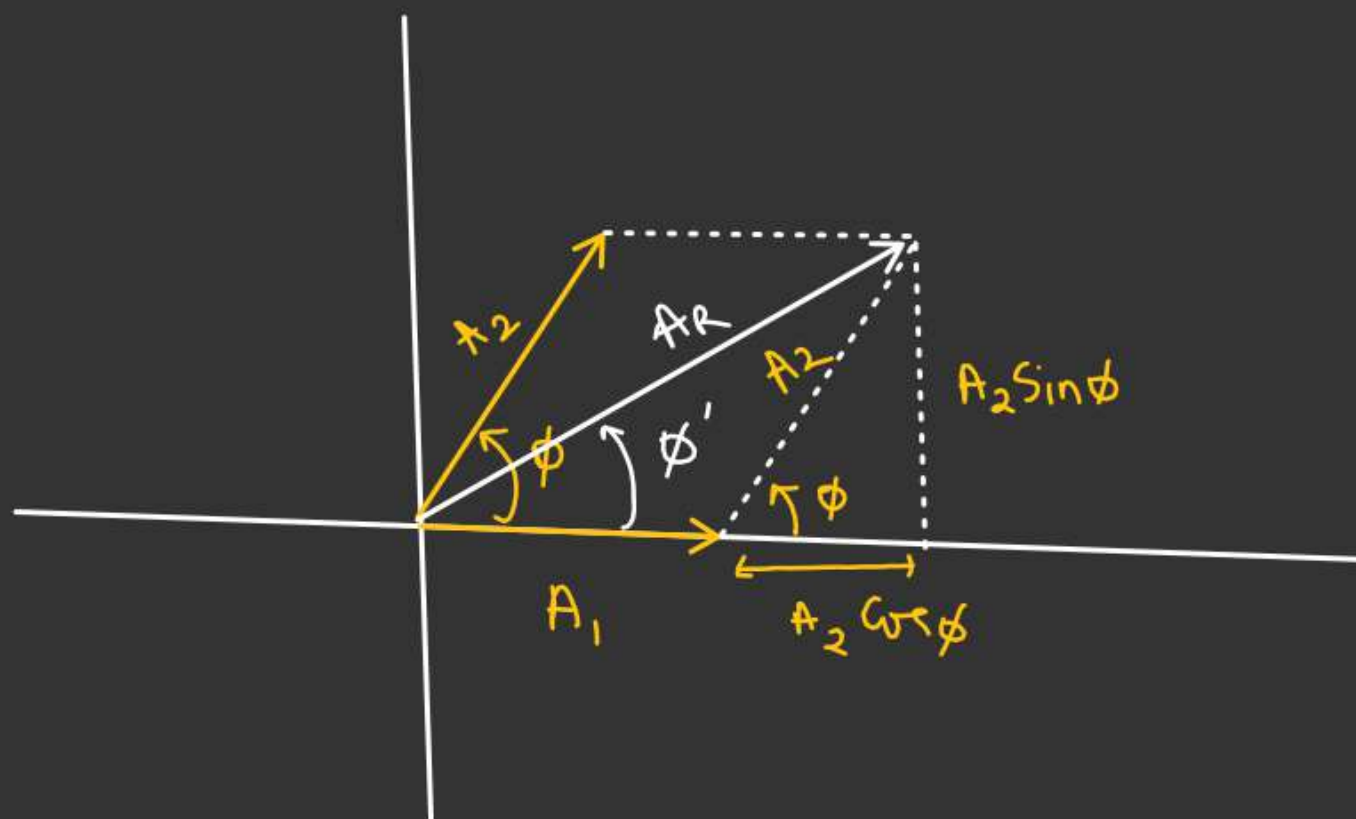

$$A_R = \sqrt{A_1^2 + A_2^2 + 2A_1A_2 \cos \phi}$$

$$\tan \phi' = \left(\frac{A_2 \sin \phi}{A_1 + A_2 \cos \phi} \right) \Rightarrow \phi' = \tan^{-1} \left(\frac{A_2 \sin \phi}{A_1 + A_2 \cos \phi} \right)$$

Q.2

$$y_1 = A \sin \omega t$$

$$y_2 = A \sin(\omega t + \pi/3)$$


$$y_3 = A \sin(\omega t - 2\pi/3)$$

$$y_R = (y_1 + y_2 + y_3)$$

$$\Downarrow$$

$$y_R = A_R \sin(\omega t + \phi)$$

$$y_R = \underline{A \sin \omega t}$$

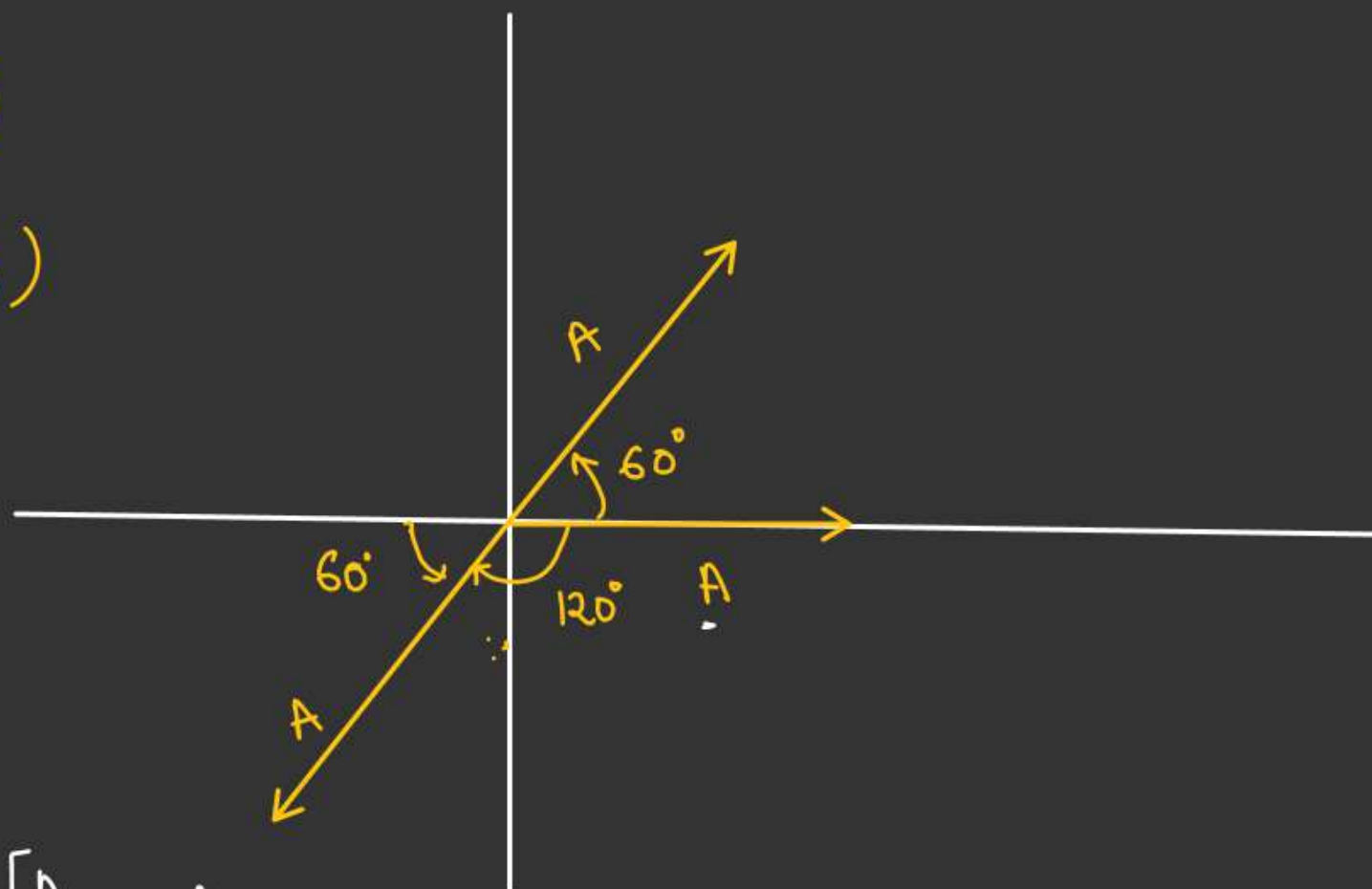

$$\begin{cases} A_R = A \\ \phi = 0^\circ \end{cases}$$

$$\# \quad y_1 = A \sin \omega t$$


$$y_2 = A \sin(\omega t + \pi/6)$$

$$y_3 = A \sin(\omega t + 2\pi/3)$$

$$y_R = y_1 + y_2 + y_3$$

$$y_R = A_R \sin(\omega t + \phi)$$
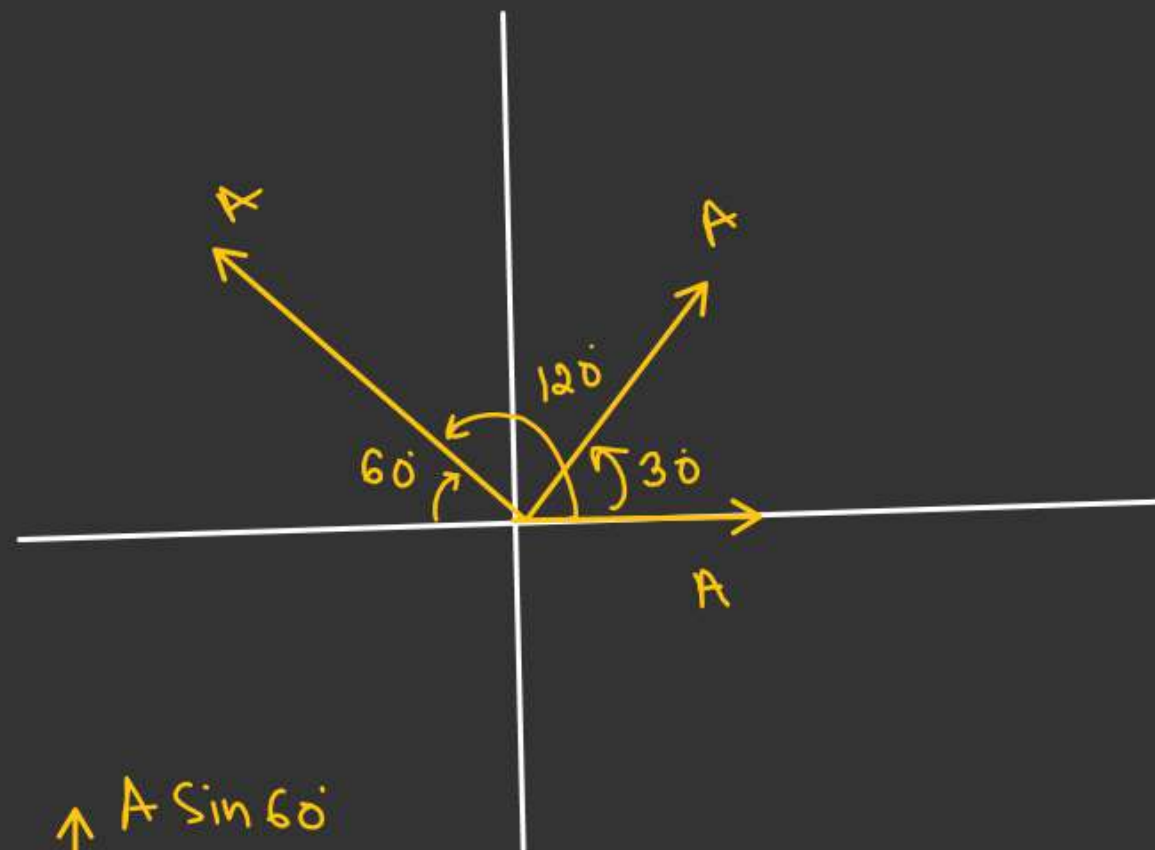
$$y_R = (\sqrt{3}+1) \frac{A}{\sqrt{2}} \sin(\omega t + \pi/4)$$



$$A_R = \sqrt{A_x^2 + A_y^2}$$

$$= \sqrt{2}(\sqrt{3}+1) \frac{A}{2}$$

$$\tan \phi = \frac{A_y}{A_x}$$

$$\phi = 45^\circ$$

$$A_x = A + \frac{\sqrt{3}A}{2} - \frac{A}{2}$$


$$= (\sqrt{3}+1) \frac{A}{2}$$

$$A_y = \frac{\sqrt{3}A}{2} + \frac{A}{2}$$

$$= (\sqrt{3}+1) \frac{A}{2}$$


$$\# \quad I = I_1 \sin \omega t + I_2 \cos \omega t$$
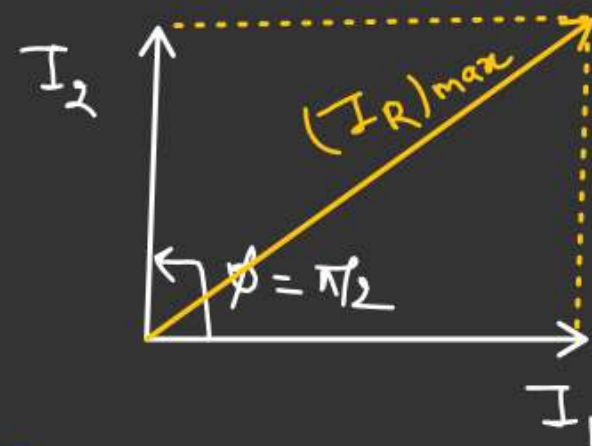
$$I = \underline{I_1} \sin \omega t + I_2 \sin \left(\omega t + \frac{\pi}{2} \right)$$



$$(I_R)_{\max} = \sqrt{I_1^2 + I_2^2}$$

$$I_{\text{rms}} = \frac{(I_R)_{\max}}{\sqrt{2}} = \sqrt{\frac{I_1^2 + I_2^2}{2}}$$

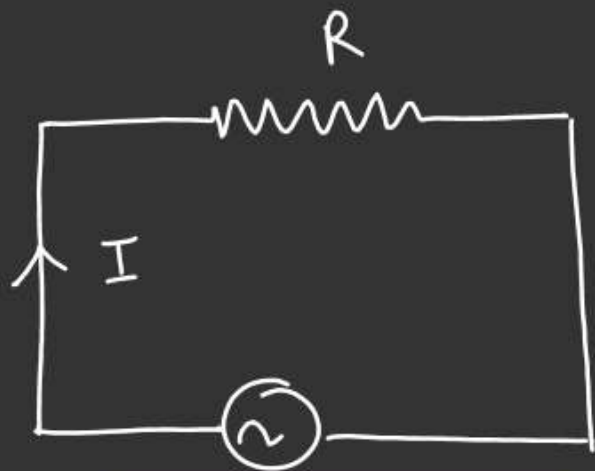A.C Ckt! →⇒ Purely resistive ckt

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$


$$\mathcal{E}_0 \sin \omega t = i R$$

$$i = \frac{\mathcal{E}_0 \sin \omega t}{R}$$

$$i = I_0 \sin \omega t$$


$$\phi = 0$$

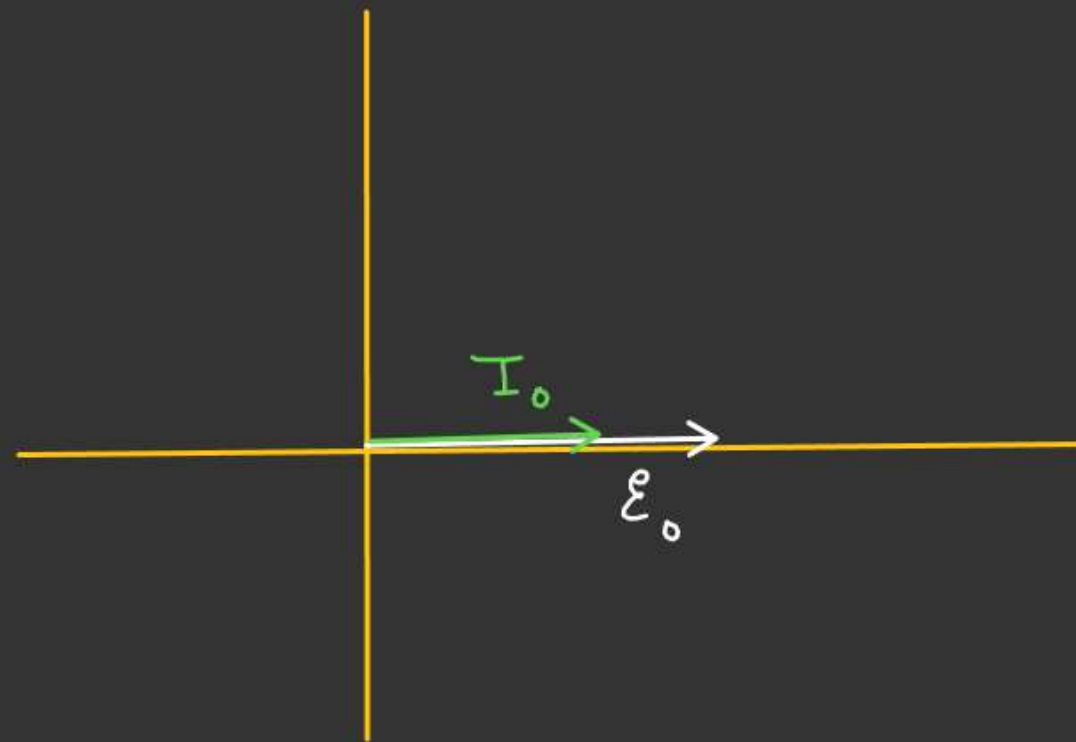Note:- In purely resistive ckt voltage and current both are in the same phase.



Purely Capacitive Ckt

Capacitance
= C

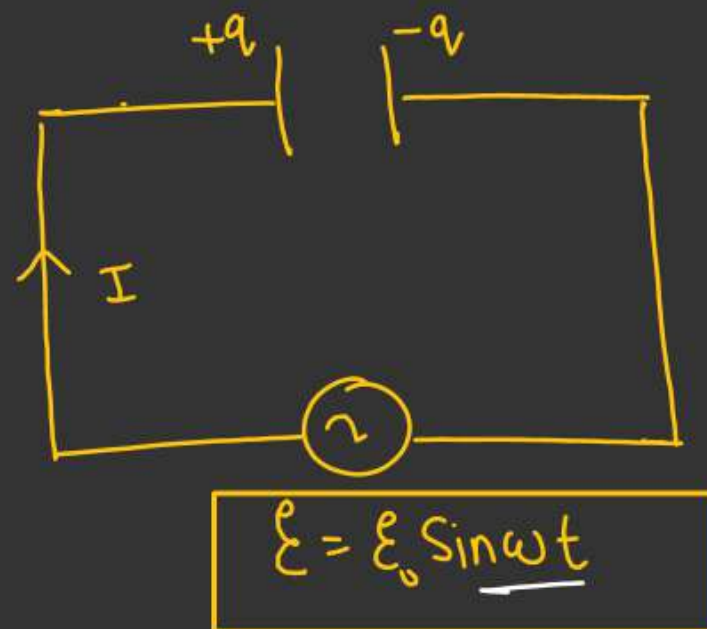

$$i = \frac{dq}{dt}$$

$$\mathcal{E}_0 \sin \omega t - \frac{q}{C} = 0$$

$$\mathcal{E}_0 \sin \omega t = \frac{q}{C}$$

Differentiating both side w.r.t time

$$\mathcal{E}_0 \omega \cos \omega t = \frac{1}{C} \left(\frac{dq}{dt} \right)$$

$$\hat{i} = \mathcal{E}_0 (\omega C) \cos \omega t$$

$$i^0 = \frac{\mathcal{E}_0}{\left(\frac{1}{\omega C} \right)} \cos \omega t$$

$$X_C = \left(\frac{1}{\omega C} \right)$$

Unit $\rightarrow \Omega$

Reactance of
Capacitive Ckt.

$$i^0 = \frac{\mathcal{E}_0}{X_C} \sin \left(\omega t + \frac{\pi}{2} \right)$$

(Current leading the
Voltage by 90°)




$$\phi = \left(+\frac{\pi}{2} \right)$$

Purely Capacitive ckt

$$E = E_0 \sin \omega t$$

$$I = \frac{E_0}{X_c} \sin(\omega t + \frac{\pi}{2})$$


$$(X_c = \frac{1}{\omega c})$$

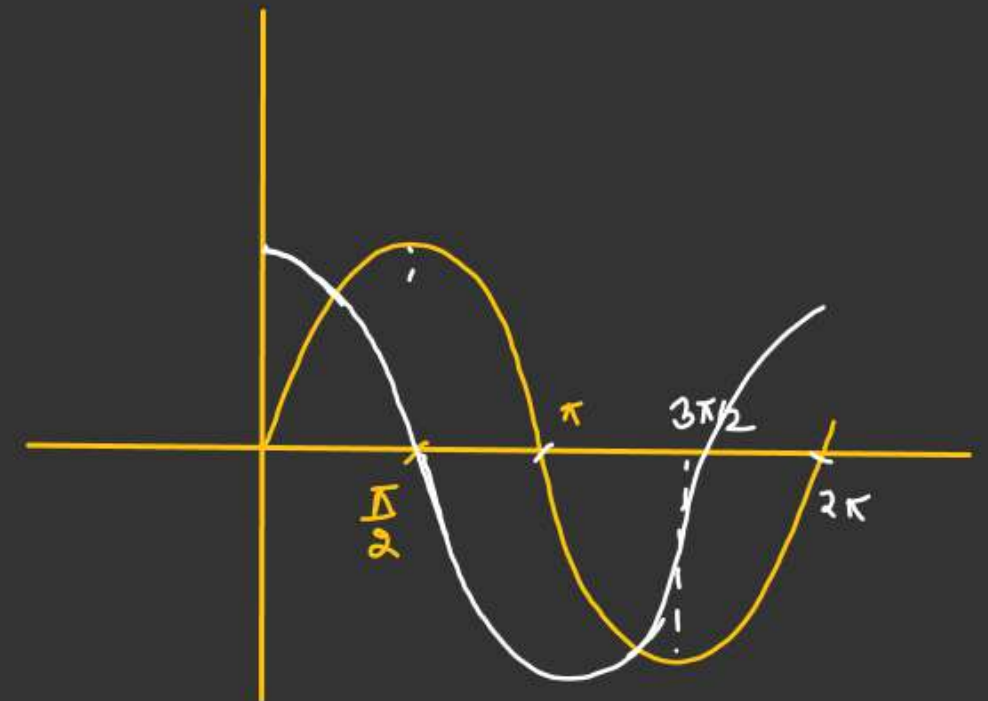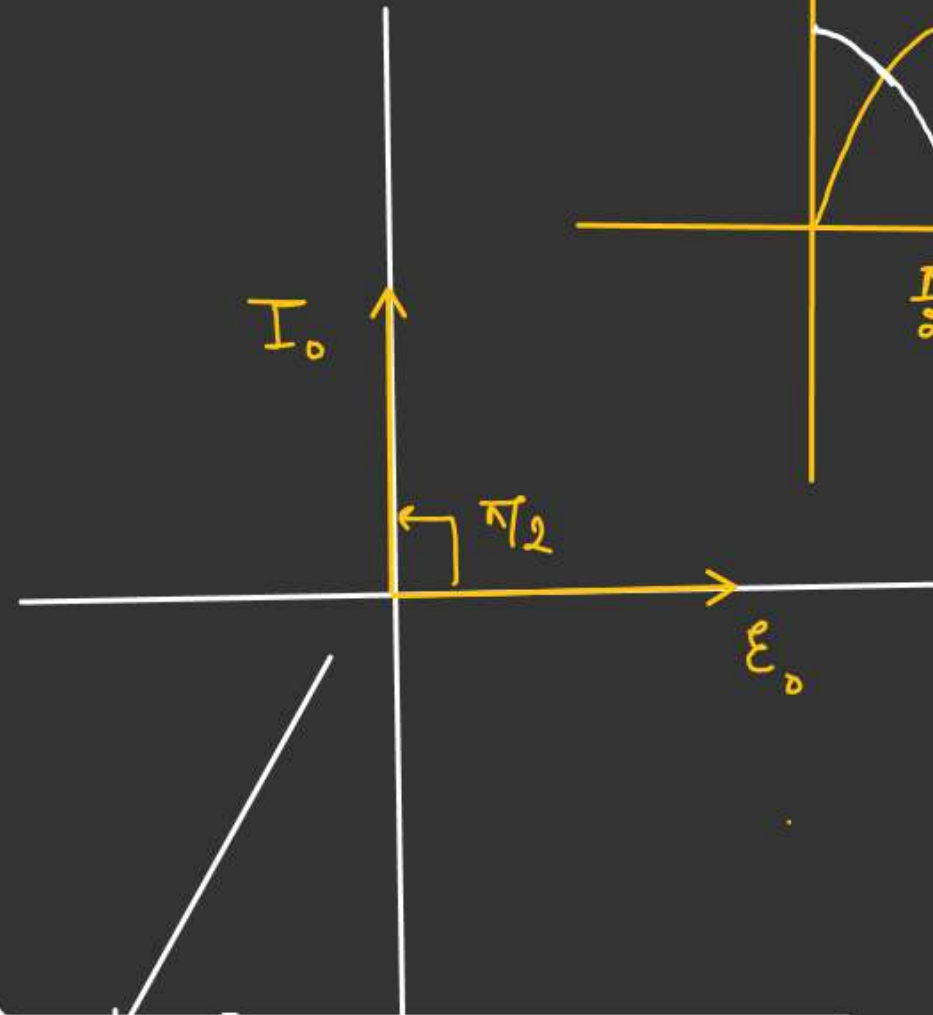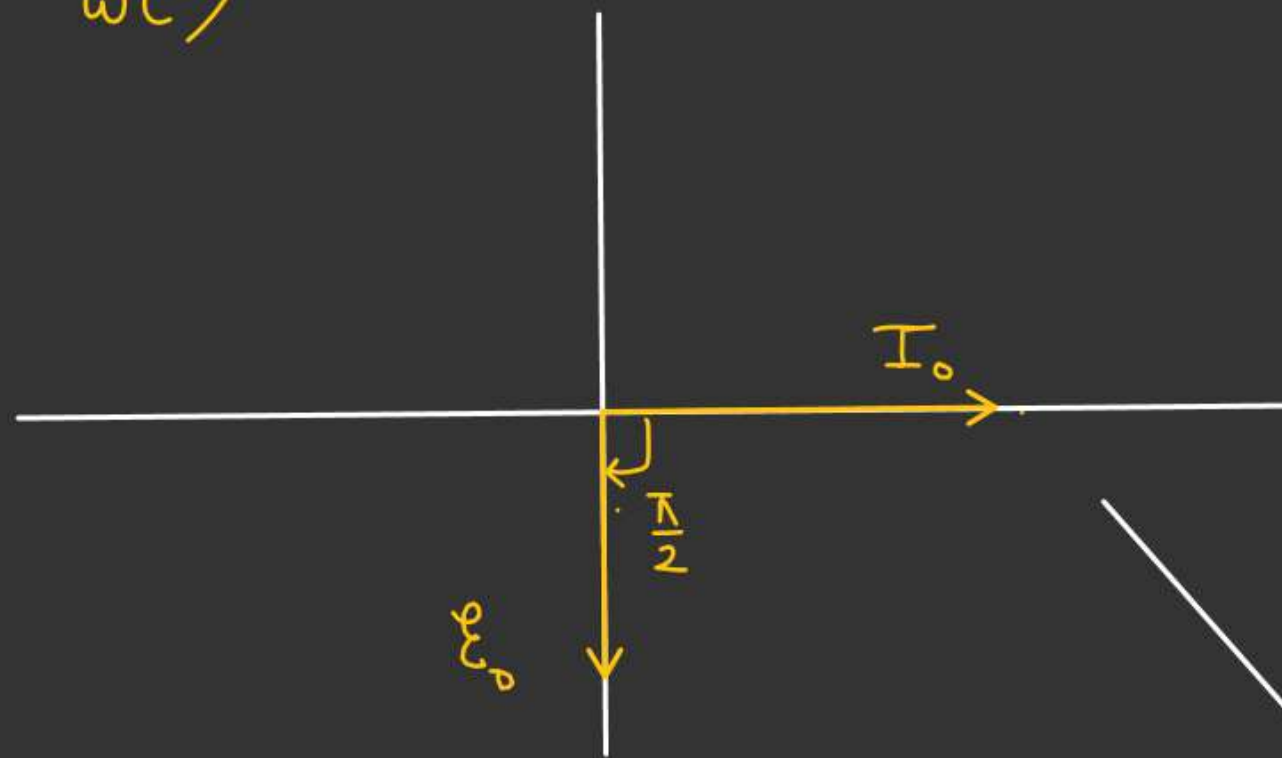

In purely Capacitive ckt
Current leading the voltage
by $\frac{\pi}{2}$

22

Purely Inductive ckt

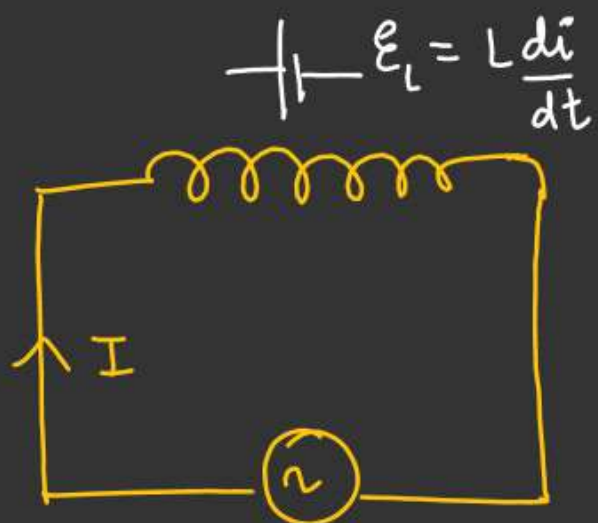

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t \quad \text{--- (1)}$$

$$\mathcal{E}_0 \sin \omega t - L \frac{di}{dt} = 0$$

$$\mathcal{E}_0 \sin \omega t = L \frac{di}{dt}$$

$$\frac{\mathcal{E}_0}{L} \int_0^t \sin \omega t = \int_0^i di$$

$$i = -\frac{\mathcal{E}_0}{\omega L} [\cos \omega t]_0^t$$

$$i = -\frac{\mathcal{E}_0}{\omega L} [\cos \omega t - 1]$$

$$i = \underbrace{\frac{\mathcal{E}_0}{\omega L}}_{\text{Constant}} - \frac{\mathcal{E}_0}{\omega L} \cos \omega t$$

$$i = -\frac{\mathcal{E}_0}{\omega L} \cos \omega t + C$$

$$i = \frac{\mathcal{E}_0}{\omega L} \sin(\omega t - \pi/2) + C \quad \text{--- (2)}$$

$$\phi = -\pi/2$$

→ In purely Inductive ckt Current lagging the Voltage by $\pi/2$.

$$\left[\begin{array}{l} X_1 = A \sin \omega t \quad \text{--- (1)} \\ X_2 = \text{Constant} + A \sin \omega t \quad \text{--- (2)} \end{array} \right]$$

Constant.

For (1)

Mean position is 0.

For (2)

Mean position = (K)

Purely Inductive ckt



$$E = E_0 \sin \omega t$$

$$I = I_0 \sin(\omega t - \pi/2)$$


$$I_0 = \frac{E_0}{\omega L} = \frac{E_0}{X_L}$$

$$X_L = \omega L$$

\Downarrow
(Reactance of Inductive ckt)

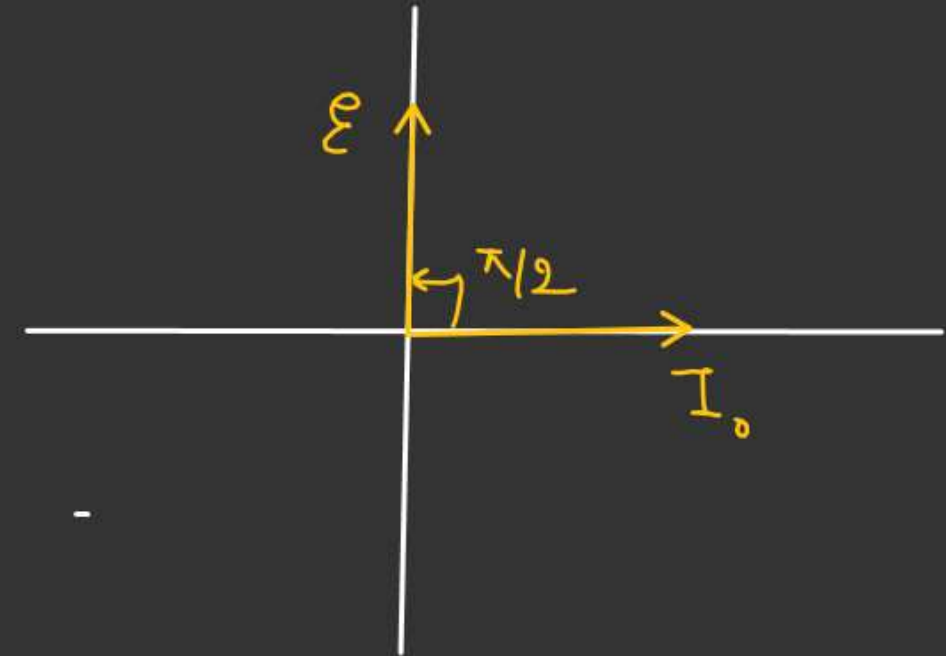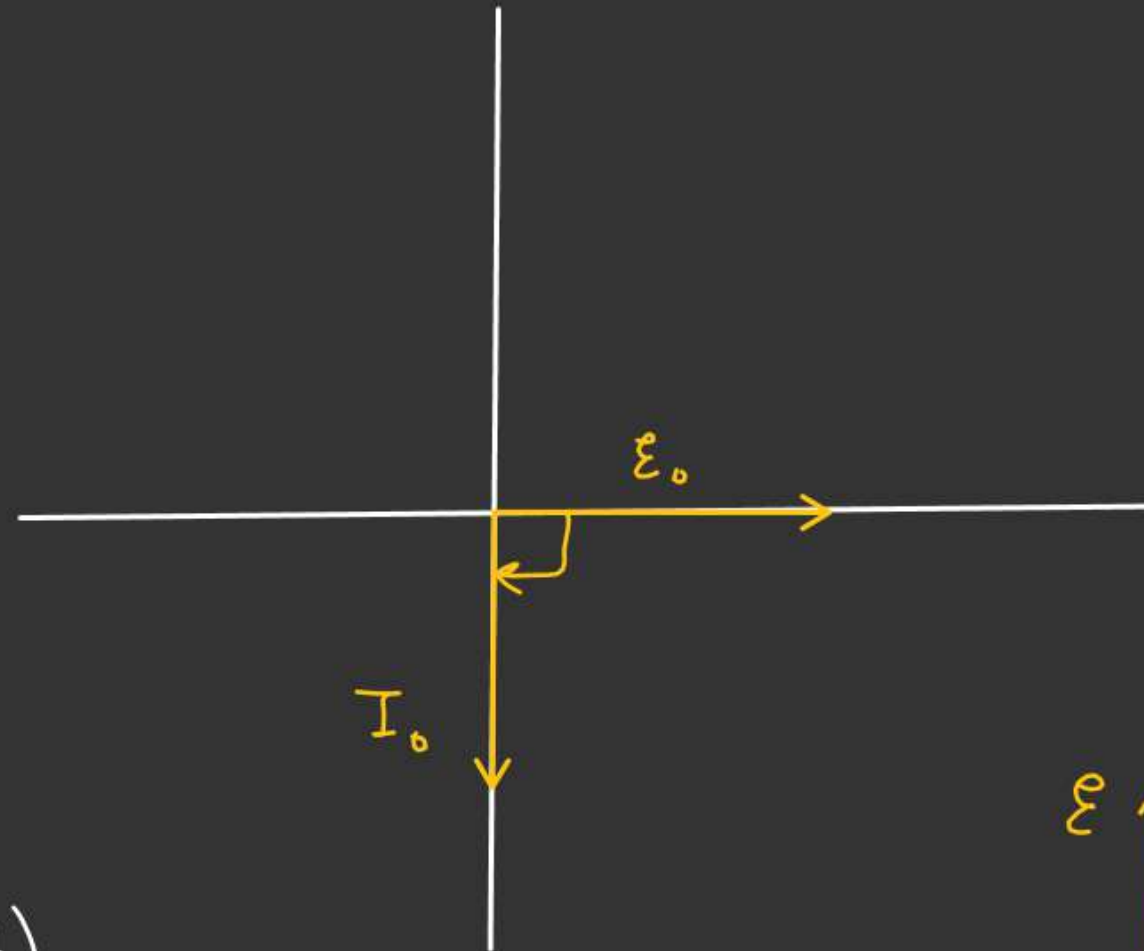

★★

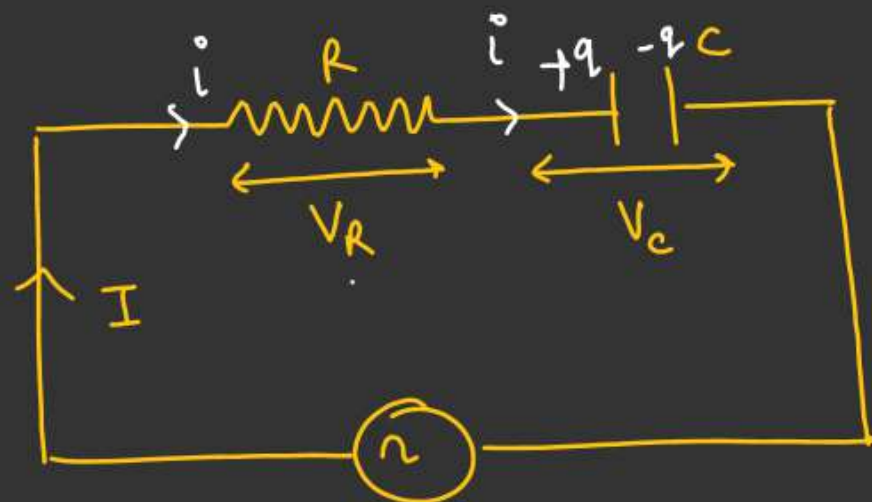R-C Ckt [R & C in Series]

$$E = E_0 \sin \omega t$$

$$\underline{V_C} = \underline{I} X_C$$

$$\frac{1}{\omega C} = X_C$$

Impedance
phasor of R-C ckt.



$V_R = iR$
 i & V_R both are
in the same
phase


$$Z = \sqrt{R^2 + X_C^2}$$

$$V_{net} = IZ$$

$$V_{net} = I \sqrt{R^2 + X_C^2}$$

$$V_{net} = \sqrt{\underline{I}^2 R^2 + \underline{I}^2 X_C^2}$$

$$V_{net} = \sqrt{V_R^2 + V_C^2}$$

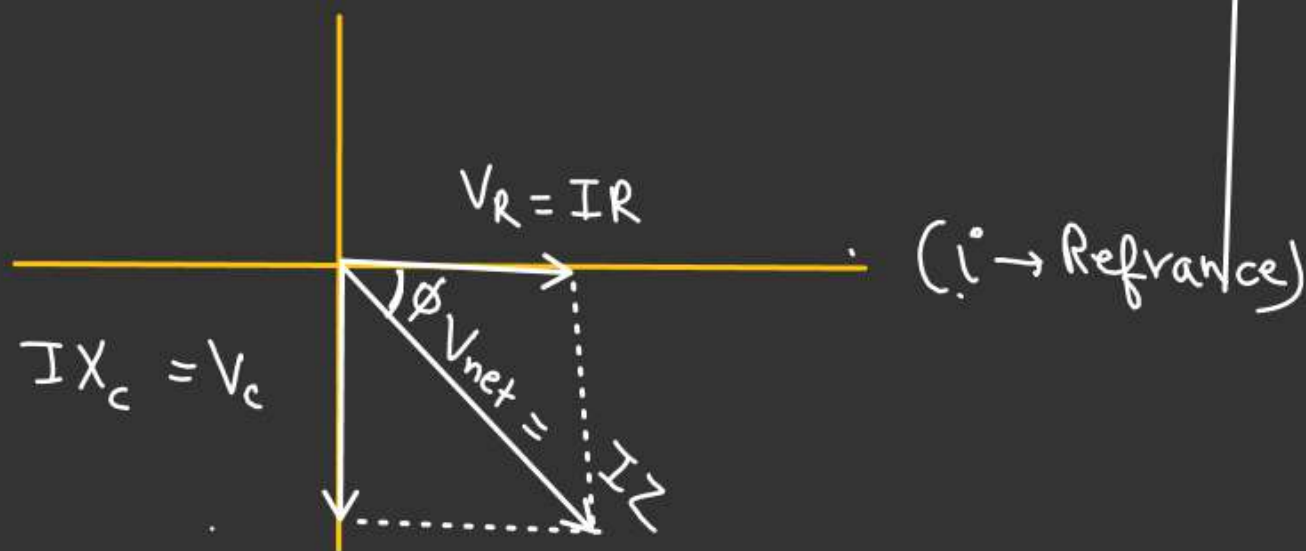

R-C Ckt.

$$e = E_0 \sin \omega t$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$i = I_0 \sin(\omega t + \phi)$$


$$\left(I_0 = \frac{E_0}{|Z|} \right)$$

$$\tan \phi = \left(\frac{|X_c|}{R} \right)$$

$$\phi = \tan^{-1} \left(\frac{|X_c|}{R} \right)$$

Phase Constant of
R-C Ckt.

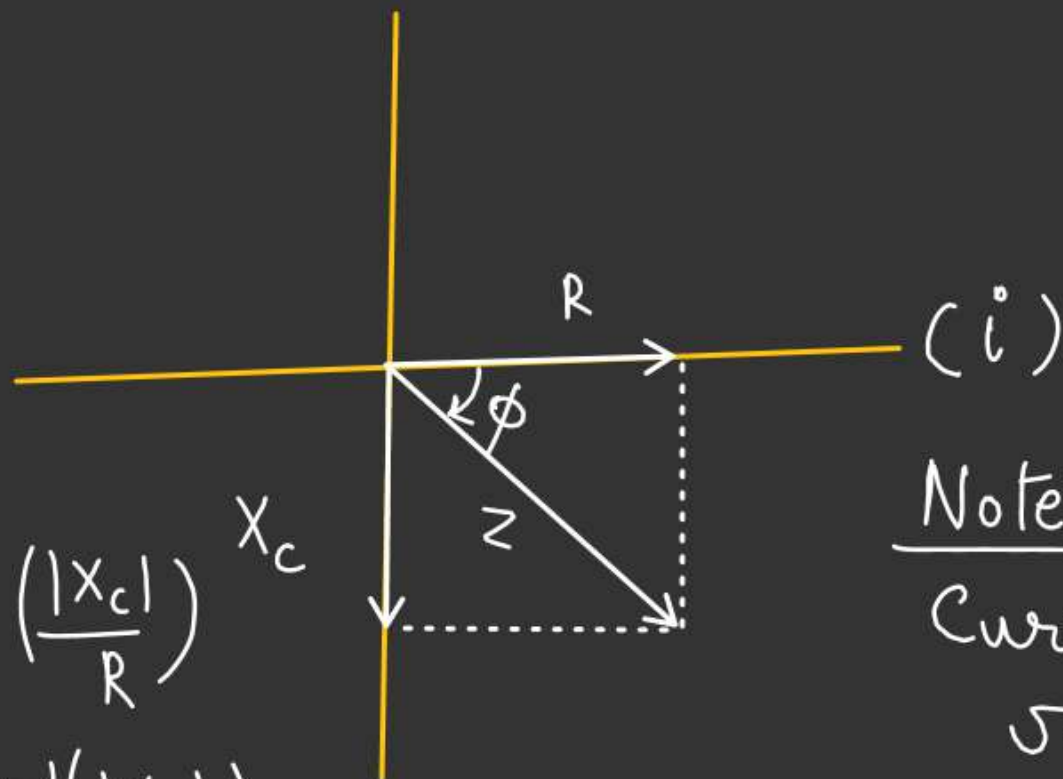$Z =$ Impedance of R-C Ckt.
 \downarrow
(Ω)



Note:- In R-C Ckt
Current leading the
Voltage by $\phi = \tan^{-1} \left(\frac{|X_c|}{R} \right)$