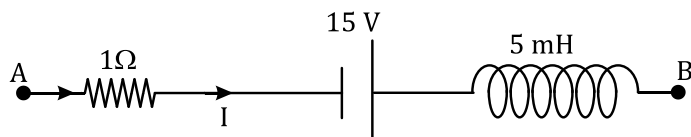


DPP 05

Solution

1. In accordance with law of potential distribution, for the given network,]

$$V_A - IR + E - L \frac{dI}{dt} = V_B$$



and as here I is decreasing ( $dI/dt$ ) is negative.

$$\text{So, } V_B - V_A = -5 \times 1 + 15 - 5 \times 10^{-3}(-10^3)$$

$$\text{i.e., } V_B - V_A = -5 + 15 + 5 = 15 \text{ V}$$

2. Inductance,  $L = 10\text{mH}$

$$\text{Voltage, } V = 20 \text{ V, } e^{-1} = 0.37$$

Resistance,  $R = 10\text{k}\Omega$ , Time  $t = 1\mu\text{s}$  The maximum current is,

$$I_{\max} = \frac{V}{R} = \frac{20}{10 \times 10^3} = 2 \times 10^{-3} \text{ A}$$


For L – R decay circuit,

$$I = I_{\max} e^{-Rt/L} = 2 \times 10^{-3} e^{\frac{-10 \times 10^3 \times 10^{-6}}{10 \times 10^{-3}}}$$

$$I = 2 \times 10^{-3} e^{-1} = \frac{74}{100} \text{ mA}$$

3. Just after closing the switch S, inductor behaves like an open circuit

$$I = 6/2 + 4 = 1 \text{ A}$$

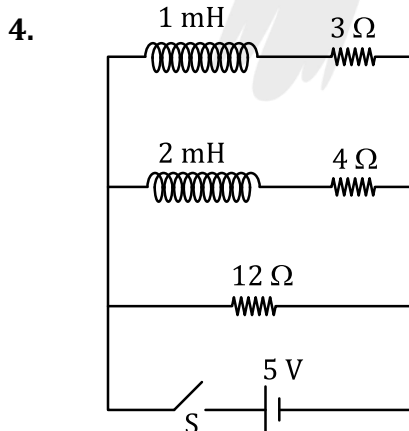

At  $t = 0$ , current will flow only in  $12\Omega$  resistance

$$\therefore I_{\min} = \frac{5}{12}$$

At  $t \rightarrow \infty$  both

$L_1$  and  $L_2$  behave as conducting wires

$$\therefore R_{\text{eff}} = \frac{3}{2}$$

$$I_{\text{max}} = \frac{10}{3}$$

$$\frac{I_{\text{max}}}{I_{\text{min}}} = 8$$

5. Initially the inductor offers infinite resistance hence  $i_1$  is 1 A. Finally, at steady state inductor offers zero resistance and current  $i_2$  is 1.25 A in the battery.

6.  $R = \frac{V}{I} \quad \tau = \frac{L}{R} = 1 \text{ ms.}$

7. Current will have to increase in order to oppose the cause (decrease in field).


8.  $I = I_1 + I_2$

$$I_1 = E/R$$

$$L \frac{dI}{dt} = E. I_2 = \frac{Et}{L}$$

$$I = E/R + \frac{Et}{L}$$

$$I = 12 \text{ A.}$$

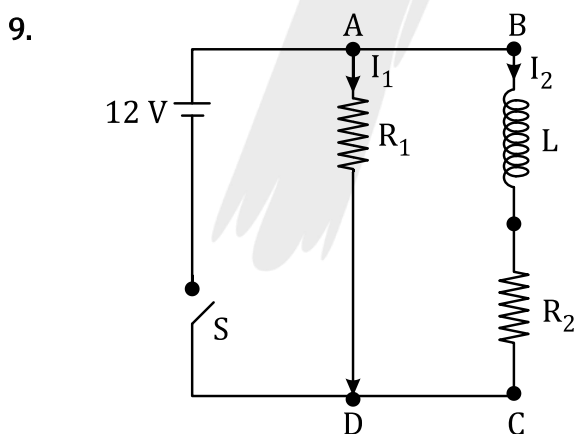

For the given R – L circuit the potential difference across  $AD = V_{BC}$  as they are parallel.

$$I_1 = E/R_1; I_2 = I_0(1 - e^{-t/\tau}) \text{ where}$$

$\tau$  = mean life or  $L/R$ .

$$\tau = t_0 \text{ (given)}$$

$$E(\text{ across BC}) = L \frac{dI_2}{dt} + R_2 I_2$$

$$I_2 = I_0(1 - e^{-t/t_0})$$

$$\text{But } I_0 = \frac{E}{R_2} = \frac{12}{2} = 6 \text{ A}$$


$$\tau = t_0 = \frac{L}{R} = \frac{400 \times 10^{-3} \text{ H}}{2 \Omega} = 0.2 \text{ s}$$

$$\therefore I_2 = 6(1 - e^{-t/0.2})$$

$$\text{Potential drop across } L = E - R_2 I_2$$

$$= 12 - 2 \times 6(1 - e^{-t/0.2}) = 12e^{-t/0.2} = 12e^{-5t} \text{ V}$$

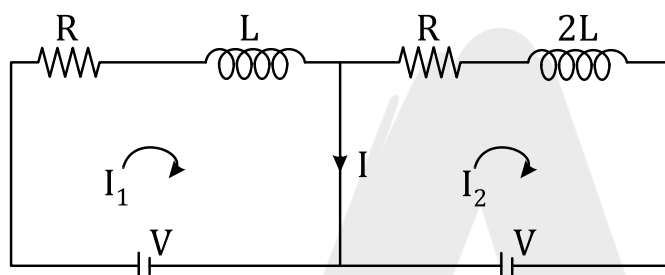10. Let  $I_1$  and  $I_2$  be the currents in both loops as shown in figure.



$$I = (I_1 - I_2)$$

$$I = \frac{V}{R} \left[ 1 - e^{-\left(\frac{R}{L}\right)t} \right] - \frac{V}{R} \left[ 1 - e^{-\left(\frac{R}{2L}\right)t} \right]$$

$$I = \frac{V}{R} \left[ e^{-\left(\frac{R}{2L}\right)t} - e^{-\left(\frac{R}{L}\right)t} \right] \quad \dots (i)$$

$$\text{For } I_{\max}, \frac{dI}{dt} = 0$$

$$-\frac{V}{2L} e^{-\left(\frac{R}{2L}\right)t} + \frac{V}{L} e^{-\left(\frac{R}{L}\right)t} = 0$$

$$e^{-\left(\frac{R}{L}\right)t} = \frac{1}{2} e^{-\left(\frac{R}{2L}\right)t} \quad \text{or} \quad e^{-\left(\frac{R}{2L}\right)t} = \frac{1}{2}$$

$$\Rightarrow \left(\frac{R}{2L}\right)t = \ln 2$$

$$\Rightarrow t = \frac{2L}{R} \ln 2 = \tau \rightarrow \text{time when } I \text{ is maximum.}$$

Using  $t$  in equation (i),

$$I_{\max} = \frac{V}{R} \left[ e^{-\frac{R}{2L} \left(\frac{2L}{R} \ln 2\right)} - e^{-\frac{R}{L} \left(\frac{2L}{R} \ln 2\right)} \right]$$

$$\text{or } I_{\max} = \frac{V}{R} \left[ \frac{1}{2} - \frac{1}{4} \right] = \frac{V}{4R}$$