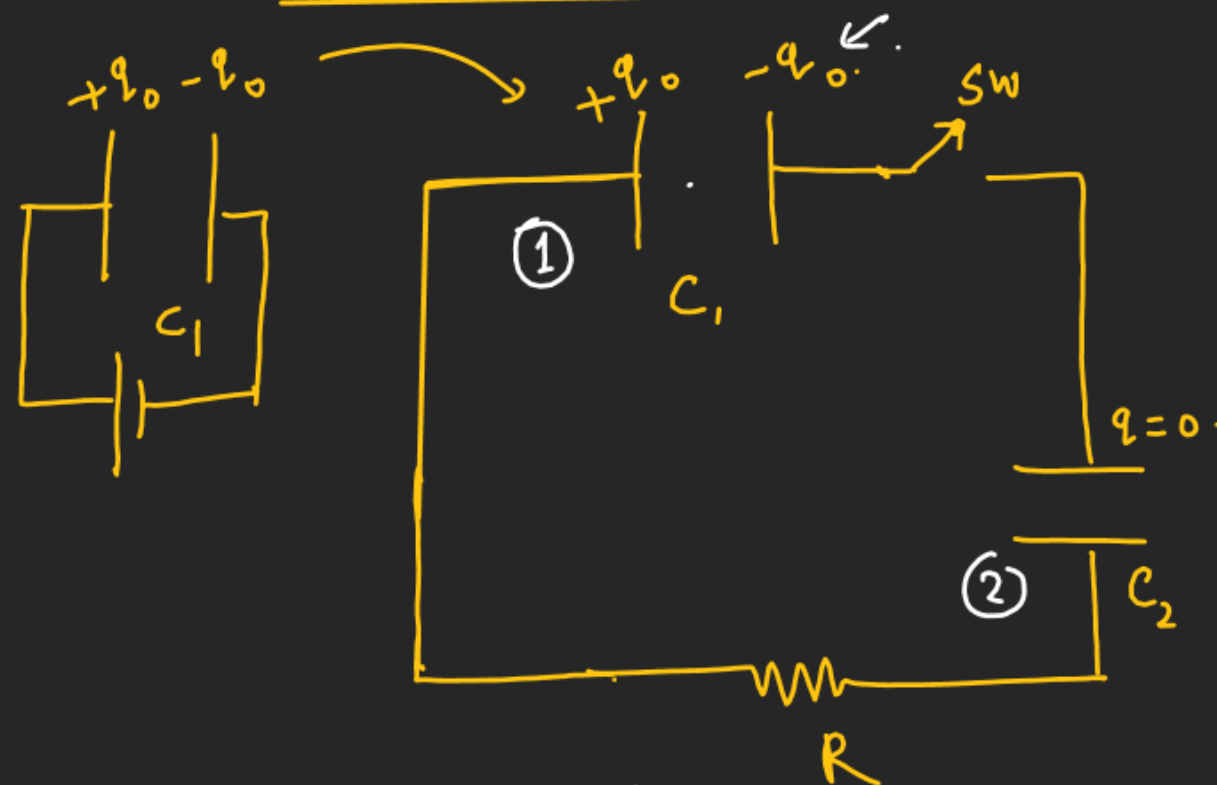


CURRENT ELECTRICITY


Case of 2-Capacitors in R-C Ckt (one discharging and other Charging)



(flow $\rightarrow (q_0 - q)$
of Charge
in the ckt)

Switch is closed at $t=0$. find $I = f(t)$.

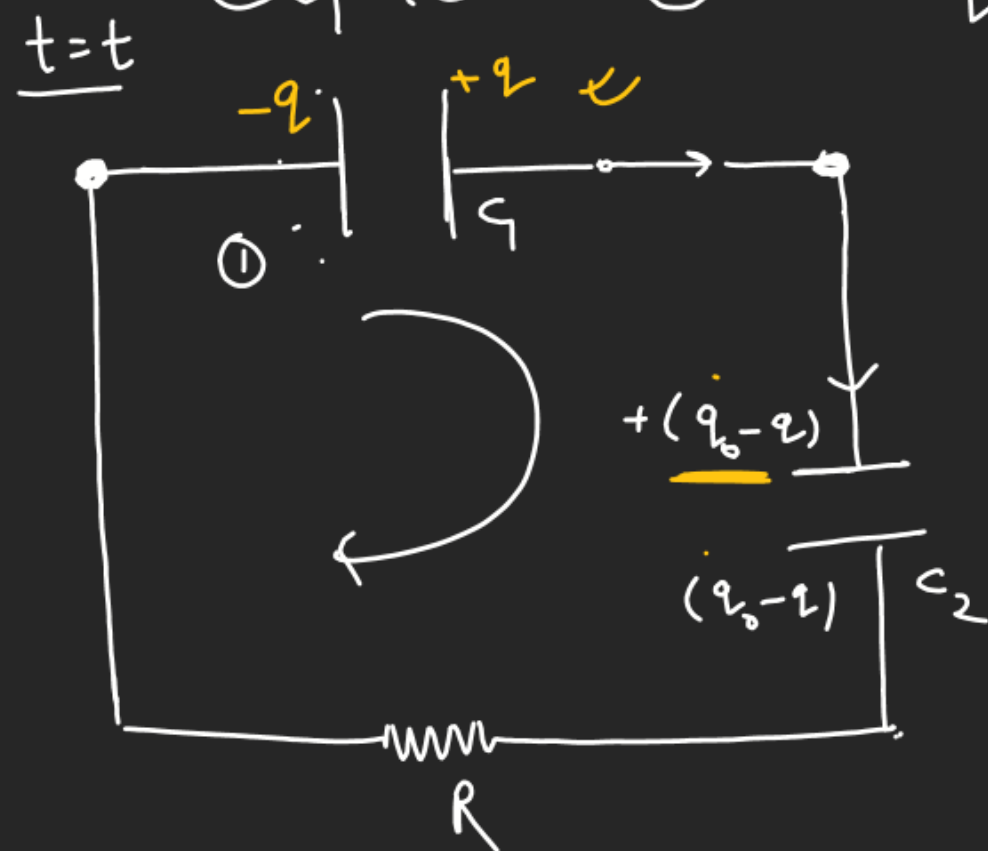At any time $t=t$; let Charge on the Capacitor (1) be q .



Charge flow in the ckt

$$I = \frac{d}{dt}(q_0 - q)$$

$$I = -\frac{dq}{dt}$$

$$[V_{C_1} = V_{C_2} + V_R]$$

$$\frac{q}{C_1} = \frac{q_0 - q}{C_2} + IR. \quad \checkmark$$

CURRENT ELECTRICITY

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C}$$

$$\frac{q}{C_1} = \left(\frac{q_0 - q}{C_2} \right) + IR$$

$$I = (-dq/dt)$$

$$q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{q_0}{C_2} - R \frac{dq}{dt}$$

$$\int_{q_0}^q \frac{dq}{Cq_0 - C_2q} = \frac{1}{RC_2C} \int_0^t dt$$

$$R \frac{dq}{dt} = \frac{q_0}{C_2} - q \left(\frac{1}{C} \right)$$

$$\frac{dq}{dt} = \frac{Cq_0 - C_2q}{RC_2C}$$

$$\ln [Cq_0 - C_2q]_{q_0}^q = \frac{1}{RC_2C} t$$

$$\ln [Cq_0 - C_2q] - \ln (Cq_0 - C_2q_0) = -\frac{1}{RC} t$$

$$\ln \left(\frac{Cq_0 - C_2q}{Cq_0 - C_2q_0} \right) = -\frac{1}{RC} t$$

$$\ln \left[\frac{Cq_0 - C_2 q}{Cq_0 - C_2 q_0} \right] = -\frac{1}{RC} t$$

$$Cq_0 - C_2 \underline{q} = (Cq_0 - C_2 q_0) e^{-\frac{t}{RC}}$$

$$C_2 q = Cq_0 - (Cq_0 - C_2 q_0) e^{-t/RC}$$

$$q = \frac{Cq_0}{C_2} - \left[\frac{Cq_0}{C_2} - q_0 \right] e^{-t/RC}$$

**

$$q = \frac{q_0 C}{C_2} + \frac{q_0 C}{C_1} e^{-t/RC}$$

$$C = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C = \left(\frac{C_1 C_2}{C_1 + C_2} \right) \checkmark$$


$$q = \frac{C_1 q_0}{C_1 + C_2} - \left[\frac{C_1 q_0}{C_1 + C_2} - q_0 \right] e^{-t/RC}$$

$$q = \left(\frac{C_1 q_0}{C_1 + C_2} \right) - \left[\frac{-C_2 q_0}{C_1 + C_2} \right] e^{-t/RC}$$

$$q = \frac{q_0}{C_1 + C_2} [C_1 + C_2 e^{-t/RC}]$$

$$q = q_0 \left(\frac{C_1}{C_1 + C_2} \right) + q_0 \left(\frac{C_2}{C_1 + C_2} \right) e^{-t/RC}$$
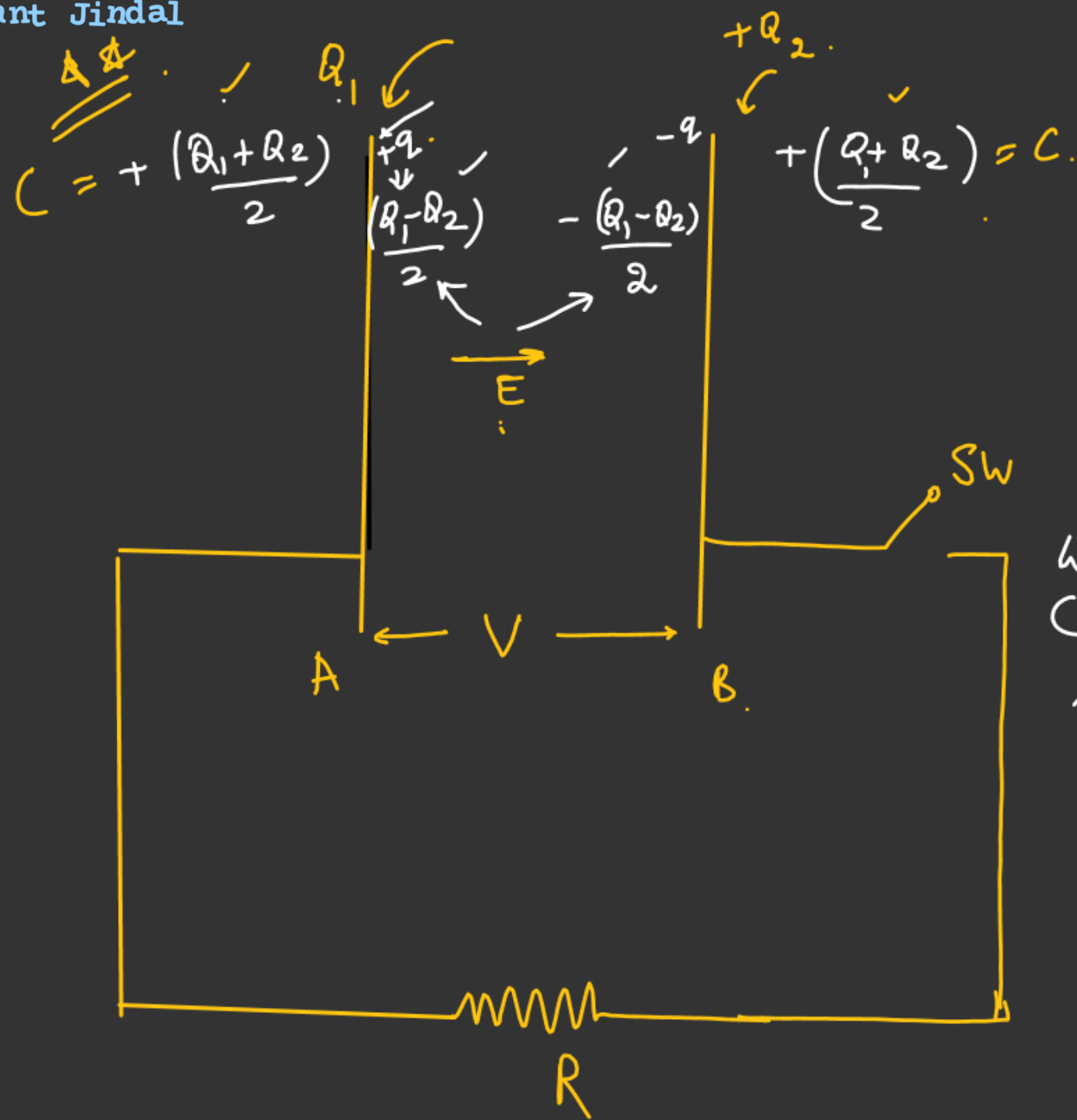
$$q = \frac{q_0}{C_2} \underbrace{\left(\frac{C_1 C_2}{C_1 + C_2} \right)}_{C} + \frac{q_0}{C_1} \underbrace{\left(\frac{C_1 C_2}{C_1 + C_2} \right)}_{C} e^{-t/RC}$$



$$q = Q_1 - \left(\frac{Q_1+Q_2}{2} \right)$$

$$q = \frac{2Q_1 - Q_1 - Q_2}{2}$$

$$q = \left(\frac{Q_1 - Q_2}{2} \right)$$

When sw is closed only charges inside the plate will change.

$$\text{At } t=0$$

$$q_0 = \left(\frac{Q_1 - Q_2}{2} \right)$$

$$q_{\text{inside}} = q_0 e^{-t/RC}$$

$$q_{\text{inside}} = \left(\frac{Q_1 - Q_2}{2} \right) e^{-t/RC}$$

Initially SW is open.

Q_1 and Q_2 be the Charges given to plate A and B.

find the Charge on plate A and B as a function of time when Switch is Closed.


take $t=0$ when sw closed.

$$(q_T)_{\text{left plate}} = \left(\frac{Q_1+Q_2}{2} \right) + \left(\frac{Q_1-Q_2}{2} \right) e^{-t/RC}$$

$$(q_T)_{\text{right plate}} = \left(\frac{Q_1+Q_2}{2} \right) - \left(\frac{Q_1-Q_2}{2} \right) e^{-t/RC}$$

H.W.

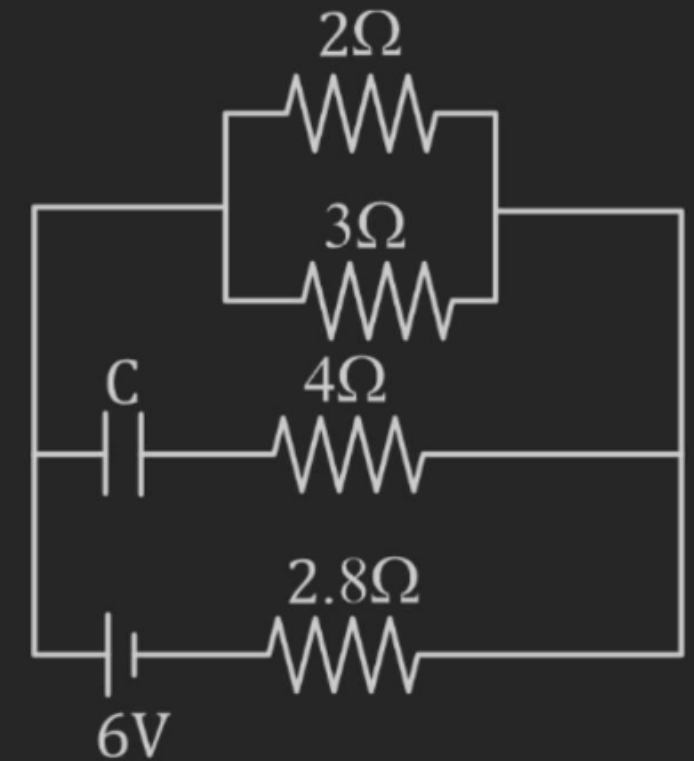- Q.4** Calculate the steady state current in the 2Ω resistor shown in the circuit in the figure. The internal resistance of the battery is negligible and the capacitance of the condenser C is 0.2 microfarad. **(1982)**



CURRENT ELECTRICITY

Q.5 A part of circuit in a steady state along with the currents flowing in the branches, the values of resistances etc., is shown in the figure.

Calculate the energy stored in the capacitor C($4\mu\text{F}$)

(1986)

Solⁿ

$$U_{4\mu\text{F}} = ??$$

At Steady state Capacitor behave as open ckt.

Potential difference across the Capacitor at Steady state $V = |V_A - V_B|$


$$V_A - (5 \times 3) - (1 \times 3) - (1 \times 2) = V_B$$

$$V_A - V_B = 20 \text{ volt}$$

$$U = \frac{1}{2} CV^2$$

$$U = \frac{1}{2} \times 4 \times 10^{-6} \times (20)^2$$

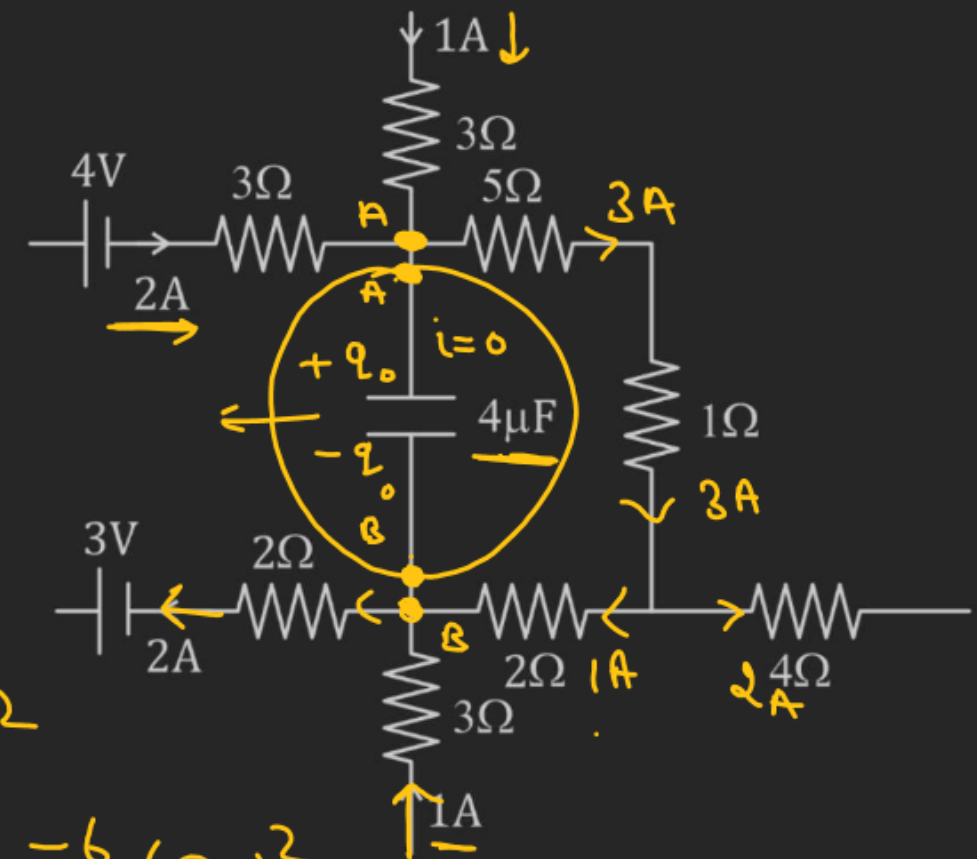
$$U = 8 \times 10^{-6} \times 10^2 = 800 \mu\text{J}$$



CURRENT ELECTRICITY

At Steady State Capacitor is fully charged acts as a open ckt.

I = Current
in the Ckt at
Steady
State.

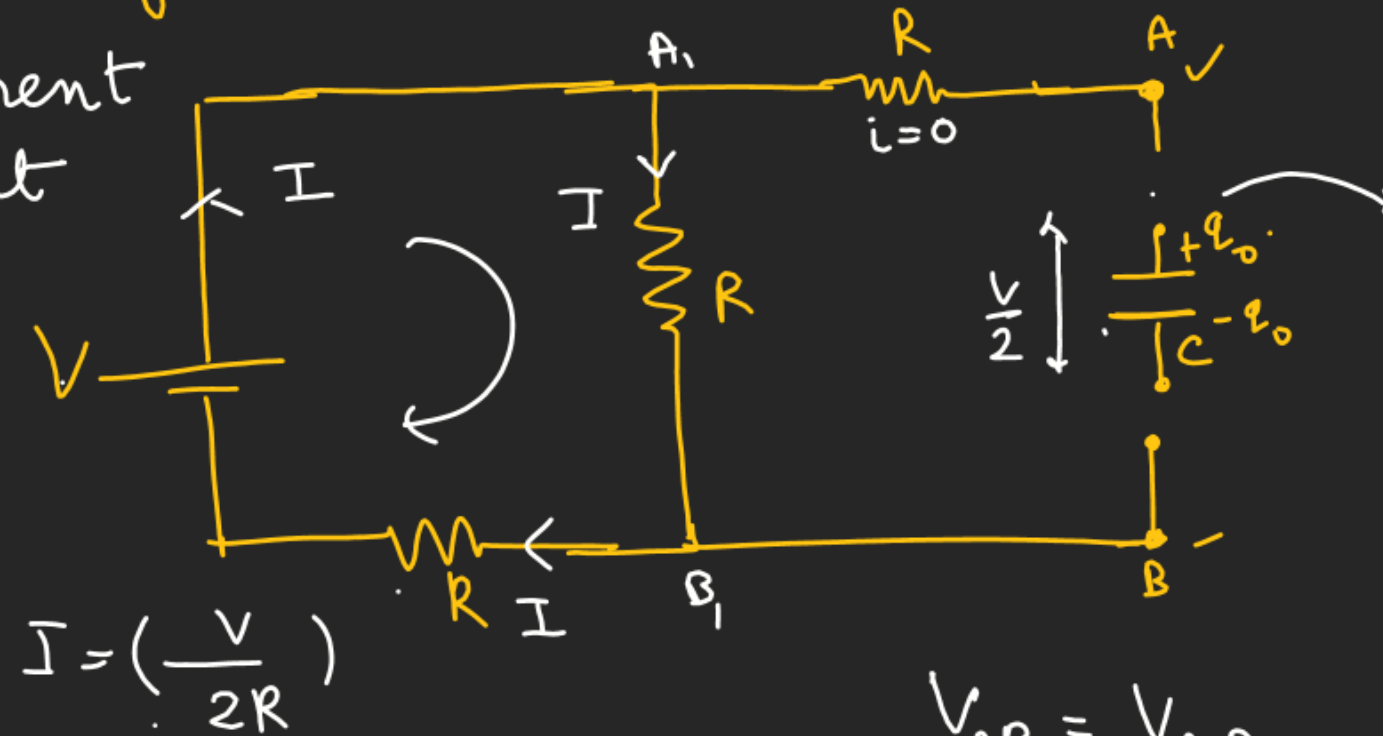

$$V_{AB} = I \cdot R$$

$$= \frac{V}{2R} \times R = \left(\frac{V}{2}\right)$$

$$V_{AB} = V_{A,B_1}$$

$$q_0 = \left(\frac{CV}{2}\right) \checkmark$$

$$q = q_0 (1 - e^{-t/\tau})$$

$$q = \frac{CV}{2} \left[1 - e^{-2t/3RC} \right]$$

CURRENT ELECTRICITY



Q.7 In the circuit shown in figure, the battery is an ideal one, with emf V . The capacitor is initially uncharged. **(1988)**

The switch S is closed at time $t = 0$.

(a) Find the charge Q on the capacitor at time t . $V \rightarrow Q \rightarrow f(t)$.

(b) Find the current in AB at time t . What is its limiting value at $t \rightarrow \infty$. $I_{AB} = f(t)$

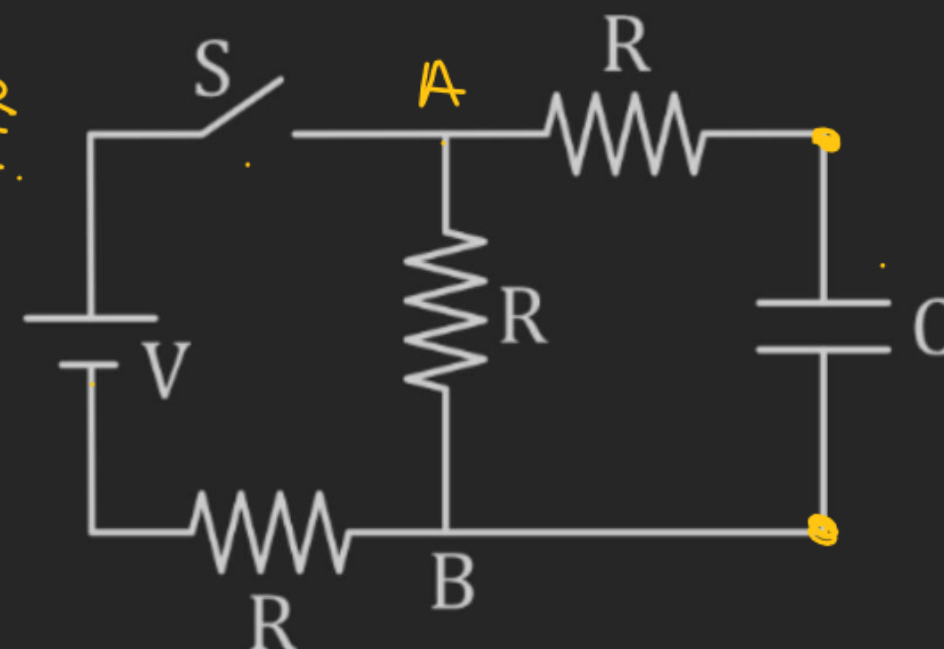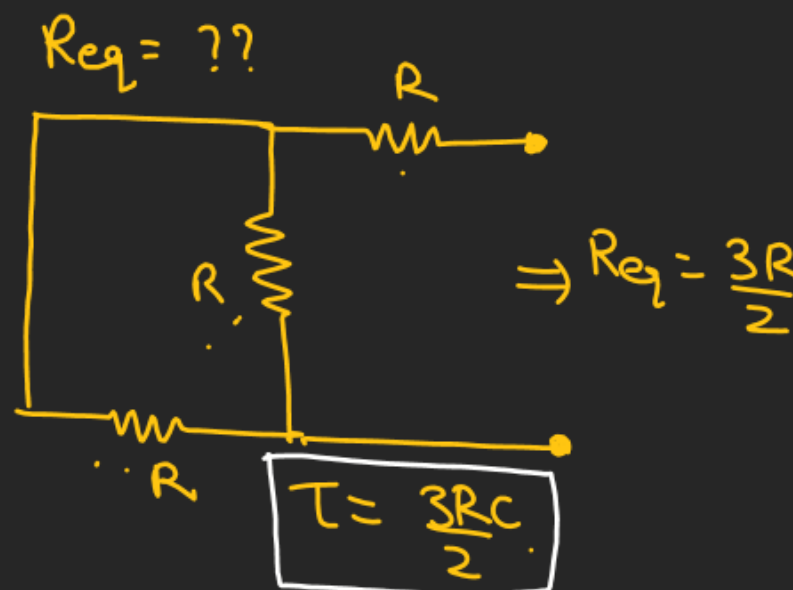
a) $q = \check{q}_0 (1 - e^{-t/\tau})$
 $\tau = R_{eq} \cdot C$



CURRENT ELECTRICITY

- Q.8 In the given circuit, the switch S is closed at time $t = 0$. The charge Q on the capacitor at any instant t is given by $Q(t) = Q_0(1 - e^{-\alpha t})$. Find the value of Q_0 and α in terms of given parameters as shown in the circuit. (2005)

$R_{eq} = ??$

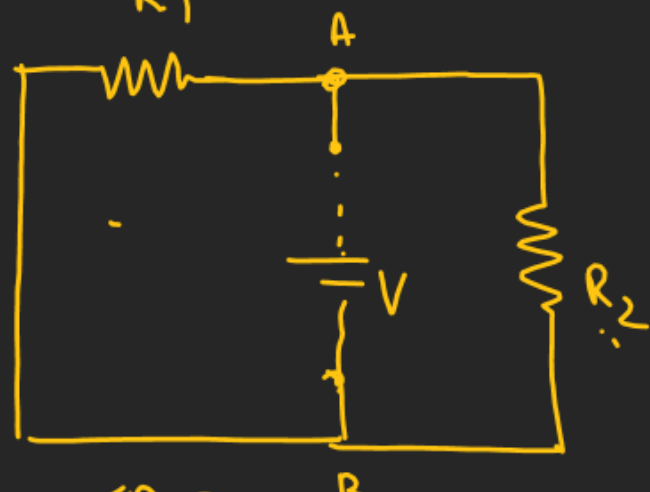


$$(R_{eq})_{AB} = \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\tau = \left(\frac{R_1 R_2 C}{R_1 + R_2} \right)$$

$$I = \left(\frac{V}{R_1 + R_2} \right)$$

$$\alpha = \frac{1}{\tau}$$
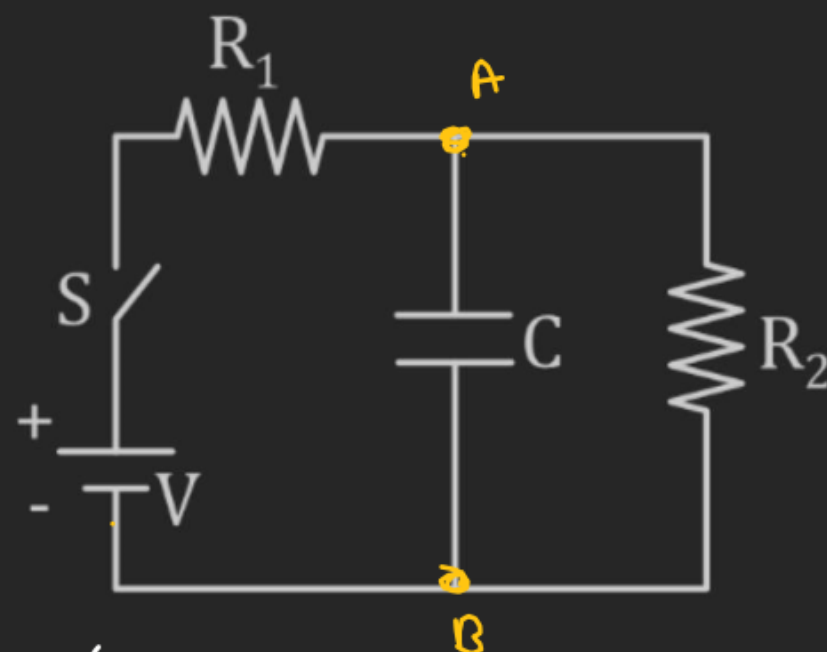
$$\alpha = \left[\frac{R_1 + R_2}{R_1 R_2 C} \right] \text{ Ans}$$




$$V_{AB} = V_{R_2} = IR_2$$

$$V_{AB} = \left(\frac{VR_2}{R_1 + R_2} \right)$$

$Q_0 = ??$, $\alpha = ??$

At the time of steady state

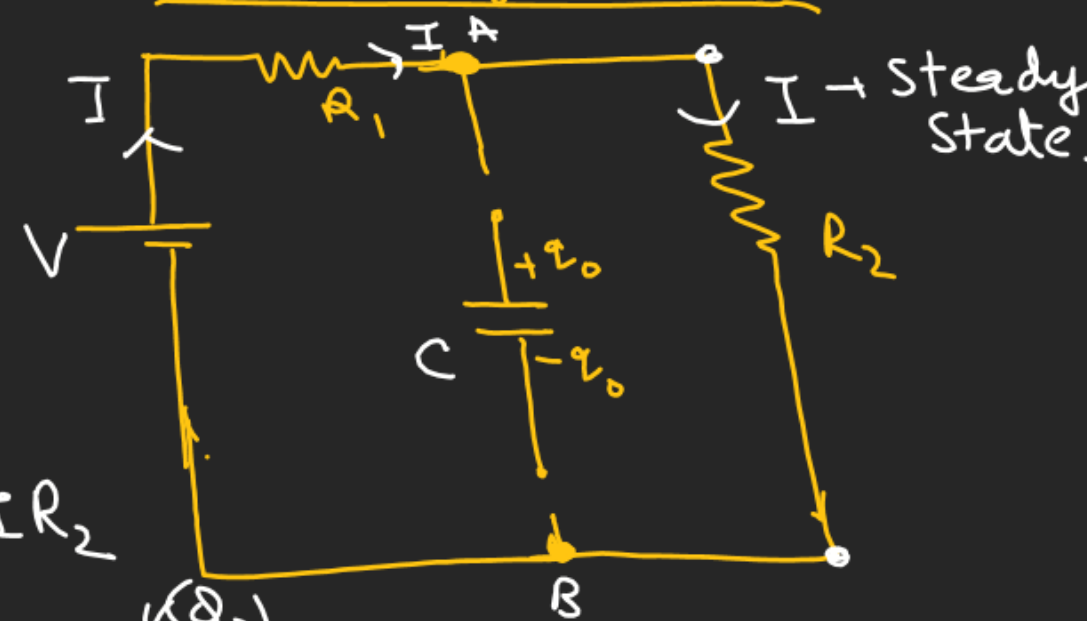

$$Q_0 = \left(\frac{CVR_2}{R_1 + R_2} \right) \text{ - Ans}$$

Maximum Charge on the Capacitor


CURRENT ELECTRICITY

Q.9 In the circuit shown below, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu\text{C}$. Then S is switched to position Q . After a long time, the charge on the capacitor is $q_2 \mu\text{C}$. **(2021)**

(a) The magnitude of q_1 is 1.33.


(b) The magnitude of q_2 is ____.

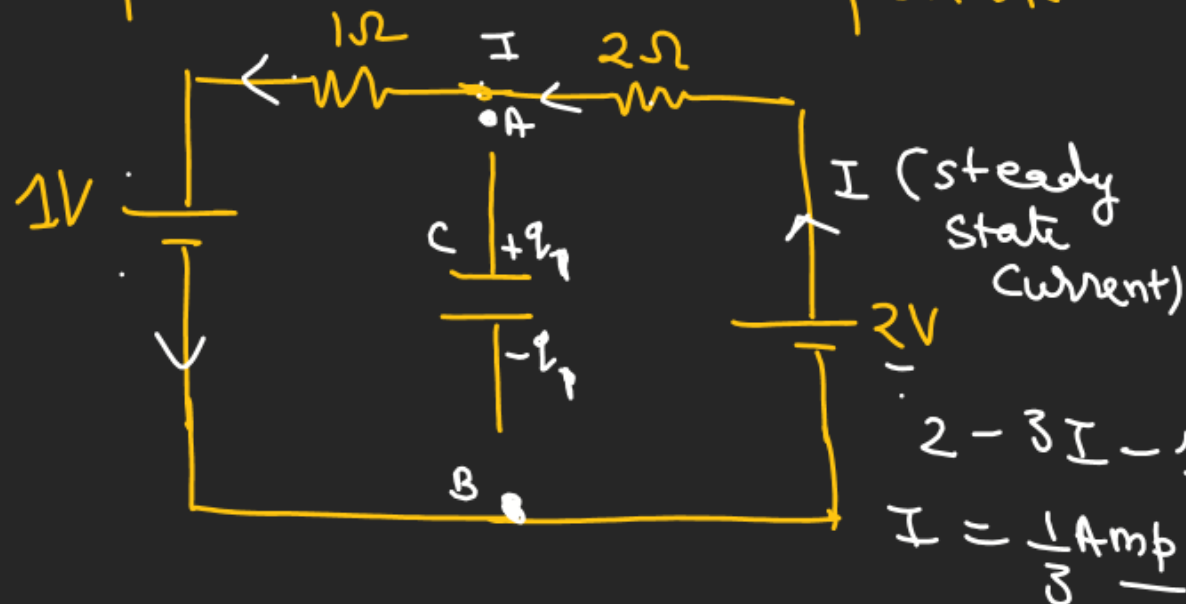a) At the time of steady state Capacitor behave as open ckt.



$$2 - 3I - 1 = 0$$

$$I = \frac{1}{3} \text{ Amp}$$

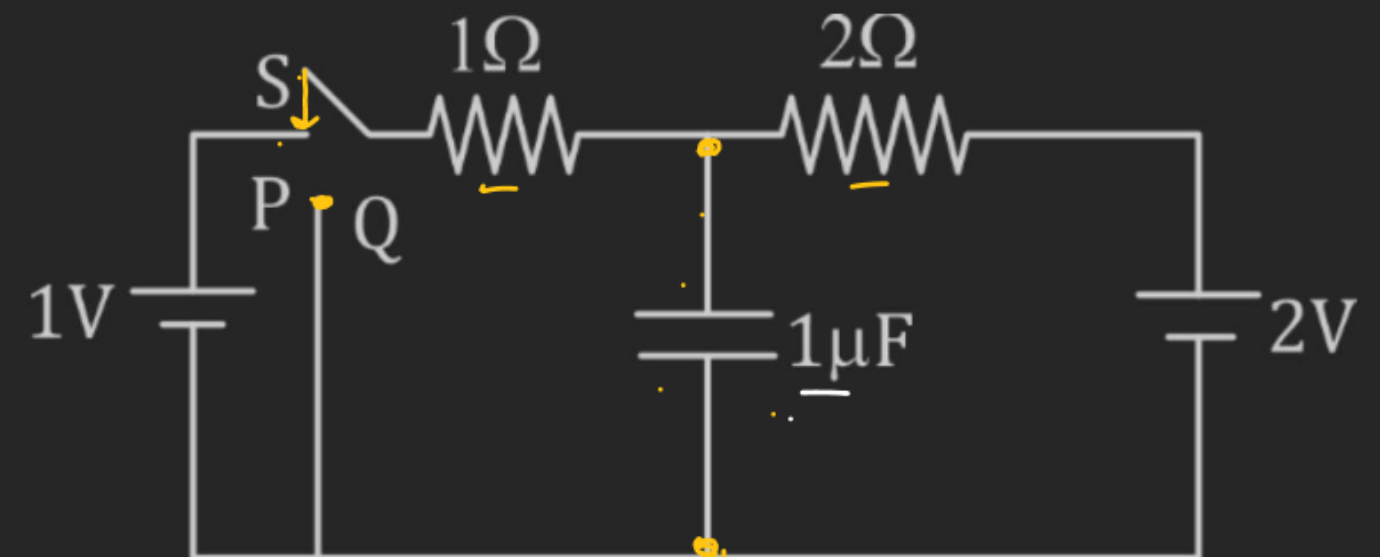

$$V_B + 2 - 2 \times \frac{1}{3} = V_A$$

$$V_A - V_B = 2 - \frac{2}{3}$$



$$= \frac{4}{3} \text{ volt}$$

$$q_1 = (1 \times 10^{-6}) \times \left(\frac{4}{3}\right)$$

CURRENT ELECTRICITY

(b) $q_2 = ??$

At the time of steady state.

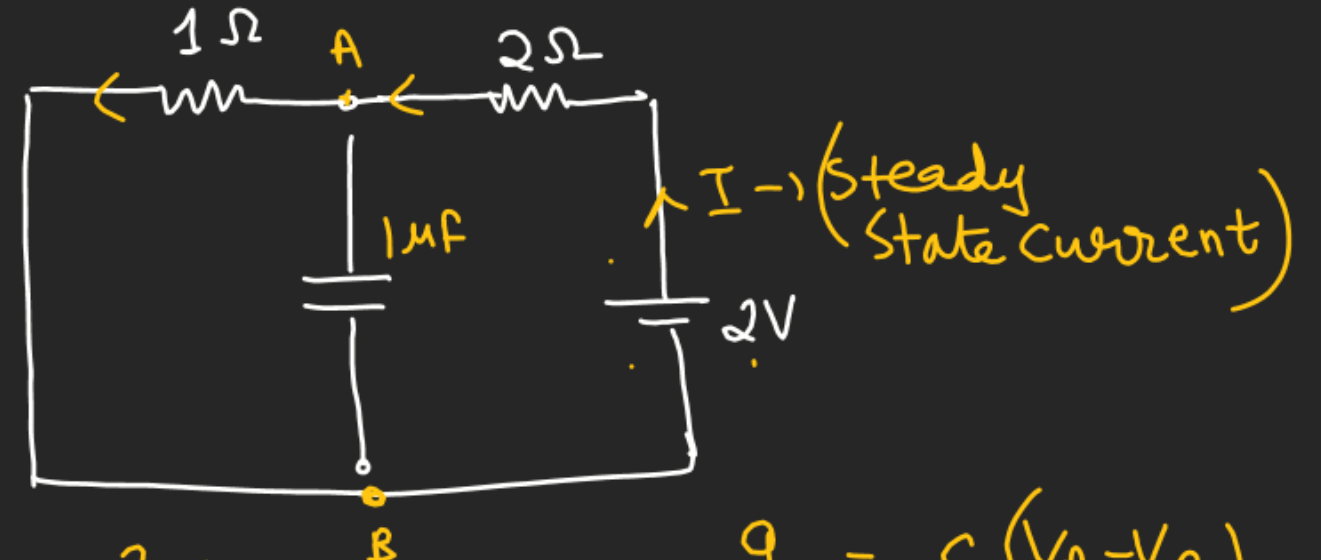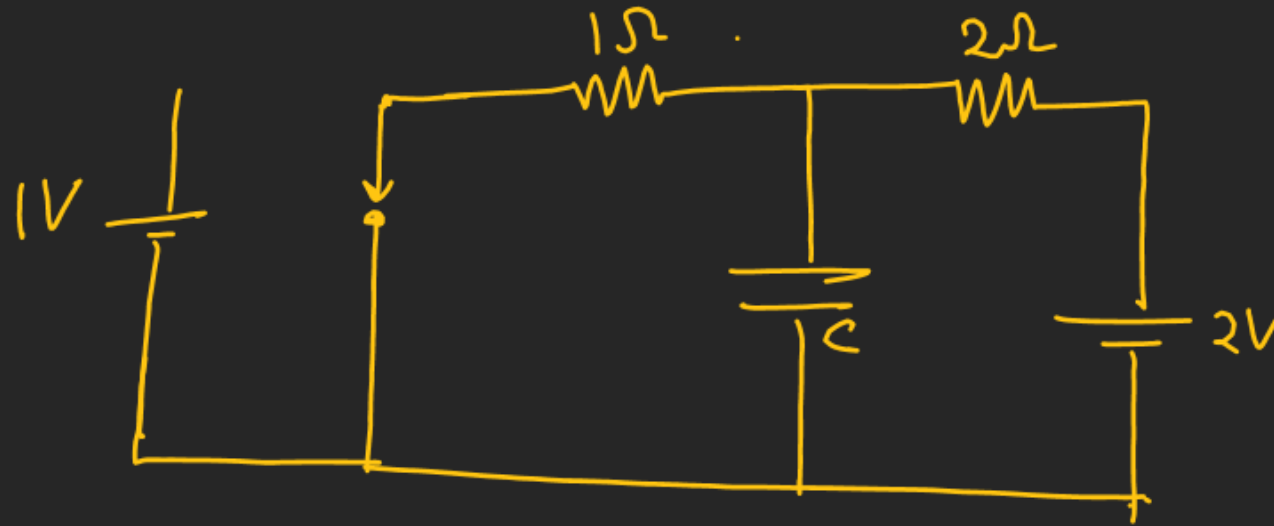

$$I = \frac{2}{3} \text{ Amp}$$

$$V_B + 2 - \frac{2}{3} \times 2 = V_A$$

$$V_A - V_B = 2 - \frac{4}{3} = \frac{2}{3} \Rightarrow$$

$$q_2 = C(V_A - V_B) \\ = 1 \times 10^{-6} \times \left(\frac{2}{3}\right) \\ = \boxed{0.66 \mu\text{C}}$$