


DPP - 6

SOLUTION

Link to View Video Solution:  [Click Here](#)

1. 1 lt. water = 1000 g

Energy required to 1lt water increase its temperature from 10°C to 40°C

$$Q = ms\Delta T$$

$$= 10^3 \times 1 \times 30 = 3 \times 10^4 \text{ Cal}$$

$$Q = 4.2 \times 3 \times 10^4 \text{ cal}$$

$$\rightarrow 836 \text{ watt} \Rightarrow 836 \text{ J/sec}$$

$$\text{Let time taken is } t \Rightarrow 836 \times t = Q$$


$$t = \frac{4.2 \times 3 \times 10^4}{836} \approx 150 \text{ sec}$$

2. Heater coil



$$E_1 = \frac{V^2}{R} t$$

Cut into two part.

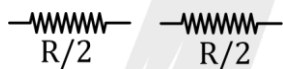

$$E_2 = \frac{V^2}{R/2} t \Rightarrow E_2 = \frac{2V^2}{R} t \Rightarrow E_2 = 2E_1$$

- 3.



25W, 220 V

$$R_1 = \frac{220 \times 220}{25}$$

$$R_1 = 22 \times 22 \times 4$$




100 W, 220 V

$$R_2 = \frac{220 \times 220}{100}$$

$$R_2 = 22 \times 22$$

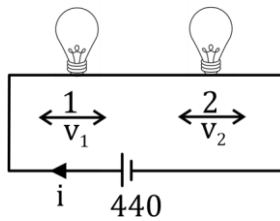Link to View Video Solution: [Click Here](#)



$$R_{eq} = 22 \times 22 \times 5$$

$$i = \frac{440}{22 \times 22 \times 5} = \frac{20}{22 \times 5} = \frac{4}{22}$$

$$i = \frac{2}{11}$$

$$V_1 = \frac{2}{11} \times 22 \times 22 \times 4$$

$$V_1 = 4 \times 4 \times 22 = 352 \text{ Volt}$$

$$V_2 = \frac{2}{11} \times 22 \times 22 = 4 \times 22$$

$$= 88 \text{ Volt}$$

Vactual > V rating for 25 watt bulb

so 25W bulb will be fuse.



4. Potential across both bulb is same


$$P_1 = \frac{6^2}{6} = 6 \text{ watt}$$

$$P_2 = \frac{6^2}{3} = \frac{36}{3} = 9 \text{ watt}$$

bulb-2 more glow then first.

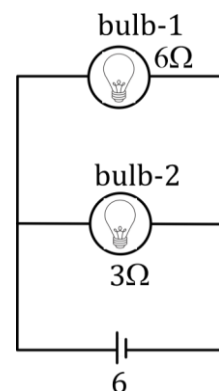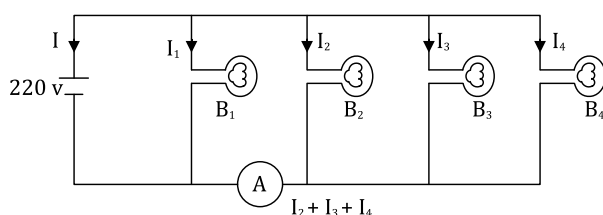5. All bulb connected parallel through battery



Link to View Video Solution:  [Click Here](#)

$$R_1 = R_2 = R_3 = R_4 = \frac{V^2}{P} = \frac{220 \times 220}{100}$$

$$R_{eq} = \frac{R}{4} = \frac{22 \times 22}{4} = 11 \times 11$$

$$i = \frac{220}{11 \times 11} = \frac{20}{11} \text{ Amp}$$

$$I_1 = I_2 = I_3 = I_4 = \frac{20}{4 \times 11} = \frac{5}{11}$$

$$\text{Reading of ammeter} = I_2 + I_3 + I_4$$

$$= \frac{3 \times 5}{11} = \frac{15}{11} \text{ Amp}$$

$$= 1.36 \text{ Amp}$$

6. Reequivalent of circuit 1

$$R_1 = 1 \Omega$$

$$P_1 = \frac{9V^2}{1} = 9V^2$$

Reequivalent of circuit 2

$$R_2 = 0.5 \Omega$$

$$P_2 = \frac{9V^2}{0.5} = 18 V^2$$

Reequivalent of circuit 3

$$R_3 = 1.5 \Omega \Rightarrow P_3 = \frac{9V^2}{3/2} = 6V^2$$

$$P_2 > P_1 > P_3$$

[Click Here](#)


7.

$$R_{eq} = \frac{3R}{2} \Rightarrow I_1 = \frac{2E}{3R}$$



when key is closed.

$$R_{eq} = 4R/3 \Rightarrow I_2 = \frac{3E}{4R}$$
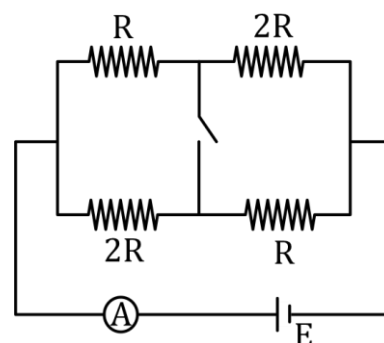
$$\frac{I_1}{I_2} = \frac{2E \times 4R}{3R \times 3E} = \frac{8}{9}$$



8.

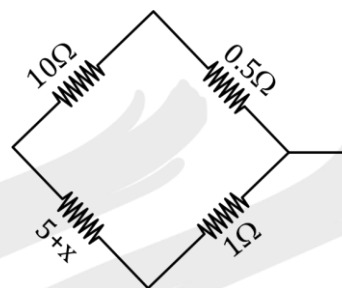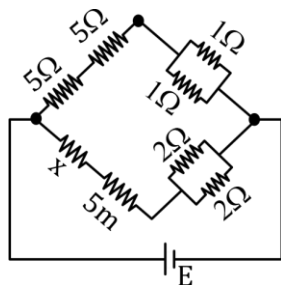



$$(5 + x)(0.5) = 1 \times 10$$

$$2.5 + 0.5x = 10$$

$$0.5x = 7.5$$

$$x = 15\Omega$$

9.

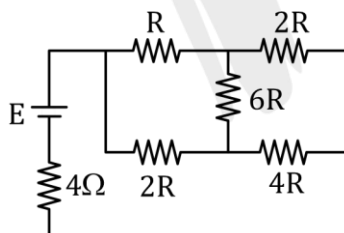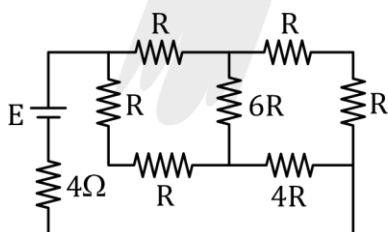


$$R_{eq} = \frac{3R \times 6R}{3R + 6R} = \frac{18R^2}{9R} = 2R$$

For maximum power

$$2R = 4\Omega$$

$$R = 2\Omega$$

Link to View Video Solution:  [Click Here](#)

10. $R_{AB} = R/2$

11. $R_{AB} = 2$ [Net resistance of infinite Series] + 1

In parallel net resistance is always less than the small estone

$$1 < R_{AB} < 3\Omega$$

Net resistance of infinite series is less than 1 .

12. $i_p = i_Q$

$$v_p > v_Q$$