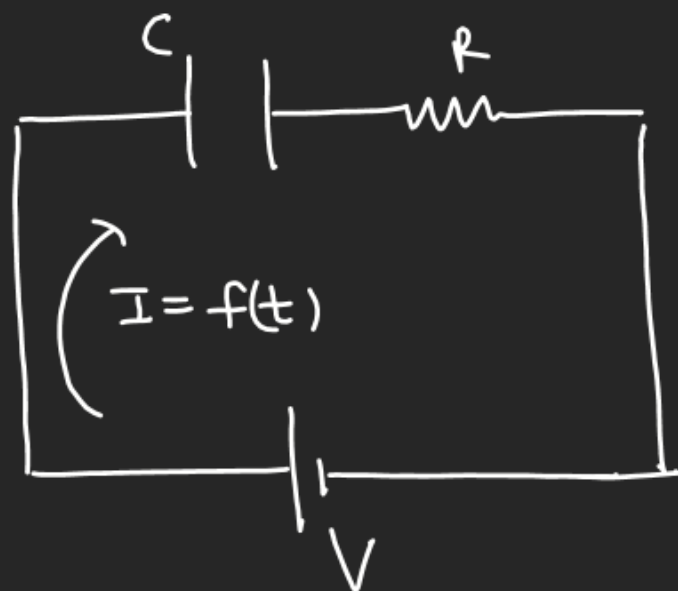


CURRENT ELECTRICITY

Power dissipated in R-C Ckt → (*) Total heat energy dissipated

$$I = I_0 e^{-t/\tau}$$

$$I_0 = \left(\frac{V}{R} \right)$$



$$P = I^2 R$$

$$P = (I_0 e^{-t/\tau})^2 R$$

$$P = (I_0^2 R) e^{-2t/\tau}$$

$$\rightarrow P = f(t)$$

$$P = \frac{dH}{dt} \Rightarrow \int_0^H dH = \int_0^\infty P \cdot dt$$

$$H = I_0^2 R \int_0^\infty e^{-2t/\tau} dt$$

$$H = I_0^2 R \int_0^\infty e^{(-\frac{2}{\tau})t} dt$$

$$H = I_0^2 R \left[\frac{e^{-\frac{2}{\tau}t}}{(-\frac{2}{\tau})} \right]_0^\infty$$

$$H = I_0^2 R \times \left(-\frac{\tau}{2} \right) [e^{-\infty} - e^0]$$

$$H = \frac{I_0^2 R \tau}{2}$$

$$I_0 = \frac{V}{R}$$

$$\int e^x \cdot dx = e^x$$

$$H = \frac{V^2}{R^2} \times R \times \frac{RC}{2}$$

$$H = \frac{1}{2} C V^2$$

$$H = U$$

$$\int e^{-\alpha x} \cdot dx = \frac{e^{-\alpha x}}{-\alpha}$$

CURRENT ELECTRICITY

$$\int e^{-\alpha x} dx = \left[\frac{e^{-\alpha x}}{-\alpha} \right]$$

44 Find avg power in the interval $t=0$ to $t=\tau$ in R-C Ckt during discharging of Capacitor:-

$$P = I^2 R$$

$$P_{\text{inst}} = (I_0^2 R e^{-2t/\tau})$$

$$P_{\text{avg}} = \frac{\frac{I = I_0 e^{-t/\tau}}{\int_0^\tau P \cdot dt}}{\int_0^\tau dt} = \frac{I_0^2 R}{\tau} \int_0^\tau e^{-\frac{2t}{\tau}} dt$$

$$P_{\text{avg}} = \frac{I_0^2 R}{\tau} \frac{[e^{-\frac{2t}{\tau}}]_0^\tau}{(-\frac{2}{\tau})} = -\frac{I_0^2 R}{2} [e^{-2} - e^0]$$

$$P_{\text{avg}} = -\frac{I_0^2 R}{2} \left(\frac{1}{e^2} - 1 \right) = \frac{I_0^2 R}{2} \left(1 - \frac{1}{e^2} \right) = \frac{V^2}{2R} \left(1 - \frac{1}{e^2} \right) \checkmark$$

$$I_0 = \frac{V}{R}$$


$$y = f(x)$$

$$y_{\text{avg}} = \left[\frac{\int_{x_i}^{x_f} y \cdot dx}{\int_{x_i}^{x_f} dx} \right]$$




Find the time when energy stored in the capacitor become half of its maximum value during discharging of capacitor??

Solⁿ

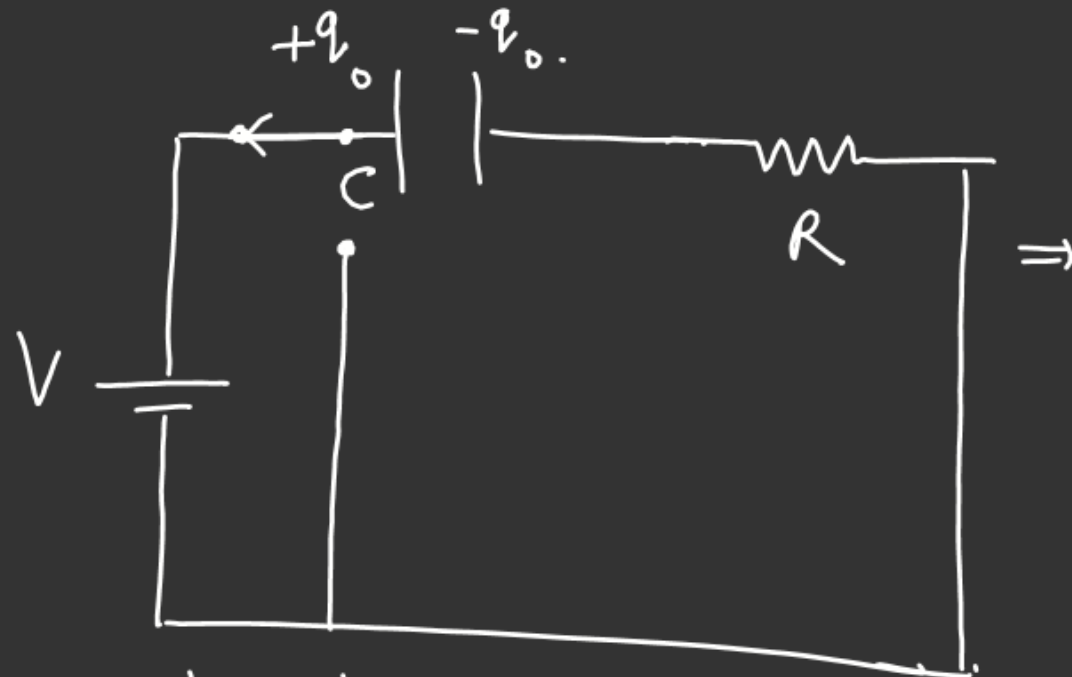

\Rightarrow

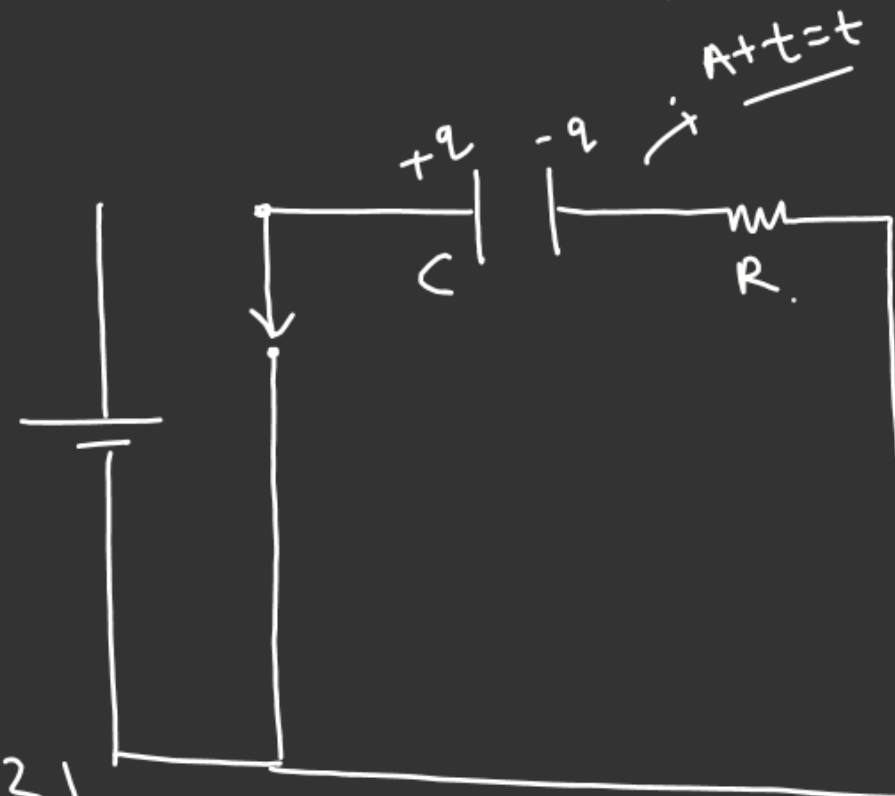

During discharging.

$q \rightarrow f(t)$

$$(q = q_0 e^{-t/\tau})$$

$$U = \frac{q^2}{2C}$$

$$U = \frac{q_0^2}{2C} (e^{-2t/\tau})$$

Energy at any instant in the capacitor during discharging

According to question

$$U_{\max} = \left(\frac{q_0^2}{2C} \right)$$

$$U = \frac{U_{\max}}{2}$$

$$\frac{q_0^2}{2C} e^{-2t/\tau} = \frac{1}{2} \left(\frac{q_0^2}{2C} \right)$$

$$\Rightarrow e^{-2t/\tau} = \frac{1}{2} \Rightarrow$$

$$-\frac{2t}{\tau} = -\ln 2$$

$$t = \left(\frac{\tau \ln 2}{2} \right) = \tau \left(\frac{0.693}{2} \right) = 0.34\tau$$

CURRENT ELECTRICITY

Q8.

During discharging of R-C Ckt
find time when

$$q = q_0 (1 - e^{-t/\tau})$$

- Current become half of its maximum value
- Charge become half of its maximum value

Solⁿ

$$I = I_0 e^{-t/\tau}$$

$$I = I_0/2$$

$$I_0 e^{-t/\tau} = (I_0/2)$$

$$e^{-t/\tau} = \frac{1}{2}$$

$$t = \tau \ln 2$$

$$q = q_0 e^{-t/\tau}$$

$$q = (q_0/2)$$

$$\frac{q_0}{2} = q_0 e^{-t/\tau}$$

$$\frac{1}{2} = e^{-t/\tau}$$


$$(-t/\tau) = \ln(1/2) = -\ln(2)$$

$$t = \tau \ln 2 \quad \checkmark$$


Initially Capacitor is uncharged. At $t=0$ SW is closed.
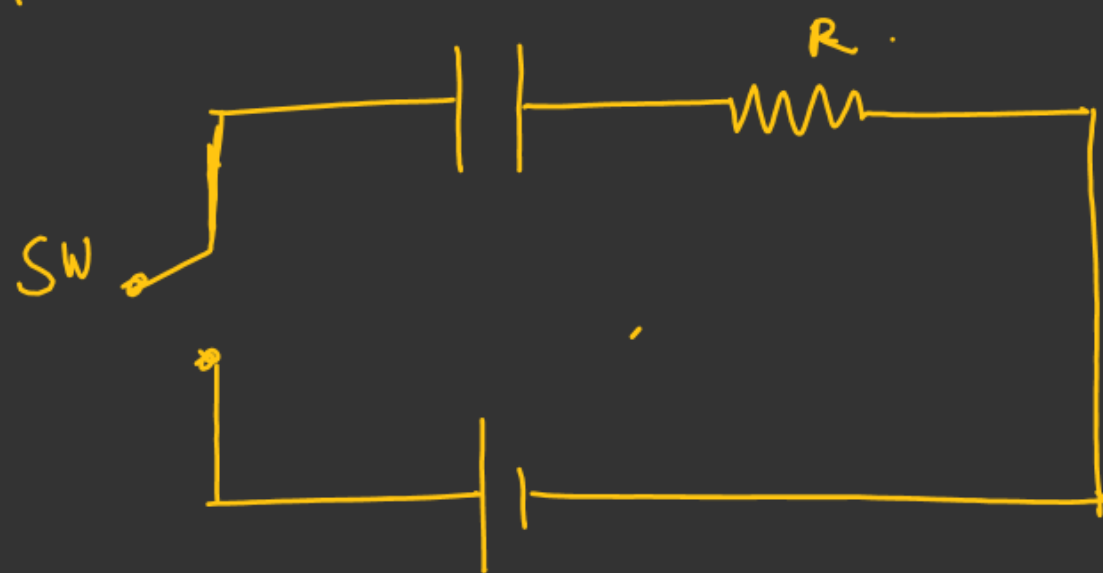
#

Find Charge on the Capacitor as a function of time if
 $R = (R_0 + \alpha t)$ (where R_0 & α are constant)



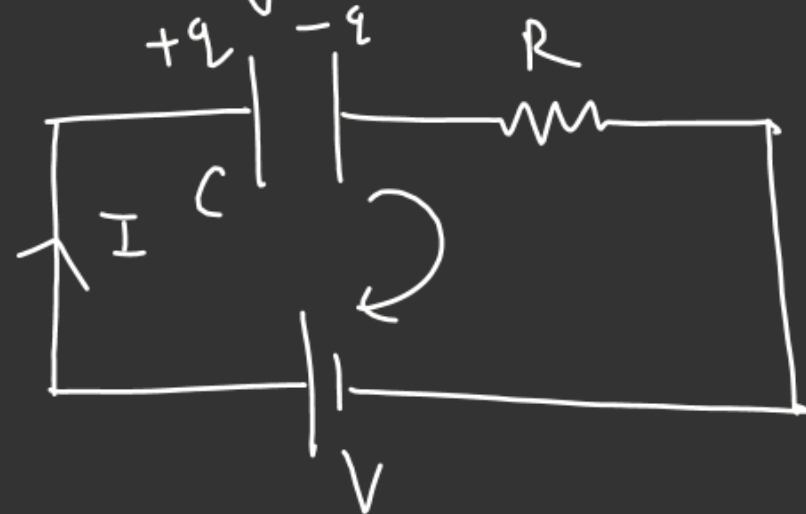let, at $t=0$, Switch is closed. at $t=t$, let
 Charge on the Capacitor be q .



K.V.L

$$V - \frac{q}{C} - iR = 0$$

$$i = +\left(\frac{dq}{dt}\right)$$

$$V - \frac{q}{C} - R \frac{dq}{dt} = 0$$

$$V - \frac{q}{C} = R \frac{dq}{dt}$$

$$\int_0^q \frac{dq}{CV - q} = \frac{1}{C} \int_0^t \frac{dt}{R_0 + \alpha t}$$

$$\frac{CV - q}{t} = CR \frac{dq}{dt}$$

CURRENT ELECTRICITY

$$\int_0^q \frac{dq}{CV - q} = \frac{1}{C} \int_0^t \frac{dt}{R_0 + \alpha t}$$

$$\frac{\ln [CV - q]_0^q}{(-1)} = \frac{1}{C} \frac{\ln [R_0 + \alpha t]_0^t}{\alpha}$$

$$\ln \left[\frac{CV - q}{CV} \right] = \frac{-1}{C\alpha} \ln \left[\frac{R_0 + \alpha t}{R_0} \right]$$

$$\ln \left[\frac{CV - q}{CV} \right] = \ln \left[\frac{R_0 + \alpha t}{R_0} \right]^{-\frac{1}{C\alpha}}$$

$$\frac{CV - q}{CV} = \left(\frac{R_0 + \alpha t}{R_0} \right)^{-\frac{1}{C\alpha}}$$


$$CV - q = CV \left[\frac{R_0 + \alpha t}{R_0} \right]^{-\frac{1}{C\alpha}}$$

$$q = CV - CV \left[\frac{R_0 + \alpha t}{R_0} \right]^{-\frac{1}{C\alpha}}$$

$$q = CV \left[1 - \left[1 + \frac{\alpha t}{R_0} \right]^{-\frac{1}{C\alpha}} \right]$$

CURRENT ELECTRICITY

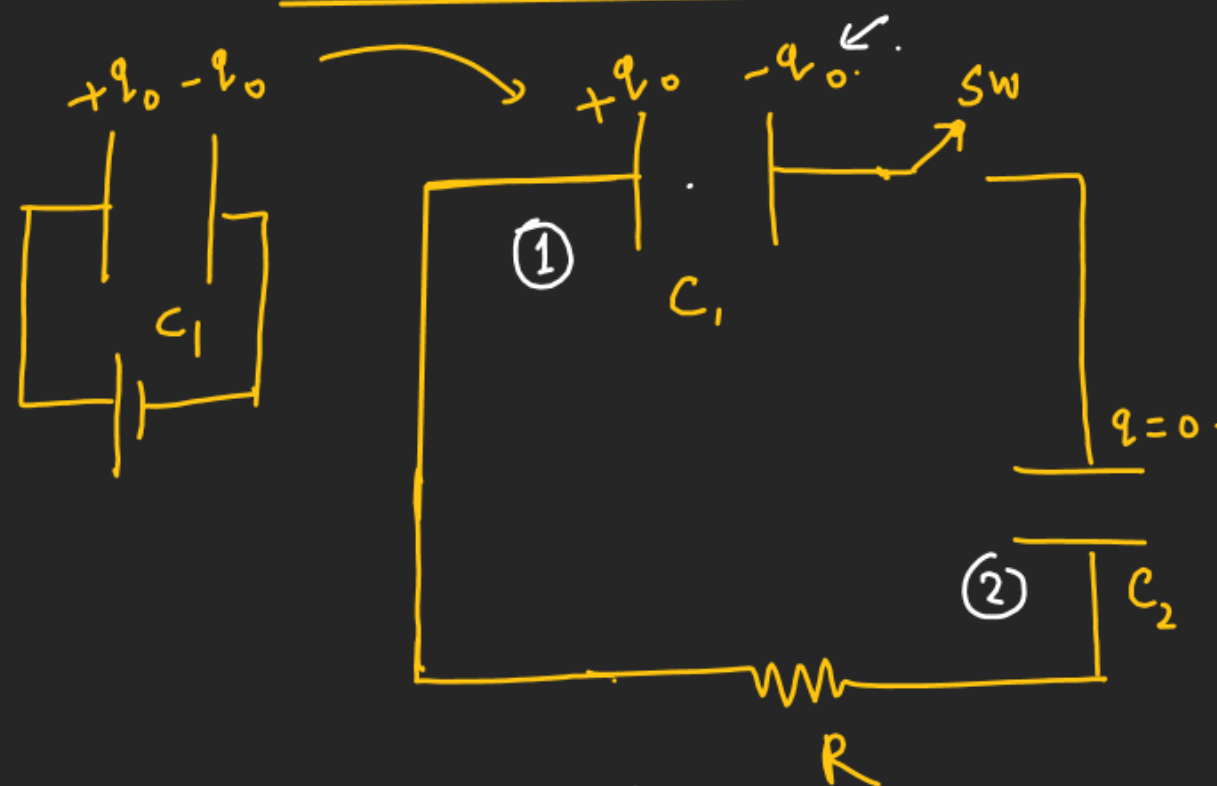
Case of 2-Capacitors in R-C Ckt (one discharging and other Charging)



(flow $\rightarrow (q_0 - q)$
of Charge
in the ckt)

Switch is closed at $t=0$. find $I = f(t)$.

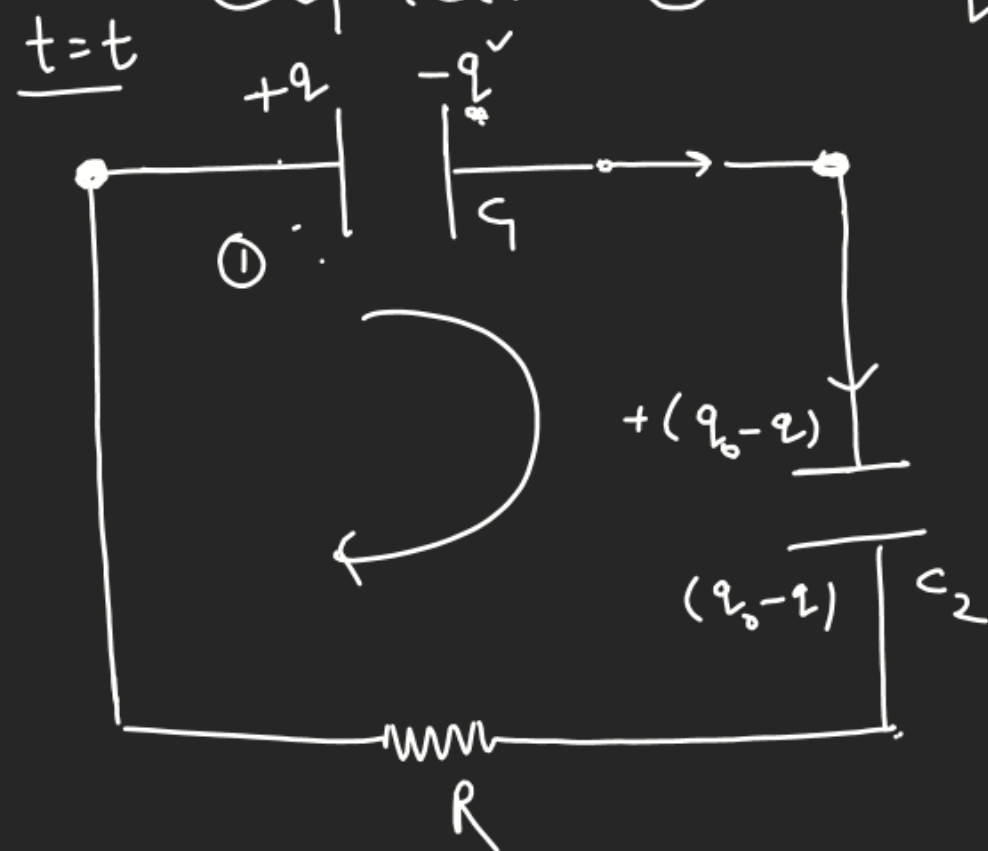At any time $t=t$; let Charge on the
Capacitor (1) be q .



Charge flow in the ckt

$$I = \frac{d}{dt}(q_0 - q)$$

$$I = -\frac{dq}{dt}$$

$$[V_{C_1} = V_{C_2} + V_R]$$

$$\frac{q}{C_1} = \frac{q_0 - q}{C_2} + IR$$

CURRENT ELECTRICITY

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C}$$

$$\frac{q}{C_1} = \left(\frac{q_0 - q}{C_2} \right) + IR$$

$$I = (-dq/dt)$$

$$q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{q_0}{C_2} - R \frac{dq}{dt}$$

$$\int_{q_0}^q \frac{dq}{Cq_0 - C_2q} = \frac{1}{RC_2C} \int_0^t dt$$

$$R \frac{dq}{dt} = \frac{q_0}{C_2} - q \left(\frac{1}{C} \right)$$

$$\frac{dq}{dt} = \frac{Cq_0 - C_2q}{RC_2C}$$

$$\ln [Cq_0 - C_2q]_{q_0}^q = \frac{1}{RC_2C} t$$

$$\ln [Cq_0 - C_2q] - \ln (Cq_0 - C_2q_0) = -\frac{1}{RC} t$$

$$\ln \left(\frac{Cq_0 - C_2q}{Cq_0 - C_2q_0} \right) = -\frac{1}{RC} t$$

$$\ln \left[\frac{Cq_0 - C_2 q}{Cq_0 - C_2 q_0} \right] = -\frac{1}{RC} t$$

$$Cq_0 - C_2 \underline{q} = (Cq_0 - C_2 q_0) e^{-\frac{t}{RC}}$$

$$C_2 q = Cq_0 - (Cq_0 - C_2 q_0) e^{-t/RC}$$

$$\boxed{q = \frac{Cq_0}{C_2} - \left[\frac{Cq_0}{C_2} - q_0 \right] e^{-t/RC}}$$

$$C = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C = \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

$$q = \frac{C_1 q_0}{C_1 + C_2} - \left[\frac{C_1 q_0}{C_1 + C_2} - q_0 \right] e^{-t/RC}$$

$$q = \left(\frac{C_1 q_0}{C_1 + C_2} \right) - \left[\frac{-C_2 q_0}{C_1 + C_2} \right] e^{-t/RC}$$

$$q = \frac{q_0}{C_1 + C_2} [C_1 + C_2 e^{-t/RC}]$$

✓