

Q.5 Find out the value of current through  $2\Omega$  resistance for the given circuit.


(2005)

(A) Zero ✓

(B) 2 A

(C) 5 A

(D) 4 A.

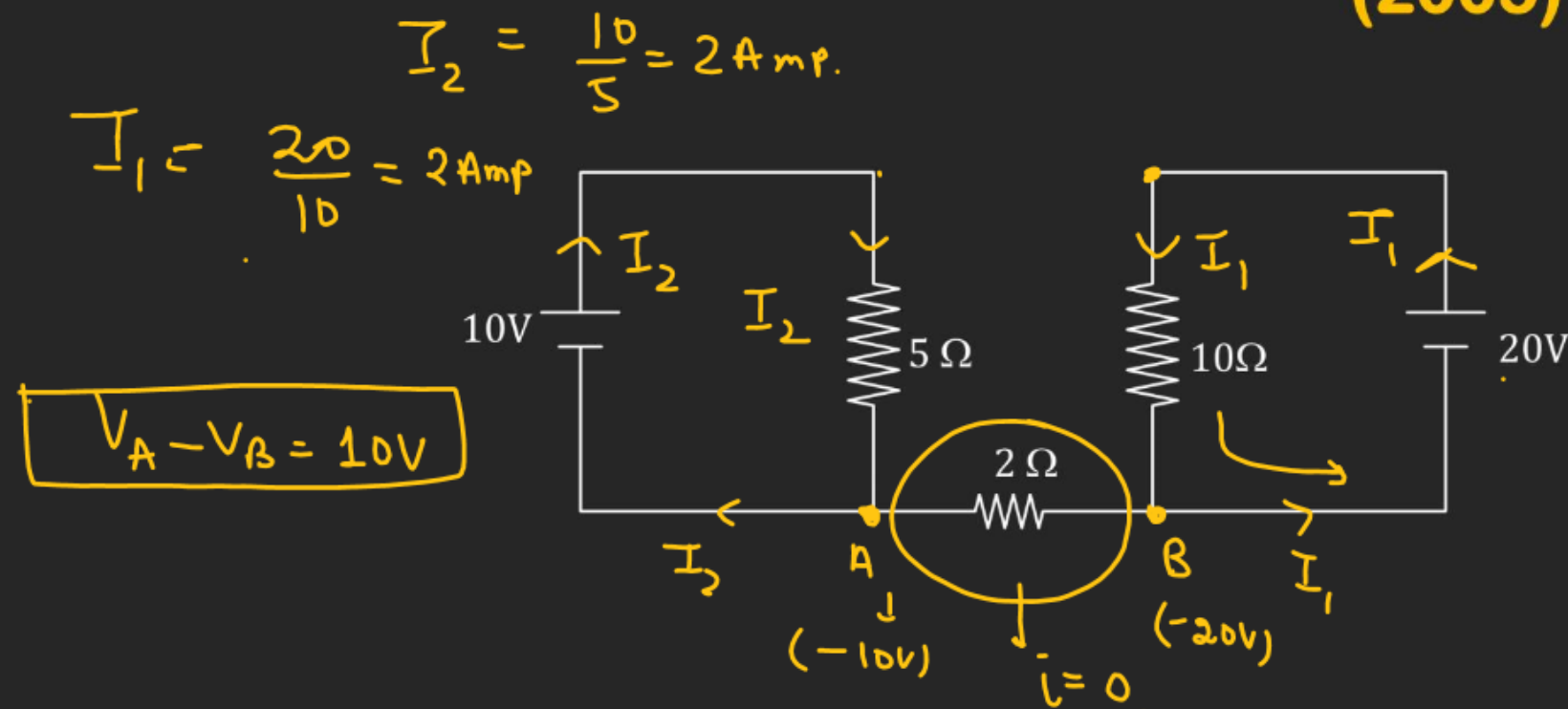

Q.6 In the circuit shown in figure the current through

(A) the  $3\Omega$  resistor is  $0.50$  A.

(B) the  $3\Omega$  resistor is  $0.25$  A.

(C) the  $4\Omega$  resistor is  $0.50$  A.



(D) the  $4\Omega$  resistor is  $0.25$  A.

$$V = I_1 R_1 = I_2 R_2$$

if  $R_1 = R_2$   
 $I_1 = I_2$

$$I = \frac{9}{(R_{eq})_{AB}}$$

$$I = \frac{9}{9} = 1 \text{ Amp.}$$

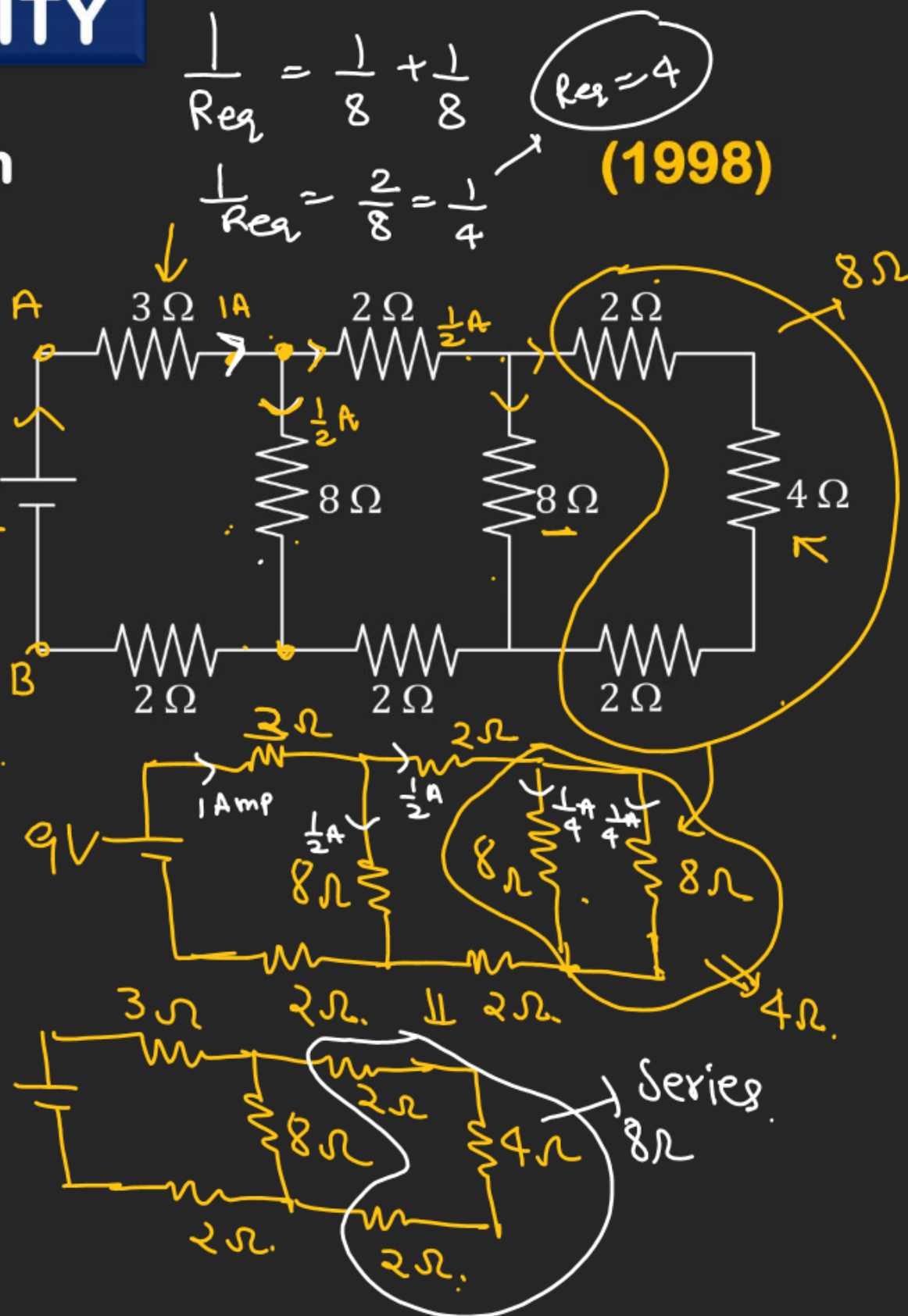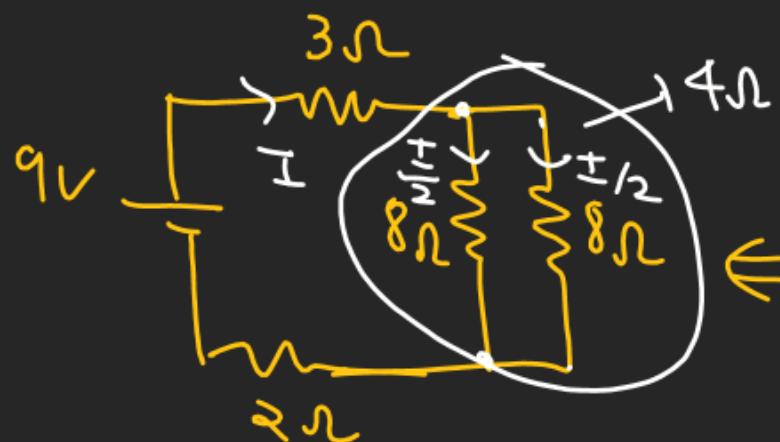

Q.7 For the circuit shown in the figure

(A) the current  $I$  through the battery is 7.5 mA

(B) the potential difference across  $R_L$  is 18 V

(C) ratio of powers dissipated in  $R_1$  and  $R_2$  is 3

(D) if  $R_1$  and  $R_2$  are interchanged, magnitude of the power dissipated in  $R_L$

will decrease by a factor of 9.

⇒ K.C.L at P

$$\frac{x-24}{2} + \frac{x}{6} + \frac{2x}{3} = 0$$

$$\left( \frac{x}{2} + \frac{x}{6} + \frac{2x}{3} \right) = 12$$

$$\frac{3x+x+4x}{6} = 12$$

$$8$$

$$8x = 72$$

$$\Rightarrow x = 9 \text{ Volt}$$

$$I = \frac{(24-9)}{2} \times 10^{-3}$$

$$I = \frac{15}{2} \times 10^{-3}$$

$$= 7.5 \text{ mA}$$

$$I_2 = \frac{9}{6} \text{ mA}$$

$$= \frac{3}{2} \text{ mA}$$

$$I_1 = \frac{15}{2} - \frac{3}{2} = \frac{12}{2} = 6 \text{ Amp}$$


$$P_{2k\Omega} = \left( \frac{15}{2} \right)^2 \times 2 \quad (2009)$$

$$P_{6k\Omega} = \left( \frac{3}{2} \right)^2 \times 6$$


$$\frac{P_{2k\Omega}}{P_{6k\Omega}} = \left( \frac{15}{2} \times \frac{2}{3} \right)^2 \times \frac{2}{6} = 25 \times \frac{1}{3}$$

$$P_{R_L} = (6)^2 \times \frac{3}{2}$$

$$= 54 \text{ watt}$$

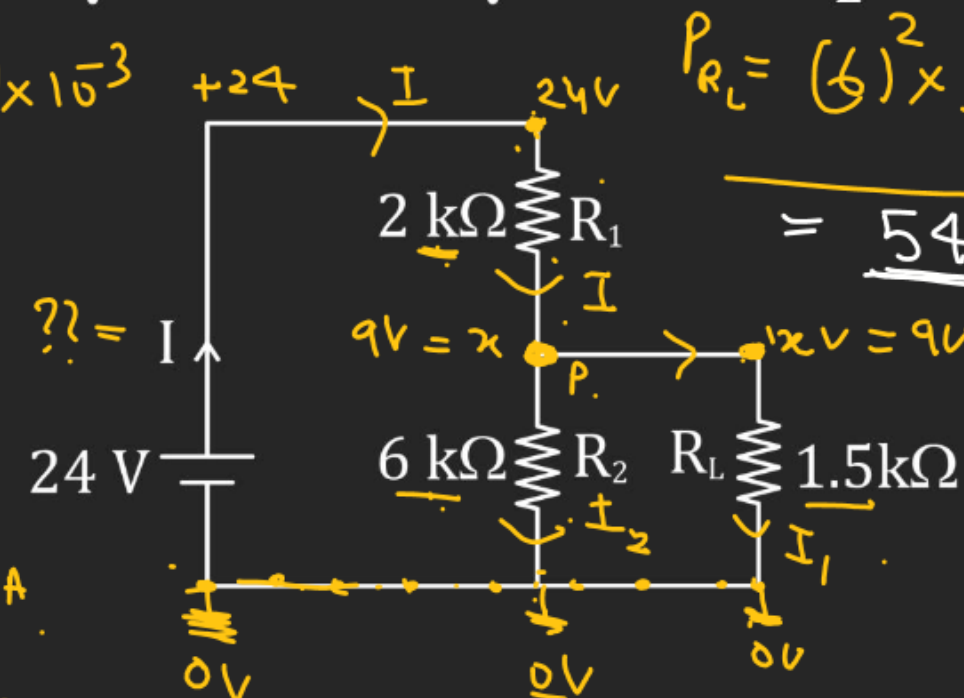

## CURRENT ELECTRICITY

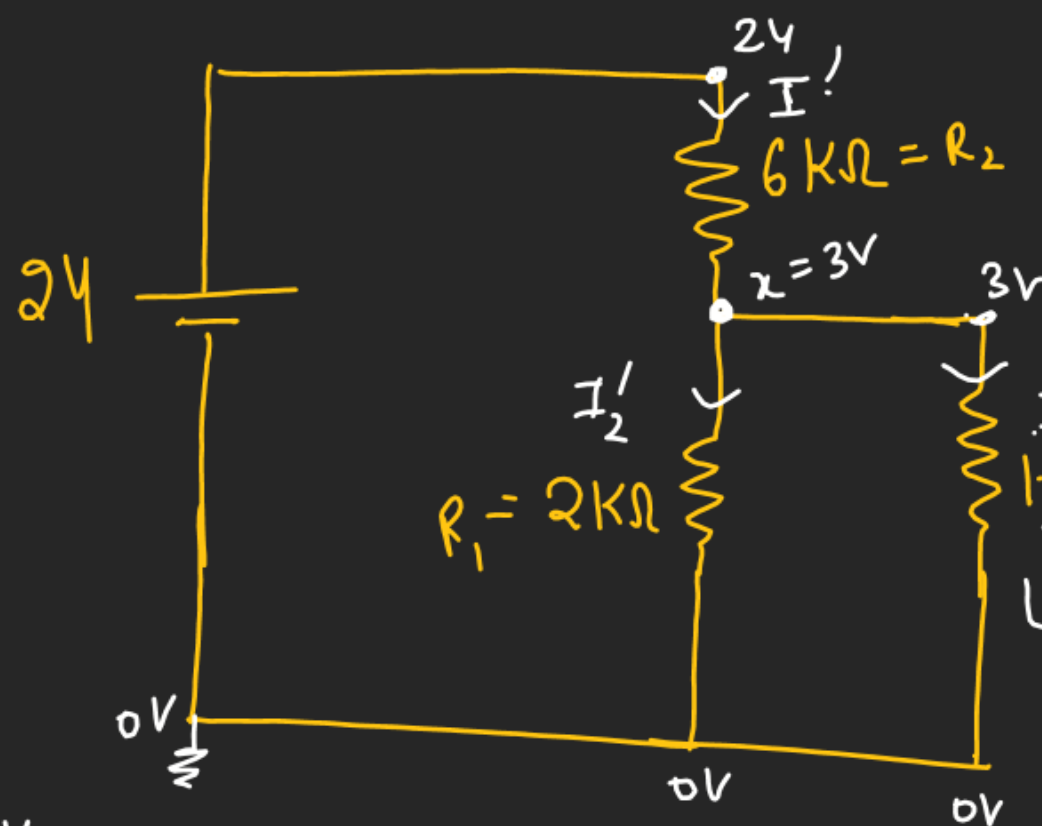

$$I' = \frac{24-3}{6} = \frac{21}{6} = 7/2 \text{ Amp.}$$

$$I'_1 = \frac{3}{3/2} = 2 \text{ Amp.}$$

$$P'_{R_L} = (I'^2_1) \times R_L$$

$$= 4 \times \frac{3}{2}$$

$$= \underline{6 \text{ watt}}$$

$$\frac{x-24}{6} + \frac{x}{2} + \frac{2x}{3} = 0$$

$$\left( \frac{x}{6} + \frac{x}{2} + \frac{2x}{3} \right) = 4 \Rightarrow 8x = 24$$

$$\frac{x+3x+4x}{6} = 4 \Rightarrow \underline{x = 3 \text{ Volt}}$$



Q.8 For the resistance network shown in the figure, choose the correct option(s).

(2012)

(A) The current through PQ is zero. ✓


~~(B)  $I_1 = 3$  A.~~

~~(C) The potential at S is less than that at Q.~~

~~(D)  $I_2 = 2$  A~~

$$R_{eq} = \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4 \Omega$$

$$I_1 = \frac{12}{4} = 3 \text{ Amp.}$$

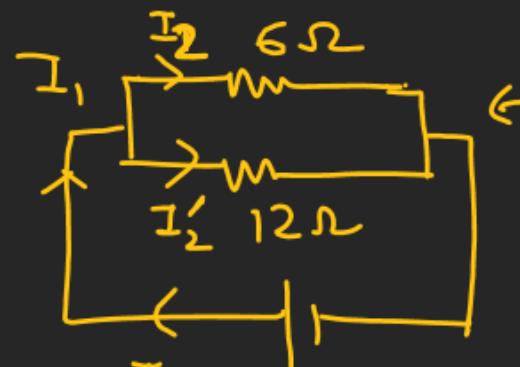



$$I_2 \cdot 6 = I_2' \cdot 12$$

$$I_2 = 2I_2'$$

$$I_2 + I_2' = 3$$

$$2I_2' + I_2' = 3$$
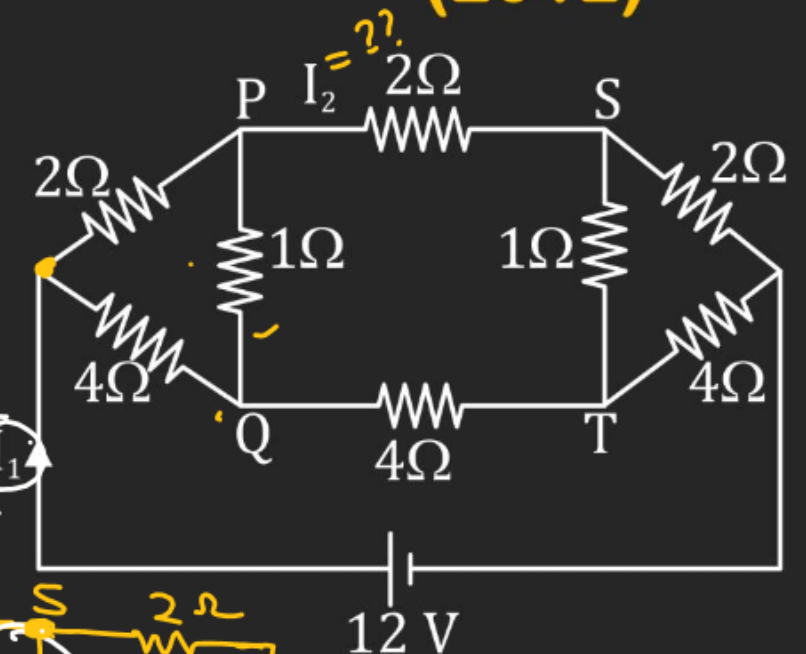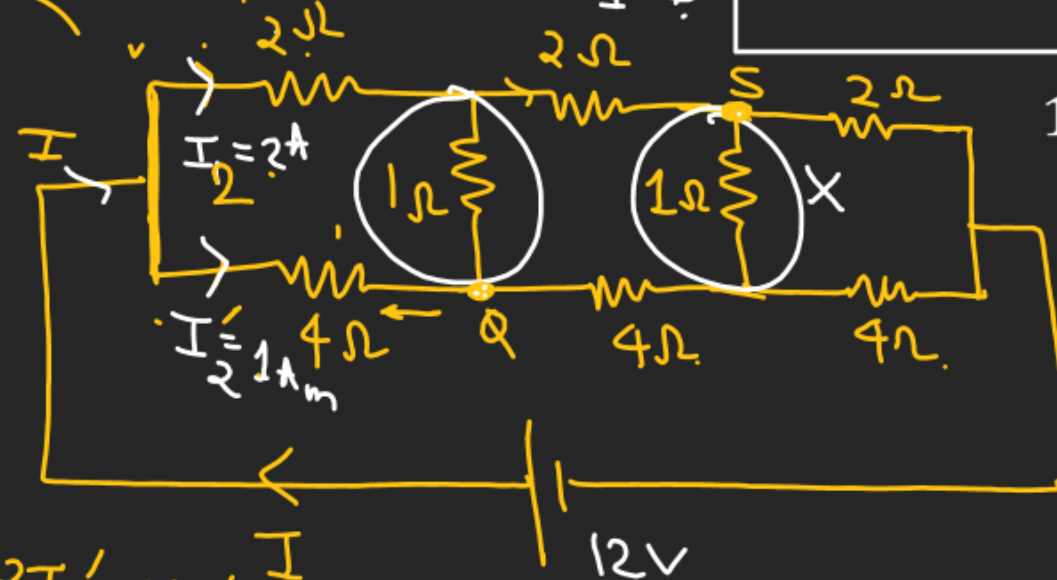
$$I_2' = 1 \text{ Amp.}, I_2 = 2 \text{ Amp.}$$



$$V_Q + 4 - 4 - 4 = V_S$$

$$V_Q - V_S = 4$$

$$V_Q = 4 + V_S$$

$$V_Q > V_S$$

**Q.10** Two ideal batteries of emf  $V_1$  and  $V_2$  and three resistances  $R_1$ ,  $R_2$  and  $R_3$  are connected as shown in the figure. The current in resistance  $R_2$  would be zero if

- (A)  $V_1 = V_2$  and  $R_1 = R_2 = R_3$  *No dependency*
- (B)  $V_1 = V_2$  and  $R_1 = 2R_2 = R_3$
- (C)  $V_1 = 2V_2$  and  $2R_1 = 2R_2 = R_3$
- (D)  $2V_1 = V_2$  and  $2R_1 = R_2 = R_3$
- A B D
- $$\frac{x+V_1}{R_1} + \frac{(x-0)}{R_2} + \frac{x-V_2}{R_3} = 0$$


$$\left(\frac{x}{R_1} + \frac{x}{R_2} + \frac{x}{R_3}\right) + \frac{V_1}{R_1} - \frac{V_2}{R_3} = 0$$

$$x\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) = \frac{V_2}{R_3} - \frac{V_1}{R_1}$$


$$x = \left[ \frac{V_2 R_1 - V_1 R_3}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} \right]$$


$$x = 0 \text{ for current in } R_2 \text{ to be zero}$$

$$V_2 R_1 = V_1 R_3$$

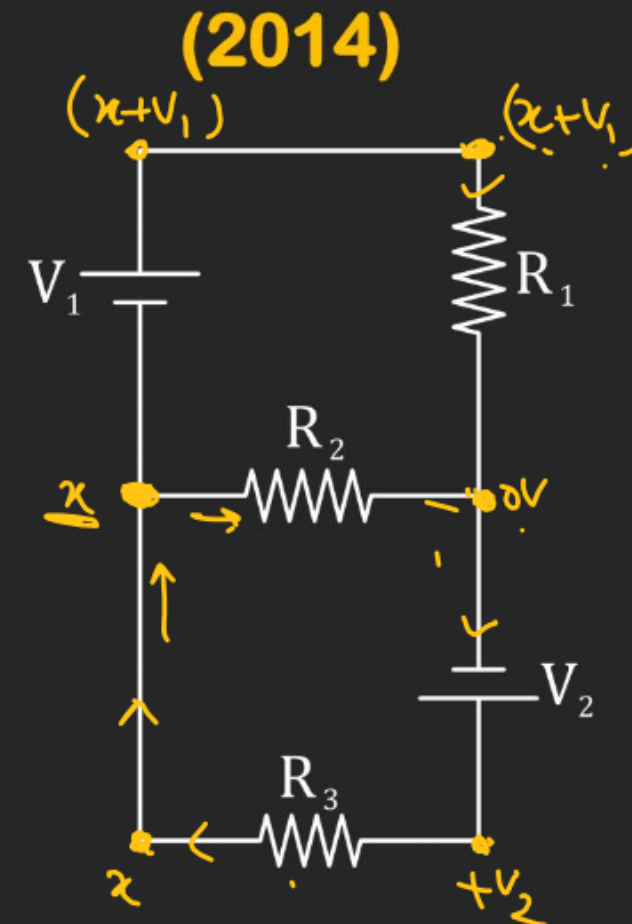

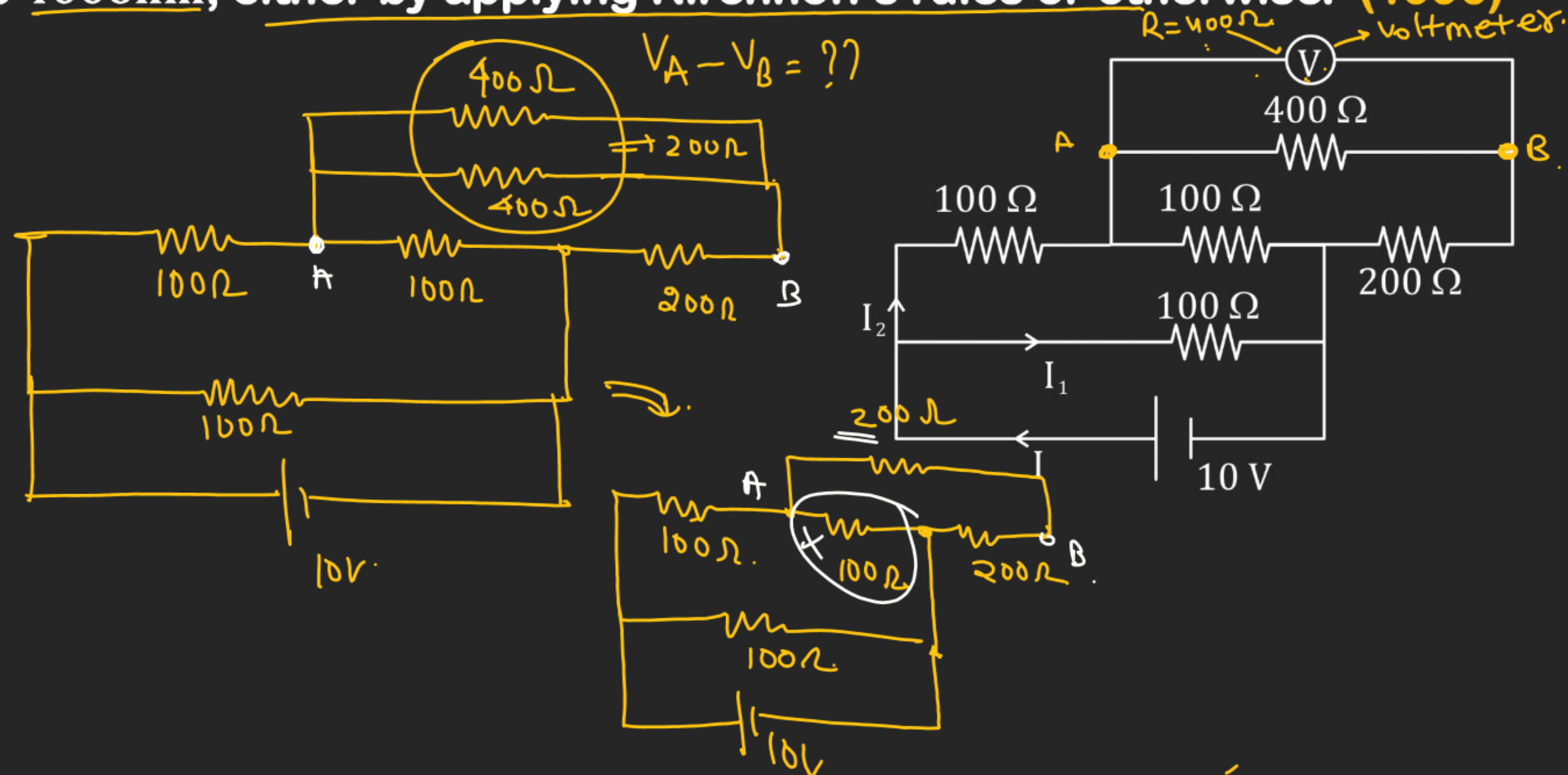**Q.12** An electrical circuit is shown in the figure. Calculate the potential difference across the resistor of 400ohm, as will be measured by the voltmeter V of resistance 400ohm, either by applying Kirchhoff's rules or otherwise. **(1996)**



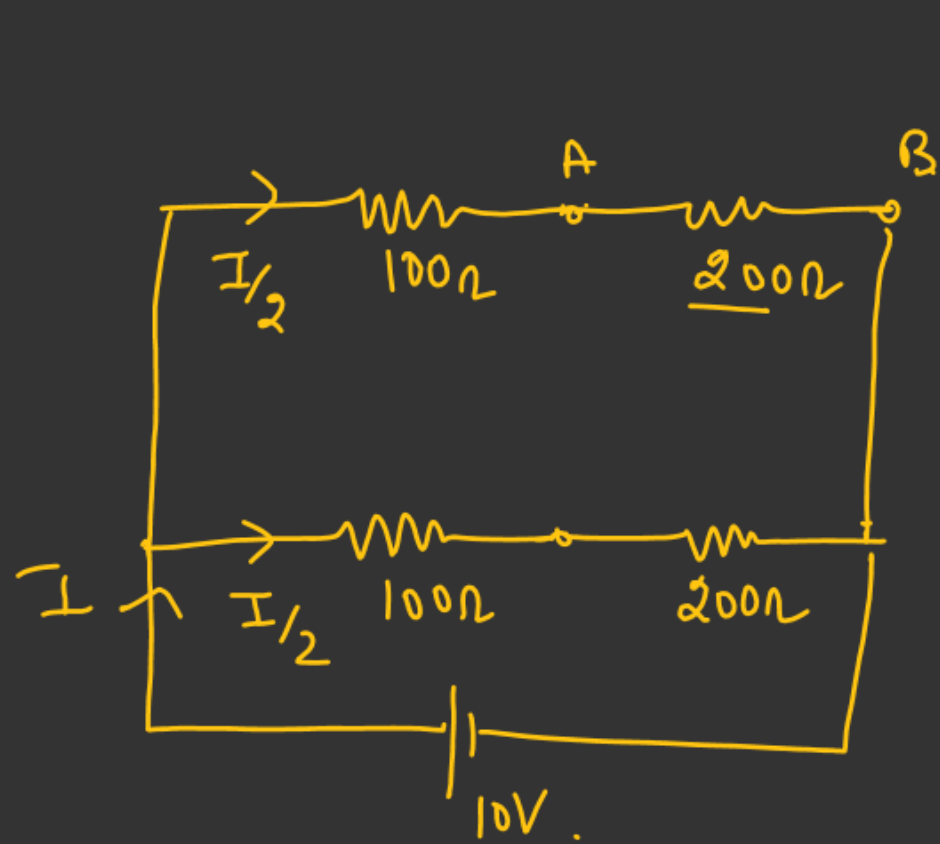

$$R_{eq} = 150\Omega$$

$$V_{AB} = \frac{1}{30} \times 200$$
$$= \frac{20}{3} \text{ Volt} \leftarrow$$

$$I = \frac{10}{150} = \left(\frac{1}{15}\right) \text{ Amp.}$$