

R-C Ckt

At $t=0$

→ Capacitor behave as zero resistance wire

At $t \rightarrow \infty$

→ Capacitor acts as a open ckt.

$$\rightarrow \begin{cases} q = q_0(1 - e^{-t/\tau}) \rightarrow \text{Charging} \\ q = q_0 e^{-t/\tau} \rightarrow \text{(Discharging)} \\ I = I_0 e^{-t/\tau} \end{cases}$$

(***) To find time constant of any R-C Ckt

Trick! → (Applicable for only one Capacitor in the Ckt)

$$\Rightarrow \tau = (R_{eq}) \cdot C$$

R_{eq} = [Equivalent resistance of the Ckt about the Capacitor]

[To find ' R_{eq} ' across the Capacitor Short all the battery i.e replaced the battery by zero resistance wire.]

R-C Ckt

At $t=0$

→ Capacitor behave as zero resistance wire

At $t \rightarrow \infty$

→ Capacitor acts as a open ckt.

$$\rightarrow \begin{cases} q = q_0(1 - e^{-t/\tau}) \rightarrow \text{Charging} \\ q = q_0 e^{-t/\tau} \rightarrow \text{(Discharging)} \\ I = I_0 e^{-t/\tau} \end{cases}$$

(***) To find time constant of any R-C Ckt


Trick! → (Applicable for only one Capacitor in the Ckt)

$$\Rightarrow \tau = (R_{eq}) \cdot C$$

R_{eq} = [Equivalent resistance of the Ckt about the Capacitor]


[To find ' R_{eq} ' across the Capacitor Short all the battery i.e replaced the battery by zero resistance wire.]

#

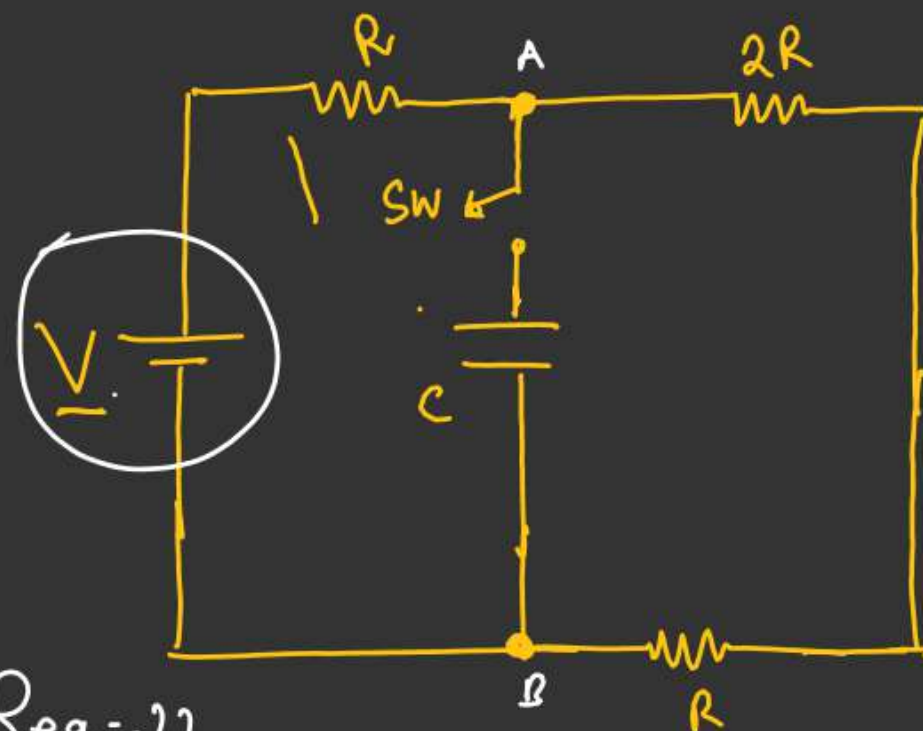Find $\tau = ??$. $R_{eq} = ??$

$$(R_{eq})_{AB} = \frac{3R \cdot R}{3R + R}$$
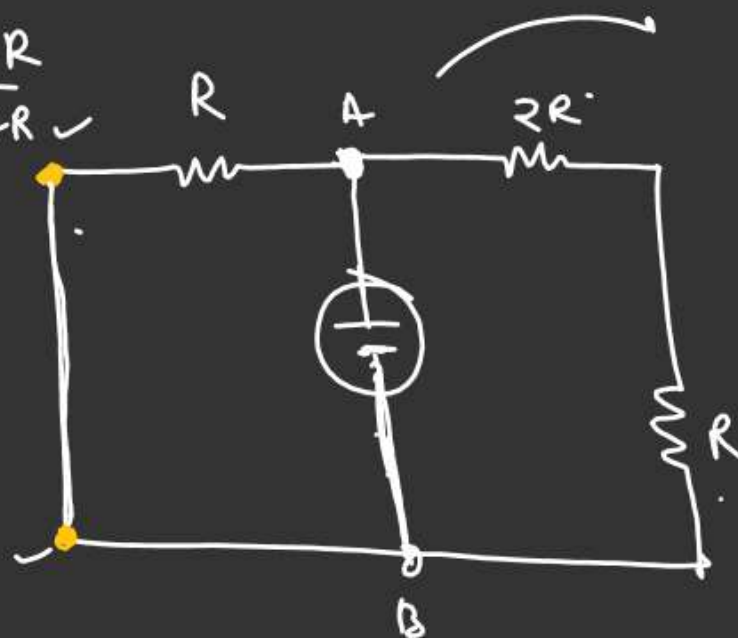
$$(R_{eq})_{AB} = \left(\frac{3R}{4}\right)$$



$$a) \tau = \frac{3RC}{4}$$

b) If capacitor is uncharged initially. Switch is closed at $t=0$. Find 'q' i.e. charge on capacitor as a function of time.


In general

$$q = q_0 (1 - e^{-t/\tau})$$

q_0 = maximum charge on the capacitor. (i.e. at the time of steady state)


$$q_0 = CV$$

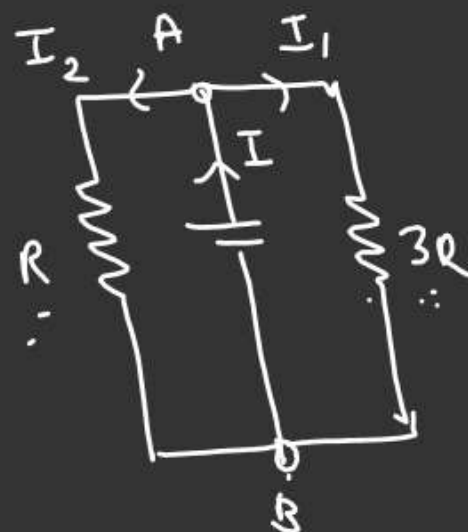→ Potential difference across the capacitor at the time of steady state



q_{\max} (At the time of steady state)

#

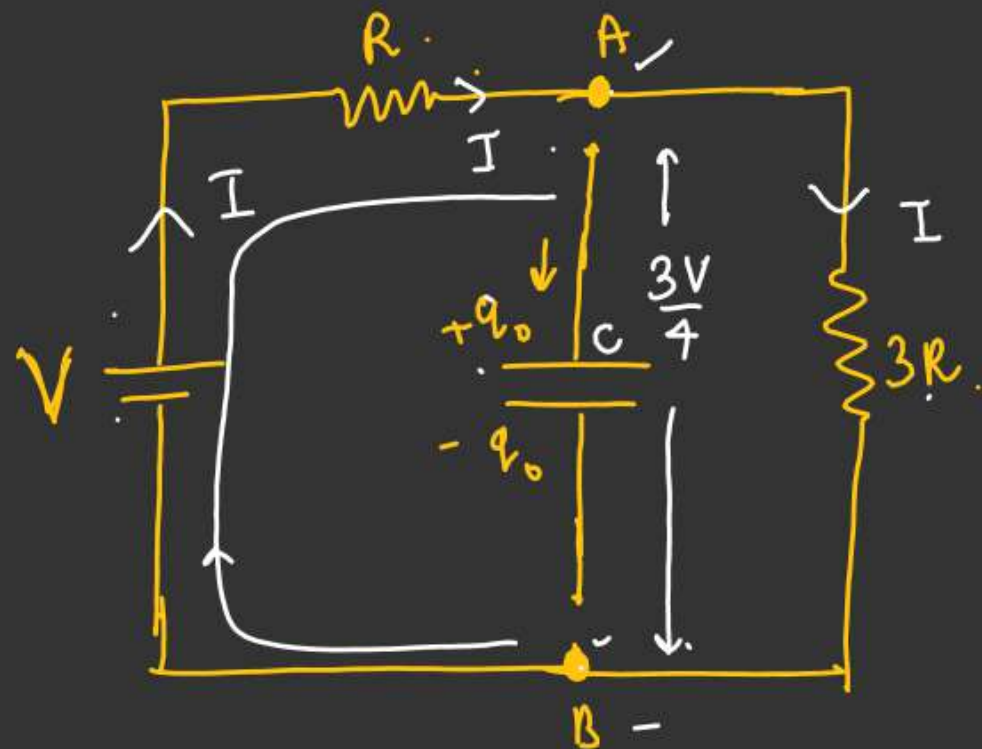

$$q_0 = \left(\frac{3CV}{4} \right)$$

$$q \rightarrow f(t)$$

$$q = q_0 (1 - e^{-t/\tau})$$

$$q = \frac{3CV}{4} \left(1 - e^{-\frac{4t}{3RC}} \right)$$



$$I = \left(\frac{V}{4R} \right)$$

$$V_B + V - IR = V_A$$

$$V_A - V_B = V - IR$$

$$= V - \frac{V}{4R} \times R$$

$$= V - \frac{V}{4} = \left(\frac{3V}{4} \right)$$

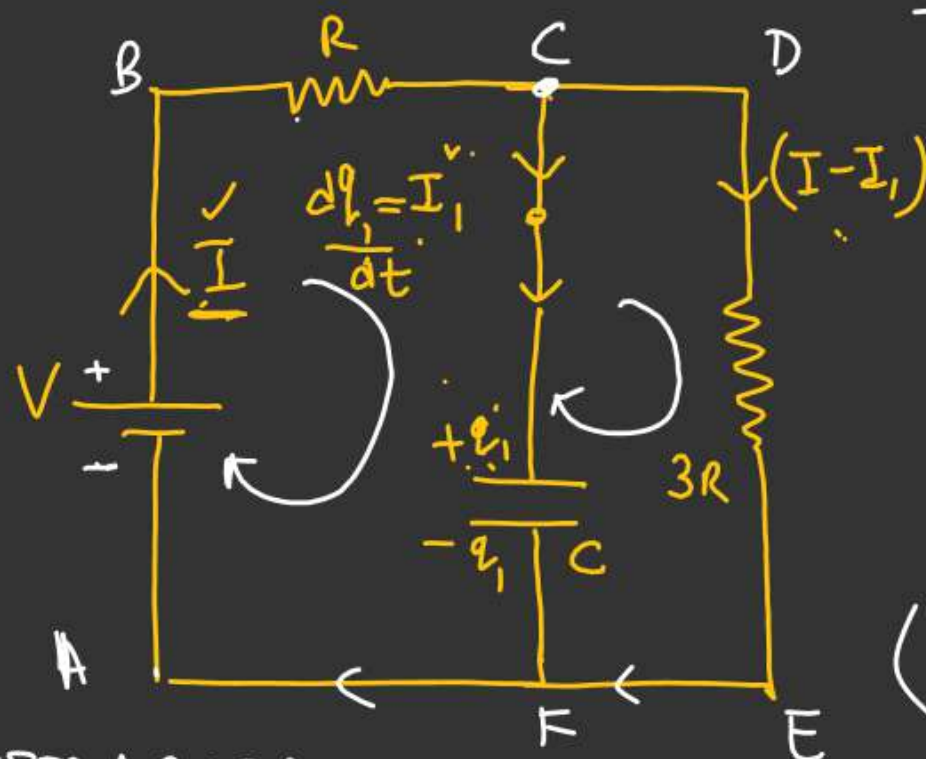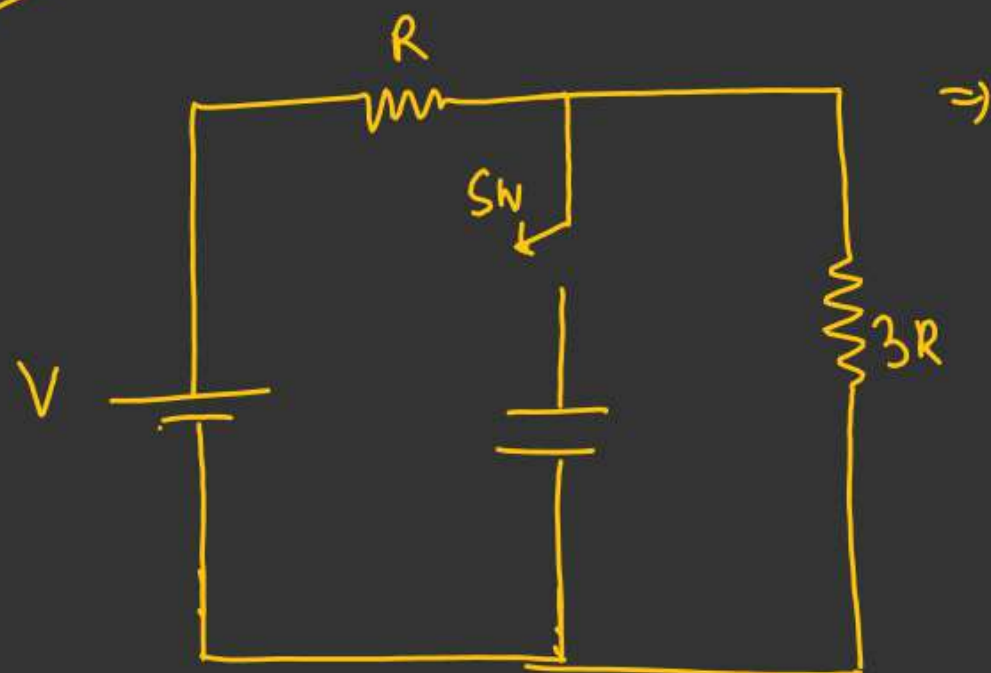Normal MethodAt $t=0$, Switch is closed.At $t=\tau$ K.V.L in the Closed loop ABCFA

$$V - \underline{I}R - \frac{q_1}{C} = 0 \quad \text{--- (1)}$$

KVL in the loop BDEAB

$$V - \underline{I}R - (I - I_1)3R = 0$$

$$V - IR - 3IR + 3I_1R = 0$$

$$V + 3I_1R = 4IR$$

$$IR = \left(\frac{V + 3I_1R}{4} \right) \quad \text{--- (2)}$$

$$I = \frac{V}{4R} + 3I_1$$

From (1) & (2)

$$V - \left(\frac{V + 3I_1R}{4} \right) - \frac{q_1}{C} = 0$$

$$\left(V - \frac{V}{4} \right) - \frac{3R}{4}I_1 - \frac{q_1}{C} = 0$$

$$\frac{3V}{4} - \frac{3R}{4} \left(\frac{dq_1}{dt} \right) - \frac{q_1}{C} = 0$$

$$\left(\frac{3V}{4} - \frac{q_1}{C} \right) = \frac{3R}{4} \left(\frac{dq_1}{dt} \right)$$

$$\frac{3V - 4q_1}{4C} = \frac{3R}{4} \left(\frac{dq_1}{dt} \right)$$

$$(3CV - 4q_1) = 3RC \left(\frac{dq_1}{dt} \right)$$

$$\int \frac{dx}{a+bx} = \ln\left(\frac{a+bx}{b}\right)$$

$$(3CV - 4q_1) = 3RC \frac{dq_1}{dt}$$

$$\int_0^{q_1} \frac{dq_1}{\underset{\substack{\downarrow \\ a}}{3CV} - \underset{\substack{\downarrow \\ b=-4}}{4}q_1} = \frac{1}{3RC} \int_0^t dt$$

$$\frac{\ln[3CV - 4q_1]_0^{q_1}}{(-4)} = \frac{1}{3RC} t$$

$$\ln\left[\frac{3CV - 4q_1}{3CV}\right] = -\frac{4}{3RC} t$$

$$3CV - 4q_1 = 3CV e^{-\frac{4t}{3RC}}$$

$$4q_1 = 3CV \left(1 - e^{-\frac{4t}{3RC}}\right)$$

$$q_1 = \left(\frac{3CV}{4}\right) \left(1 - e^{-\frac{4t}{3RC}}\right)$$

$$q_1 = \frac{3CV}{4} \left(1 - e^{-\frac{t}{\left(\frac{3RC}{4}\right)}}\right)$$

$$q = q_0 (1 - e^{-t/\tau})$$

$$(q_0 = \frac{3CV}{4}, \tau = \frac{3RC}{4})$$

$$I_1 = \frac{dq_1}{dt}$$

$$q_1 = \frac{3CV}{4} - \frac{3CV}{4} e^{-\frac{4t}{3RC}}$$

$$\frac{dq_1}{dt} = -\frac{3CV}{4} e^{-\frac{4t}{3RC}} \left(-\frac{4}{3RC}\right)$$

$$I_1 = \frac{V}{R} e^{-\frac{4t}{3RC}}$$

$I_1 \rightarrow f(t)$ in Capacitor


$$I \rightarrow f(t)$$

$$I = \frac{V}{4R} + 3I_1$$

$$I = \frac{V}{4R} + \frac{3V}{R} e^{-\frac{4t}{3RC}}$$

Find $\tau = ?$


a)

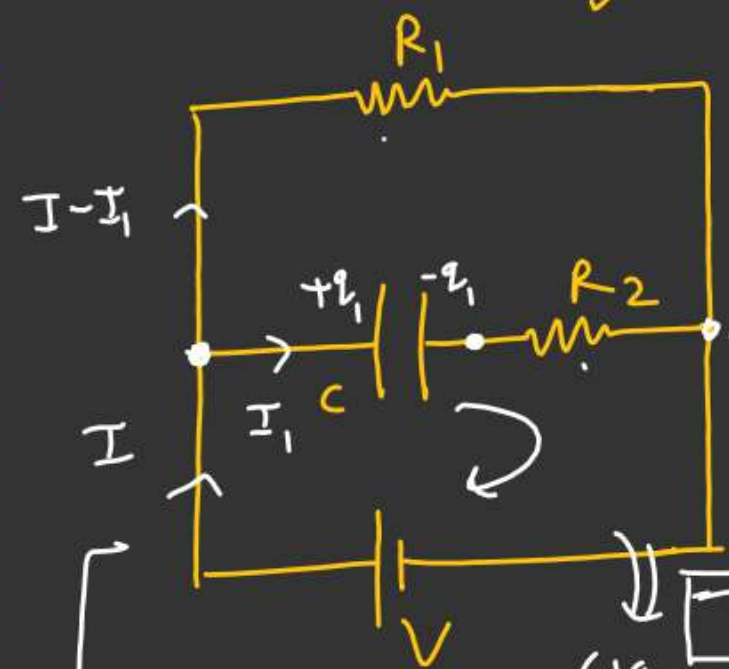


$$\tau = R_2 C$$

$$V - \frac{q_1}{C} - I_1 R_2 = 0$$

Trick

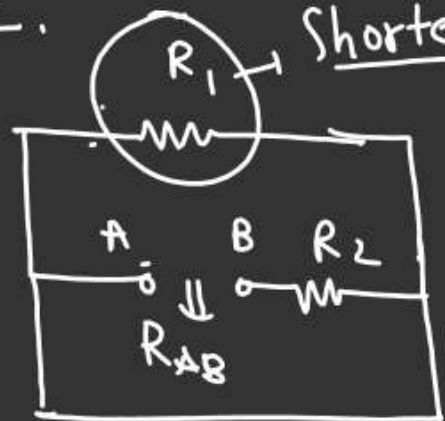


Shorted

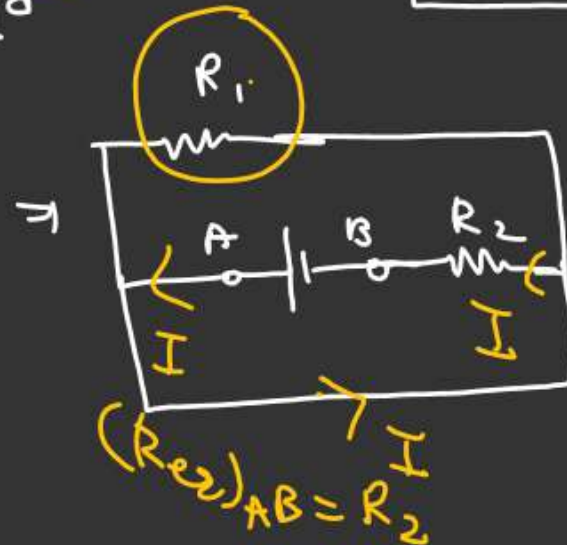


$$(R_{eq})_{AB} = R_2$$

b)

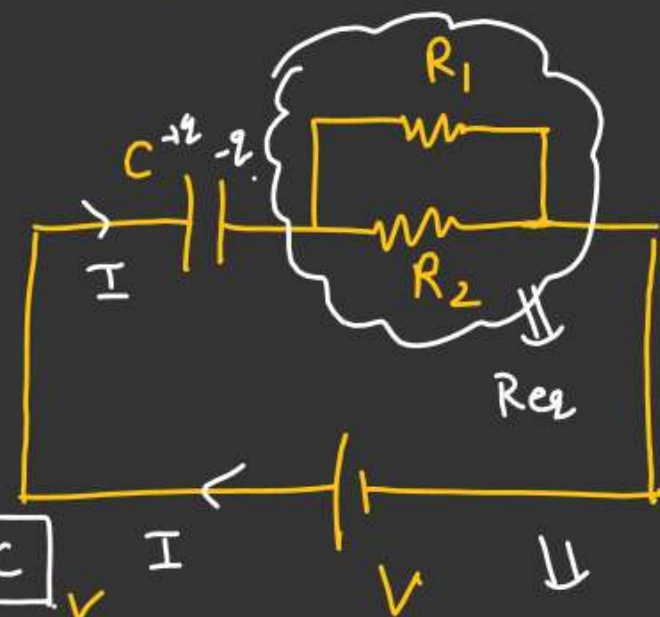


\Downarrow

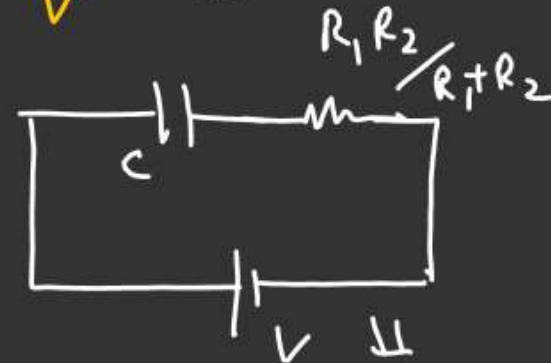

$$\tau = \frac{R_1 R_2 C}{R_1 + R_2}$$

c)

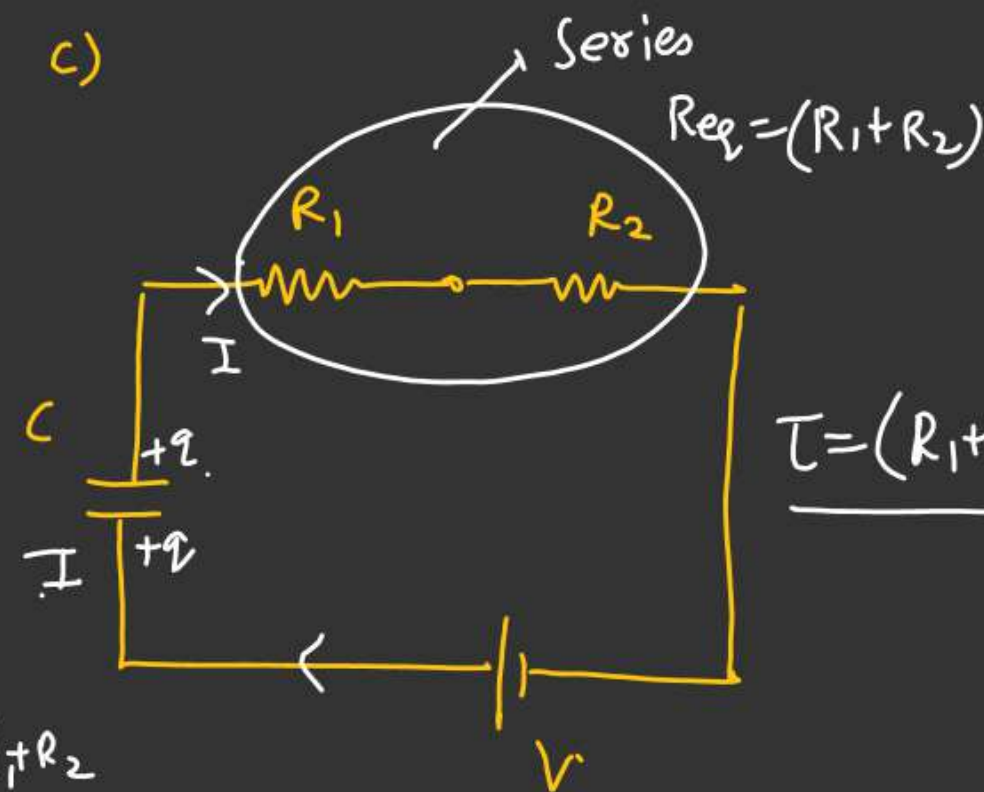


$$\tau = (R_1 + R_2) C$$

Nishant Jindal

28

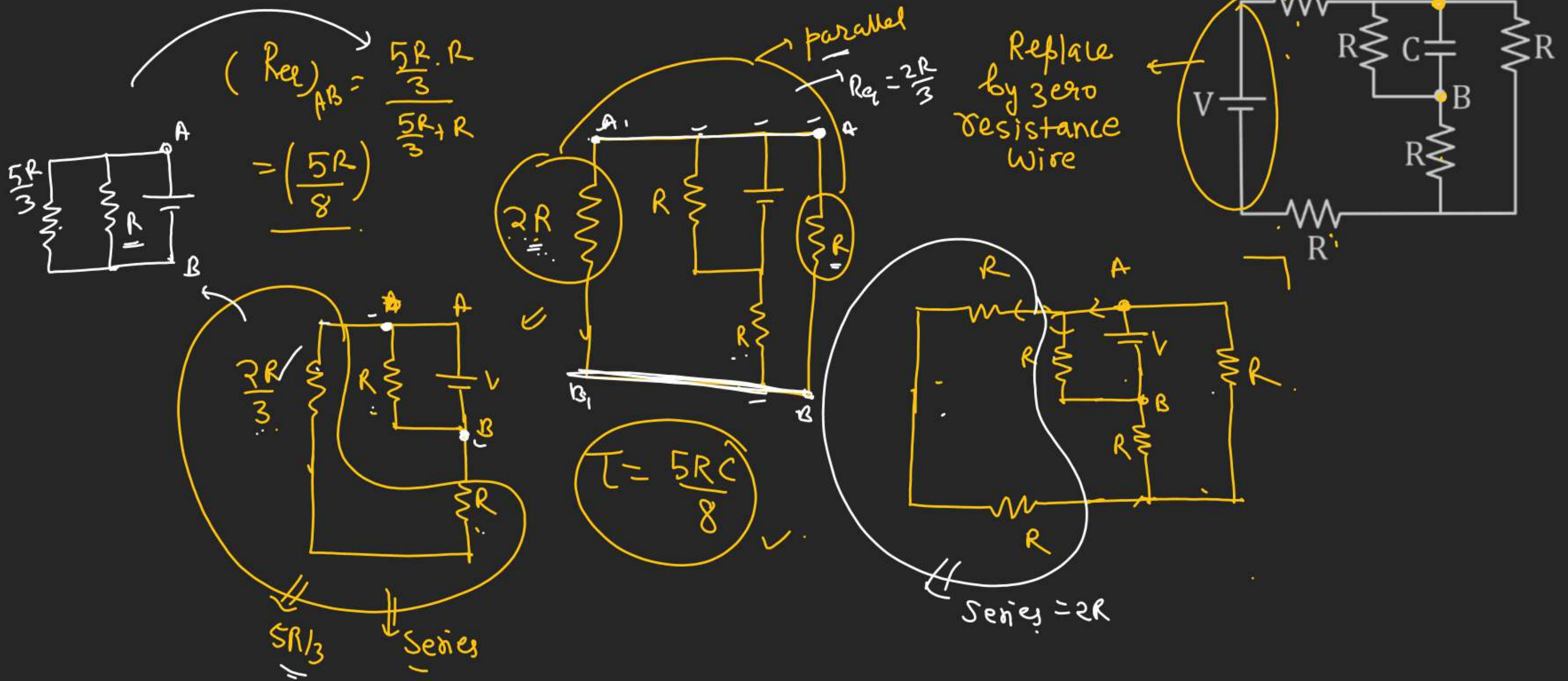Q.1 Calculate the constant of a circuit as shown in Fig. $\tau = ??$




CURRENT ELECTRICITY

CURRENT ELECTRICITY

Q.2 In the given circuit, with steady current, the potential drop across the capacitor must be

- (A) V
- (B) V/2
- (C) V/3
- (D) 2V/3.

At the time of Steady state.

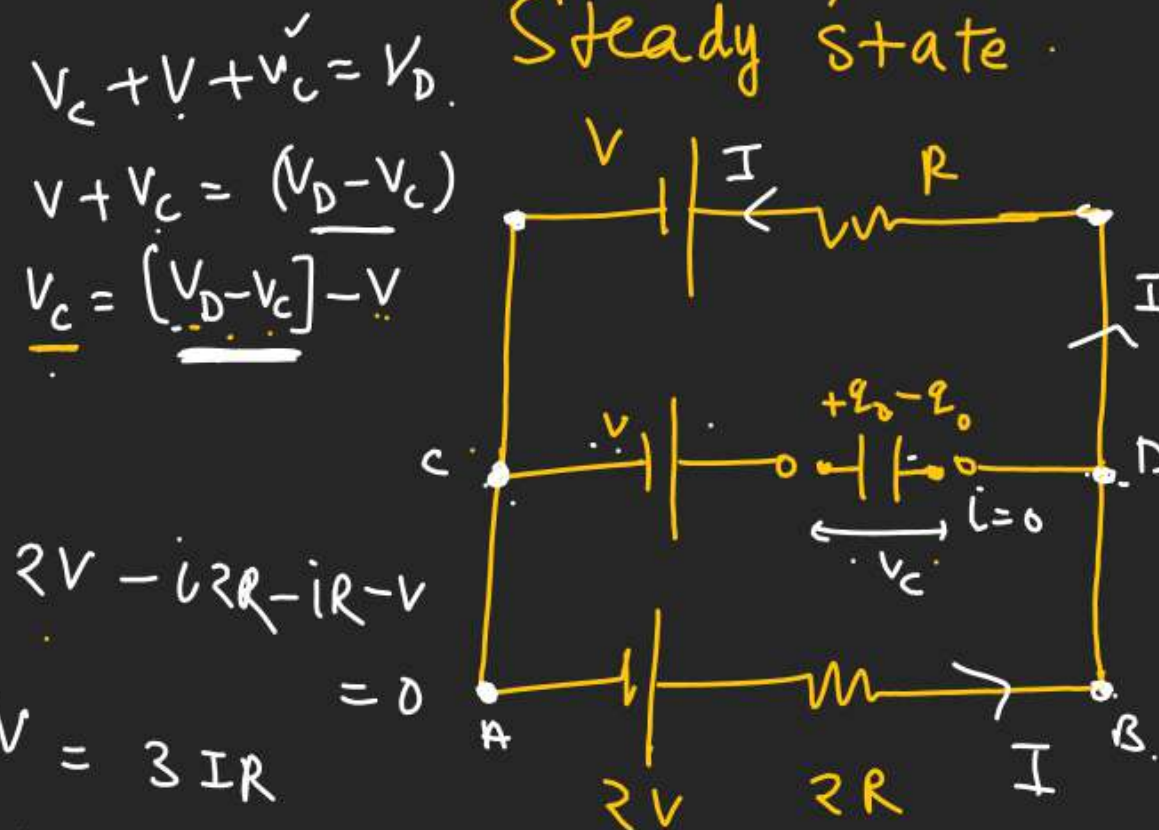

$$2V - i2R - iR - V = 0$$


$$V = 3IR$$

$$I = \left(\frac{V}{3R}\right)$$

$$V_A + 2V - I2R = V_B$$

$$V_A - V_B = 2IR - 2V = \left(2R \times \frac{V}{3R} - 2V\right) = \frac{2V}{3} - 2V = -\frac{4V}{3}$$

$$2V - I2R + V_C - V = 0 \quad (2001)$$

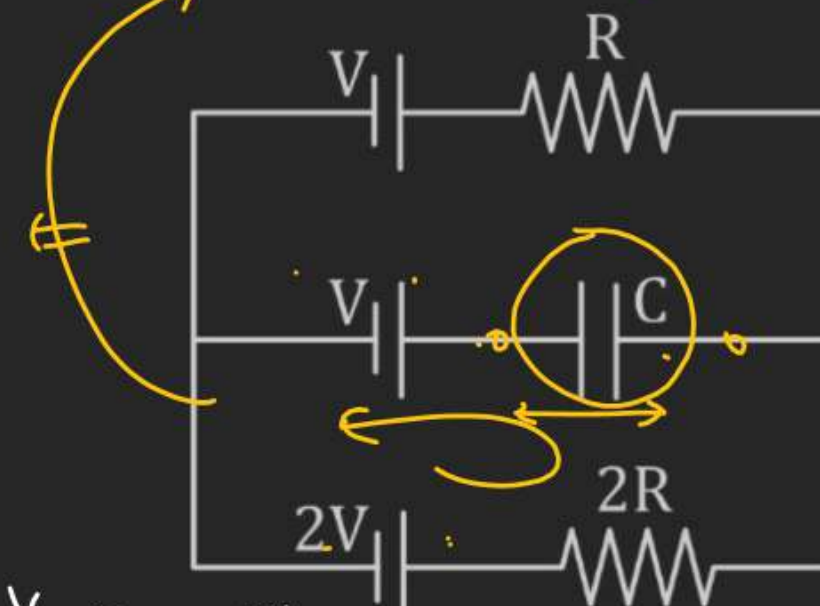


$$V_C - V_D = -\frac{4V}{3} \Rightarrow V_D - V_C = \frac{4V}{3}$$

$$V_C = \frac{4V}{3} - V = \frac{V}{3}$$

CURRENT ELECTRICITY

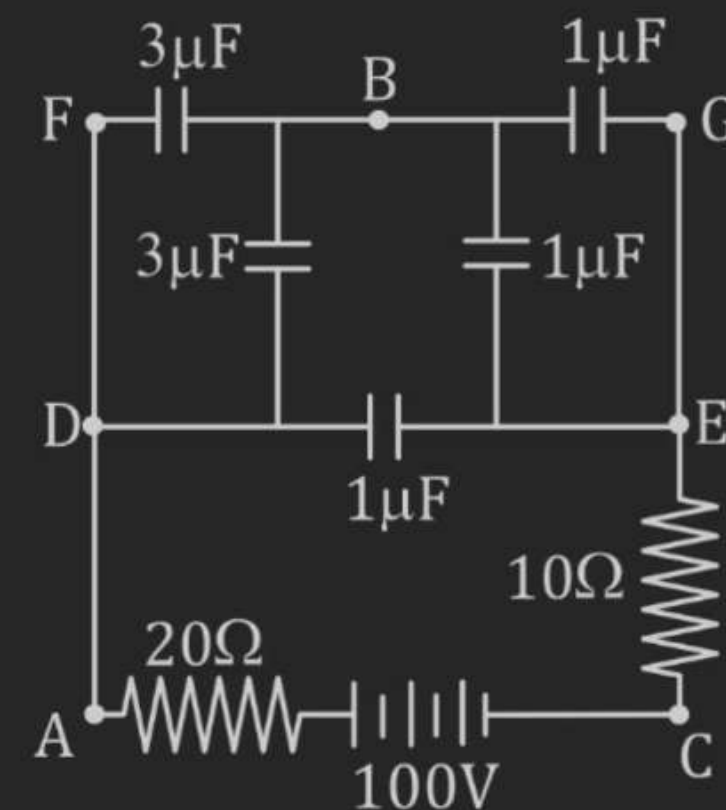
Q.3 Find the potential difference between the points A and B and between the points B and C in the steady state. **(1979)**



H.W.

CURRENT ELECTRICITY

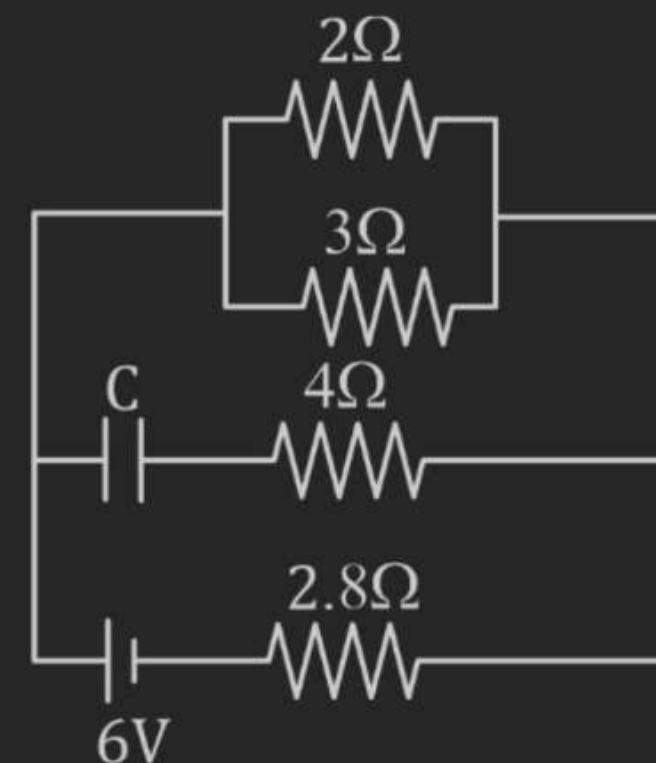
- Q.4** Calculate the steady state current in the 2Ω resistor shown in the circuit in the figure. The internal resistance of the battery is negligible and the capacitance of the condenser C is 0.2 microfarad. **(1982)**



H.W
Q.5 A part of circuit in a steady state along with the currents flowing in the branches, the values of resistances etc., is shown in the figure.

Calculate the energy stored in the capacitor $C(4\mu\text{F})$

(1986)

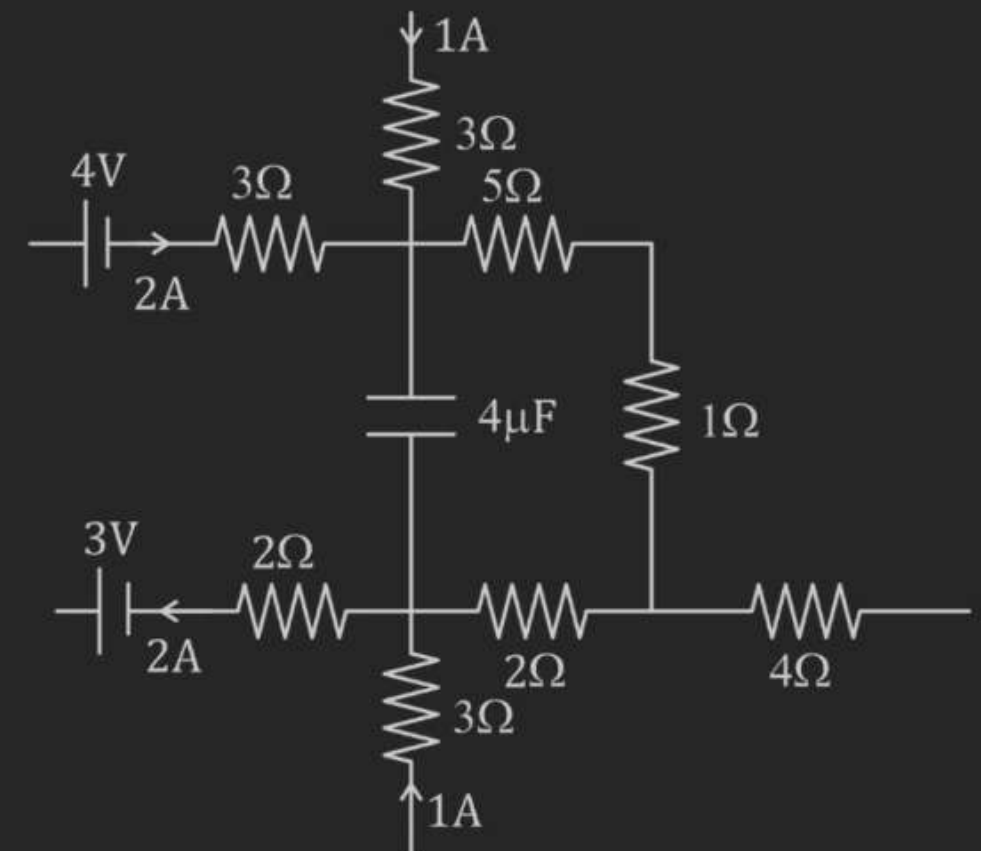

H.W.

CURRENT ELECTRICITY


Q.6 In the given circuit

$$E_1 = 3E_2 = 2E_3 = 6 \text{ volt}$$

$$R_1 = 2R_4 = 60 \text{ ohm}$$

$$R_3 = 2R_2 = 40 \text{ ohm}$$

$$C = 5 \mu\text{F}.$$

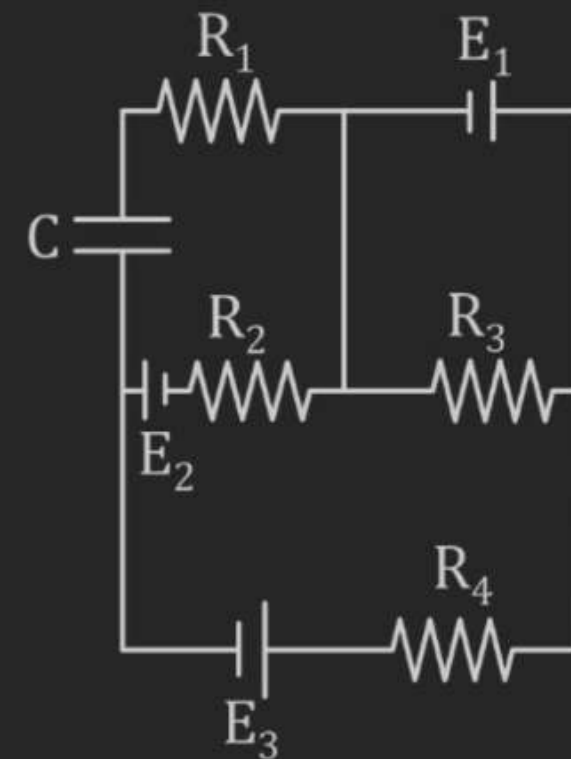Find the current in R_3 and the energy stored in the capacitor.**(1988)**


CURRENT ELECTRICITY

Q.7 In the circuit shown in figure, the battery is an ideal one, with emf V . The capacitor is initially uncharged. **(1988)**

The switch S is closed at time $t = 0$.


(a) Find the charge Q on the capacitor at time t .

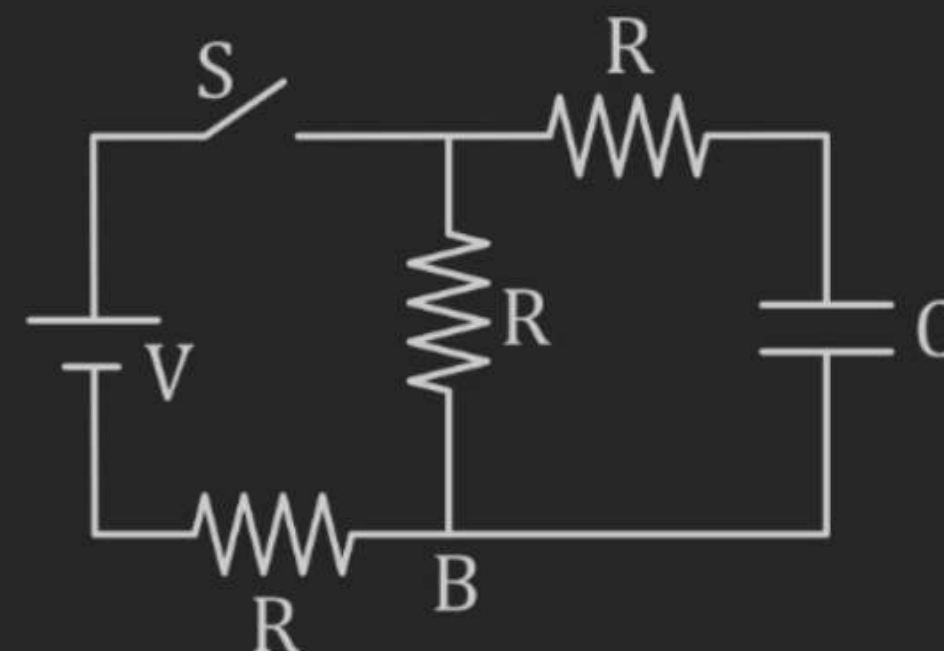(b) Find the current in AB at time t . What is its limiting value at $t \rightarrow \infty$.



CURRENT ELECTRICITY

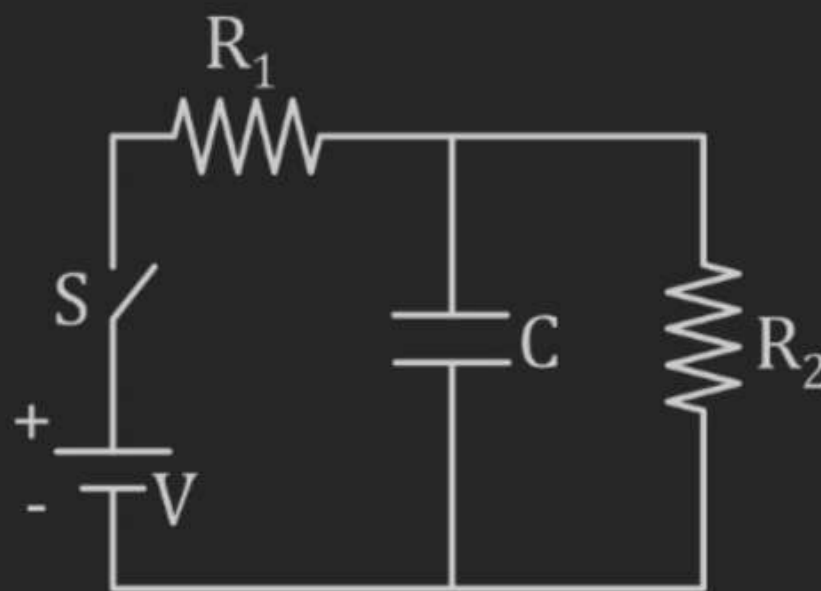- Q.8** In the given circuit, the switch S is closed at time $t = 0$. The charge Q on the capacitor at any instant t is given by $Q(t) = Q_0(1 - e^{-\alpha t})$. Find the value of Q_0 and α in terms of given parameters as shown in the circuit. **(2005)**



CURRENT ELECTRICITY

Q.9 In the circuit shown below, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu\text{C}$. Then S is switched to position Q . After a long time, the charge on the capacitor is $q_2 \mu\text{C}$. **(2021)**

(a) The magnitude of q_1 is _____.

(b) The magnitude of q_2 is _____.

