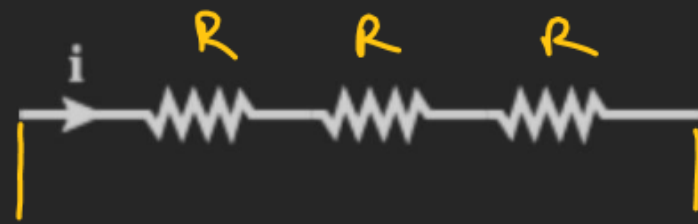



Q.2 Three resistance of equal value are arranged in the different combinations as shown below. Arrange them in increasing order of power dissipation.



$$R_{eq} = 3R$$

(I)


$$P = i^2 R_{eq}$$

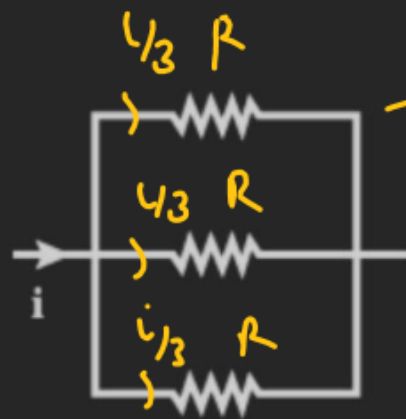

(III)


$$P_3 = \left(\frac{1}{3}i\right)^2 \times R \times 3 = \frac{i^2 R}{3}$$

$$R_{eq} = \frac{R}{3}$$

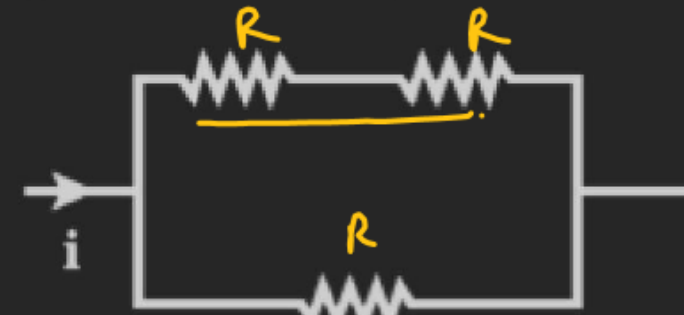

(II)
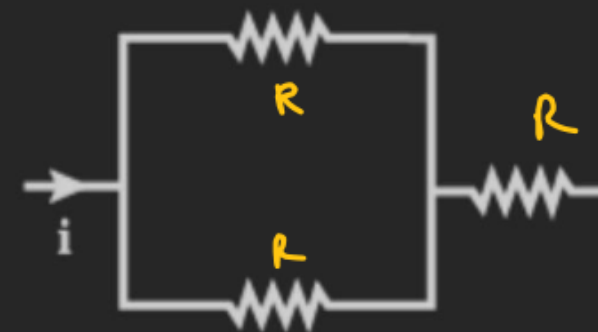
$$R_{eq} = \frac{2R \cdot R}{2R + R} = \frac{2R}{3}$$




(IV)

$$R_{eq} = \frac{R}{2} + R = \frac{3R}{2}$$

$$\text{III} < \text{II} < \text{IV} < \text{I}$$

Q.3 Six identical resistors are connected as shown in the figure. The equivalent resistance will be

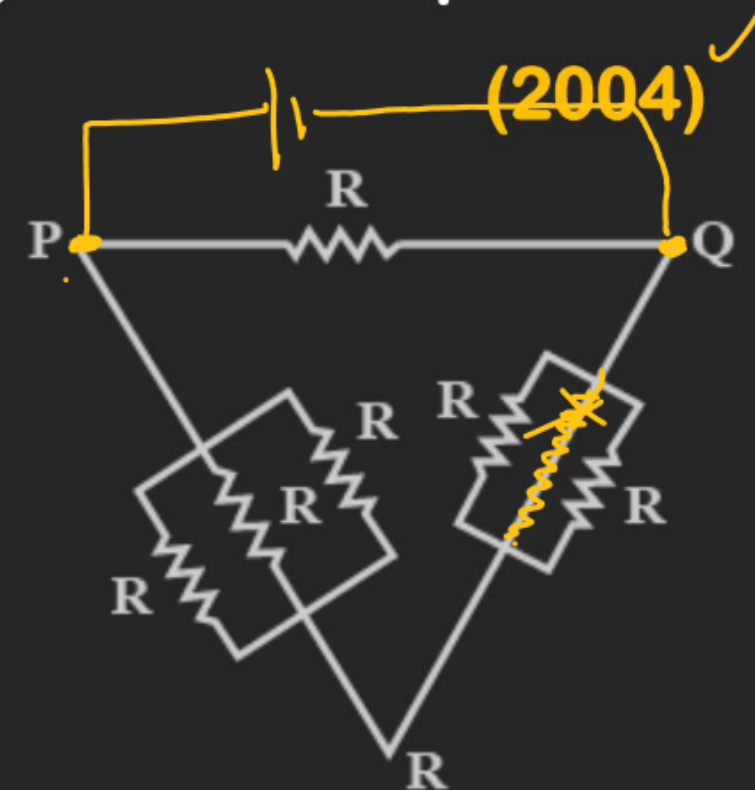- (A) maximum between P and R
- (B) maximum between Q and R
- ✓ (C) maximum between P and Q
- (D) all are equal.




**Q.4** Figure shows three resistor configurations  $R_1$  and  $R_2$  and  $R_3$  connected to 3 V battery. If the power dissipated by the configuration  $R_1$ ,  $R_2$  and  $R_3$  is  $P_1$ ,  $P_2$  and  $P_3$  respectively, then **(2008)**

(A)  $P_1 > P_2 > P_3$

(B)  $P_1 > P_3 > P_2$


☒ (C)  $P_2 > P_1 > P_3$

(D)  $P_3 > P_2 > P_1$

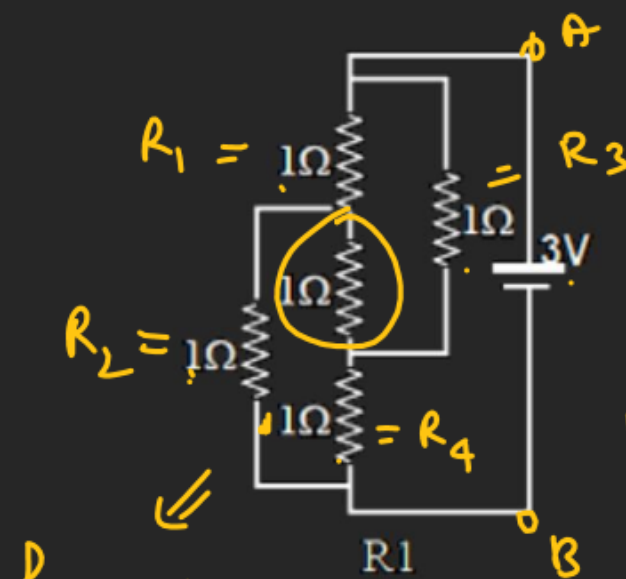


Handwritten calculations:  
 $R_{eq} = 1\Omega$   
 $P = 9 \text{ watt}$

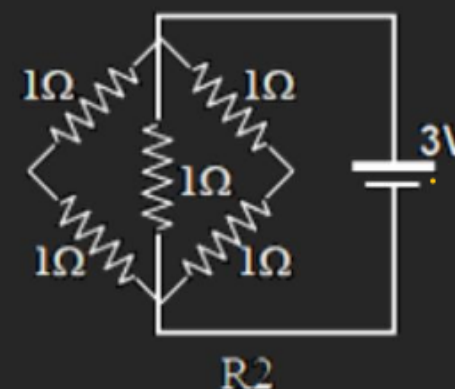Handwritten formula:  $P = \frac{V^2}{R_{eq}}$




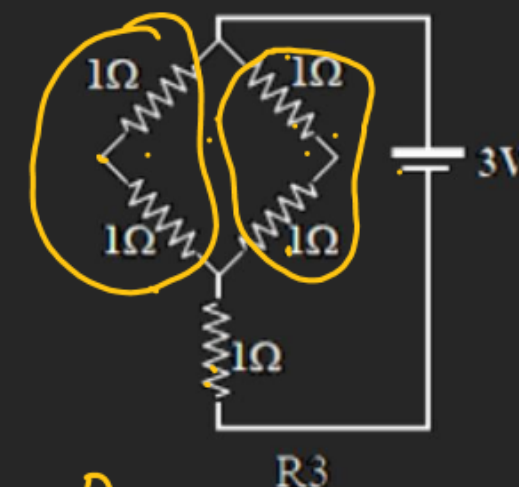Handwritten calculations for  $P_2$ :  
 $P_2 = \frac{9}{1/2} = 18 \text{ Watt}$   
 $R_{eq} = \frac{1}{2} + 1 + \frac{1}{2} = 1 + 1 = 2$   
 $(R_{eq} = \frac{1}{2})$



Handwritten calculations for  $P_3$ :  
 $R_{eq} = 2\Omega$   
 $P = \frac{V^2}{R} = \frac{9}{2}$

Q-5: - S<sub>1</sub> open

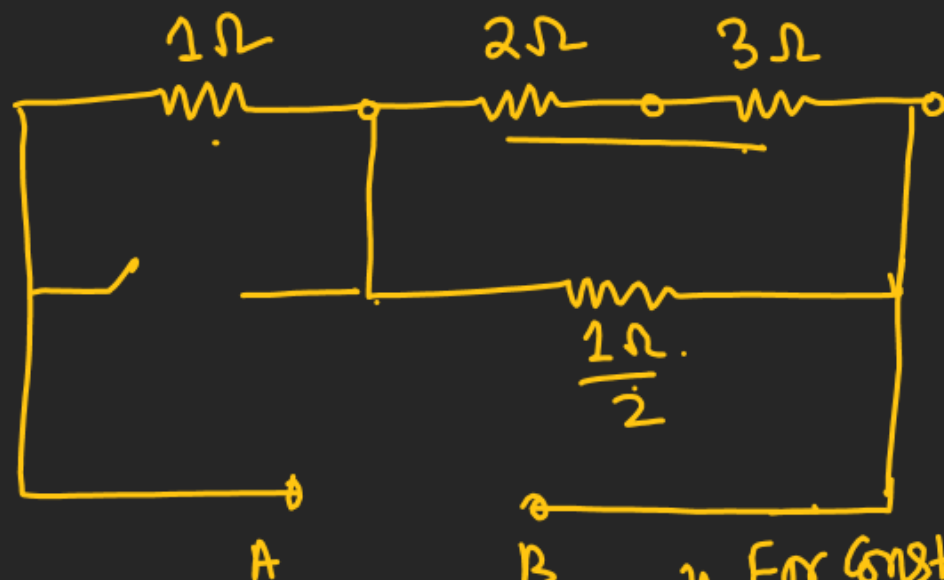

$$(R_{eq})_1 = 1 + \left( \frac{5 \times 1/2}{5 + 1/2} \right)$$

$$= 1 + \frac{5/2}{11/2}$$

$$= \left( \frac{16}{11} \right) \Omega$$

For constant voltage source  $\frac{1}{(R_{eq})_2} = 1 + \frac{1}{2} + \frac{1}{3}$

$$\frac{1}{(R_{eq})_2} = \frac{6+3+2}{6}$$

$$\frac{1}{(R_{eq})_2} = 11/6$$

$$(R_{eq})_2 = (6/11)$$

$$\frac{P_1}{P_2} = \frac{(R_{eq})_2}{(R_{eq})_1}$$

$$\frac{P_1}{P_2} = \frac{6}{11} \times \frac{11}{16}$$

$$\frac{P_1}{P_2} < 1$$



When Constant Current Source Connected.

$$P = I^2 R$$

$$\frac{P_1}{P_2} = \frac{(R_{eq})_1}{(R_{eq})_2}$$

$$\frac{P_1}{P_2} = \frac{16}{11} \times \frac{11}{6}$$

$$\boxed{P_1 > P_2}$$



**Q.5** In circuit-1 and circuit-2 shown in the figures,  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$  and  $R_3 = 3\Omega$ .  $P_1$  and  $P_2$  are the power dissipations in circuit-1 and circuit-2 when the switches  $S_1$  and  $S_2$  are in open conditions, respectively.  $Q_1$  and  $Q_2$  are the power dissipations in circuit-1 and circuit-2 when the switches  $S_1$  and  $S_2$  are in closed conditions, respectively. Which of the following statement(s) is(are) correct?

(A) When a voltage source of 6 V is connected across A and B

in both circuits,  $P_1 < P_2$ .

(B) When a constant current source of 2 amp is connected across


A and B in both circuits,  $P_1 > P_2$  ✓

(C) When a voltage source of 6 V is connected across A and B in


Circuit-1,  $Q_1 > P_1$ .

(D) When a constant current source of 2 amp is connected across

A and B in both circuits,  $Q_2 < Q_1$ .

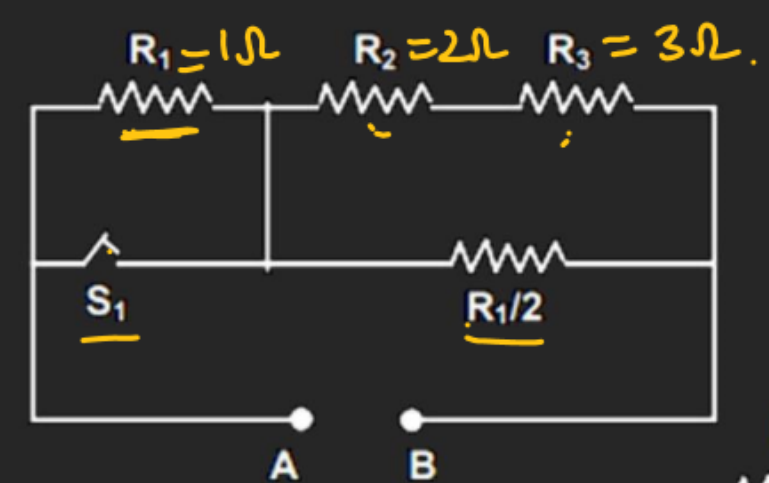

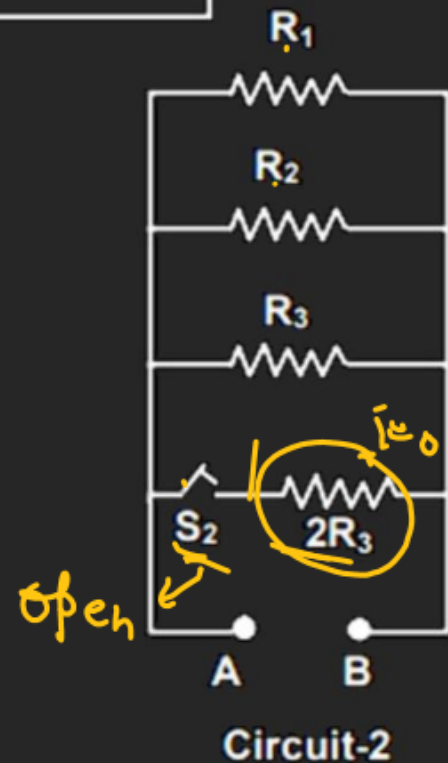$S_1$  &  $S_2$  open,  
( $R_{eq}$ )<sub>1</sub> =




(2022)

# CURRENT ELECTRICITY

## Maximum Power transfer theorem

Q-5 When  $S_1$  and  $S_2$  closed.

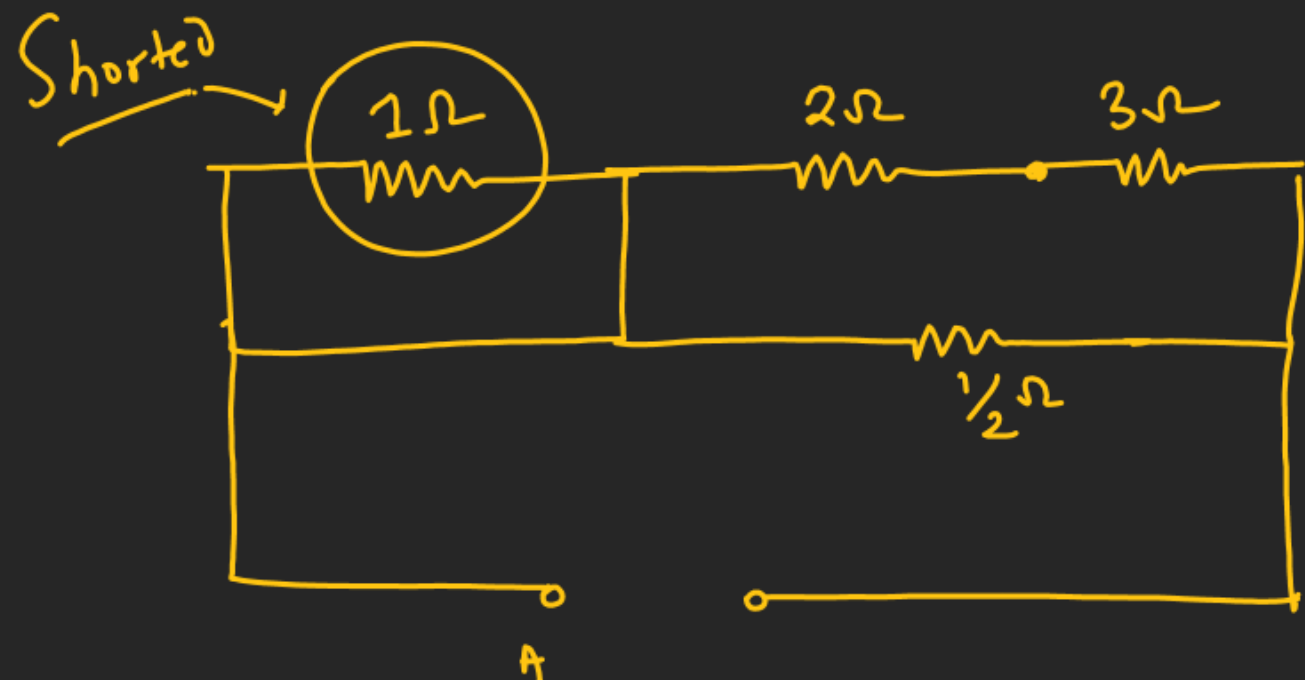

$$(R_{eq})_1 = \frac{5 \times \frac{1}{2}}{5 + \frac{1}{2}} = \frac{5/2}{11/2} = \frac{5}{11}$$



$$\frac{1}{(R_{eq})_2} = \frac{1}{2} + 1 + \frac{1}{3} + \frac{1}{6}$$

$$= \frac{3}{2} + \frac{3}{6}$$

$$\frac{1}{(R_{eq})_2} = \frac{3}{2} + \frac{1}{2} = 2$$

$$(R_{eq})_2 = \frac{1}{2}$$

When Voltage Source

$$\frac{Q_1}{Q_2} = \frac{(R_{eq})_2}{(R_{eq})_1} = \frac{1}{2} \times \frac{11}{5} = \frac{11}{10}$$

$$Q_1 > Q_2$$

When Constant Current apply

$$\frac{Q_1}{Q_2} = \frac{(R_{eq})_1}{(R_{eq})_2} = \frac{5 \times 2}{11} = \frac{10}{11}$$

$$Q_1 < Q_2$$

$$P = I^2 R \Rightarrow P \propto R \quad (i=c)$$


$$P = \frac{V^2}{R}$$

$$P \propto \frac{1}{R} \Rightarrow V=c$$

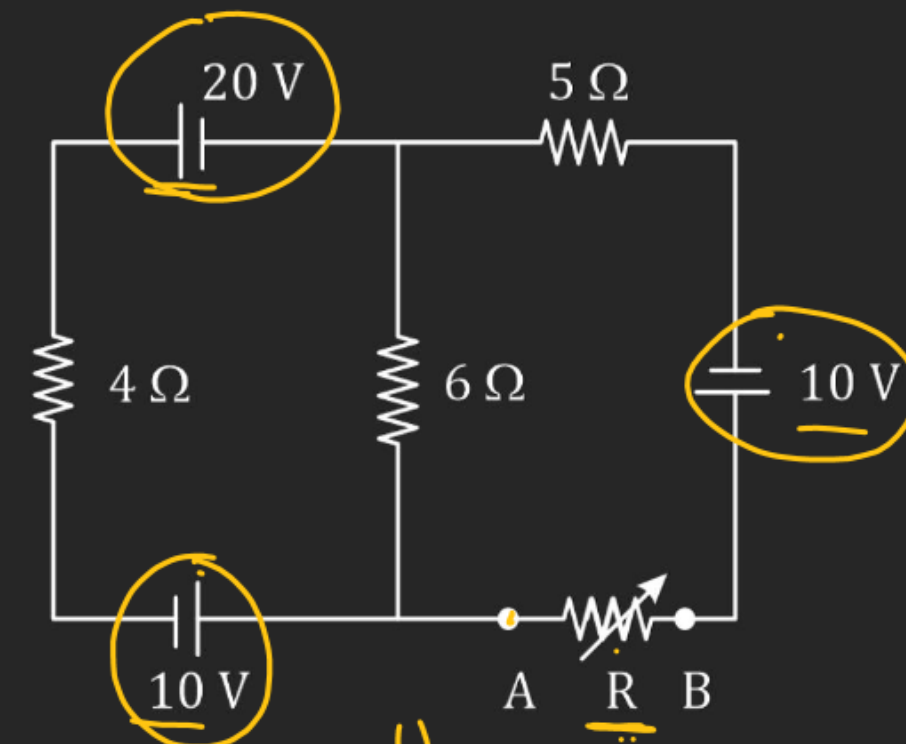**Q.7** In the circuit shown in figure, find the value of resistance  $R$  at which the power transferred to this resistance will be maximum.

⇒ Trick Find  $(R_{eq})$  across AB of the Ckt.

[for this short the battery i.e. replaced the battery by zero resistance wire]



$$(R_{eq})_{AB} = \left[ \frac{(4 \times 6)}{4+6} \right] + 5$$

$$= \frac{24}{10} + 5$$

$$= \frac{12}{5} + 5 = \frac{12+25}{5} = \frac{37}{5} \Omega$$



$(R_{eq})_{A-B} = ??$




For maximum  $R = r$ .



**Q.8** In the circuit shown in figure, for what value of  $R$  will the power consumed by this resistance will be maximum.

H.W

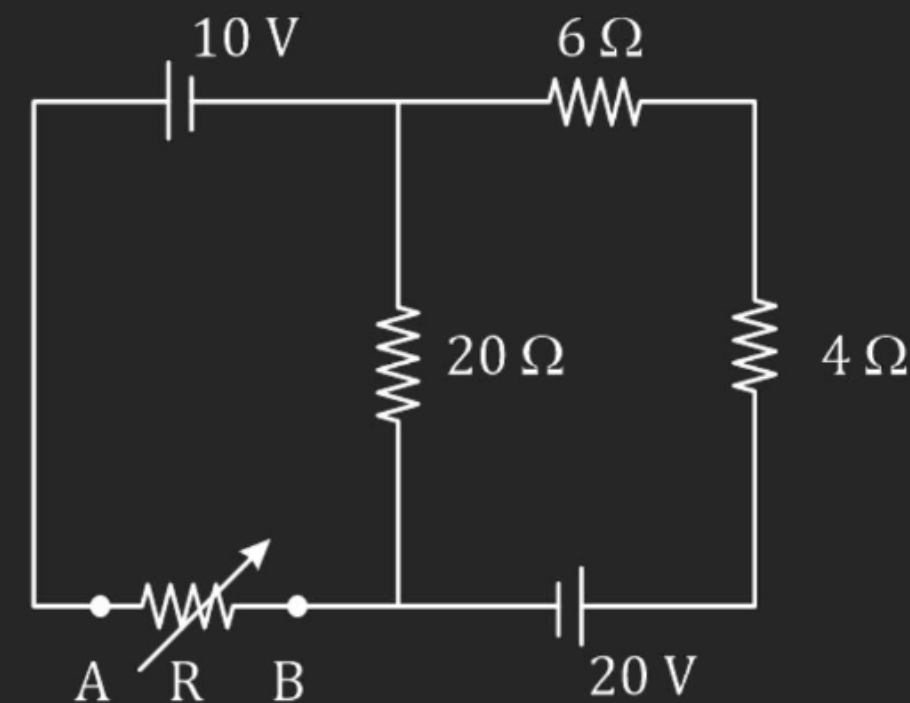



**Q.9** 12 cells each having the same EMF are connected in series and are kept in a closed box. Some of the cells are wrongly connected. This battery is connected in series with an ammeter and two cells identical with the others. The current is 3 A when the cells and battery aid each other and is 2 A when the cells and battery oppose each other. How many cells in the battery are wrongly connected?

**Q.10** In order to heat a liquid an electric heating coil is connected to a cell of emf  $E = 12\text{ V}$  and internal resistance  $r = 1\Omega$ . There are three options for selecting the resistance ( $R$ ) of the heating coil.  $R$  can be chosen as  $1\Omega$ ,  $2\Omega$  or  $4\Omega$ . The cell has a rating of  $2000\text{mAh}$  (milli Ampere hour) and it is to be used to heat the liquid till it expires. [The cell maintains constant emf till it lasts]

(a) Which value of  $R$  will you choose so that maximum heat ( $H_0$ ) is transferred to the liquid before the cell expires? Calculate  $H_0$ .

(b) Which value of  $R$  will you choose so that heat is transferred to the liquid at fastest possible rate? What percentage of  $H_0$  (as obtained in (a)) is transferred to the liquid in this case by the time the cell expires?

