


DPP - 8

SOLUTION

Link to View Video Solution:  [Click Here](#)


1. $I_g = 10 \text{ mA}$ (maximum current in galvanometer)

$$I = 100 \text{ mA}$$

$$I_g r_g = (I - I_g) s$$

$$10 \times 100 = 90 \times S$$

$$S = \frac{100}{9} \Omega$$

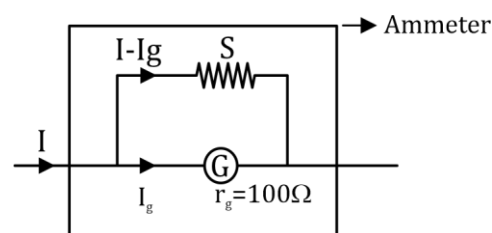

2. Let main current is I .

$$I_g = \frac{I \times 10}{100} = \frac{I}{10} \Rightarrow r_g = 99 \Omega$$

$$(I - I_g) S = I_g r_g$$

$$\frac{9I}{10} \times S = \frac{I}{10} \times 99 \Rightarrow S = \frac{99}{9} = 11 \Omega$$

3. $\frac{1}{5} \times G = \frac{4}{5} I \times 4$



$$\Rightarrow G = 16 \Omega$$

When additional shunt of 4Ω used

$$I_g \times 16 = (I - I_g)^2$$

$$16 I_g = 2I - 2I_g$$

$$I_g = \frac{I}{9}$$

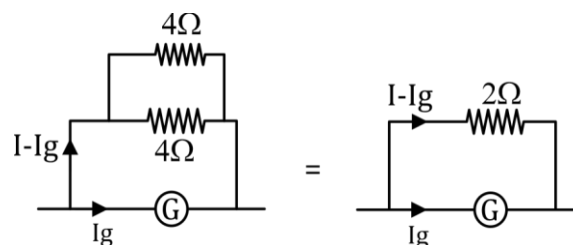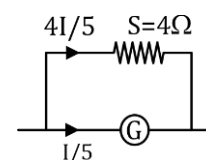

Link to View Video Solution: [Click Here](#)

4. \Rightarrow First If voltmeter is not connected

$$\text{then } I_{\text{Ckt}} = \frac{5}{110} = \frac{1}{22} \text{ Amp}$$

$$V_{R_1} = IR = \frac{1}{22} \times 50 = \frac{25}{11} \text{ volt} = 2.27 \text{ V}$$

when voltmeter is connected

$$(R_{\text{eq.}})_{\text{Ckt}} = 40 + 20 + \frac{50 \times 1000}{1050} = 60 + \frac{5000}{105}$$

$$(R_{\text{eq.}})_{\text{Ckt}} = \frac{6300 + 5000}{105} = \frac{11300}{105}$$

$$I_1 = \frac{5 \times 105}{11300} = \frac{105}{2260} = \frac{21}{452}$$

$$I_0 \times 1000 = (I_1 - I_0) 50$$

$$I_0 \times 20 = I_1 - I_0$$

$$21I_0 = I_1$$



$$I_0 = \frac{I_1}{21} = \frac{21}{21 \times 452} = \frac{1}{452}$$

$$\text{Reading of Voltmeter} = I_0 R_V$$

$$= \frac{1}{452} \times 1000$$

$$V = 2.21 \text{ Volt}$$

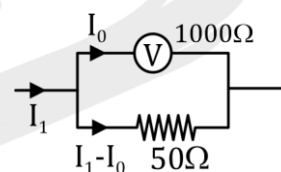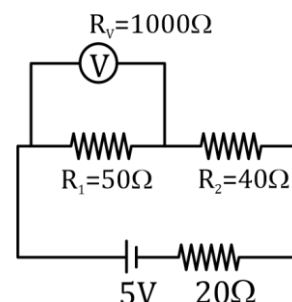
$$\% \text{ error in reading} = \frac{2.27 - 2.21}{2.27} \times 100 \Rightarrow 2.6 \%$$



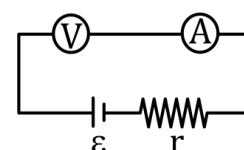
5. resistance of voltmeter is very high Current in Circuit is very

low & Potential across the voltmeter approx the emf of battery

because resistance of ammeter is very Low.



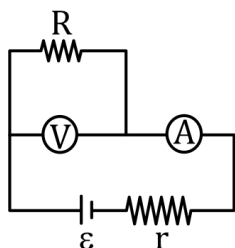Link to View Video Solution: [Click Here](#)



when a resistance connected parallel to (V) overall resistance of circuit decrease & current in circuit increase.

So potential across ammeter increase & across voltmeter decrease.

6. A voltmeter of range 10V.

7. $I_g = 2 \times 10^{-4}$ Amp

$r_g = 50\Omega$

$I = 12$ Amp at full deflection

$$(I - I_g)S = I_g r_g$$

$$I - I_g \simeq I$$

$$12 \times S = 2 \times 10^{-4} \times 50$$

$$S = \frac{10^{-2}}{12} = 0.83 \times 10^{-3}\Omega$$


8. Initial reading are

$$V = \frac{\epsilon r_V}{r_V + r_A} \quad \text{--- (i)}$$

current in ammeter Initially

$$I = \frac{\epsilon}{r_V + r_A}$$

finally after connection of resistance

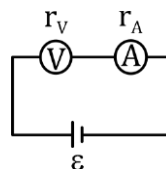

Link to View Video Solution: [Click Here](#)

$$I^1 = \frac{\varepsilon}{r_A + \frac{r_V R}{r_V + R}}$$

final reading of voltmeter

$$V_f = \frac{V}{k} = \varepsilon - \frac{\varepsilon r_A}{r_A + \frac{r_V R}{r_V + R}} \quad \text{--- (ii)}$$

$$I_f = kI = \frac{\varepsilon}{r_A + \frac{r_V R}{r_V + R}} \quad \text{--- (iii)}$$

$$I_f = KI$$

$$\frac{\varepsilon}{r_A + \frac{r_V R}{r_V + R}} = \frac{k\varepsilon}{r_V + r_A}$$

$$\text{from equation (ii)} \quad \frac{V}{k} = \varepsilon - \frac{k\varepsilon r_A}{r_V + r_A}$$

$$\Rightarrow \frac{\varepsilon r_V}{k(r_V + r_A)} = \varepsilon - \frac{k\varepsilon r_A}{r_A + r_V}$$

$$\frac{r_V}{k(r_V + r_A)} = \frac{r_A + r_V - kr_A}{(r_V + r_A)}$$


$$r_V - \frac{r_V}{k} = kr_A - r_A$$


$$r_V \left(\frac{k-1}{k} \right) = r_A(k-1)$$

$r_V = kr_A$ put the value in

$$\text{equation I} \Rightarrow V = \frac{\varepsilon r_V}{r_V + r_V/k} \Rightarrow V = \frac{k\varepsilon}{(k+1)}$$
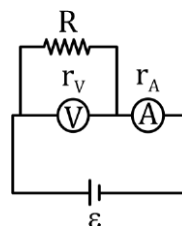
$$V_f = \frac{V}{k} = \frac{\varepsilon}{k+1}$$



Link to View Video Solution:  [Click Here](#)

9. For range 1 volt, galvanometer and R_1 is series.

$$I_g = \frac{V}{G+R_1} \Rightarrow 10^{-3} = \frac{1}{50+R_1}$$

$$\Rightarrow R_1 = 950\Omega$$

For 10 volt, galvanometer & R_1 , R_2 are series

$$I = \frac{10}{G + R_1 + R_2}$$

$$10^{-3} = \frac{10}{50+950+R_2} \Rightarrow R_2 = 9k\Omega$$

For range 100 V, Galvanometer, R_1 , R_2 & R_3 are in series

$$I = \frac{100}{G + R_1 + R_2 + R_3} \Rightarrow R_3 = 90k\Omega$$