

Boolean Algebra

$A \rightarrow$ It is input or output of any digital Ckt.

$$A + 0 = A$$

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + \bar{A} = 1$$

$$A \cdot A = A$$

$$A + \bar{A} = 1$$

$$A \cdot \bar{A} = 0$$

$$\overline{\overline{A}} = A$$

LOGIC GATES

$$\left. \begin{array}{l} A + B = B + A \\ A \cdot B = B \cdot A \end{array} \right\} \text{Commutative property.}$$


$$\left. \begin{array}{l} A + (B + C) = (A + B) + C \\ A \cdot (B \cdot C) = (A \cdot B) \cdot C \end{array} \right\} \text{Associative law.}$$

$$(A + B) \cdot (C + D) = A \cdot C + A \cdot D + B \cdot C + B \cdot D$$


De-Morgan's Theorem (Distributive)

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$


$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

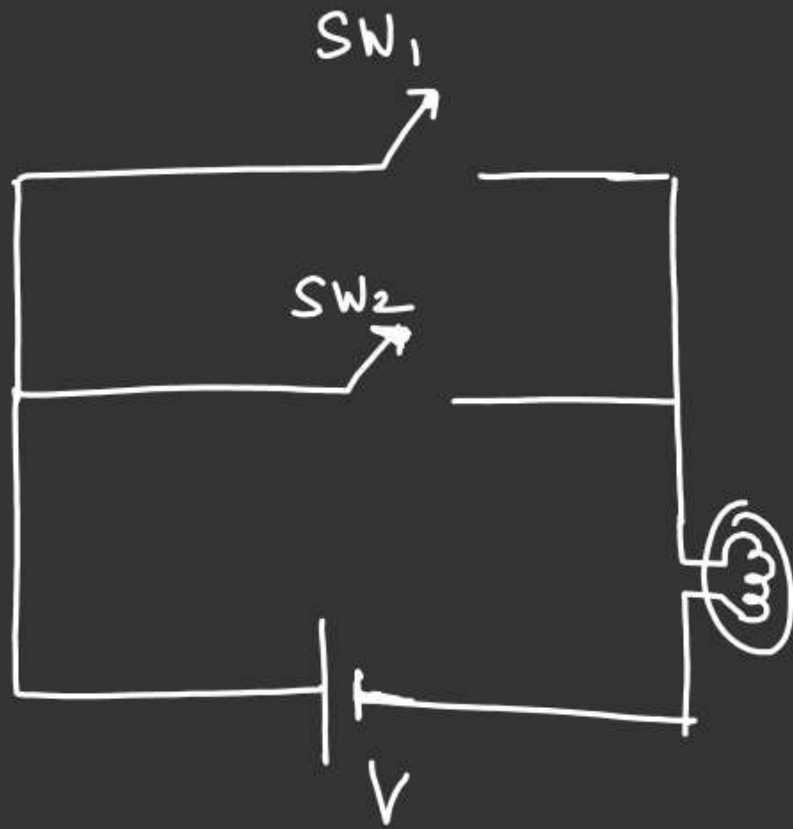LOGIC GATES (JEE MAINS)AABoolean operationOR - operation (+)


SW ₁	SW ₂	Bulb
Open	Open	Not Glow
Closed	Open	Glow
Open	Closed	Glow
Closed	Closed	Glow

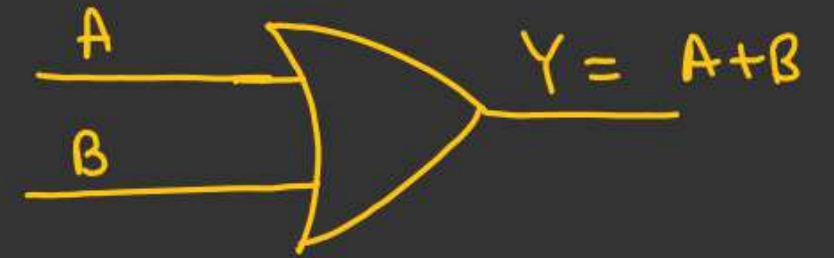OR GATETRUTH TABLE


A	B	Y = A + B
0	0	0
1	0	1
0	1	1
1	1	1

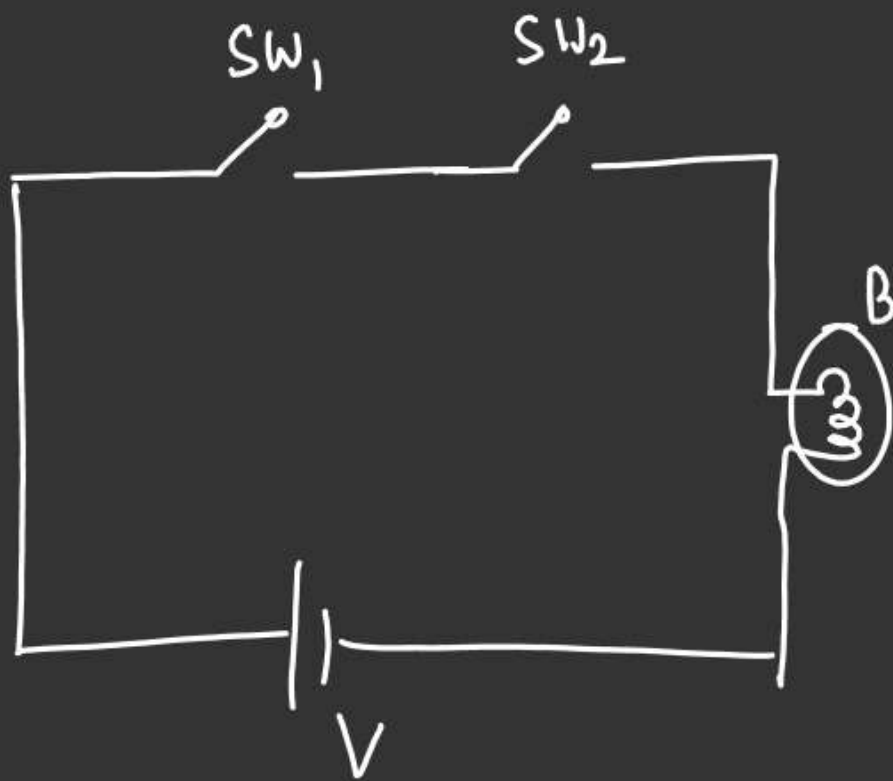LOGIC GATES (JEE MAINS)AND Operation (X)

SW ₁	SW ₂	Bulb
open	open	Not glow
Closed	open	Not glow
open	Closed	Not glow
Closed	Closed	glow

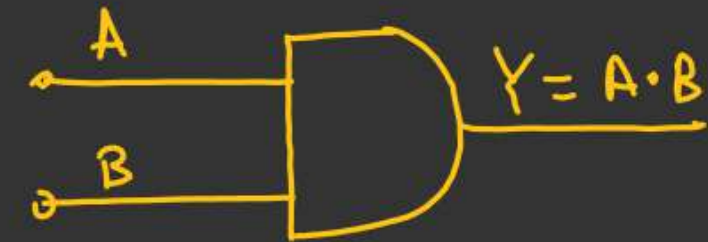AND GATETruth table

A	B	Y = A · B
0	0	0
1	0	0
0	1	0
1	1	1

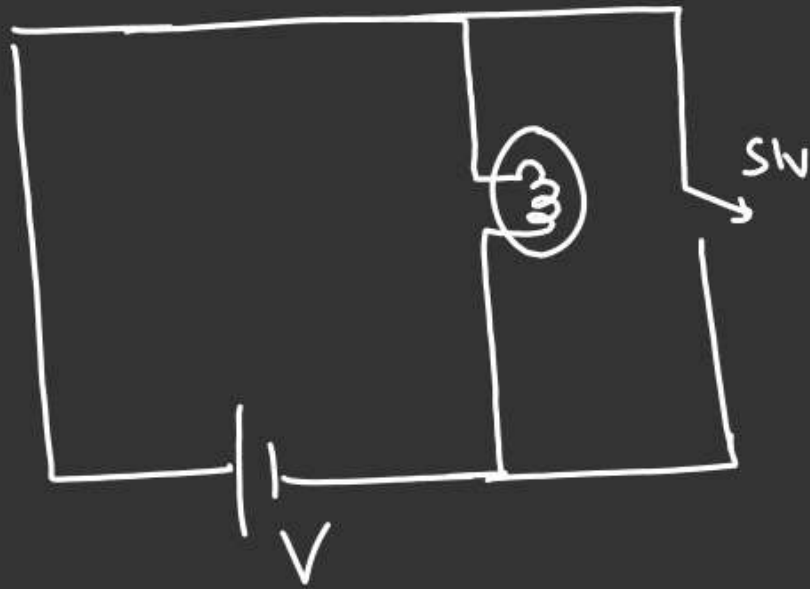LOGIC GATES (JEE MAINS)Q4NOT operation (Bar)

SW	Bulb
Open	Glow.
Closed	Not Glow.



NOT-Gate

A	$Y = \bar{A}$
0	1
1	0

LOGIC GATES (JEE MAINS)NAND Gate (Universal gate)

L (AND + NOT)


Truth table.

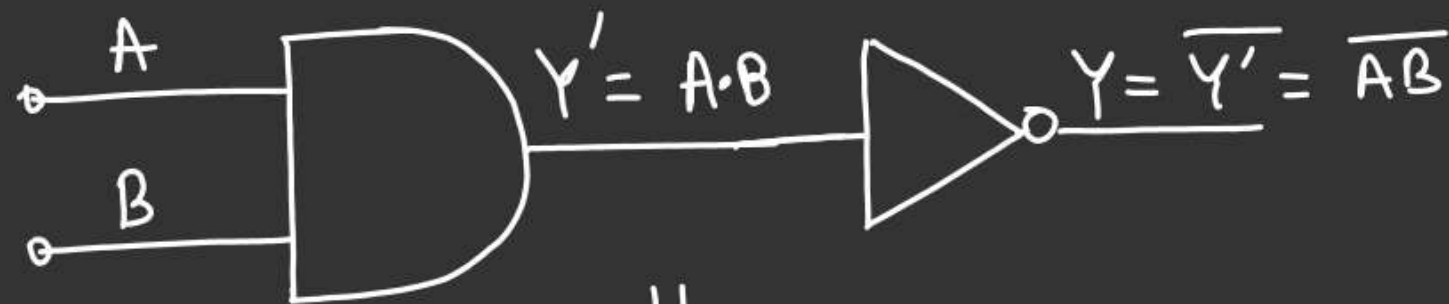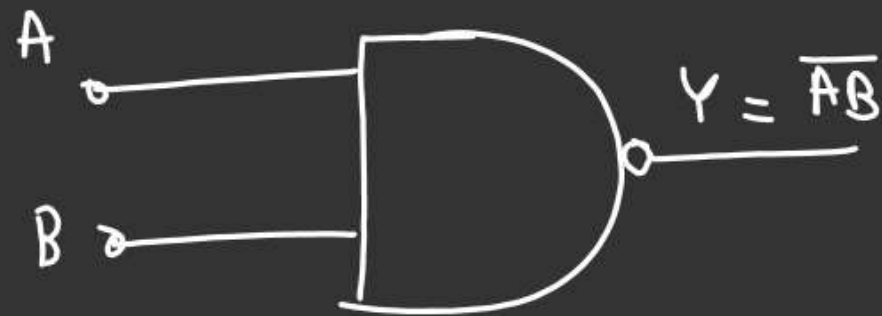 \Downarrow 

A	B	$Y' = A \cdot B$	$Y = \overline{AB}$
0	0	0	1
1	0	0	1
0	1	0	1
1	1	1	0

LOGIC GATES (JEE MAINS)NOR gate (Universal gate)Truth table


↳ [OR + NOT gate]

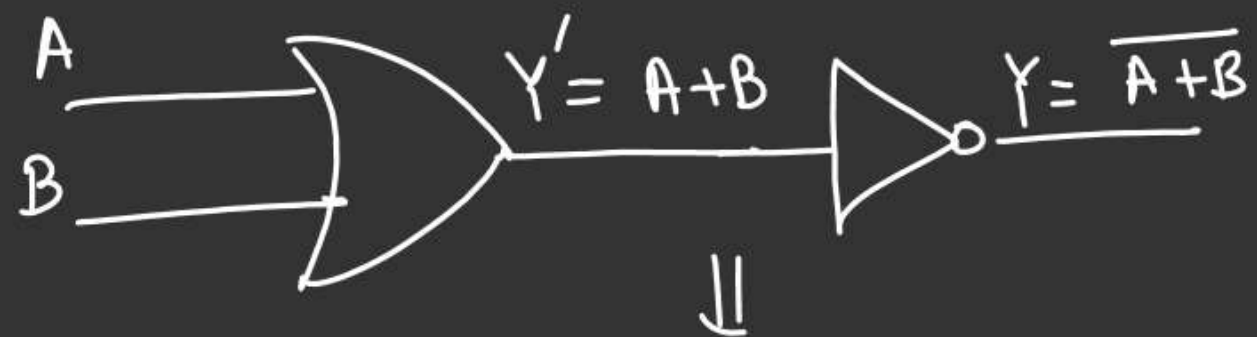

A	B	$Y' = A + B$	$Y = \overline{A + B}$
0	0	0	1
1	0	1	0
0	1	1	0
1	1	1	0

LOGIC GATES (JEE MAINS)✖✖ XOR gate

↳ [OR + AND + NOT gate]

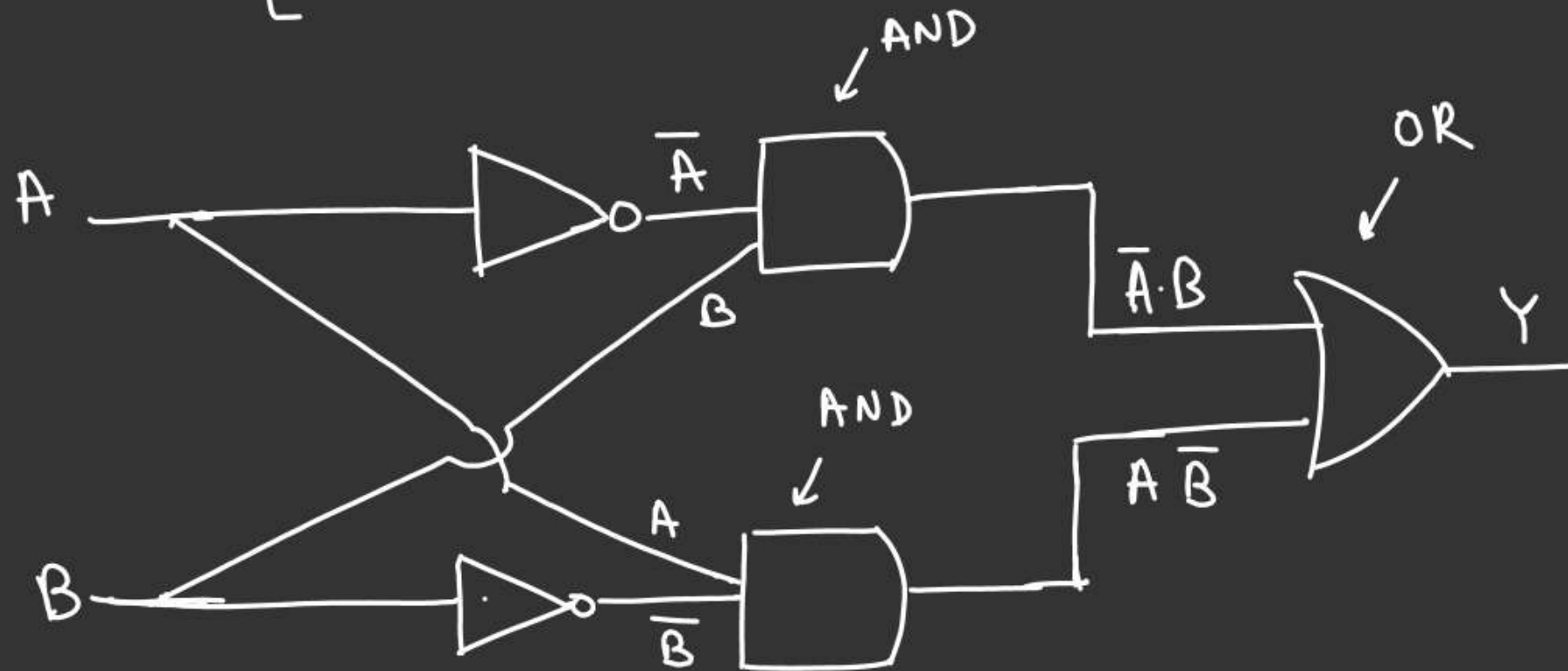

$$Y = (\bar{A}B + A\bar{B})$$


Truth table

A	B	$\bar{A}B$	$A\bar{B}$	$Y = \bar{A}B + A\bar{B}$
0	0	0	0	0
1	0	0	1	1
0	1	1	0	1
1	1	0	0	0

LOGIC GATES (JEE MAINS)

A & B are input
Q. Q. of OR-Gate.
 output waveform = ??

$$Y = \underline{A + B}$$

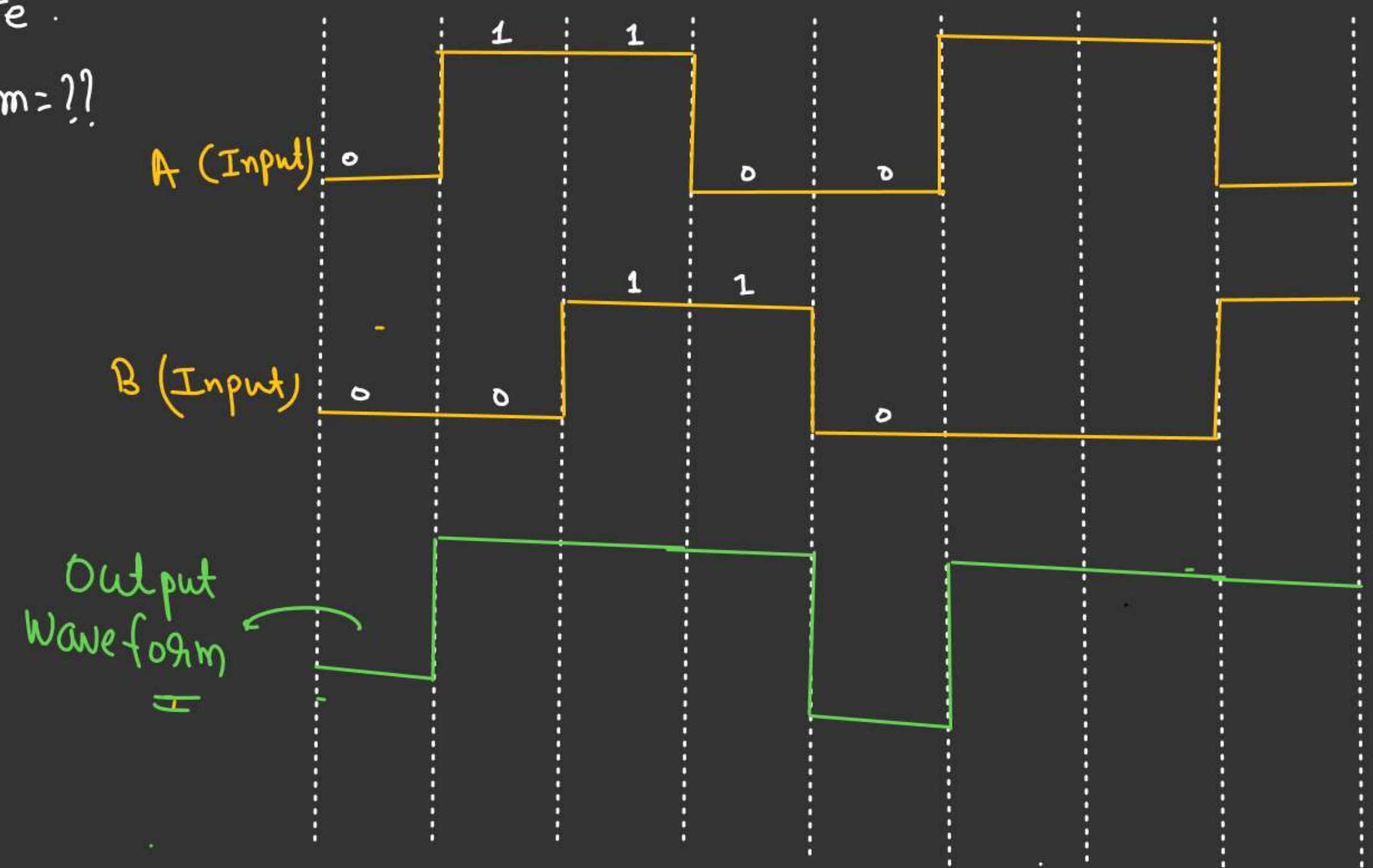


LOGIC GATES (JEE MAINS)Q.1: AND GATE

A & B input of And gate
Output wave form = ??

$$Y = A \cdot B$$

Output
wave form

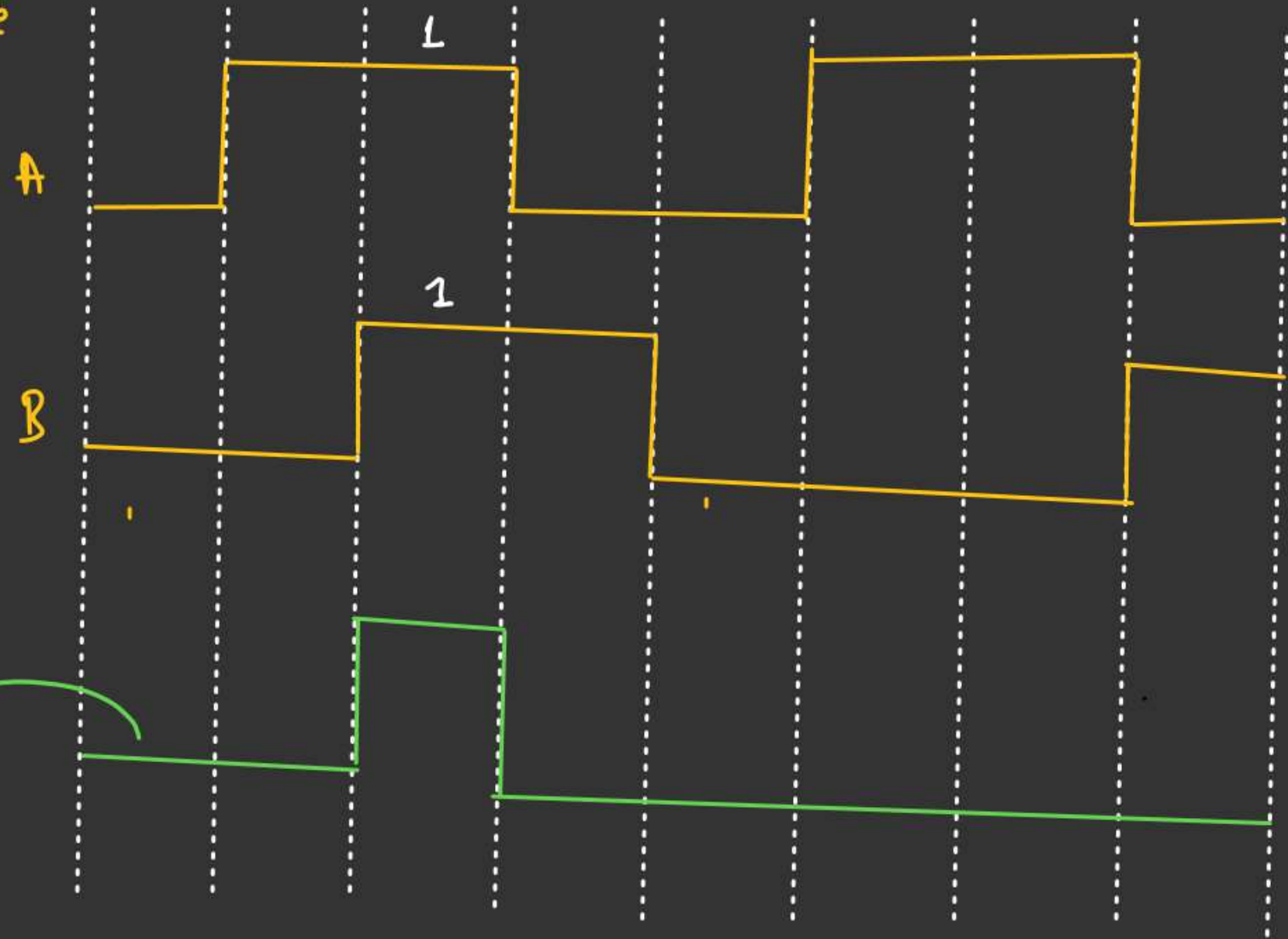


NOT-Gate

$$Y = \overline{A}$$

Output
 $Y = \overline{A}$

A

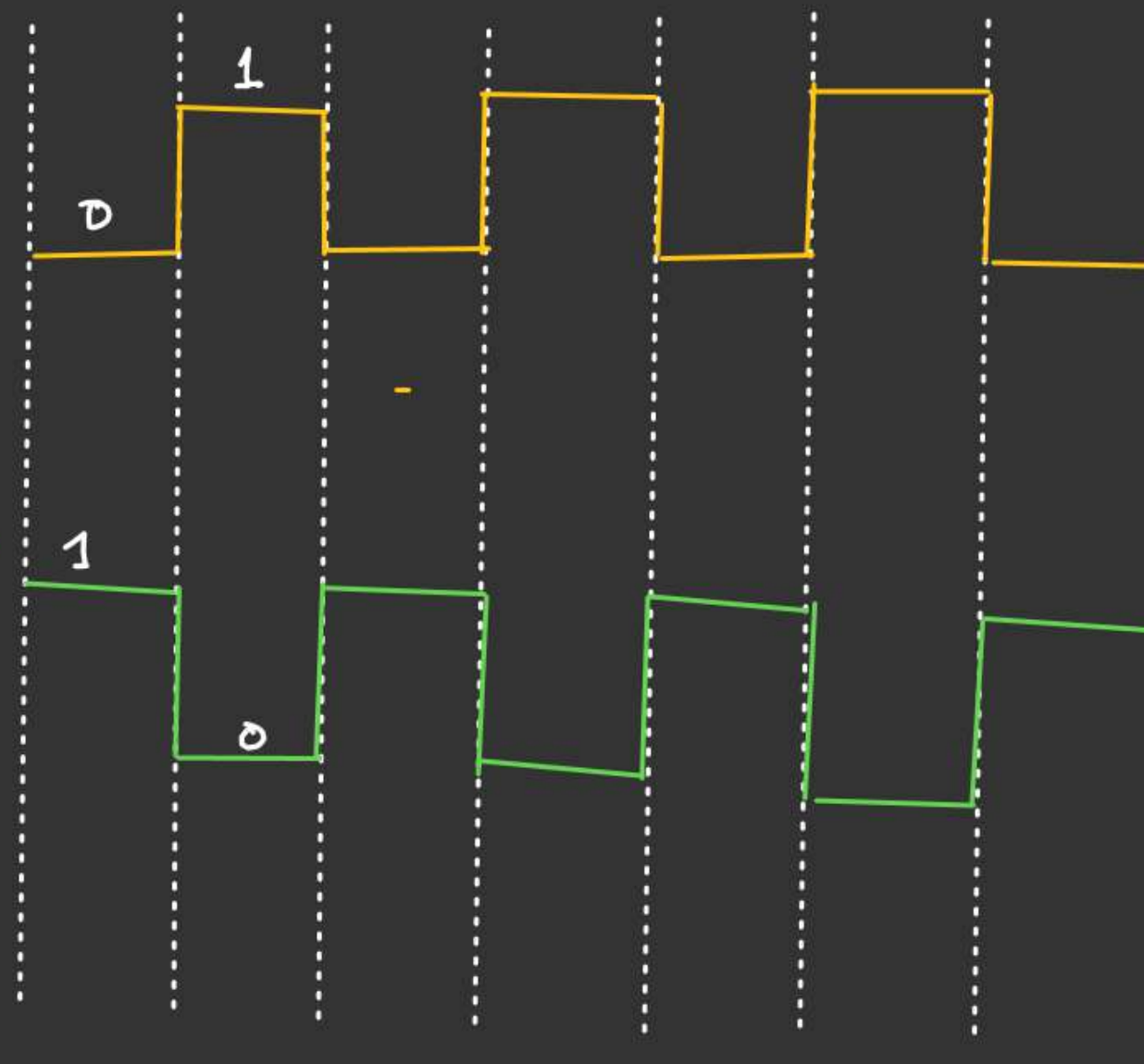

LOGIC GATE


Q.1 Identify the gate from the following:

(A) NOT gate

(B) AND gate

(C) OR gate ✓

(D) None of these

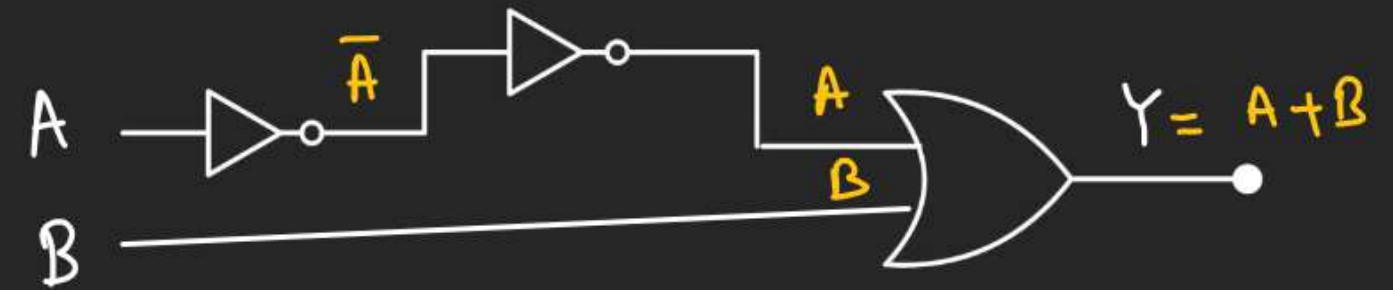

Q.2 Which of the following is not correct?

(A) $\overline{\overline{A} \cdot \overline{B}} = A + B$

(B) $\overline{\overline{A} \cdot \overline{B}} = A \cdot B$

(C) $\overline{\overline{(A \cdot B)} \cdot \overline{(A \cdot B)}} = AB + AB$

(D) $\overline{1} + \overline{1} = 1$

LOGIC GATE


Q.3 For the given logic circuit,

Which of these is correct?

- ~~(A)~~ $y = 0$ for $X_1 = X_3 = 0$ and $X_2 = 1$
~~(B)~~ $y = 0$ for $X_1 = X_2 = X_3 = 0$
~~(C)~~ $y = 1$ for $X_1 = X_2 = X_3 = 1$
~~(D)~~ $y = 1$ for $X_1 = X_2 = 1$ and $X_3 = 0$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$
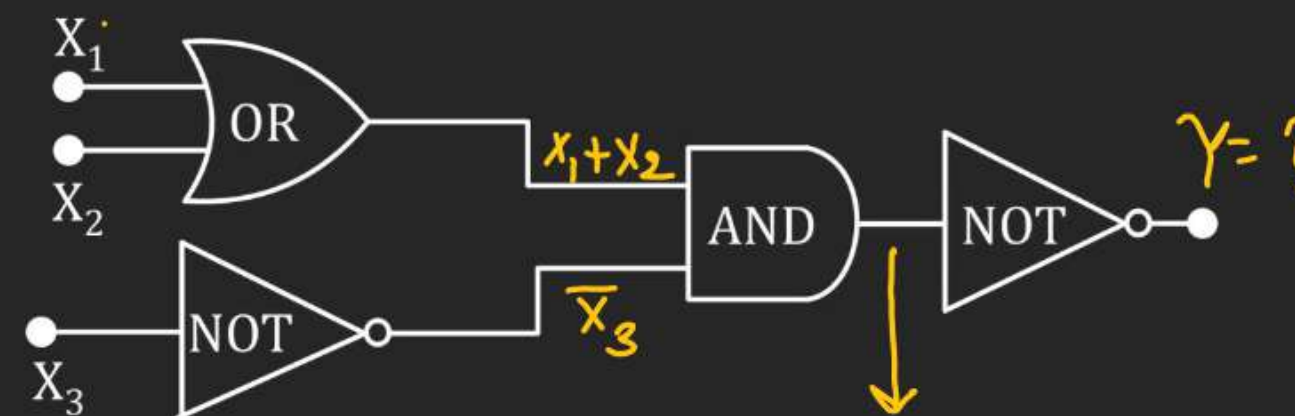
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



$$(X_1 + X_2) \cdot \overline{X_3}$$

$$Y = \underbrace{(X_1 + X_2)}_A \cdot \underbrace{\overline{X_3}}_B$$

$$Y = \overline{X_1 + X_2} + \overline{\overline{X_3}}$$

$$Y = (\overline{X_1} \cdot \overline{X_2} + X_3)$$

Q.4 In the Boolean algebra, $(\overline{A} \cdot \overline{B}) \cdot A$ equals to

(A) $\overline{A} + \overline{B}$

(B) A ✓

(C) $\overline{A} \cdot \overline{B}$

(D) $A + B$

$$= (\overline{A \cdot B}) \cdot A$$

$$= (\overline{A} + \overline{B}) \cdot A$$

$$= (A + B) \cdot A$$

$$= A \cdot A + B \cdot A$$

$$= A + B \cdot A$$

$$= A (B + 1)$$

$$= \underbrace{A}_{1} \underbrace{(B + 1)}_{1}$$

LOGIC GATE

Q.5 In order to obtain an output $Y = 1$ from the circuit of figure, the inputs must be

	A	B	C
(1)	0	1	0
(2)	1	0	0
(3)	1	0	1
(4)	1	1	0



$$Y = (A+B) \cdot C$$

LOGIC GATE

Q.6 With reference to figure, which of the following is possible?

(A) $A = 0, B = 0, X = 1$


(B) $A = 0, B = 1, X = 0$

✓ (C) $A = 0, B = 0, X = 0$

✓ (D) $A = 1, B = 1, X = 0$

XOR Gate

$$X = (\bar{A}B + B\bar{A})$$

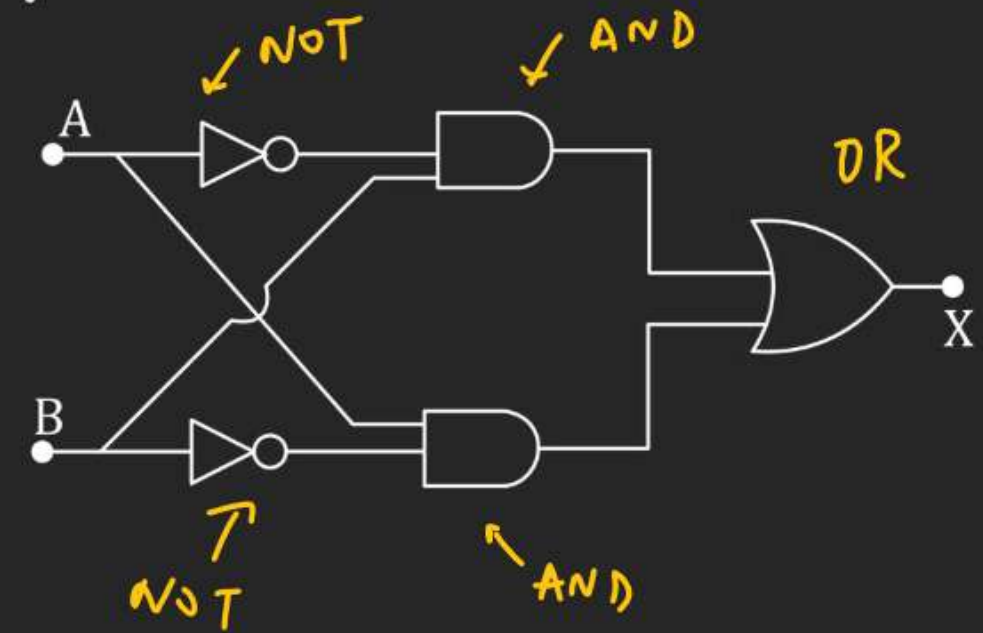

LOGIC GATE


Q.7 Name the gate represented by the following circuit:

(1) OR gate

(2) XOR gate ✓✓

(3) AND gate

(4) NAND gate

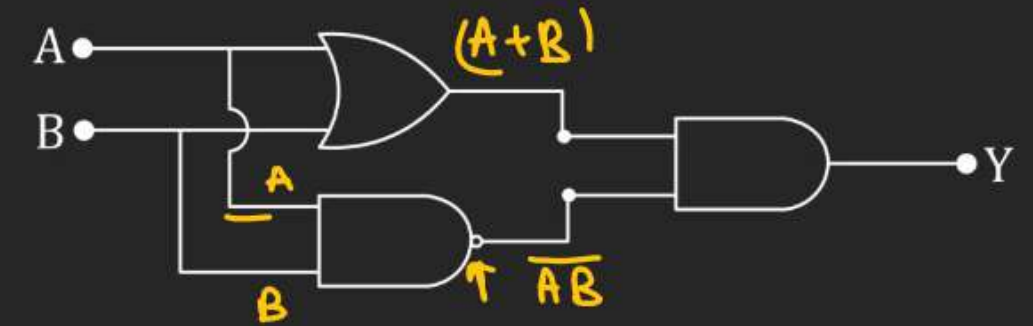

$$Y = (A+B) \cdot (\overline{AB})$$

$$Y = (A+B) \cdot (\overline{A} + \overline{B})$$

$$Y = \underbrace{A \cdot \overline{A}}_{\downarrow 0} + A\overline{B} + B\overline{A} + \underbrace{B\overline{B}}_{\downarrow 0}$$


$$Y = \underline{A\overline{B} + B\overline{A}}$$

LOGIC GATE

H-W

Q.8 The combination of 'NAND' gates shown here under (figure) are equivalent to

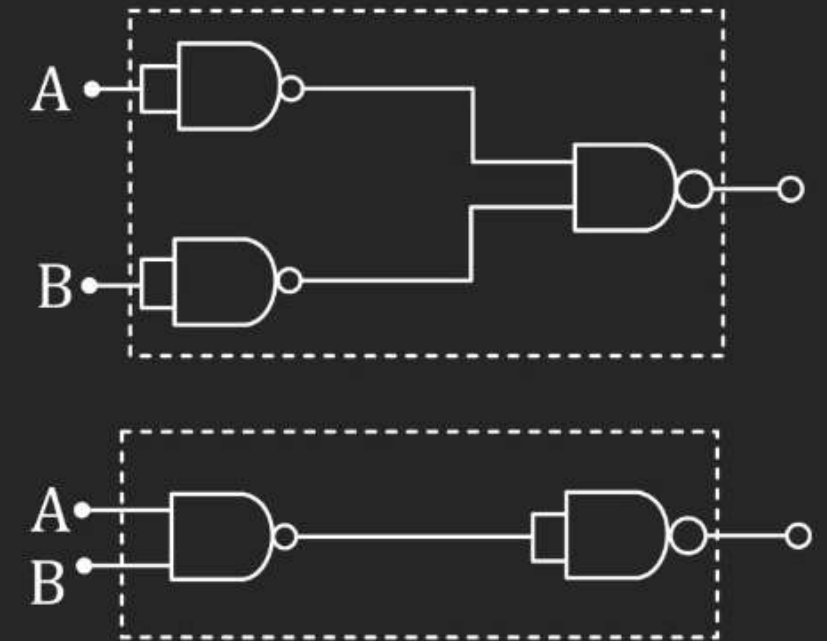- (A) An OR gate and an AND gate respectively**
- (B) An AND gate and a NOT gate respectively**
- (C) An AND gate and an OR gate respectively**
- (D) An OR gate and a NOT gate respectively.**



LOGIC GATE*H.W.*

Q.9 The following truth table corresponds to the logic gate where A and B represent inputs and X represents output.

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

(A) NAND

(B) AND

(C) XOR

(D) OR

LOGIC GATE

H.W.


Q.10 For the given combination of gates, if the logic states of inputs A, B, C are as follows $A = B = C = 0$ and $A = B = 1, C = 0$, then the logic states of output D are

(A) 0,0

(B) 0,1

(C) 1,0

(D) 1,1

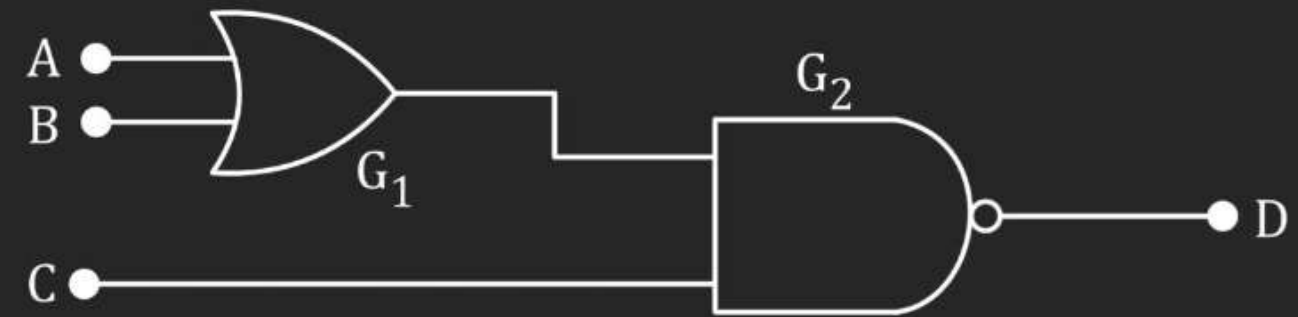

LOGIC GATE

H.W.


Q.11 To get an output 1 from the circuit shown in the figure, the input must be

(A) $A = 0, B = 1, C = 0$

(B) $A = 1, B = 0, C = 0$

(C) $A = 1, B = 0, C = 1$

(D) $A = 1, B = 1, C = 0$

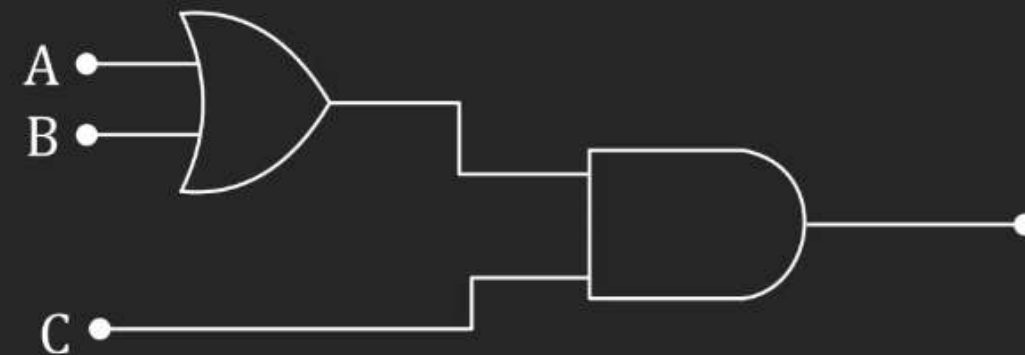

LOGIC GATE

H.W.


Q.12 The figure below gives a system of logic gates. From the study of truth table, it can be found that to produce a high output (1) at R, we must have

(A) $X = 0, Y = 1$

(B) $X = 1, Y = 1$

(C) $X = 1, Y = 0$


(D) $X = 0, Y = 0$

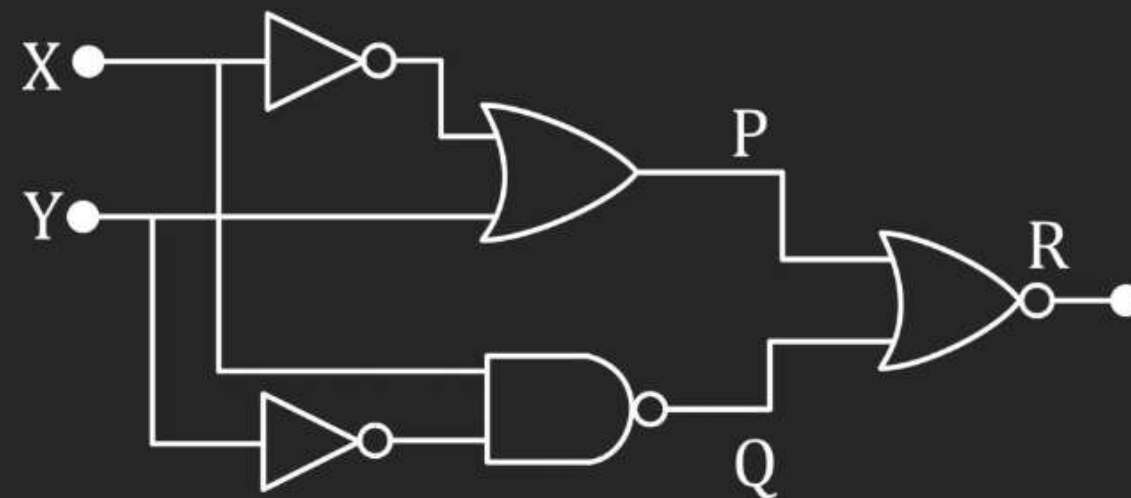

LOGIC GATE

H.W
Q.13 The combination of gates shown below produces

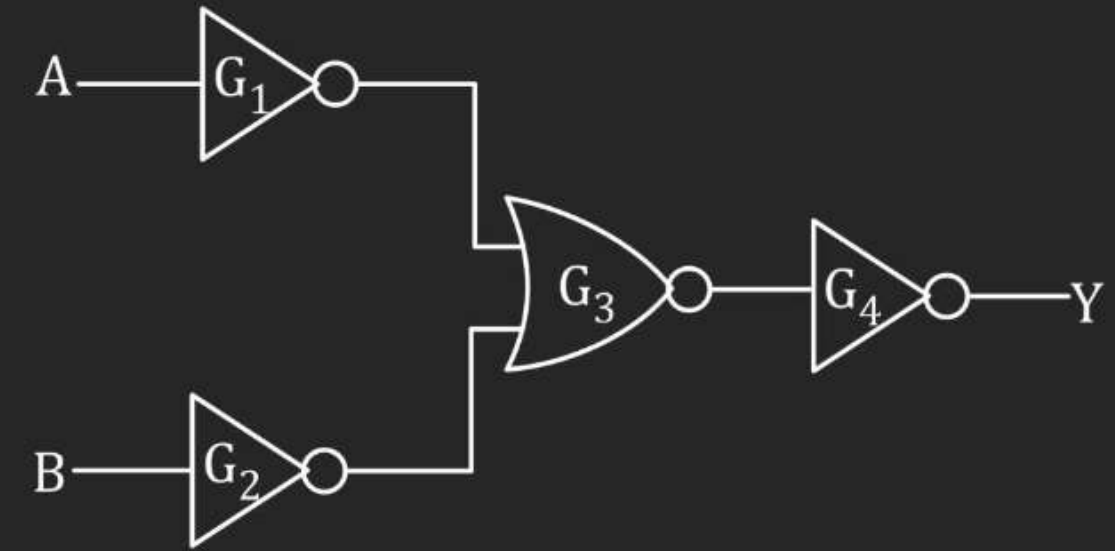- (A) AND gate
- (B) XOR gate
- (C) NOR gate
- (D) NAND gate



LOGIC GATE

H.W

Q.14 The figure shows two NAND gates followed by a NOR gate. The system is equivalent to the following logic gate

- (A) OR
- (B) AND
- (C) NAND
- (D) None of these

