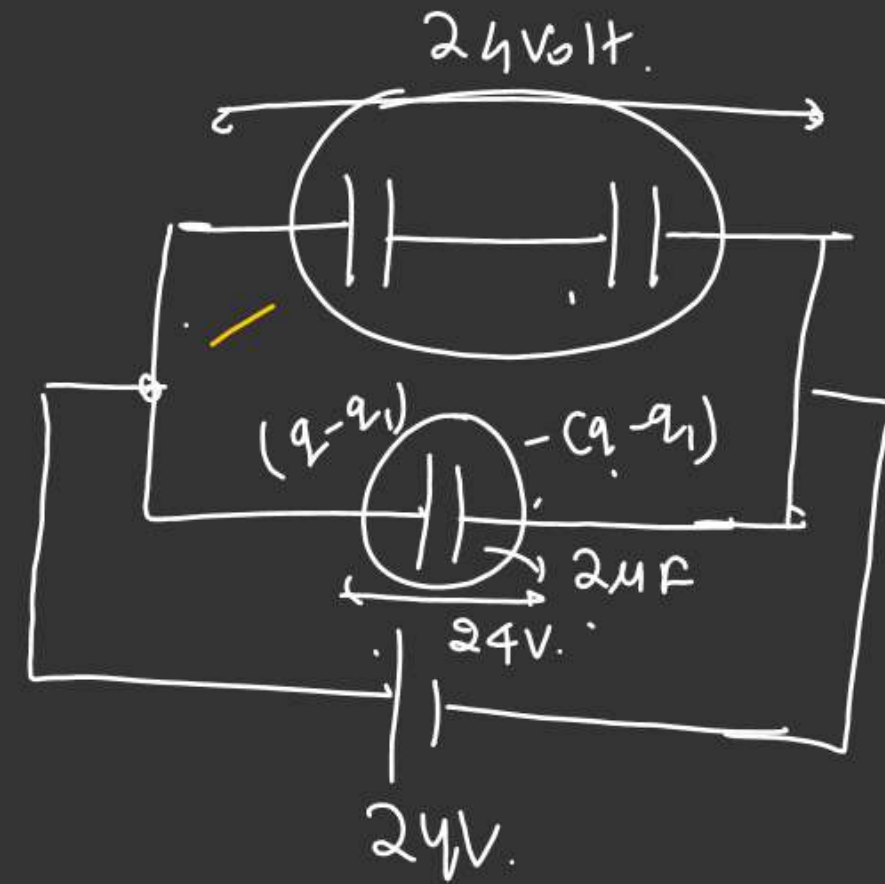




$$\begin{aligned}
 q &= C_{eq} \cdot V \\
 &= (6 \times 24) \mu C \\
 &= \underline{144 \mu C}
 \end{aligned}$$

$$\begin{aligned}
 \frac{q - q_1}{2} &= 24 \text{ Volt} \\
 q - q_1 &= 48 \\
 q_1 &= (144 - 48) \\
 &= \underline{96 \mu C} \quad \checkmark
 \end{aligned}$$






Capacitive Ckt

↳ K.C.L (Krichhoff's Current Law)

↳ "Conservation of Charge"

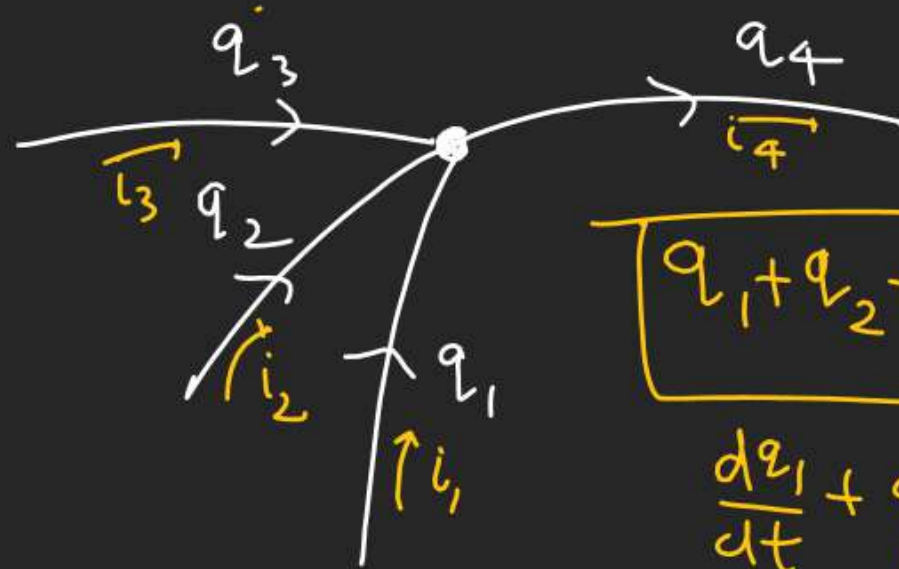Sum of incoming Charge is equal to  
Sum of outgoing Charge across any node or junction



$$q_1 + q_2 + q_3 = q_4$$

$$\frac{dq_1}{dt} + \frac{dq_2}{dt} + \frac{dq_3}{dt} = \frac{dq_4}{dt}$$

$$i_1 + i_2 + i_3 = i_4$$

K.V.L :- "Krichhoff's Voltage Law"

↳ [Sum of all the potential drop in a close loop is equal to zero]

Sign-Convention :-



Sign-Convention of battery :- (i) While moving

$\mathcal{E} = (\text{Constant})$



$$V_B - V_A = \mathcal{E}$$

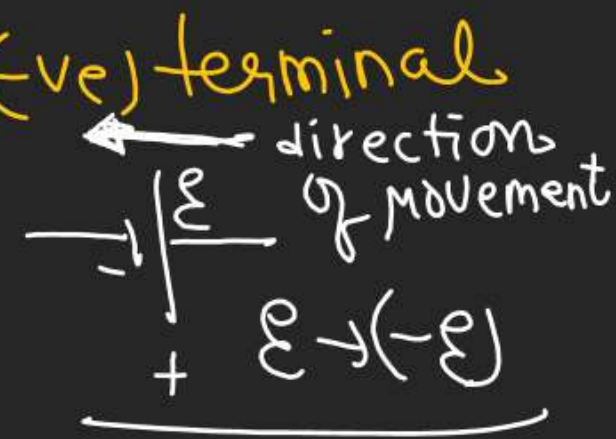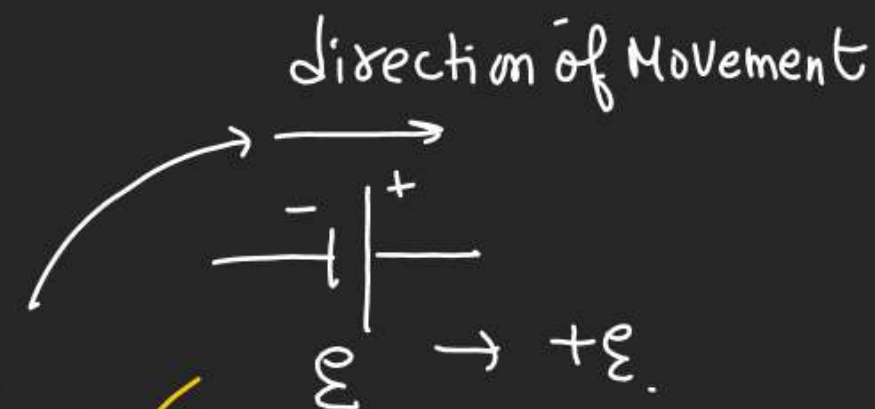
(ii) While moving from (+ve) terminal of battery to (-ve) terminal of battery  $\rightarrow (-\mathcal{E})$  ✓





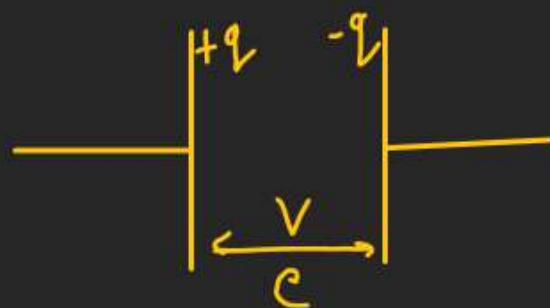
**Capacitive Ckt** →**CAPACITOR**

Sign-Convention for Capacitor :- ① While moving from +ve plate of Capacitor to -ve plate we assume potential drop.




$$q = CV$$

$$V = (q/C)$$

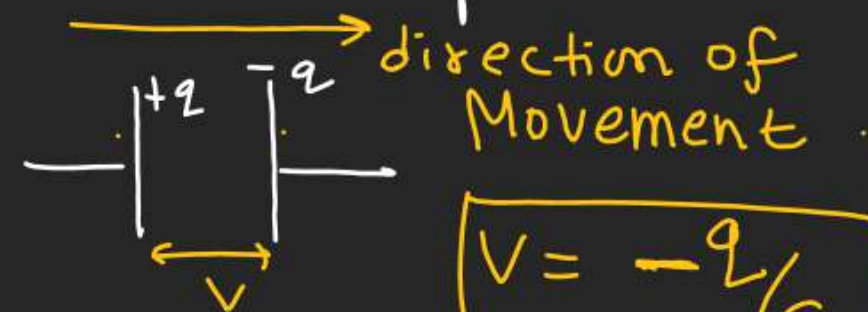

$$V = -q/C$$

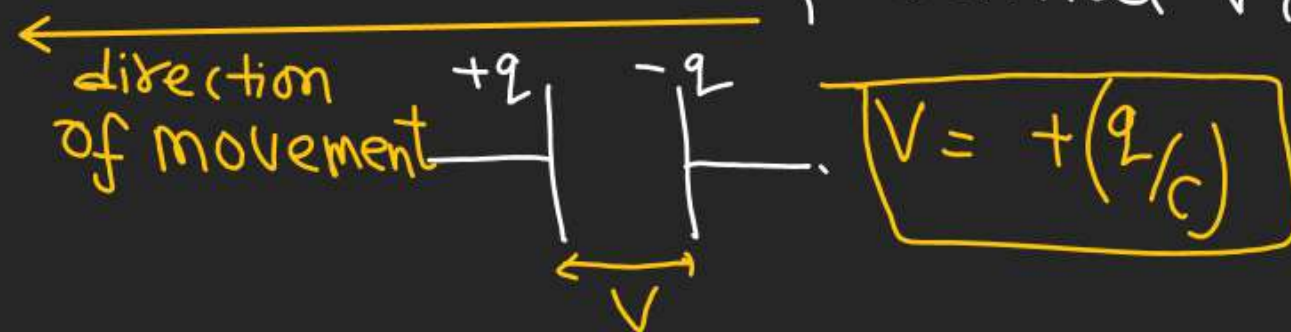② While moving from -ve plate of Capacitor to +ve plate we assume potential rise.



$$V = +(q/C)$$

## Capacitive Ckt

## CAPACITOR

→ K.V.L in close loop  
ABCDEFA : →

$$+4 - \frac{q}{2} - \frac{q_1}{3} - 2 = 0$$

$$2 = \frac{q}{2} + \frac{q_1}{3}$$

$$12 = 3q + 2q_1 \quad \text{--- (1)}$$

K.V.L in closed loop ABEFA

$$-\frac{q}{2} - \frac{(q - q_1)}{1} + 4 = 0$$


$$\frac{q}{2} + \frac{(q - q_1)}{1} = 4$$

$$q + 2(q - q_1) = 8$$

$$3q - 2q_1 = 8 \quad \text{--- (2)}$$

$$2q_1 = 12 - 3q \quad \text{From (1)}$$
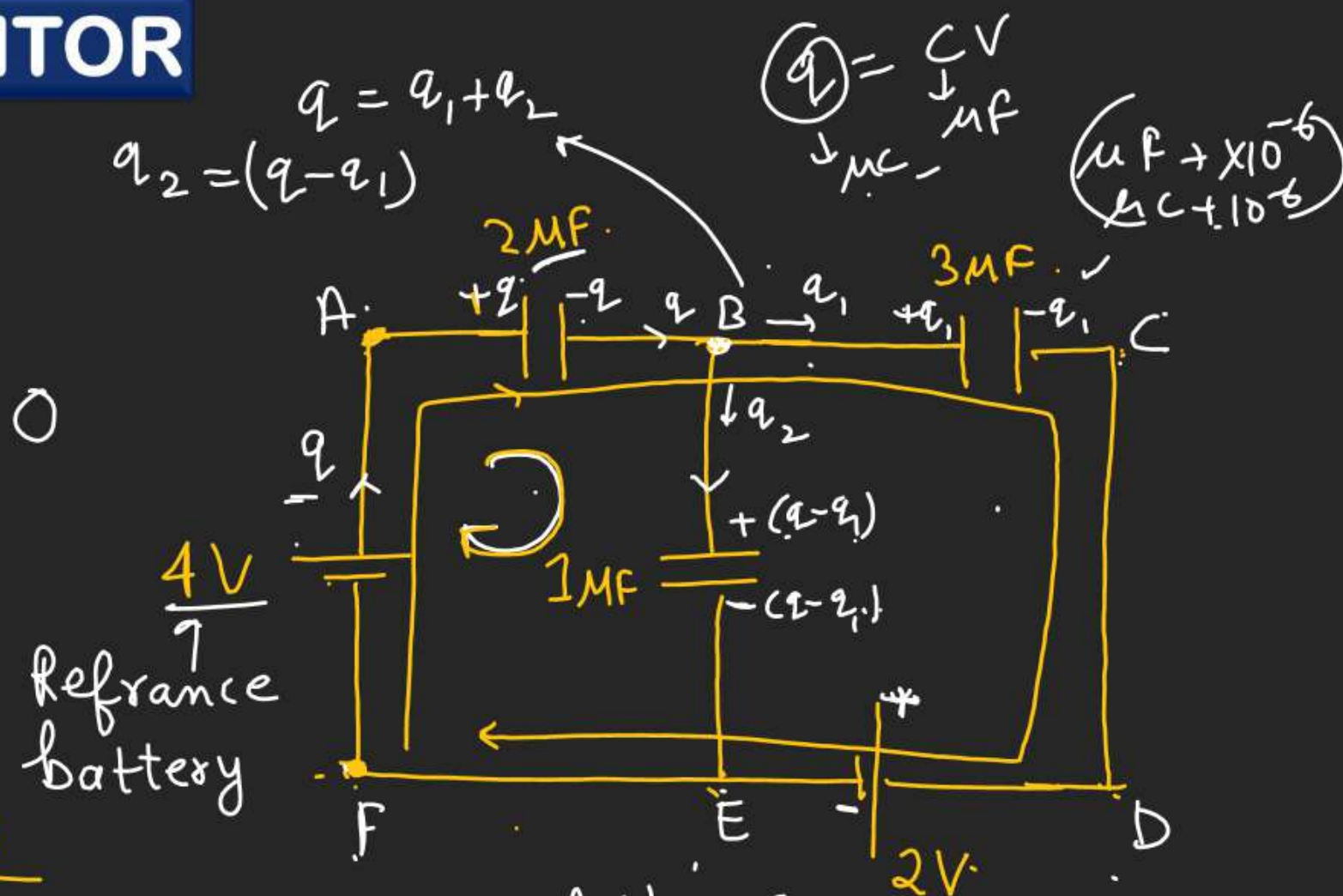
$$q_1 = \left(6 - \frac{3q}{2}\right) = 6 - \frac{3}{2} \times \frac{10}{3} = 1 \mu\text{C} \quad \checkmark$$




Adding (1) + (2)

$$6q = 20$$
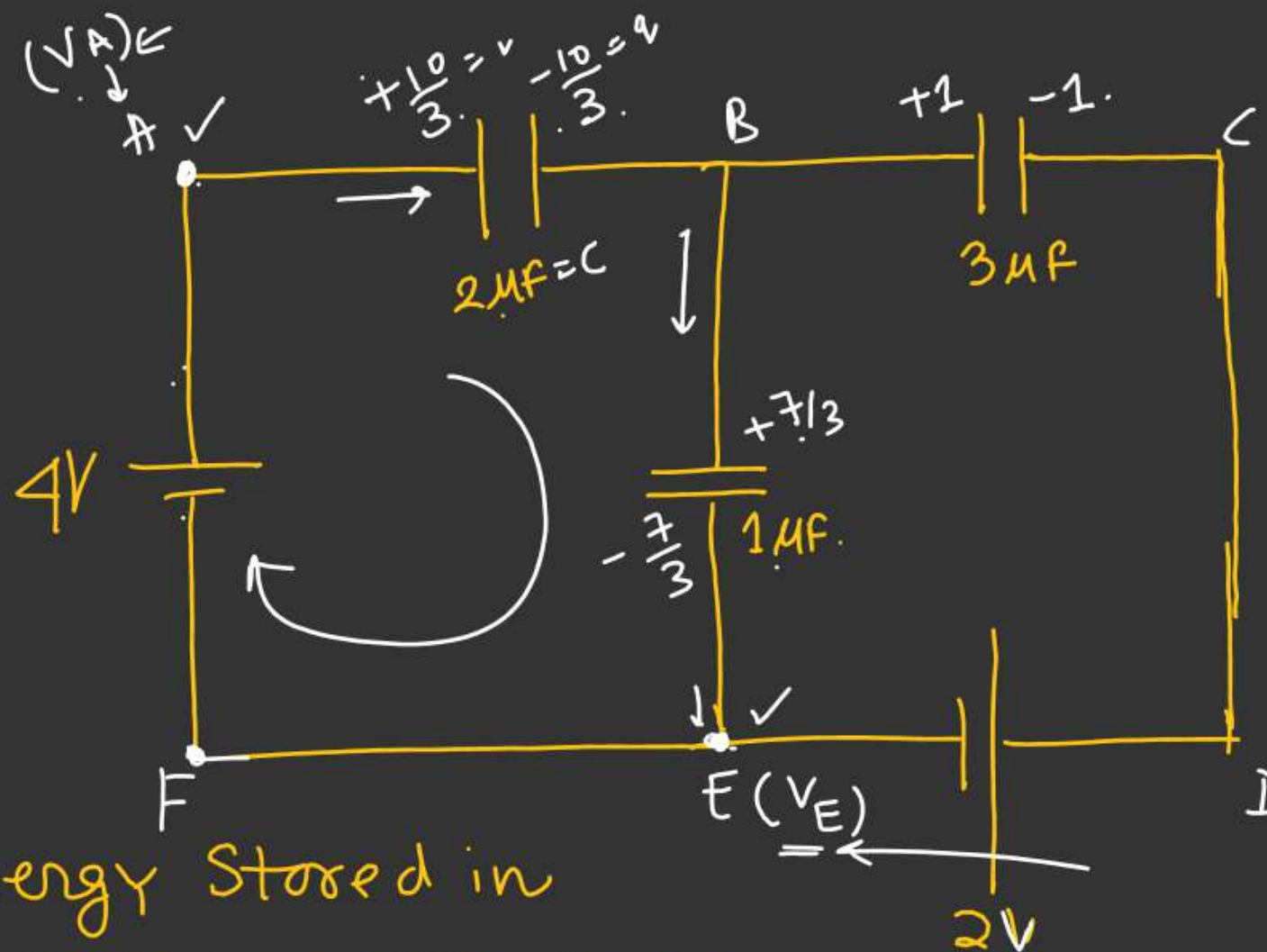
$$q = \frac{20}{6} = \left(\frac{10}{3} \mu\text{C}\right) \quad \checkmark$$





⇒ Energy Stored in Capacitor 2μF, 3μF & 1μF.

$$\Rightarrow U_{2\mu F} = \frac{q^2}{2C} = \frac{(\frac{10}{3})^2}{2 \times 2} = \left(\frac{100}{36}\right) \mu J \checkmark$$

$$V_A - V_E = ??$$

$$V_A - \left(\frac{10}{3 \times 2}\right) - \frac{7}{3} = V_E$$

$$\underline{V_A - V_E} = \left(\frac{10}{6} + \frac{7}{3}\right)$$

$$= \frac{10 + 14}{6} = \frac{24}{6}$$

$$= \textcircled{+4 \text{ Volt}} \checkmark$$

$$\underline{V_A > V_E}$$

## Capacitive Ckt

## CAPACITOR

$$C, C, C \rightarrow \text{Series} = \frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} \Rightarrow C_{eq} = \frac{C}{3}$$

**Q.2** If 100 volts of potential difference is applied between a and b in the circuit of figure (31-W2a), find the potential difference between c and d.


$$C_{eq} = (2 + 6) \mu F$$

$$= 8 \mu F$$

$$Q = C_{eq} \cdot V$$


$$= (8 \times 100) \mu C$$

$$= 800 \mu C$$

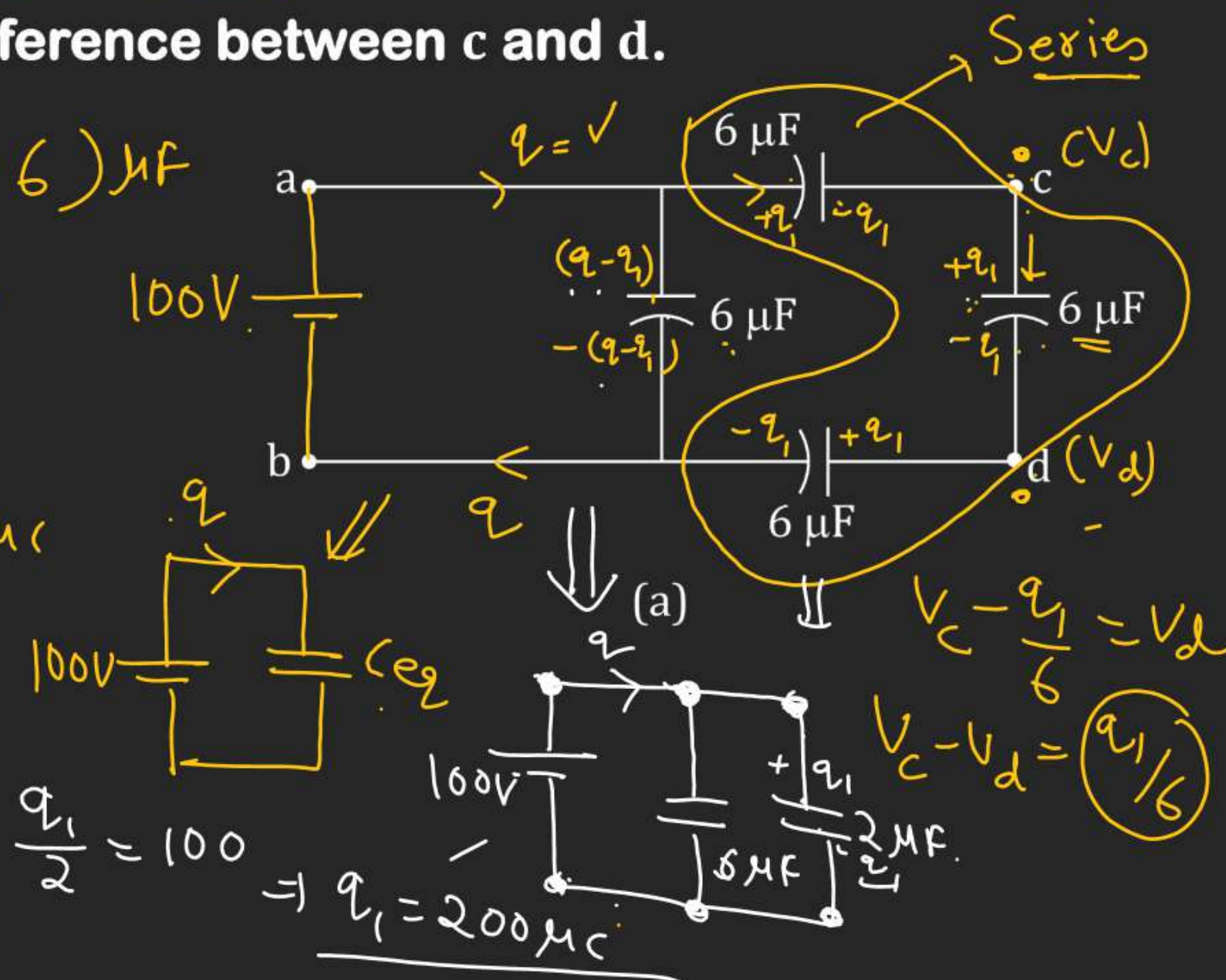



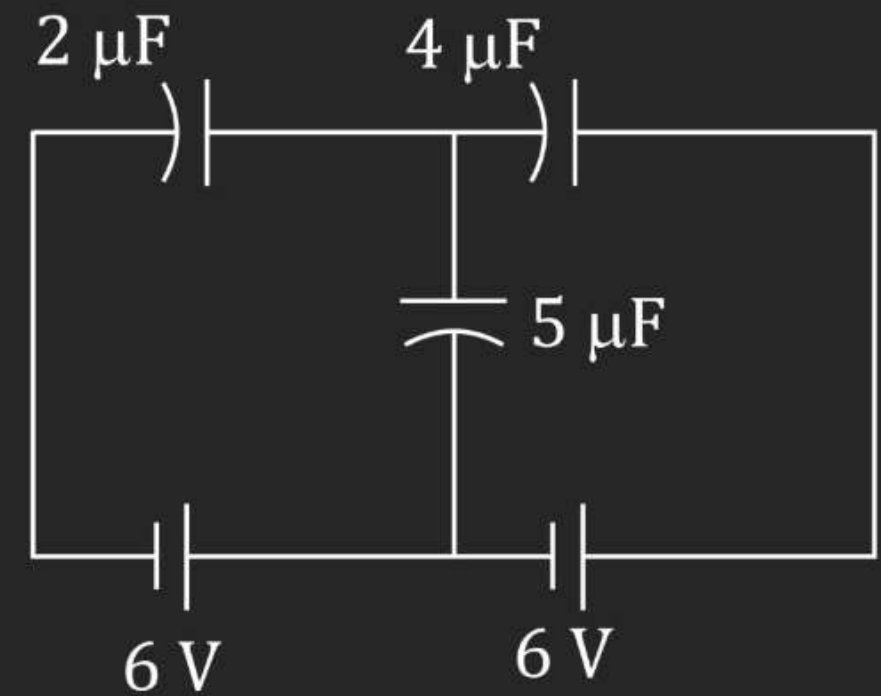Q.3 Find the charges on the three capacitors shown in figure (a).



(a)

H.W.

## CAPACITOR

**Q.6** A circuit has a section AB shown in Fig. The emf of the source equals  $\varepsilon = 10\text{ V}$ , the capacitor capacitances are equal to  $C_1 = 1.0\mu\text{F}$  and  $C_2 = 20\mu\text{F}$ , and the potential difference  $V_A - V_B = 5.0\text{ V}$ . Find the voltage across each capacitor.





H.W.

## CAPACITOR

**Q.7** In a circuit shown in Fig. find the potential difference between the left and right plates of each capacitor.

