

DPP - 9

SOLUTION

Link to View Video Solution: [Click Here](#)

1. $4 \times DC = Y \times AD$

$\Rightarrow 4 \times 60 = Y \times 40$

$Y = 6\Omega$


For y $R_f = 6(1 + 6.3 \times 10^{-4} \times 100)$

$R_f = 6[1 + 0.063] = 1.063 \times 6$

$R_f = 6.378\Omega$

After heating Y, resistance of Y is 6.378Ω

Y connected with a unknow resistance R.

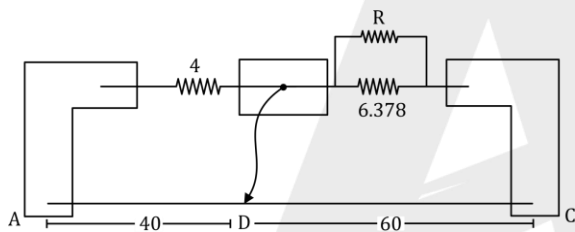


$4 \times 60 = 40 \times \frac{R(6.378)}{R + 6.378}$

$6R + 6 \times 6.378 = 6.378 \times R$

$0.378R = 6 \times 6.378$

2. $\frac{R}{20} = \frac{x}{80} \Rightarrow \frac{R}{x} = \frac{1}{4}$

$x = 4R$ (i)

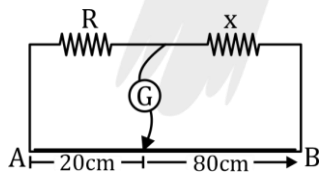

When 10Ω connected in parallel to R.



$\frac{\left(\frac{10R}{10+R}\right)}{10} = \frac{x}{90}$

$\Rightarrow x = 50\Omega$

3. $\frac{R_1}{x} = \frac{l}{100-l}$

$\Rightarrow \frac{100}{x} = \frac{20}{80}$

$x = 400\Omega$

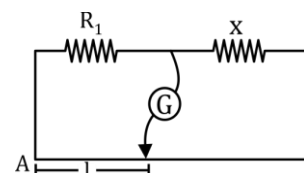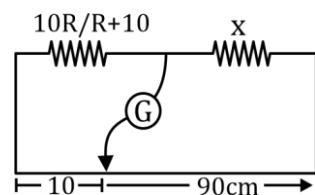

Link to View Video Solution: [Click Here](#)


$$x = \frac{\rho l}{A} = \frac{\rho l}{\left(\frac{\pi d^2}{4}\right)} \Rightarrow d = 1 \text{ mm} \Rightarrow d = 1 \times 10^{-3}$$

$$400 = \frac{\rho \times 20 \times 10^{-3}}{\pi \times 10^{-6}} \times 4$$

$$5 \times \pi \times 10^{-3} = \rho$$

$$\rho = 5\pi \times 10^{-3}$$

4.

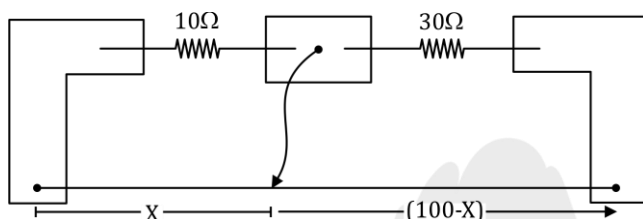


$$30x = (100 - x)10$$

$$3x = 100 - x$$

$$x = 25 \text{ cm}$$

when resistance Interchanged

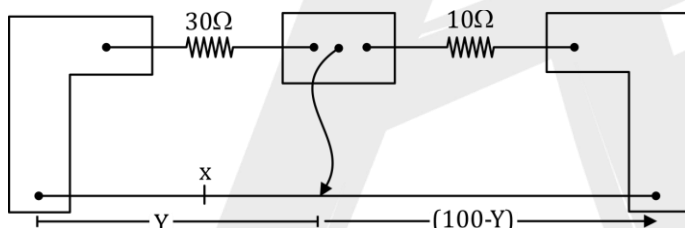

$$10Y = 30(100 - Y) \Rightarrow Y = 300 - 3Y$$

$$4Y = 300 \Rightarrow Y = 75$$

So balance point shift by $y - x$

$$= 75 - 25 = 50 \text{ cm}$$

5. $R \times 60 = 90 \times 40$

$$R = \frac{180}{3} = 60\Omega$$


$$\frac{R}{90} = \frac{l}{(100-l)} \quad [l = 40 \text{ cm}]$$

$$R = 90 \cdot \frac{l}{(100-l)} \Rightarrow \frac{\Delta R}{R} = \frac{\Delta l}{l} + \frac{\Delta l}{(100-l)} = \frac{0.1}{40} + \frac{0.1}{60}$$

$$\Delta R = 0.25 \Rightarrow R = (60 \pm 0.25)\Omega$$

6. most sensitive when the resistance of all the four arms of bridge is same

For the resistor B the value of x is the most accurate answer.

Link to View Video Solution:  [Click Here](#)

7. $\frac{R}{X} = \frac{\ell}{100 - \ell}$

$$\Rightarrow X = \frac{R(100 - \ell)}{\ell}$$

For 1, $X = \frac{100 \times 40}{60} = \frac{2000}{3} \Omega = 667 \Omega$

For 2, $X = \frac{100 \times 87}{13} = \frac{8700}{13} \Omega = 669 \Omega$

For 3, $X = \frac{10 \times 98.5}{1.5} = \frac{1970}{3} \Omega = 656 \Omega$

For 4, $X = \frac{1 \times 99}{1} = 99 \Omega$

Clearly, we can see that the value of X calculated

CASE-4 is inconsistent with the other values.

Hence, the correct answer is (D).

8. The ratio $\frac{AC}{CB}$ will remain unchanged.

9. Since $\frac{dR}{d\ell} = \frac{K}{\sqrt{\ell}}$

$$\Rightarrow \int_0^R dR = K \int_0^\ell \frac{d\ell}{\sqrt{\ell}} \quad \Rightarrow R = 2K\sqrt{\ell}$$

$$\Rightarrow \frac{R}{R'} = \frac{2K\sqrt{\ell}}{2K(1 - \sqrt{\ell})} = \frac{\sqrt{\ell}}{1 - \sqrt{\ell}}$$

Since $R = R'$

$$\Rightarrow \frac{\sqrt{\ell}}{1 - \sqrt{\ell}} = 1 \quad \Rightarrow 2\sqrt{\ell} = 1$$

$$\Rightarrow \ell = \frac{1}{4} = 0.25 \text{ m} \quad \text{Hence, the correct answer is (C).}$$