
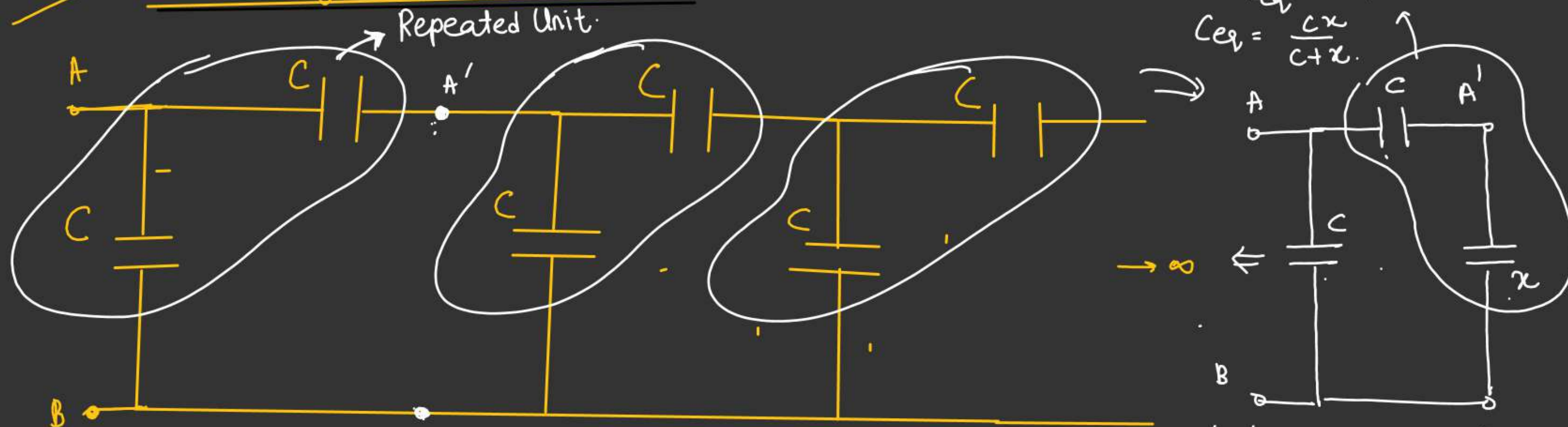


(Q) Case of infinite ladder:->

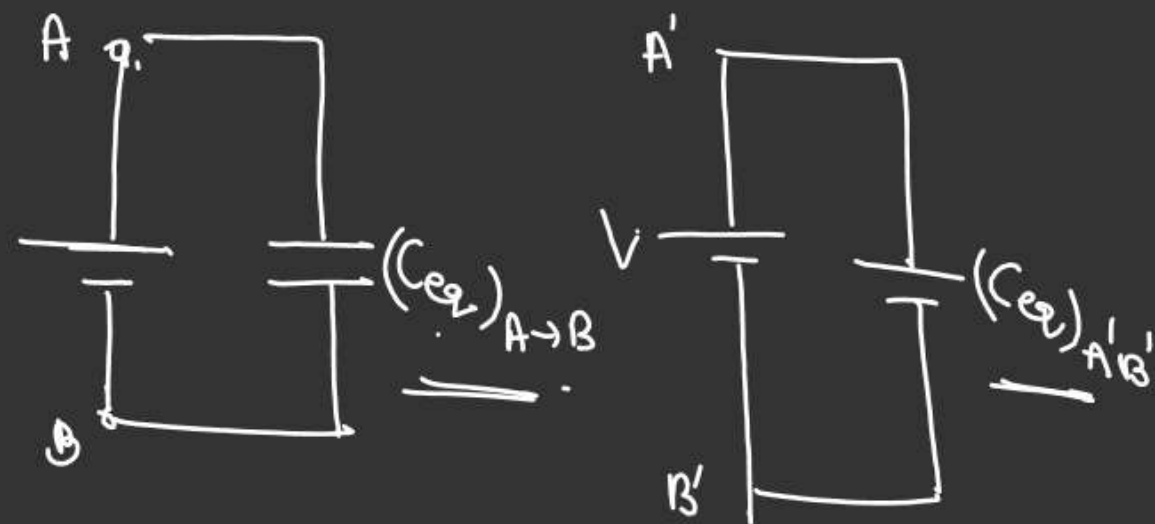

Ckt is identical w.r.t AB or A'B'

$$(C_{eq})_{AB} = (C_{eq})_{A'B'} = x \checkmark$$




$$x = \frac{Cx}{C+x} + C \Rightarrow x(C+x) = Cx + C(C+x)$$

$$x^2 - Cx - C^2 = 0 \Rightarrow x = \frac{C \pm \sqrt{C^2 + 4C^2}}{2}$$

$$\frac{C(1+\sqrt{5})}{2} \text{ Ans (} \pm \text{ve Roots)}$$



(*)

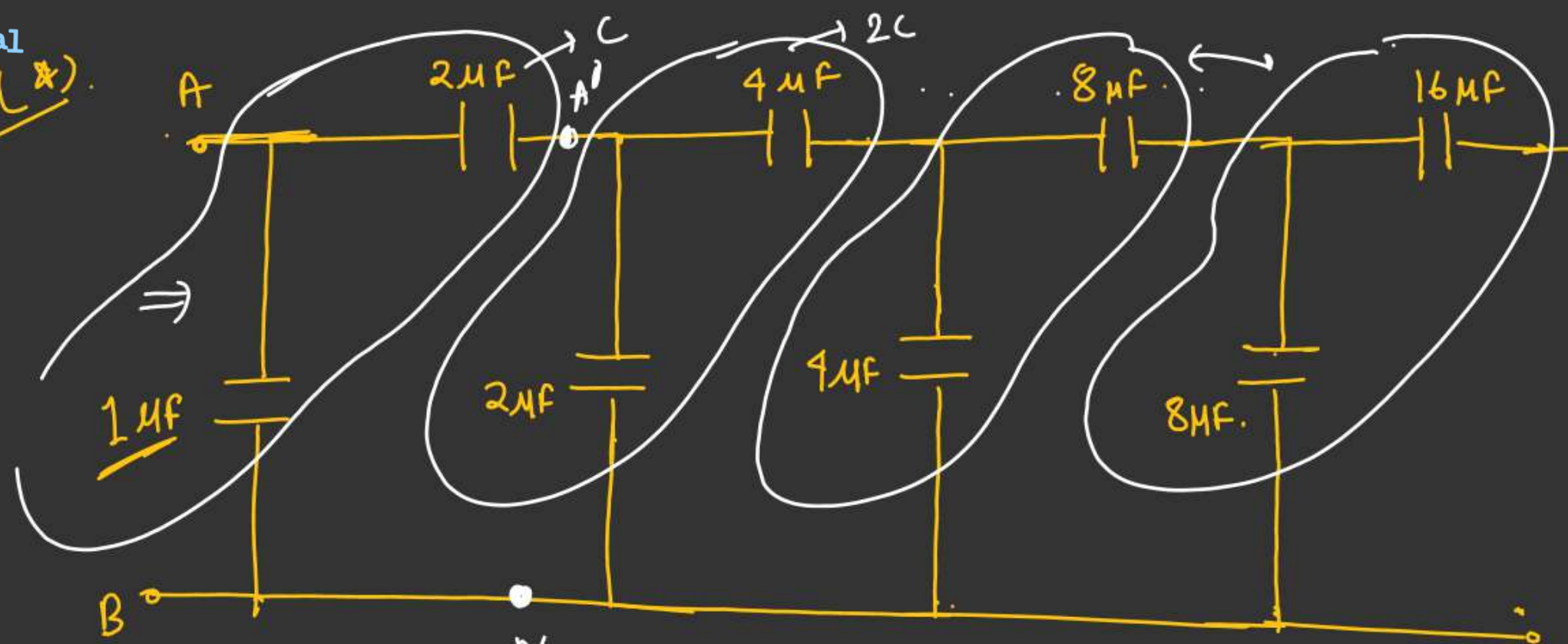


$\frac{1}{\gamma} (C_{eq})_{A'B'} = (C_{eq})_{A-B}$

$(C_{eq})_{A-B} = ??$

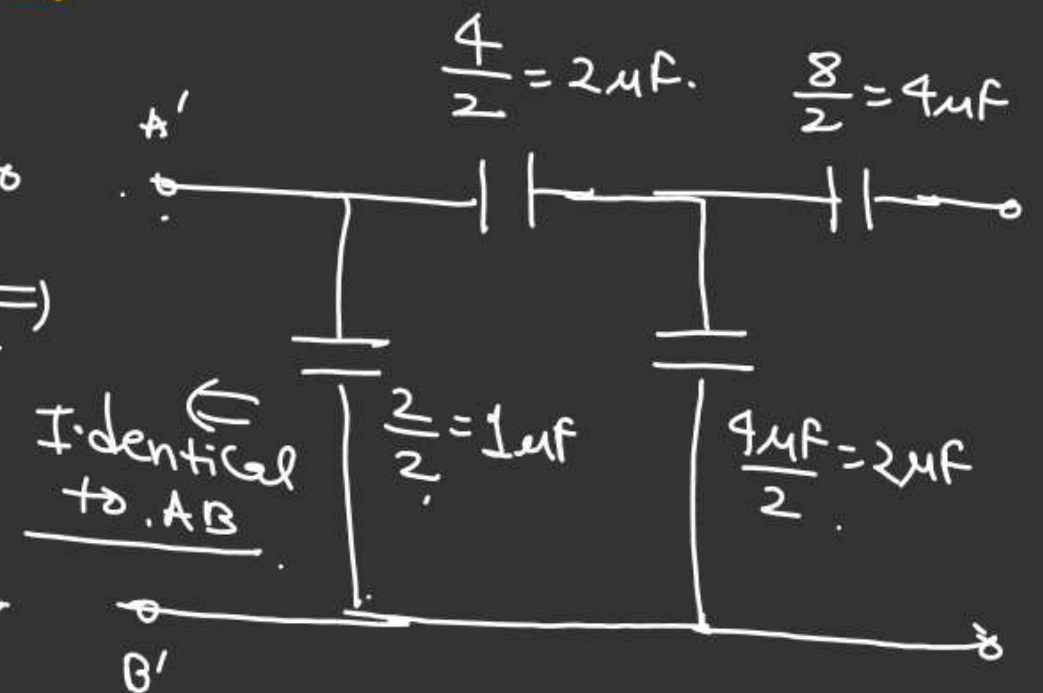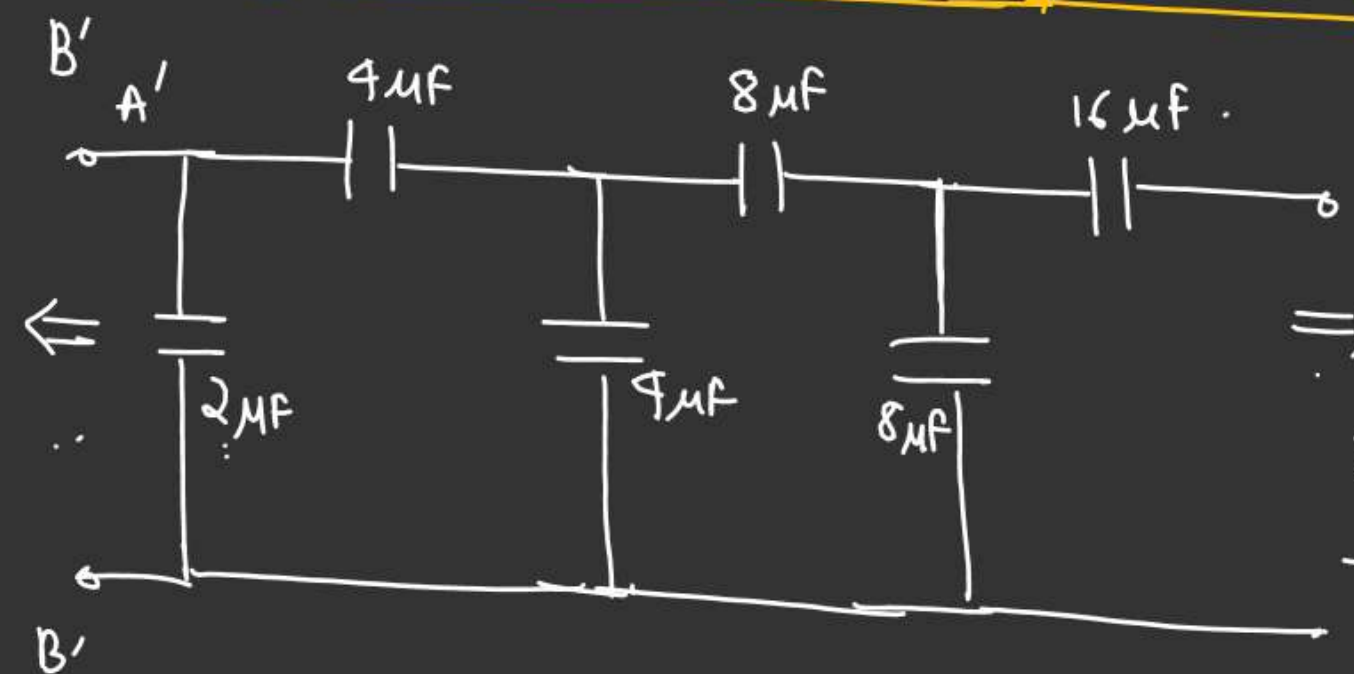$(C_{eq})_{A'B'} = \underline{\gamma} \checkmark$



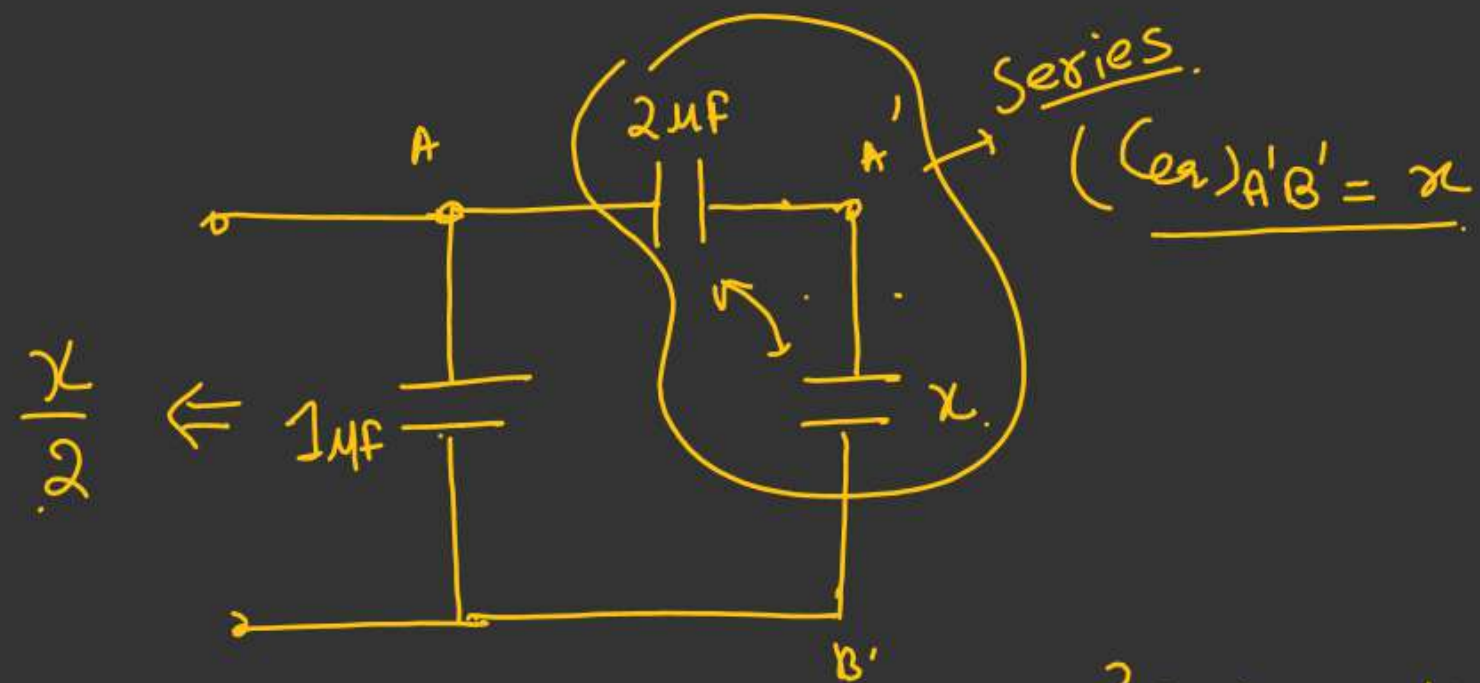

$$\frac{2x}{2+x} + 1 = \frac{x}{2}$$

$$\Rightarrow \frac{2x + 2 + x}{2+x} = \frac{x}{2}$$

$$\Rightarrow 2(3x+2) = x(2+x)$$

$$\Rightarrow \underline{6x+4} = \underline{2x+x^2}$$

$$x^2 - 4x - 4 = 0$$


$$x = \frac{4 \pm \sqrt{16+16}}{2}$$

$$x = \frac{4(1 \pm \sqrt{2})}{2}$$

$$x = \underline{2(1+\sqrt{2})} \text{ Ans } \checkmark$$

Equivalent capacitance (Symmetry) CAPACITOR

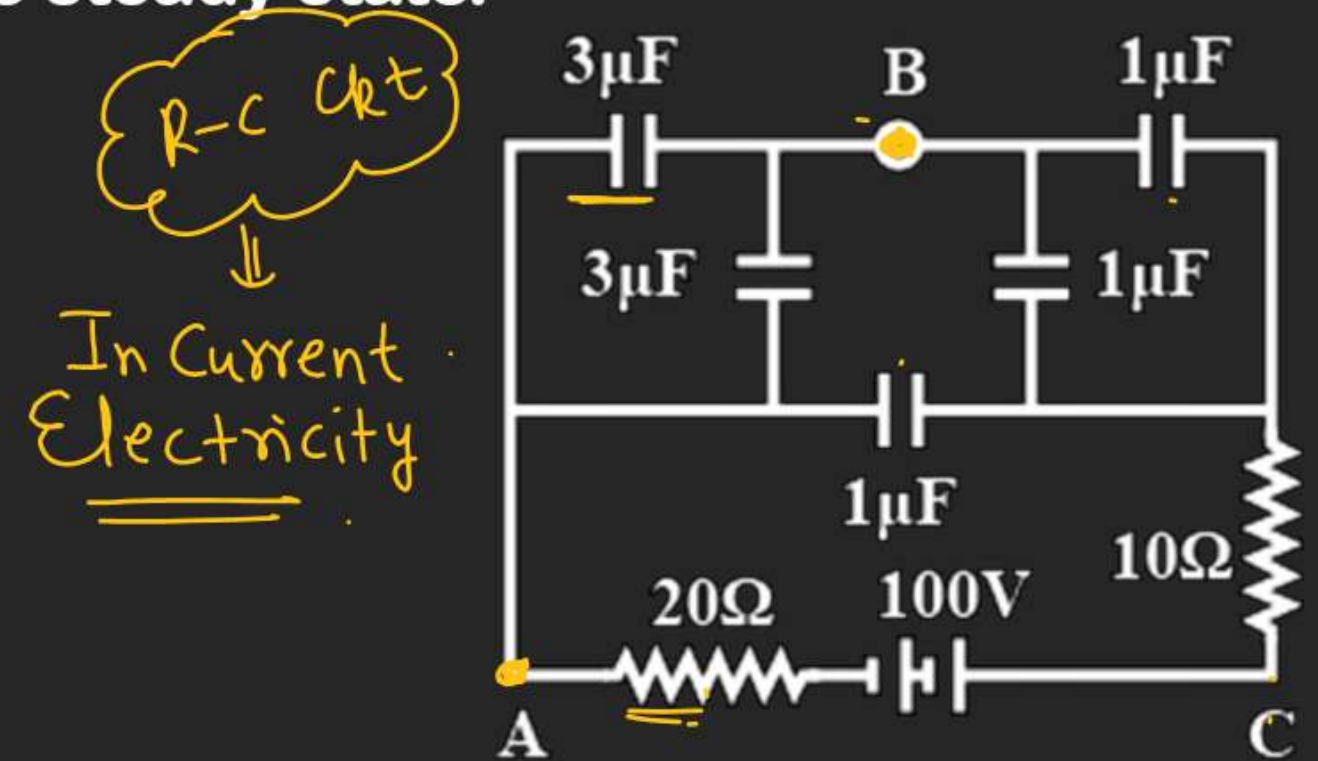Q.1 *H.W.* In circuit shown in figure calculate the potential difference between the points A and B and between the points B and C in the steady state.




- (iii) Infinite number of identical capacitors each of capacitance $1\mu\text{F}$ are connected as shown in figure. Find the equivalent capacitance of system between the terminals A and B shown in figure.

$$C_{eq} = C + \frac{C}{2} + \frac{C}{4} + \frac{C}{8} + \frac{C}{16} + \frac{C}{32} - \dots - \infty$$

$$C_{eq} = C \left[1 + \frac{1}{2} + \frac{1}{2^2} + \frac{1}{2^3} + \frac{1}{2^4} + \frac{1}{2^5} - \dots - \infty \right]$$
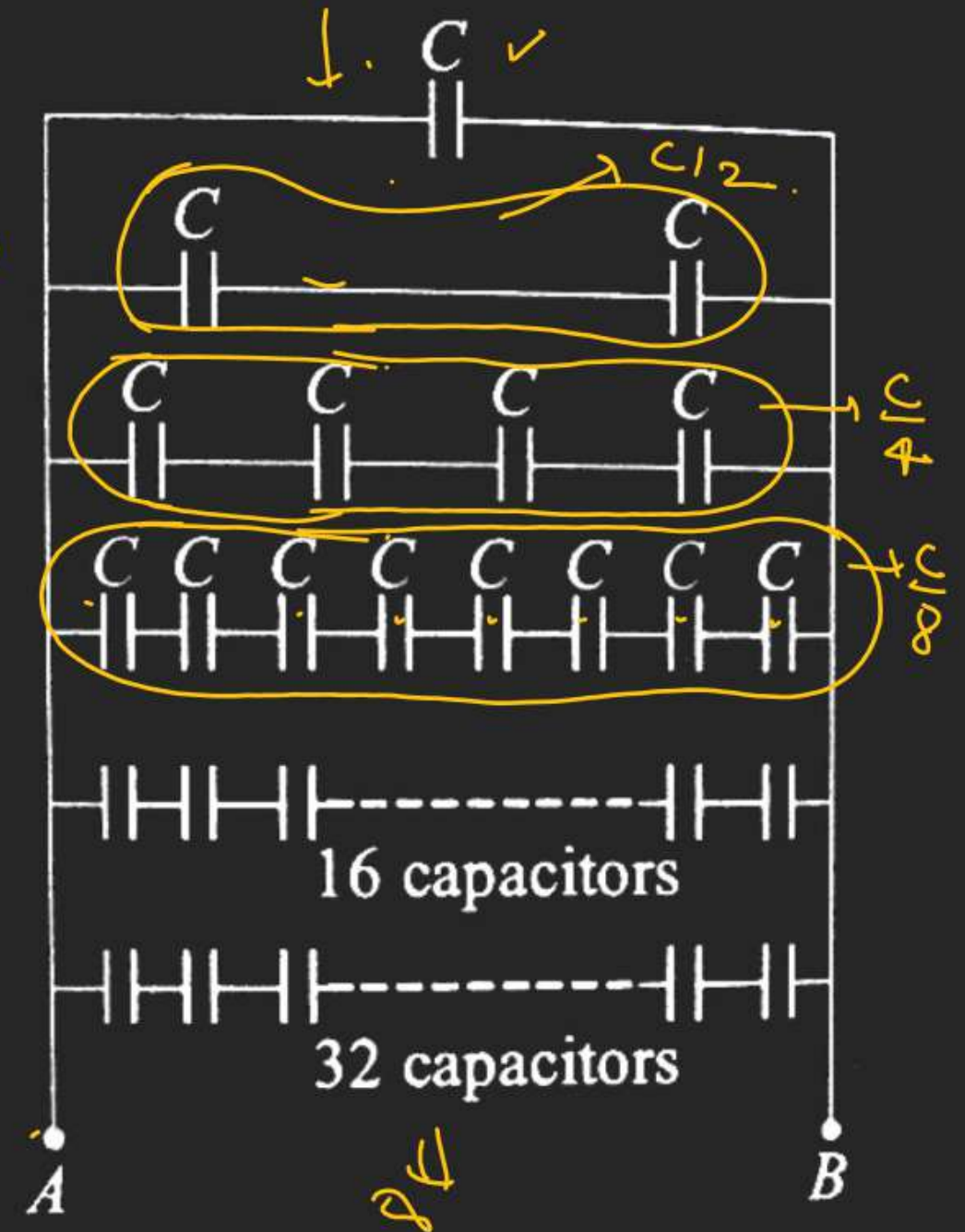
$$C_{eq} = C \left[\frac{1}{1 - \frac{1}{2}} \right] = \frac{2C}{1} = \underline{2\mu\text{F}} \text{ Ans}$$



Equivalent capacitance (Symmetry) CAPACITOR



$$(C_{eq})_{A-B} = ??$$

H.W.

$$\frac{C_1}{C_2} = \frac{C_3}{C_4} = \frac{2}{1}$$

$$\frac{C_2}{C_5} = \frac{C_4}{C_6} = \frac{1}{2}$$

$$(C_{eq})_{A-B} = 6 \mu F$$

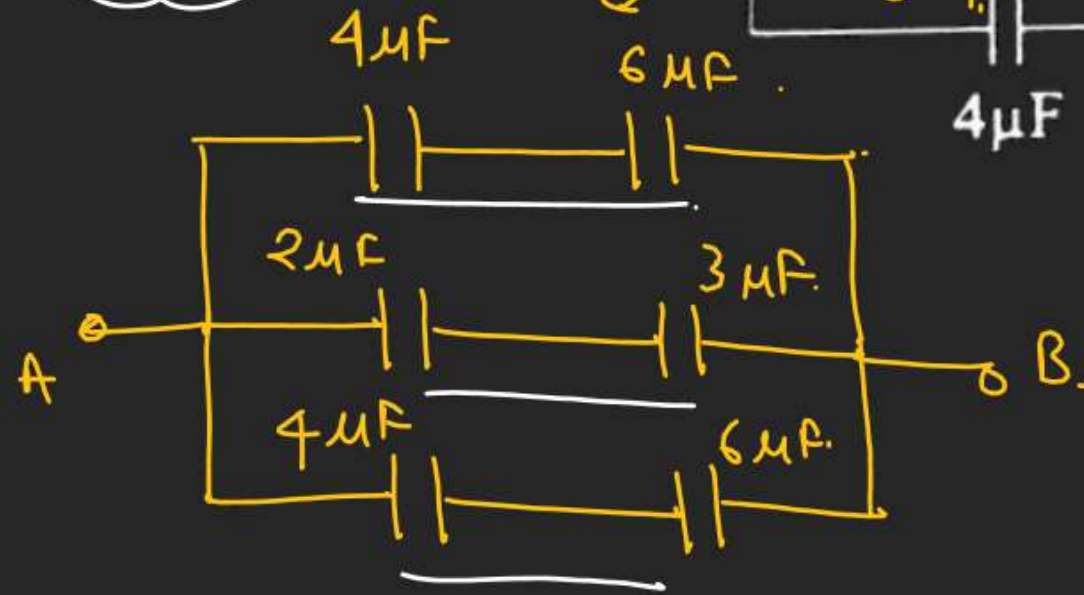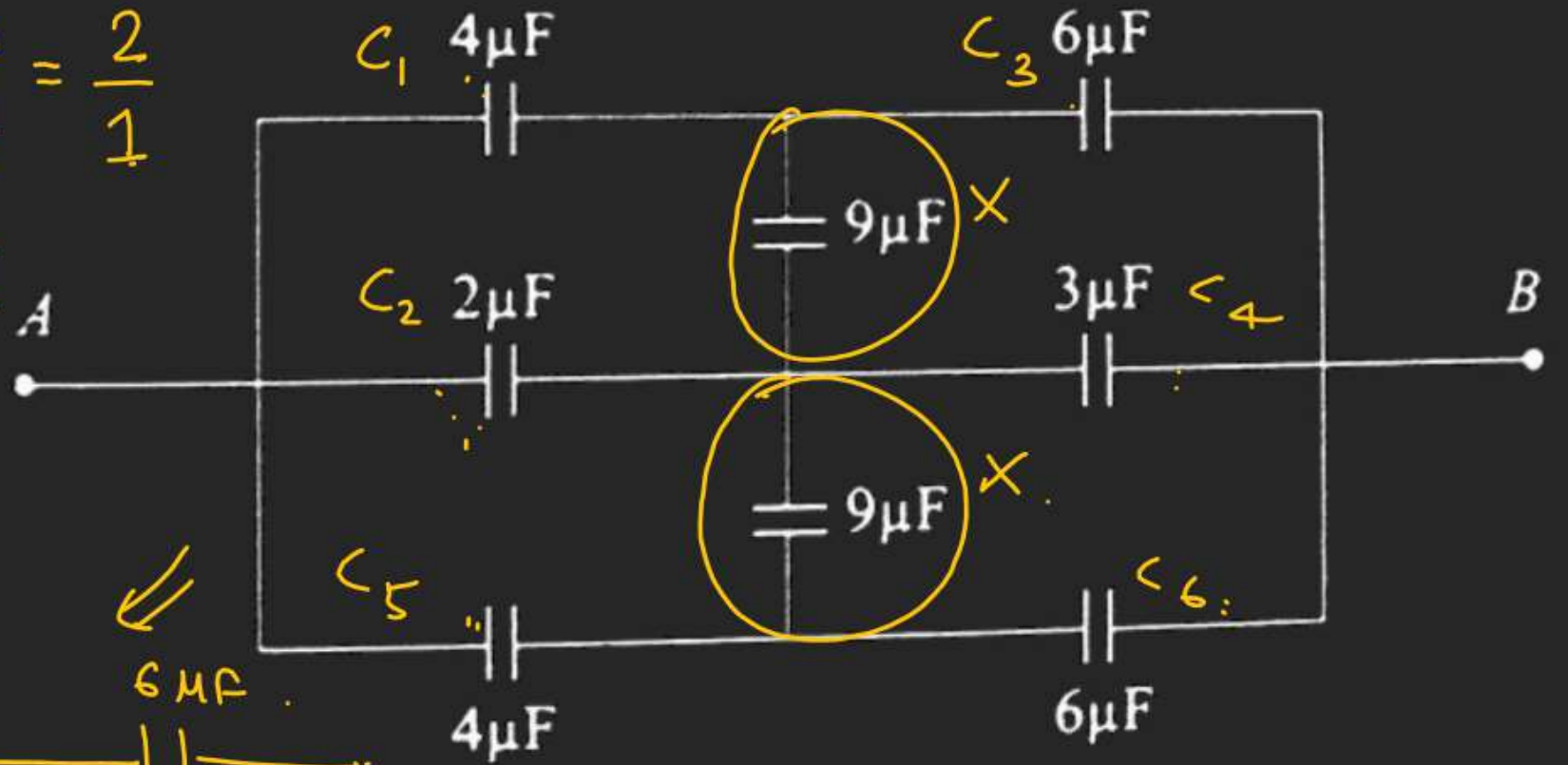

Equivalent capacitance (Symmetry)

CAPACITOR


H.W

$$\frac{1}{C_{eq}} = \frac{1}{2} + \frac{1}{3} + 1$$


$$\frac{1}{C_{eq}} = \frac{3+2+6}{6}$$

$$\frac{1}{C_{eq}} = \frac{11}{6} \mu F$$

$$C_{eq} = \frac{6}{11} \mu F$$

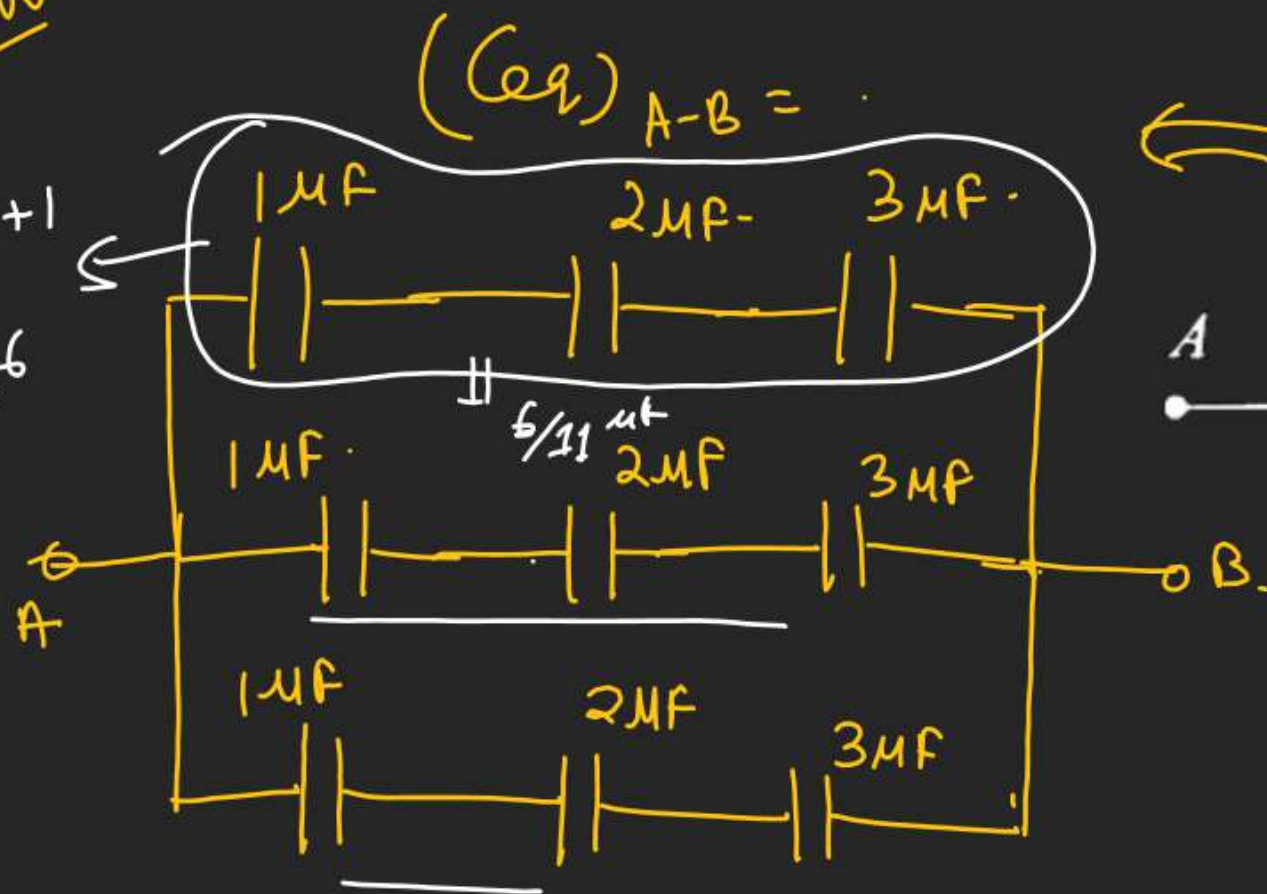
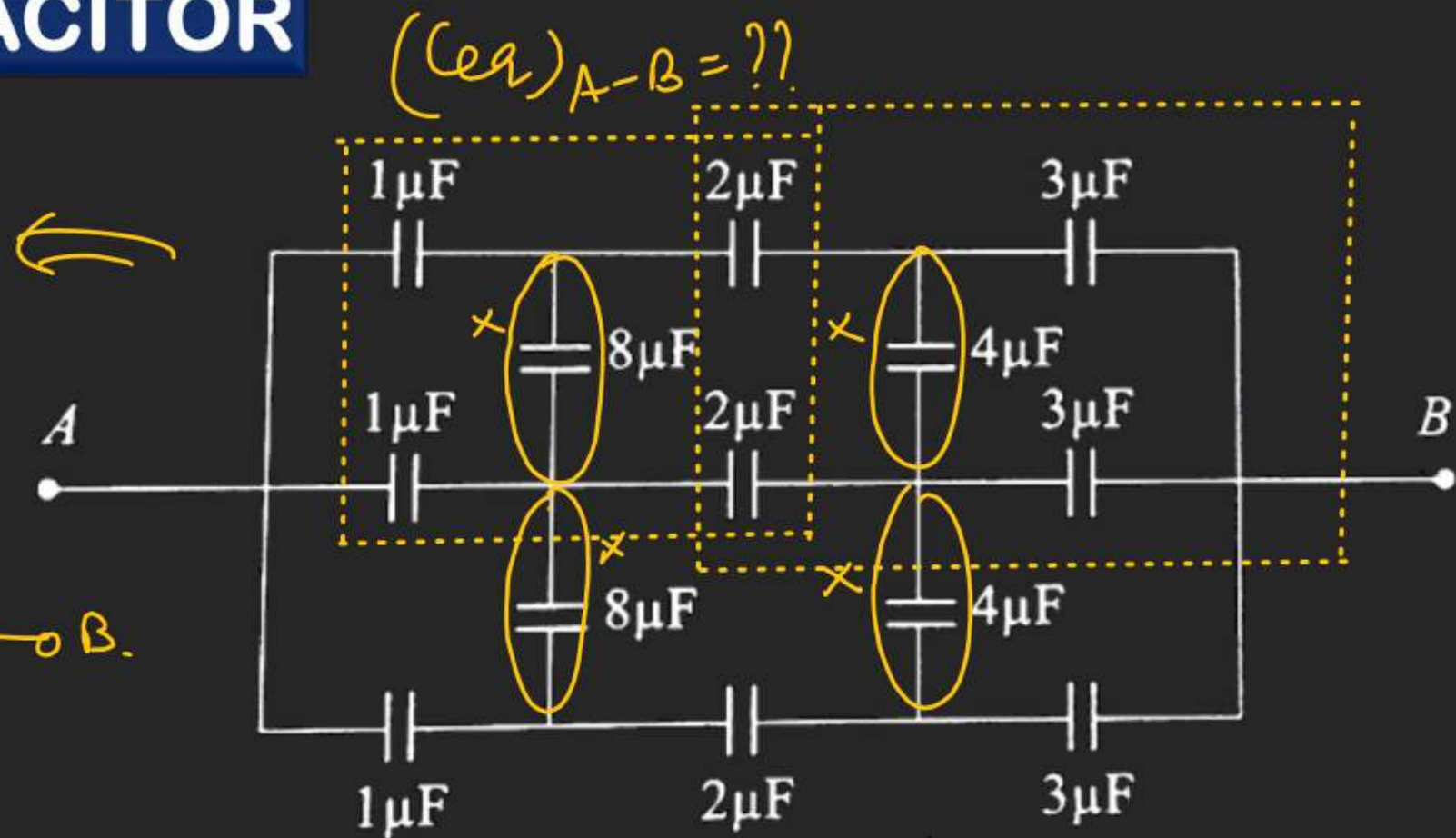
$$(C_{eq})_{A-B} = 3 \times \frac{6}{11} = \left(\frac{18}{11} \mu F \right)$$



Equivalent capacitance (Symmetry)



CAPACITOR

$$(C_{eq})_{A-B} = ??$$

H.W

Sol^mNote!

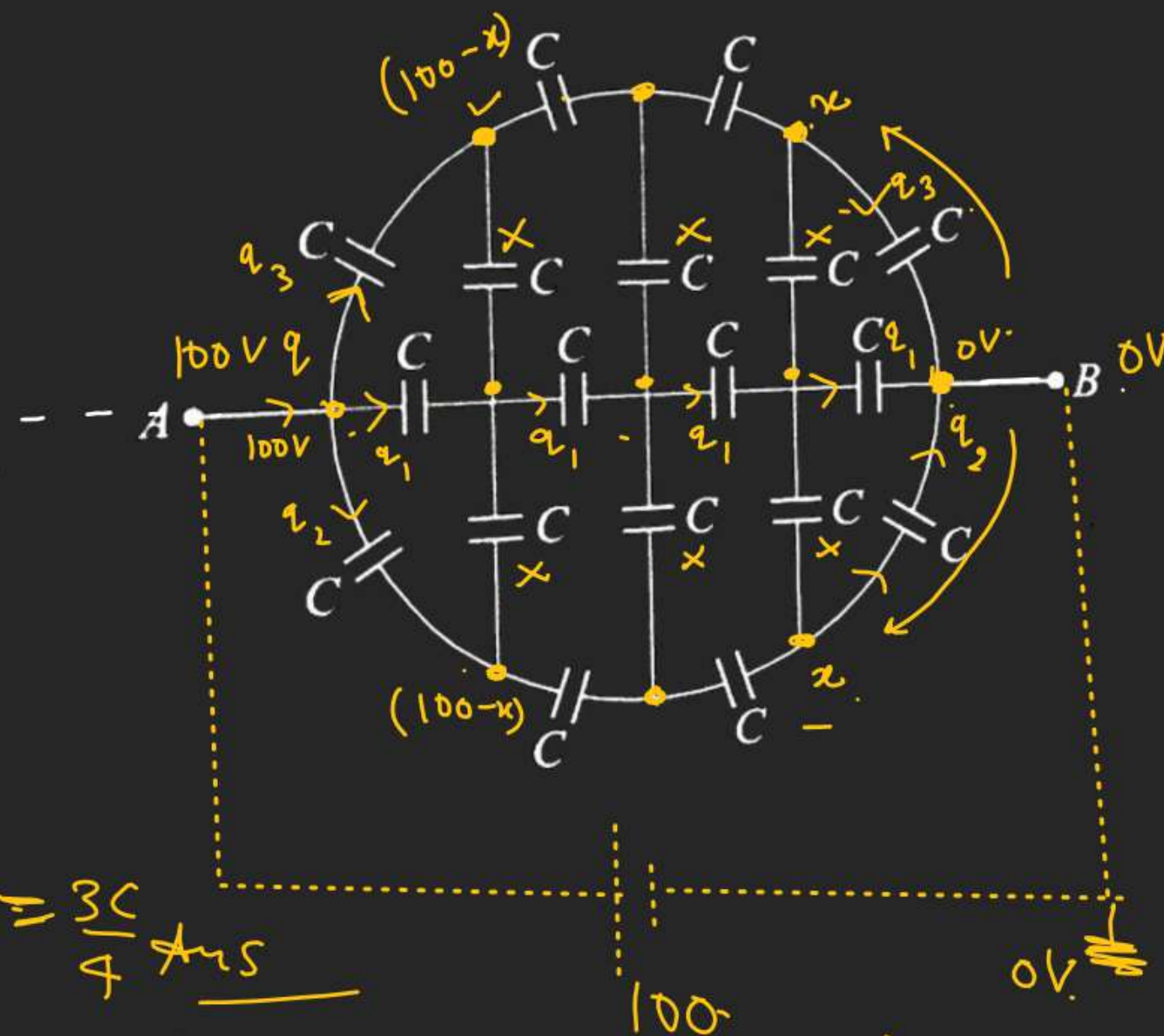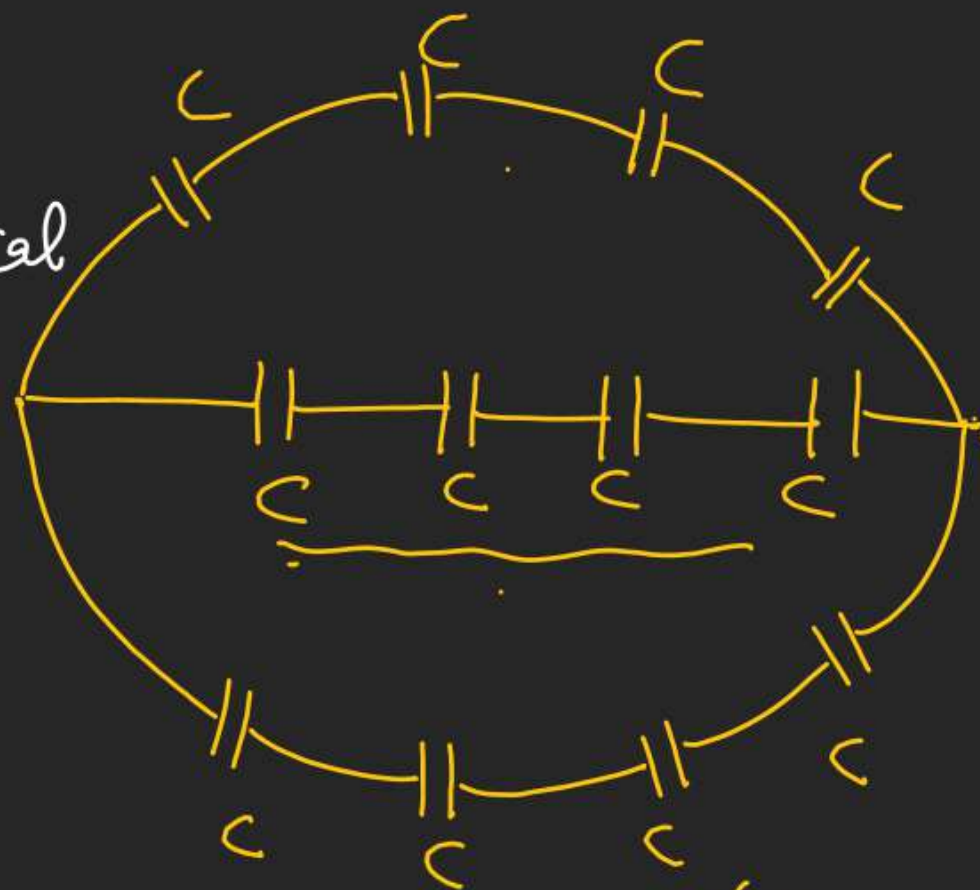Nodes Symmetrical
about any axis of
Symmetry are
at same
potential.




$$(C_{eq})_{A-B} = \frac{3C}{4} \text{ Ans}$$


Equivalent capacitance (Symmetry) CAPACITOR

$$(C_{eq})_{A-B} = ??$$

H.W.

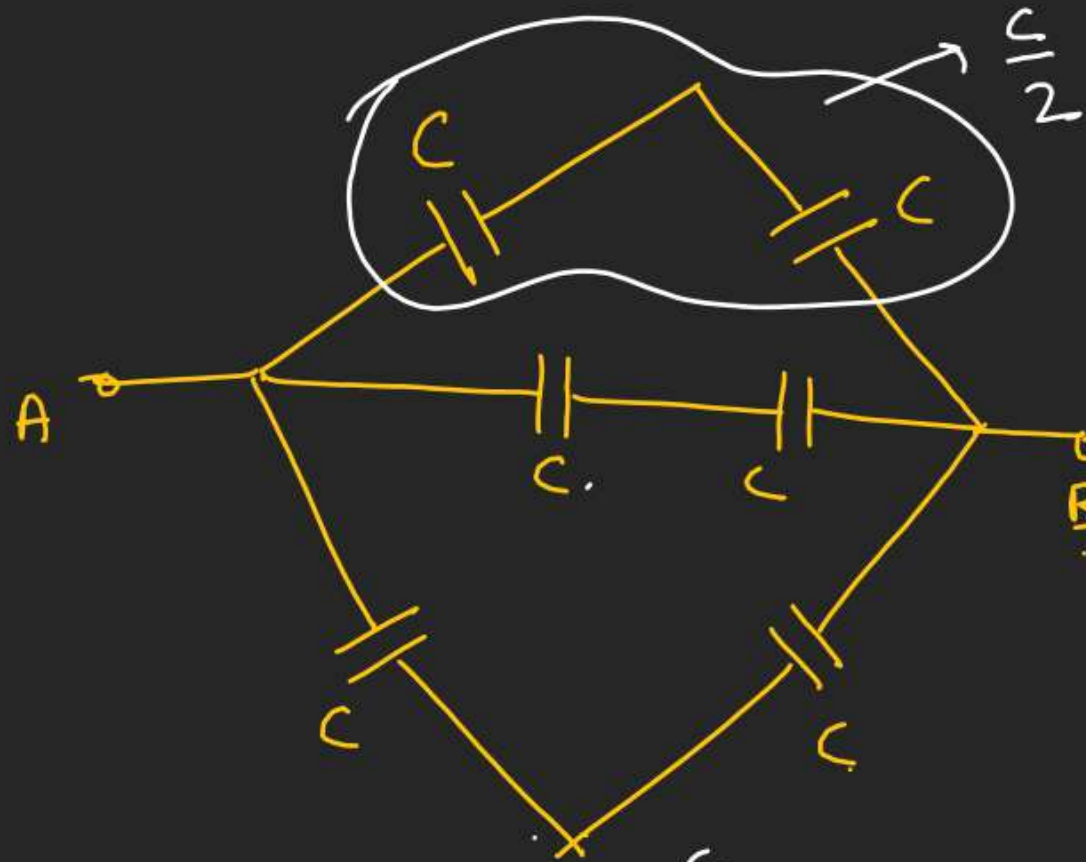
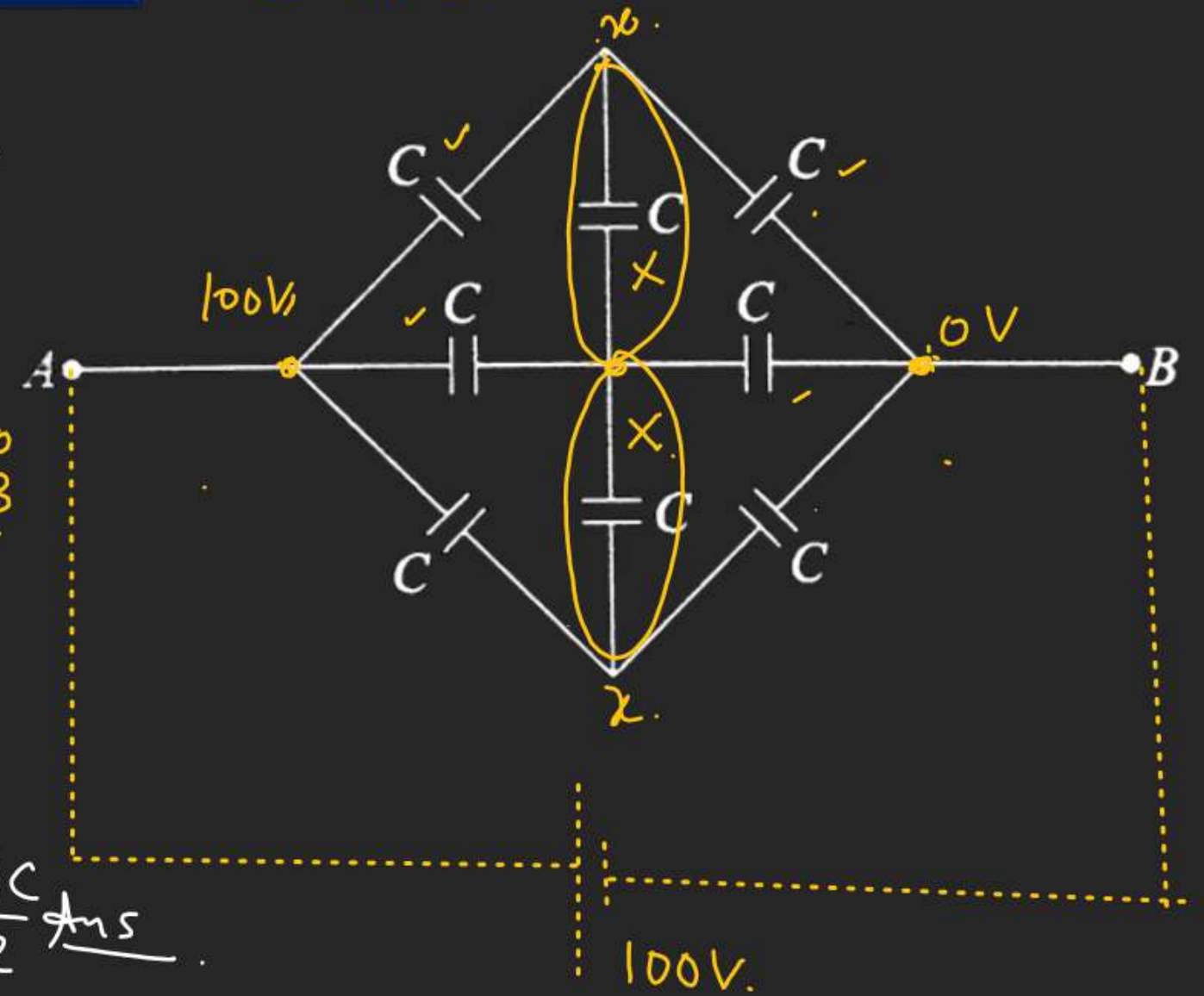
$$(C_{eq})_{A-B} = \frac{3C}{2} \text{ Ans}$$



Equivalent capacitance (Symmetry)

CAPACITOR

$$(C_{eq})_{A-B} = ??$$

H.W

$$C(x-50) + (x-0)C + (x-100)2C = 0$$

$$x-50 + x + 2x-200 = 0$$

$$4x = 250$$

$$x = \frac{250}{4} = \left(\frac{125}{2}\right) \checkmark$$

$$x = 62.5 \text{ Volt}$$


$$q = q_1 + q_2 + q_3$$

$$C_{eq}(100) = \underline{(50)C} + (x-0)C + (100-x)2C$$

$$(C_{eq})_{100} = 250C - xC$$

$$(C_{eq})_{100} = \left(250C - \frac{125}{2} \times C\right) = 125C \left(2 - \frac{1}{2}\right) = \left(125C \times \frac{3}{2}\right)$$
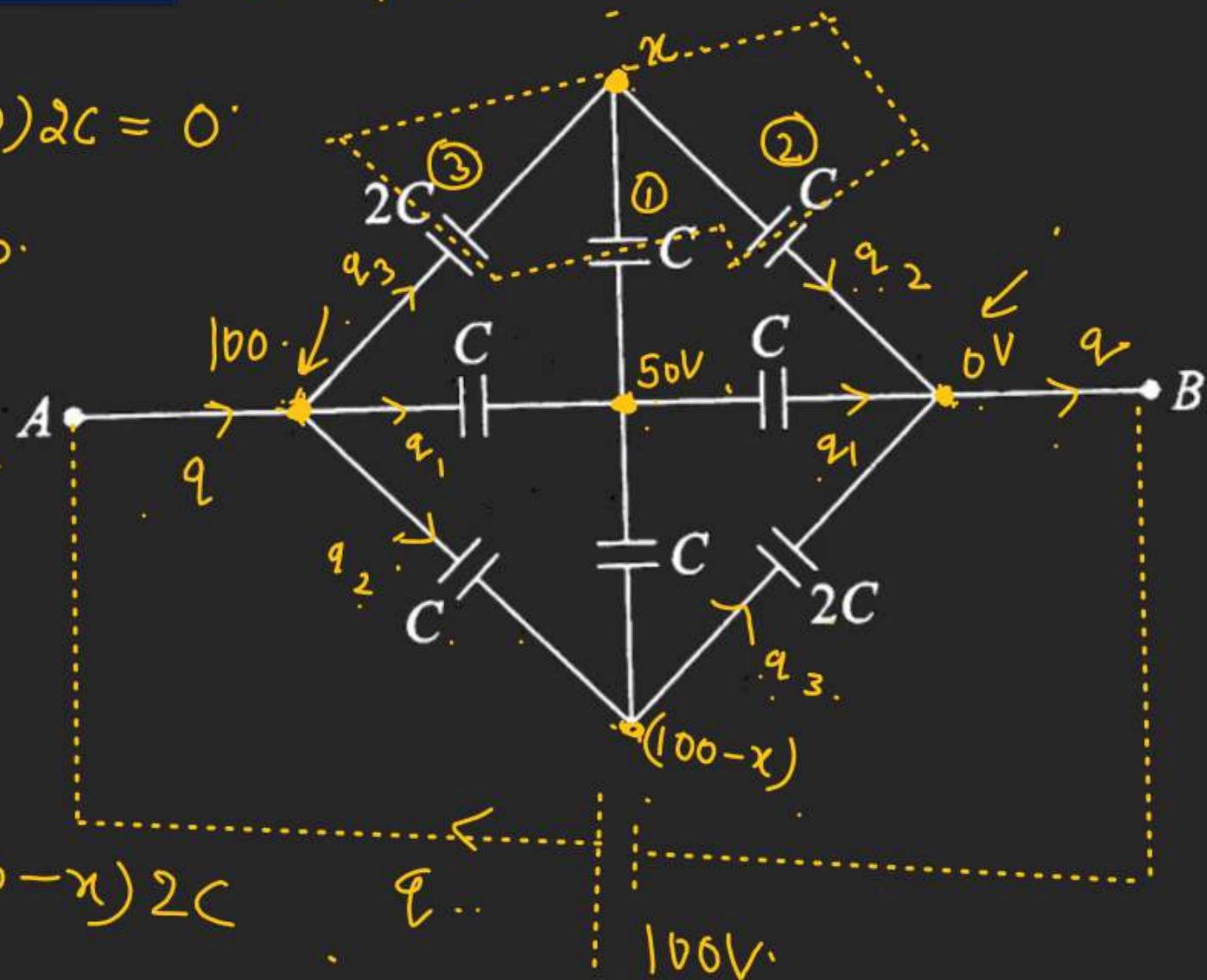
$$C_{eq} = \frac{125C \times 3}{2 \times 100} = \left(\frac{15C}{8}\right) \underline{\text{Ans}}$$



Equivalent capacitance (Symmetry) CAPACITOR $(C_{eq})_{A-B} = ?$

H.W

$$V_A = V_B = V_C = V_D = V_E$$

$$(C_{eq})_{AB} = ? \left(\frac{9C}{4} \right)$$

