

Power in Case of bulb



Bulb

Rated Value
↳ (Power)
↳ (Voltage)

[∵ Bulb Safely work if voltage and power of the bulb is less than or equal to rated value]

⇒ R ⇒ Resistance of the bulb calculated w.r.t Rated Value.

$$P = \frac{V^2}{R}$$

$$\Rightarrow \boxed{R = \frac{V^2}{P}}$$

V → Rated Voltage
 P → Rated power.

#



Power dissipated across the bulb: →

$$R = \left(\frac{V_r^2}{P_r} \right) \quad V_r \& P_r \rightarrow (\text{Rated Value})$$

$$R = \frac{(220)^2}{(100)}$$

$$I = \left(\frac{110}{R} \right)$$


$$P = I^2 R = \frac{(110)^2}{R^2} \times R = \frac{(110)^2}{R} = \frac{(110)^2}{(220)^2} \times 100$$

$$P = 25 \text{ watt} \quad \checkmark$$

Ex.


Series combination of bulb :-

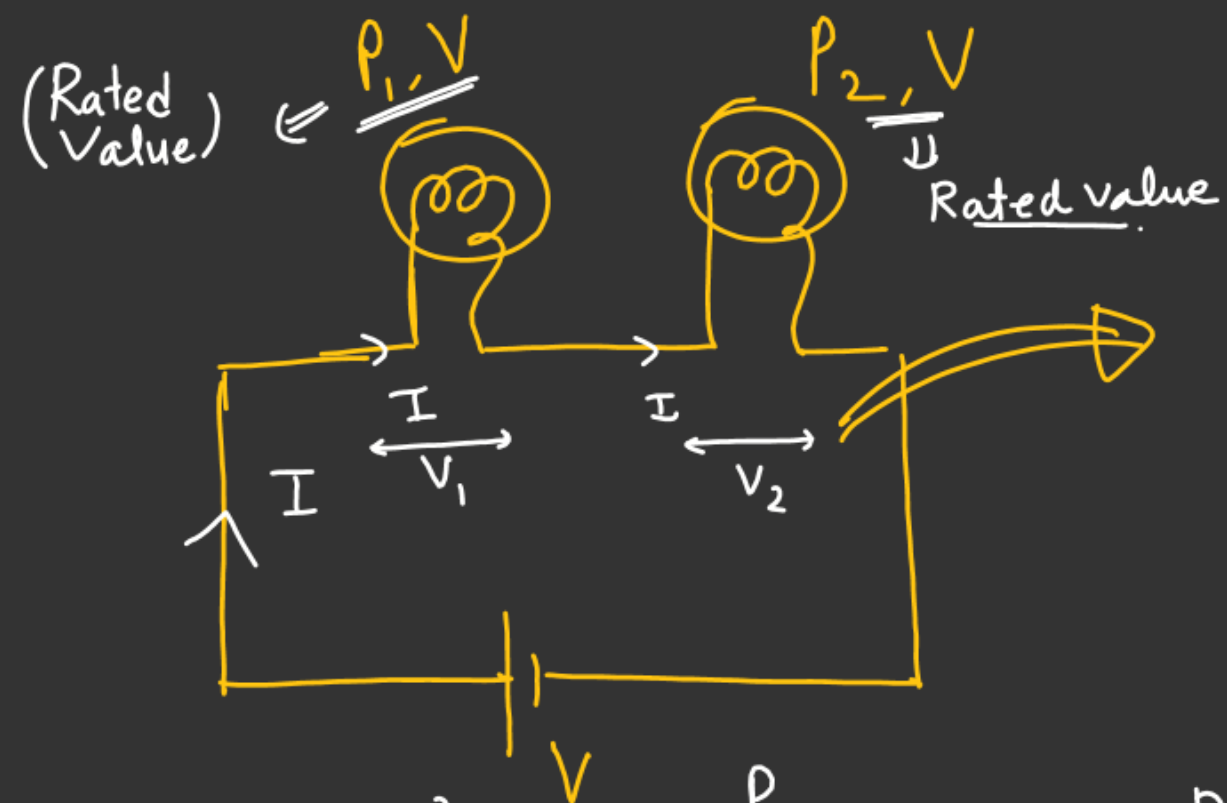Condition :- \rightarrow [Rated voltage and Supply voltage same]



$$R_1 = \left(\frac{V^2}{P_1} \right)$$

$$R_2 = \left(\frac{V^2}{P_2} \right)$$

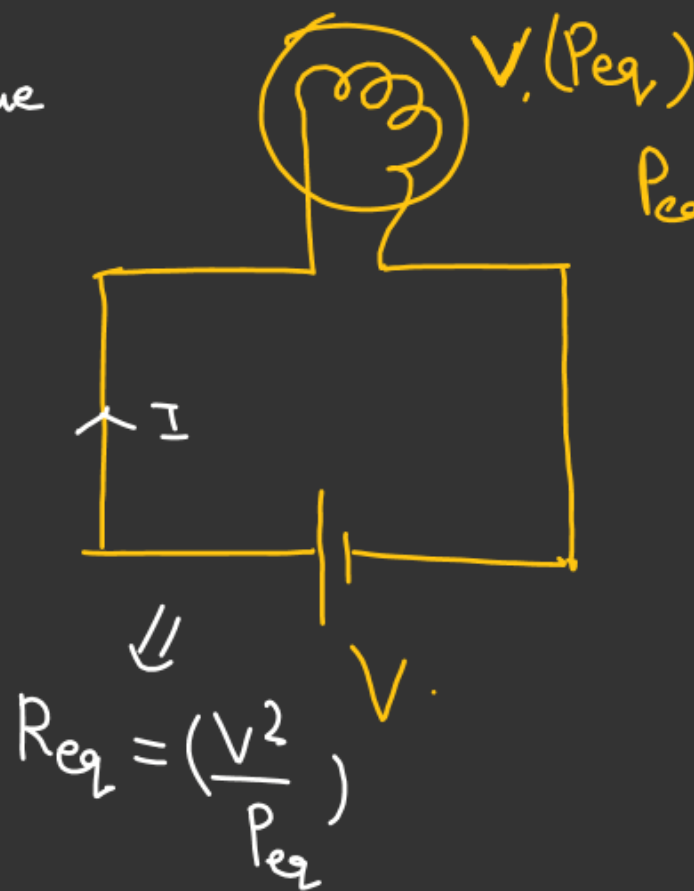

$$R_{eq} = \left(\frac{V^2}{P_{eq}} \right)$$

$$V = V_1 + V_2$$

$$I R_{eq} = I R_1 + I R_2$$

$$\Downarrow$$

$$R_{eq} = R_1 + R_2$$

$$\frac{V^2}{P_{eq}} = \frac{V^2}{P_1} + \frac{V^2}{P_2}$$

$$\boxed{\frac{1}{P_{eq}} = \frac{1}{P_1} + \frac{1}{P_2}}$$

\Rightarrow [Apply when rated voltage is same as source voltage]



(A)

Bulbs in parallel combination

Condition! - [Source voltage and rated voltage same]

$$R_1 = \frac{V^2}{P_1}$$

$$R_2 = \frac{V^2}{P_2}$$

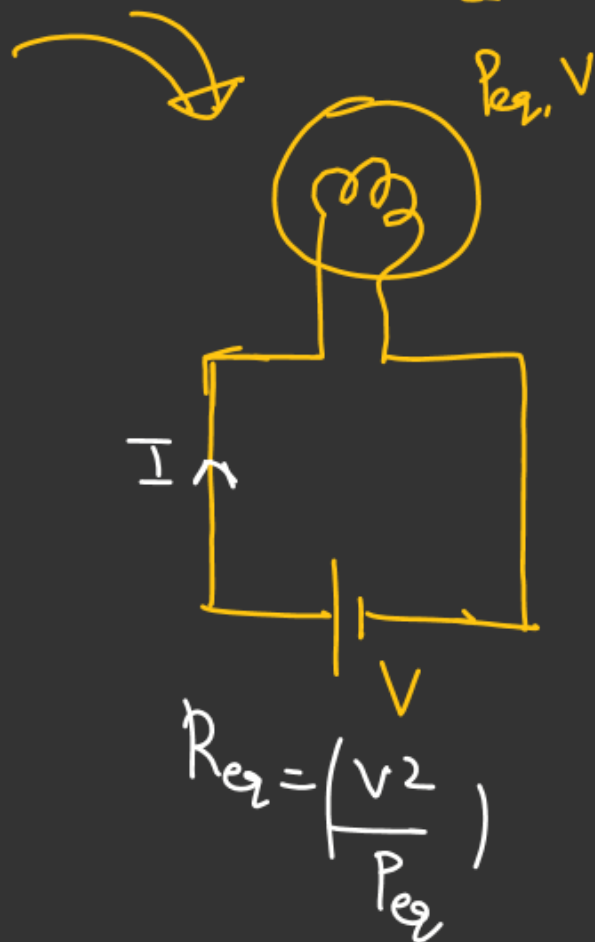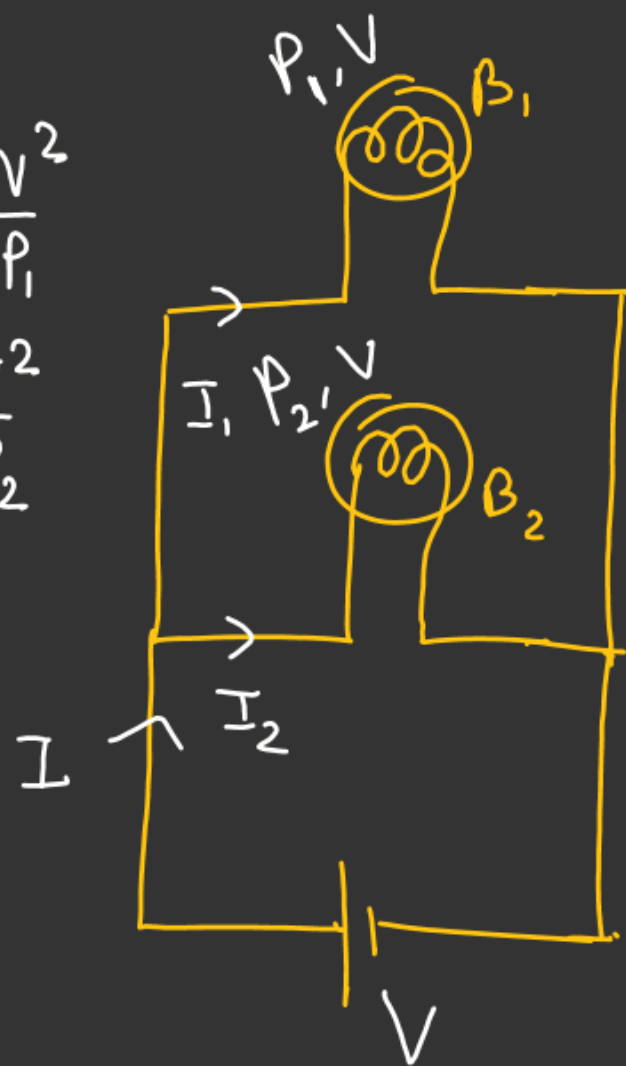

$$I = I_1 + I_2$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{\left(\frac{V^2}{P_{eq}} \right)} = \frac{1}{\left(\frac{V^2}{P_1} \right)} + \frac{1}{\left(\frac{V^2}{P_2} \right)}$$

$$P_{eq} = P_1 + P_2$$

⇒ Apply when rated and supply voltage is same.

#

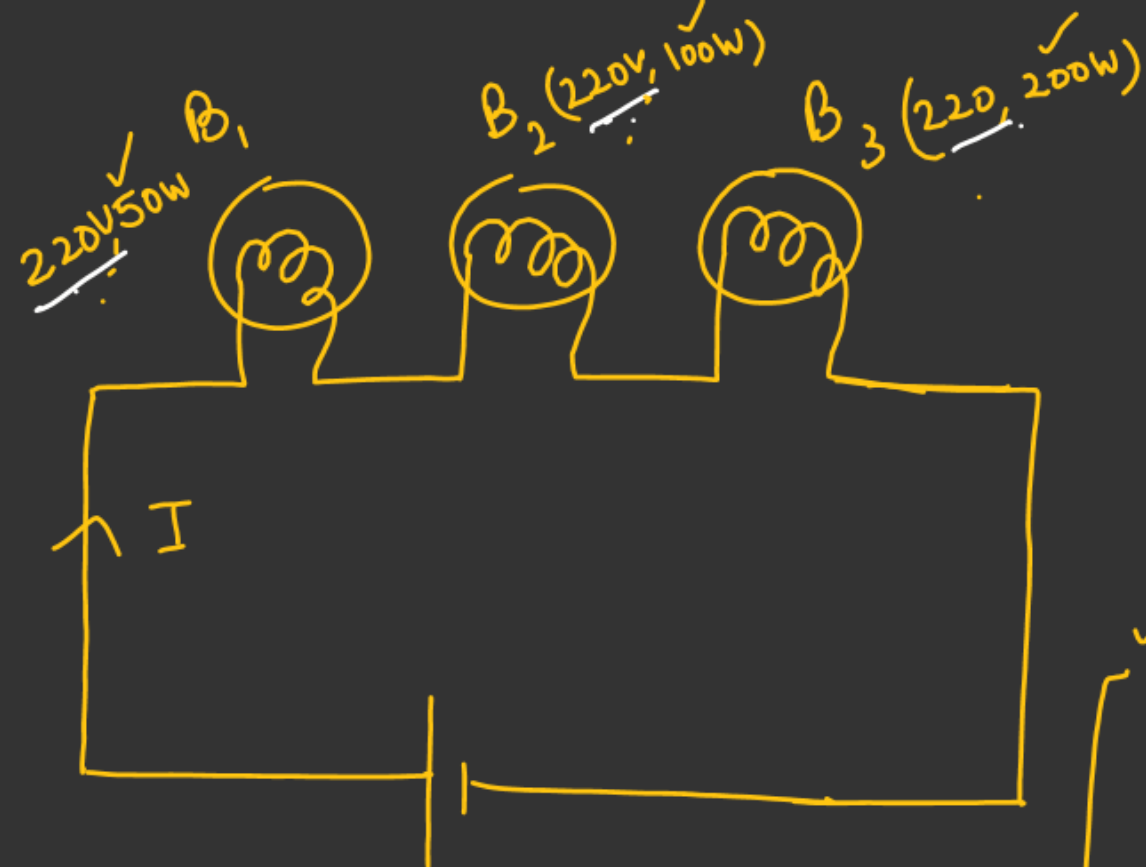

For bulb to work
Successfully

$$P \leq P_{\text{rated}}$$

$$(P_1, P_2 \& P_3) > (P_{eq})$$

(All the bulb work
Successfully work)

- a) Total power dissipated. $(220V) \checkmark$
- b) Which bulb's fuse or operate successfully.

$$\frac{1}{P_{eq}} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3}$$

$$\frac{1}{P_{eq}} = \left(\frac{1}{50} + \frac{1}{100} + \frac{1}{200} \right)$$

$$\frac{1}{P_{eq}} = \frac{4+2+1}{200} = \frac{7}{200}$$

$$P_{eq} = \left(\frac{200}{7} \right) \text{ Watt. } \checkmark$$

$$= \underline{\underline{28.55}} \checkmark$$

$$I = \frac{220}{R_{eq}} = \frac{220}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{(220)^2}{50}$$

$$R_2 = \frac{(220)^2}{100}$$

$$R_3 = \frac{(220)^2}{200}$$

$$(P_1)_{\text{consume}} \checkmark$$

$$= I^2 R_1$$

$$(P_2)_{\text{consume}} \checkmark$$


$$= I^2 R_2$$

$$(P_3)_{\text{consume}} = I^2 R_3$$

CURRENT ELECTRICITY

Q.1 A circuit consists of a battery, a resistor R and two light bulbs A and B as shown: If the filament in lightbulb A burns out, then the following is true for light bulb B :

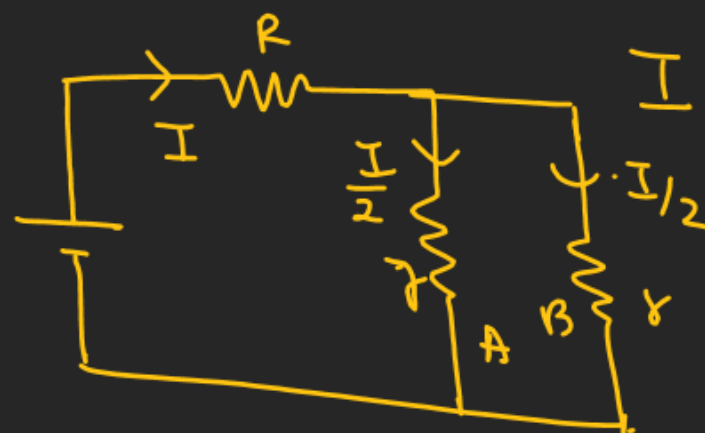- (A) it is turned off
- (B) its brightness does not change
- (C) it gets dimmer
- ☒ (D) it gets brighter





When bulb A operate

$$(R_{eq})_{ckt} = (R + \frac{r}{2})$$

$$I = \left(\frac{V}{R + \frac{r}{2}} \right) = \left(\frac{2V}{2R + r} \right)$$

$$P_B = (I/2)^2 \cdot r$$

$$P_B = \left(\frac{I^2 r}{4} \right)$$

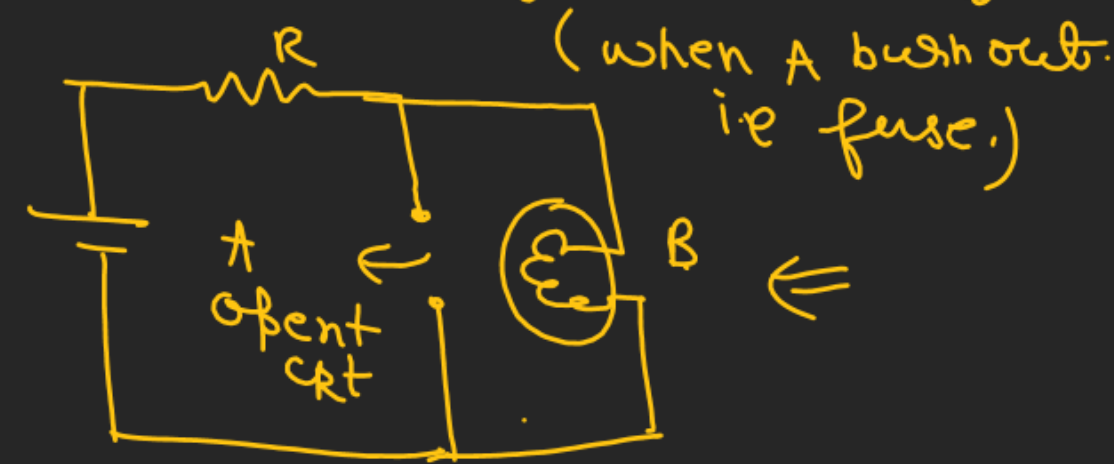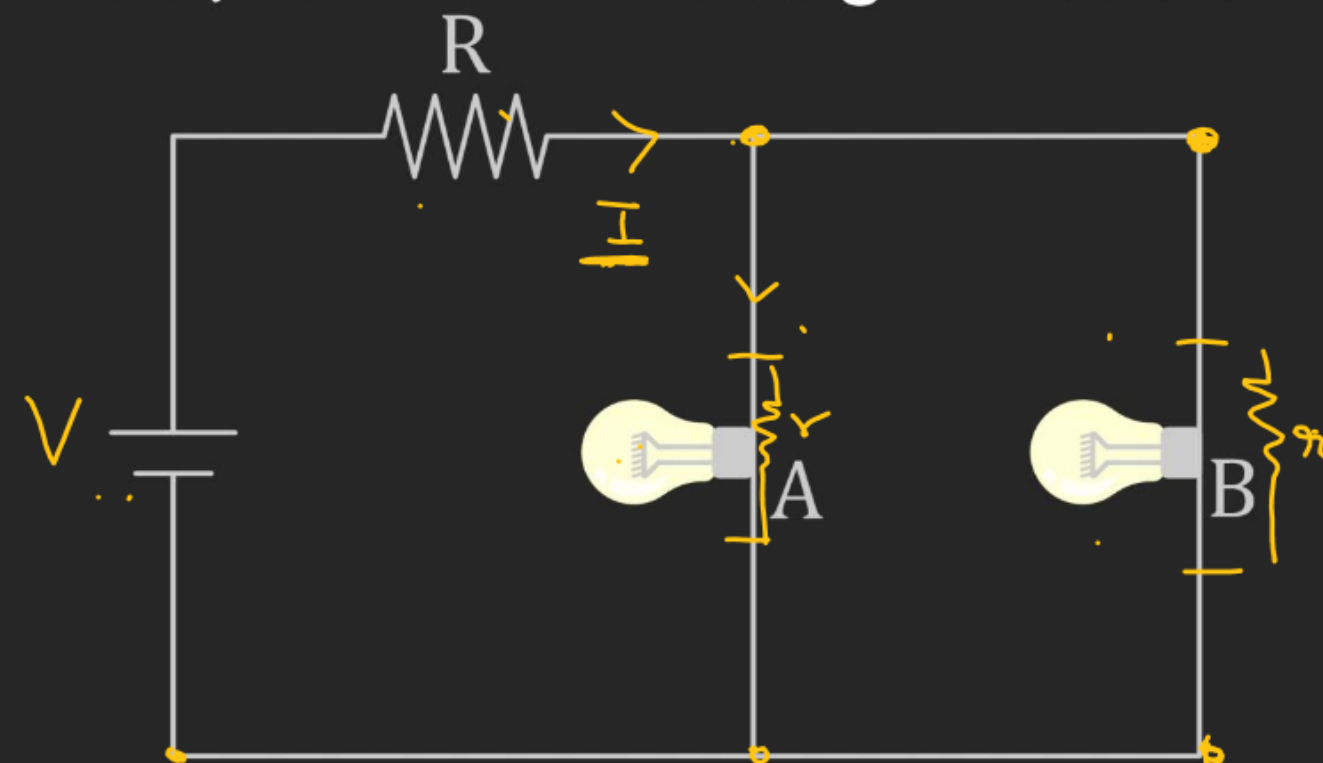

$$P_B = I^2 \left(\frac{r}{4} \right)$$


$$P_B = \left(\frac{2V}{2R+r} \right)^2 \times \left(\frac{r}{4} \right)$$

$$\frac{P_B}{P'_B} = \frac{\cancel{4V^2} \times \cancel{r}}{(2R+r)^2 \cancel{4}} \times \frac{(R+r)^2}{\cancel{r^2}}$$

$$\frac{P_B}{P'_B} = \left(\frac{R+r}{2R+r} \right)^2 \Rightarrow < 1$$

$$\boxed{P_B < P'_B}$$

When bulb A fuse:

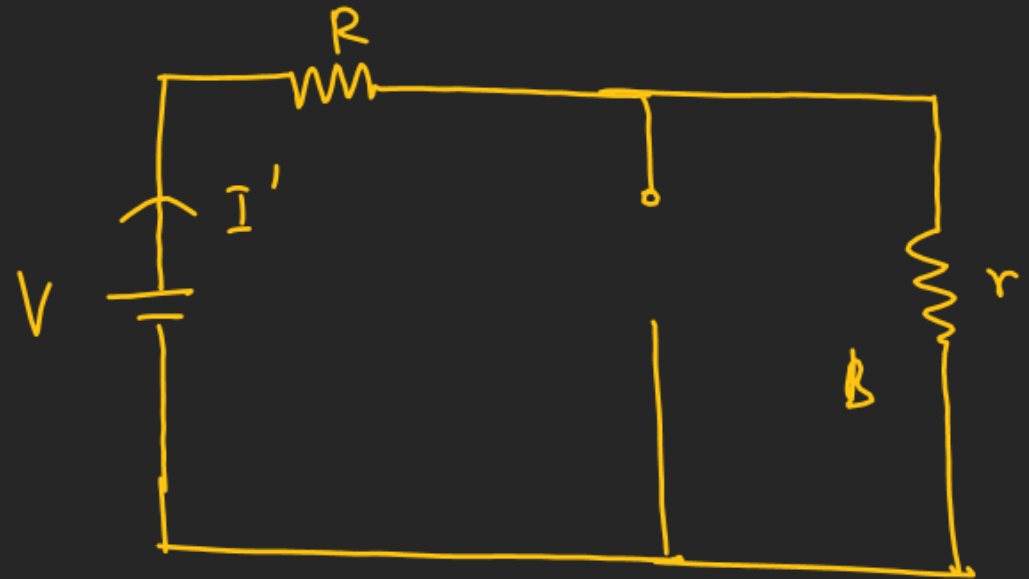

$$I' = \frac{V}{R_{eq}} = \left(\frac{V}{R+r} \right)$$

$$P'_B = (I')^2 r = \left(\frac{V}{R+r} \right)^2 r$$

CURRENT ELECTRICITY

Q.2 Two lamps, each with a resistance of 50Ω , are connected in series. The lamps will fuse if a power of more than 200 W is dissipated in it. What is the maximum voltage that can be applied to the circuit?

(A) 100 V

(B) 140 V

(C) 200 V ✓

(D) None


Rated voltage of the bulb. $200\text{ W} = P$

$$\frac{V^2}{R} = P$$

$$V^2 = (P \times R)$$

$$V^2 = (200 \times 50)$$

$$V = \sqrt{10000} = 100\text{ Volt}$$

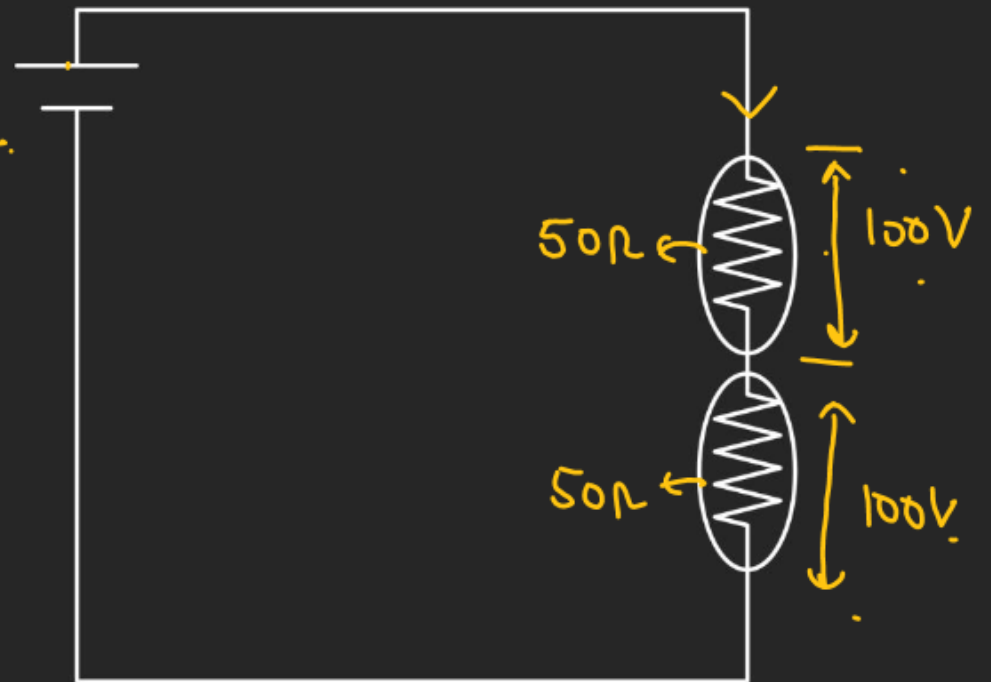

CURRENT ELECTRICITY

Q.3 In the circuit diagram, all the bulbs are identical. Which bulb will be the brightest?

(A) A

(B) B

(C) C ✓

(D) D

$$P_A: P_B: P_C: P_D = ??$$

$$I = \frac{3 \times 10}{5r} = \left(\frac{6}{r}\right) \text{ Amp}$$

$$I_1 + I_2 = I$$


$$I_1^2 r = I_2^2 r$$

$$I_2 = (2I_1)$$

$$3I_1 = I$$

$$I_1 = (I/3)$$

$$I_2 = 2I/3$$

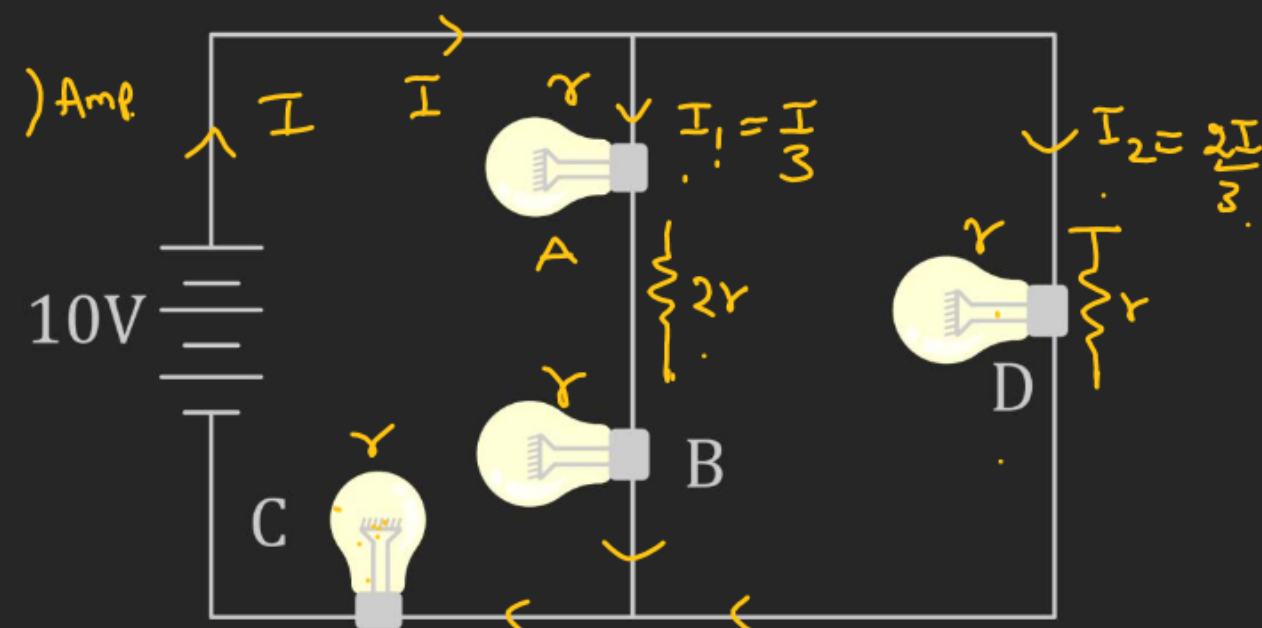

$$\begin{cases} P_C = I^2 r \\ P_B = P_A = I_1^2 r \\ P_D = I_2^2 r \end{cases}$$

$$2r/3 + r$$

H.W.

CURRENT ELECTRICITY

Q.4 A torch bulb rated as 4.5 W, 1.5 V is connected as shown in fig. the e.m.f. of the cell, needed to make the bulb glow at full intensity is :

(A) 4.5 V

(B) 1.5 V

Ans. (C) 2.67 V

(D) 13.5 V

