
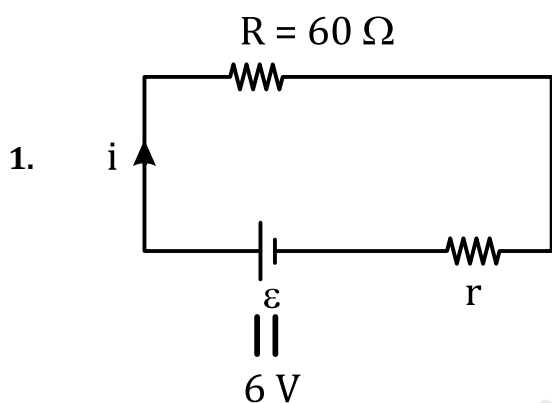


DPP - 4

Link to View Video Solution:  [Click Here](#)





$$P = \frac{E^2}{R + r}$$

$$i = \frac{E}{R + r}$$

$$\Rightarrow 0.4 = \frac{6^2}{60 + r}$$

$$r = 30 \Omega$$

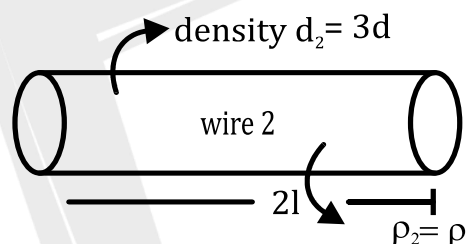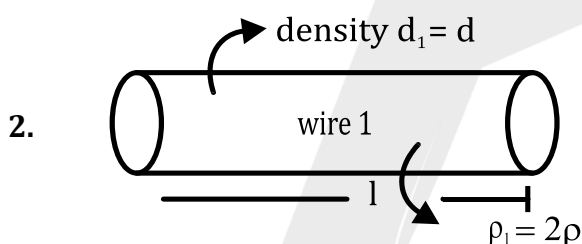

First resistance of wire 1

mass of wire 1 = mass of wire 2

$$R_1 = \frac{2\rho(l)}{A_1}$$


$$d \cdot A_1 \times l = 3d \cdot A_2 \times 2l$$


$$A_1 = 6A_2$$

$$P_1 = \frac{V^2}{R_1} = \frac{V^2}{\frac{2\rho l}{A_1}} = \frac{V^2 A_1}{2\rho l} = 10 \text{ W}$$

$$P_2 = \frac{V^2}{R_2} = \frac{V^2}{\frac{\rho(2l)}{A_2}} = \frac{V^2 A_2}{2\rho l} = \frac{V^2 A_1}{6 \times 2\rho l} = \frac{10}{6}$$

$$P_2 = \frac{5}{3} \text{ watt.}$$

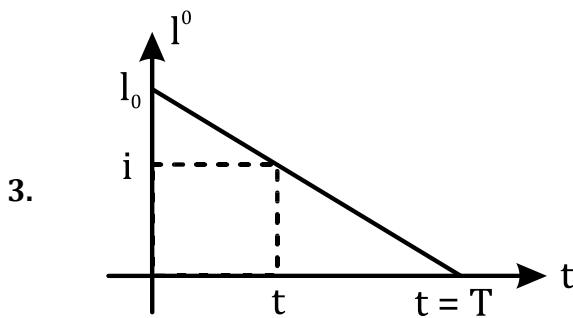Link to View Video Solution:  [Click Here](#)



$$q = \frac{1}{2} \times i_0 T = \frac{i_0 T}{2}$$

$$i_0 = \frac{22}{T}$$

$$L = I_0 - \frac{L_0}{T} t$$

$$L = \frac{2q}{T} \left(1 - \frac{t}{T} \right)$$

heat produced from 0 to T is given as

$$H = \int_0^T L^2 R dt \Rightarrow \text{After Solving}$$

$$H = \frac{4}{3} \frac{q^2 R}{T}$$

4. marked rating 220 V, 100 W

$$i = \frac{V}{R} = \frac{220}{R} = \frac{220}{\frac{220 \times 220}{100}}$$

$$R = \frac{V^2}{P} = \frac{220 \times 220}{100}$$

$$i = \frac{100}{220} = \frac{10}{22} = \frac{5}{11} \text{ Amp}$$

5. $\left. \begin{array}{l} 500 \text{ W} \\ V = 200 \text{ volt} \end{array} \right\} \Rightarrow \text{rating}$

$$R = \frac{V^2}{P} = \frac{200 \times 200}{500} = 80 \Omega$$


$$H = \frac{V_{\text{real}}^2}{R} t = \frac{160 \times 160}{80} \times 20 \times 60$$

$$= 2 \times 160 \times 1200$$


$$= 24000 \times 16$$

$$H = 384 \text{ KJ.}$$

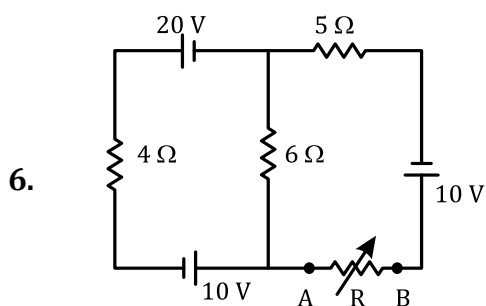Link to View Video Solution: [Click Here](#)



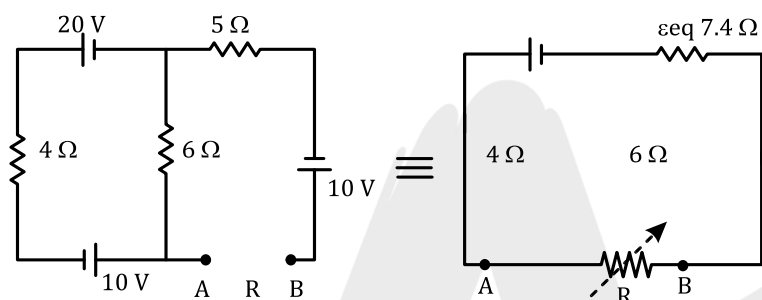⇒ first we find internal resistance Across A & B




$$R = 7.4 \Omega$$

7. $I = 1 \text{ Amp}$

$$V = 2.0 \text{ Volt}$$

$$E = 2.6 \text{ V}$$

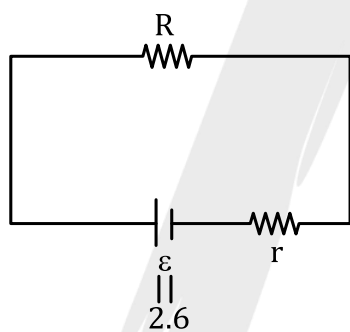

$$i = \frac{2 \cdot 6}{R + r}$$

$$1 = \frac{2 \cdot 6}{R + r} \Rightarrow r + R = 2 \cdot 6$$

$$\varepsilon - ir = 2$$


$$2 \cdot 6 - r = 2$$

$$r = 0.6 \Omega$$



$$R = 2r$$

$$P_{\text{battery}} = I^2 r = 1^2 \times 0.6 = 0.6 \text{ W}$$

$$\& P_R = I^2 \times R = 1 \times 2 = 2 \text{ W}$$

Link to View Video Solution:  [Click Here](#)

8.

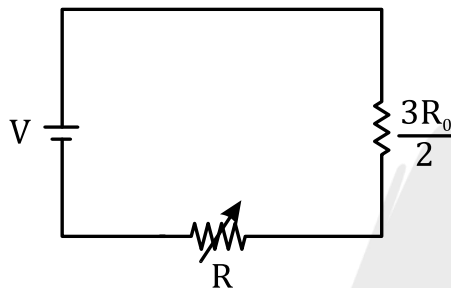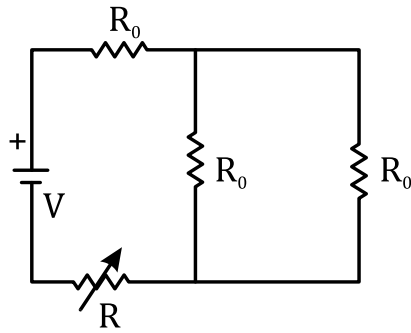

$R = \frac{3R_0}{2}$ For maximum Power dissipation

9. heat generated & transferred to surrounding is always proportional to the exposed area.

$$Q \propto A$$

consider l & r are filament length & radius

$$A = 2\pi rl$$

$$\text{So } P = \frac{V^2}{R} = k \cdot 2\pi rl$$

At steady state

$$R = \frac{\rho l}{A} = \frac{\rho l}{\pi r^2} = \frac{\rho l}{\frac{\pi D^2}{4}}$$

$$R = \frac{4\rho l}{\pi D^2}$$

$$\Rightarrow \frac{V^2}{R} = P \Rightarrow V^2 = \frac{4k\rho l^2}{D}$$

$$\Rightarrow \ln(V)^2 = \ln \frac{4k\rho l^2}{D}$$

$$\Rightarrow \text{diff both side} \Rightarrow \frac{2dD}{V} = -\frac{dD}{D} \quad n\% = -2\%$$