
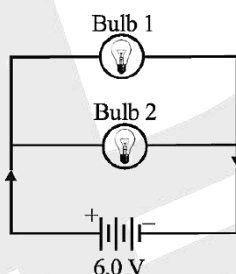


DPP-6




- Time taken by a 836 W heater to heat one litre of water from  $10^{\circ}\text{C}$  to  $40^{\circ}\text{C}$  is:  
(A) 150 s (B) 100 s (C) 50 s (D) 200 s
- A heater coil is cut into two equal parts and only one part is now used in the heater. The heat generated will now be:  
(A) Four times (B) Doubled (C) Halved (D) One fourth
- Two electric bulbs marked 25 W – 220 V and 100 W – 220 V are connected in series to a 440 V supply. Which of the bulbs will fuse?  
(A) Neither (B) Both (C) 100 W (D) 25 W
- A 6.0 volt battery is connected to two light bulbs as shown in figure. Light bulb-1 has resistance 3 ohm while light bulb-2 has resistance 6 ohm. Battery has negligible internal resistance. Which bulb will glow brighter?

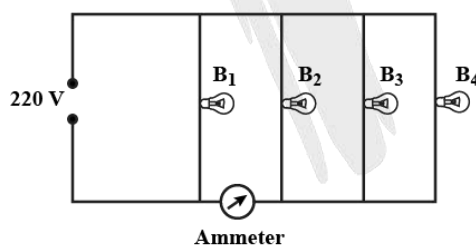

- (A) Bulb-1 will glow more first and then its brightness will become less than bulb-2  
(B) Bulb-1  
(C) Bulb-2  
(D) Both glow equally
- Four bulbs  $B_1$ ,  $B_2$ ,  $B_3$  and  $B_4$  of 100 W each are connected to 220 V main as shown in the figure. The reading in an ideal ammeter will be:



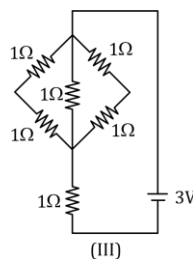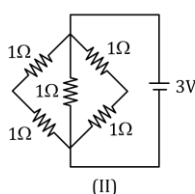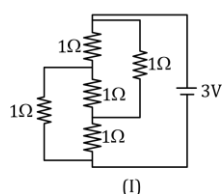- (A) 0.45 A (B) 0.90 A (C) 1.35 A (D) 1.80 A
- The figure shows three circuits I, II, and III which are connected to a 3 V battery. If the powers dissipated by the configurations I, II, and III are  $P_1$ ,  $P_2$  and  $P_3$  respectively, then




- (A)  $P_1 > P_2 > P_3$  (B)  $P_1 > P_3 > P_2$  (C)  $P_2 > P_1 > P_3$  (D)  $P_3 > P_2 > P_1$


(Physics)

CURRENT ELECTRICITY

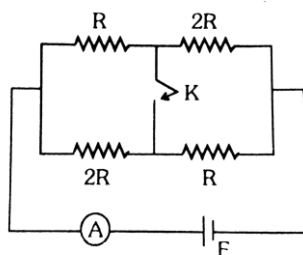
7. The ratio of currents as measured by ammeter in two cases (when the key is open and when the key is closed) is



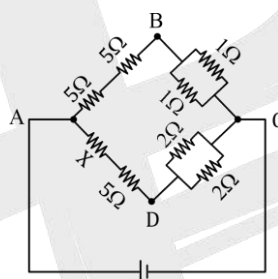
- (A)  $\frac{9}{8}$  (B)  $\frac{10}{11}$  (C)  $\frac{8}{9}$  (D) None of these
8. In the given bridge the value of X for which the potential difference between the points B and D will be zero, is



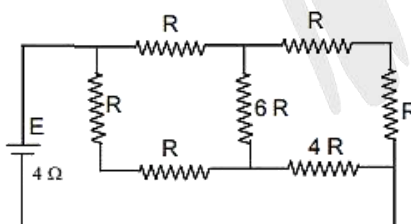- (A)  $5\Omega$  (B)  $10\Omega$  (C)  $15\Omega$  (D)  $20\Omega$
9. A battery of internal resistance  $4\Omega$  is connected to a network of resistances as shown. In order that the maximum power can be delivered to the network, the value of R in ohm should be



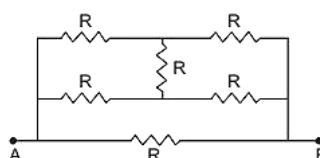- (A)  $\frac{4}{9}$  (B) 2 (C)  $\frac{8}{3}$  (D) 18
10. In the network shown below, the equivalent resistance between A and B is



(Physics)

CURRENT ELECTRICITY


(A)  $\frac{R}{2}$

(B)  $R$

(C)  $2R$

(D)  $4R$

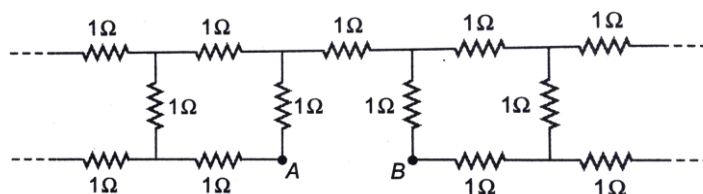11. Each resistor shown in figure is an infinite network of resistance  $1\Omega$ . The effective resistance between points A and B is




(A) less than  $1\Omega$

(B)  $1\Omega$

(C) more than  $1\Omega$  but less than  $3\Omega$

(D)  $3\Omega$

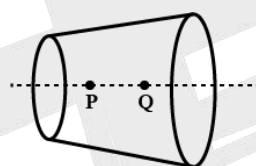12. A wire has a non-uniform cross-section as shown in figure. A steady current flows through it. The drift speed of electrons at points P and Q is  $v_P$  and  $v_Q$ .



(A)  $v_P = v_Q$

(B)  $v_P < v_Q$

(C)  $v_P > v_Q$

(D) Data Insufficient

---

ANSWER KEY

1. (A) 2. (B) 3. (D) 4. (B) 5. (C) 6. (C) 7. (C)  
8. (C) 9. (B) 10. (A) 11. (C) 12. (C)

