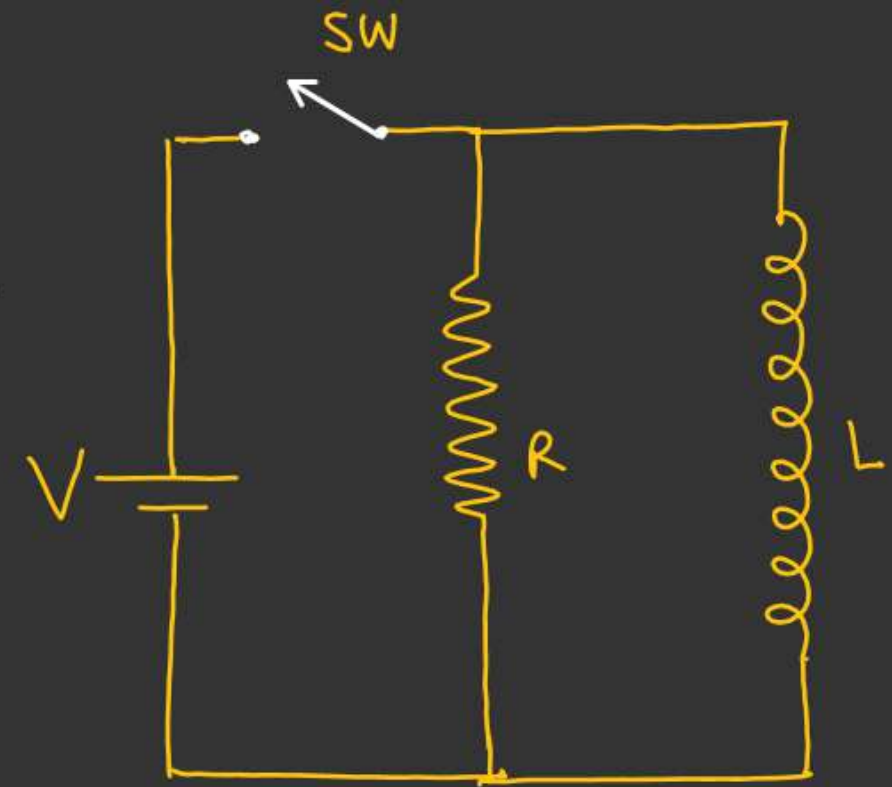




Case when L & R parallel to each other

At $t=0$, Switch is closed.

- Find
- Current as a function of time in the inductor.
 - Find time when current in the inductor & resistor become equal



$$I = i_1 + i_2$$

$$I = \text{Constant}$$

$$0 = \frac{dI}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = -\frac{di_1}{dt} \quad \text{--- (1)}$$

KVL in loop cdefc

$$-L \frac{di_2}{dt} + i_1 R = 0$$

$$i_1 R = L \frac{di_2}{dt}$$

$$i_1 R = L \left(-\frac{di_1}{dt} \right)$$


$$\int_I^i \frac{di_1}{i_1} = -\frac{R}{L} \int_0^t dt$$

$$\ln\left(\frac{i_1}{I}\right) = -\frac{R}{L} t$$


$$i_1 = I e^{-\frac{R}{L} t}$$

$$i_1 = \frac{V}{R} e^{-\frac{R}{L} t}$$

$$At \ t=0$$

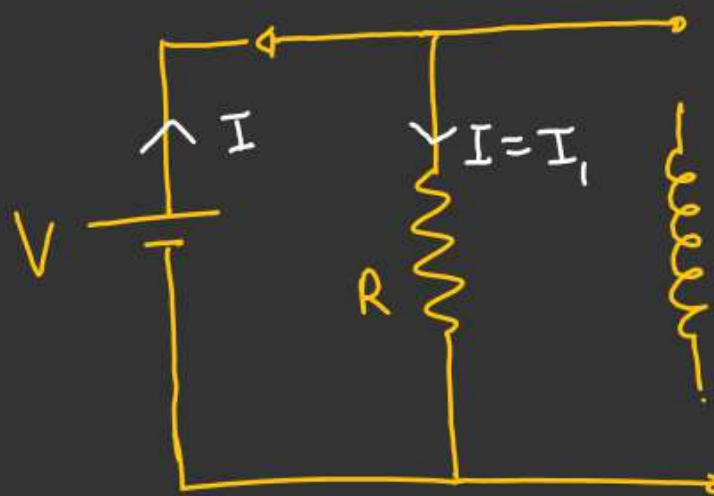

$$I_1 \text{ at } t=0 = (V/R)$$

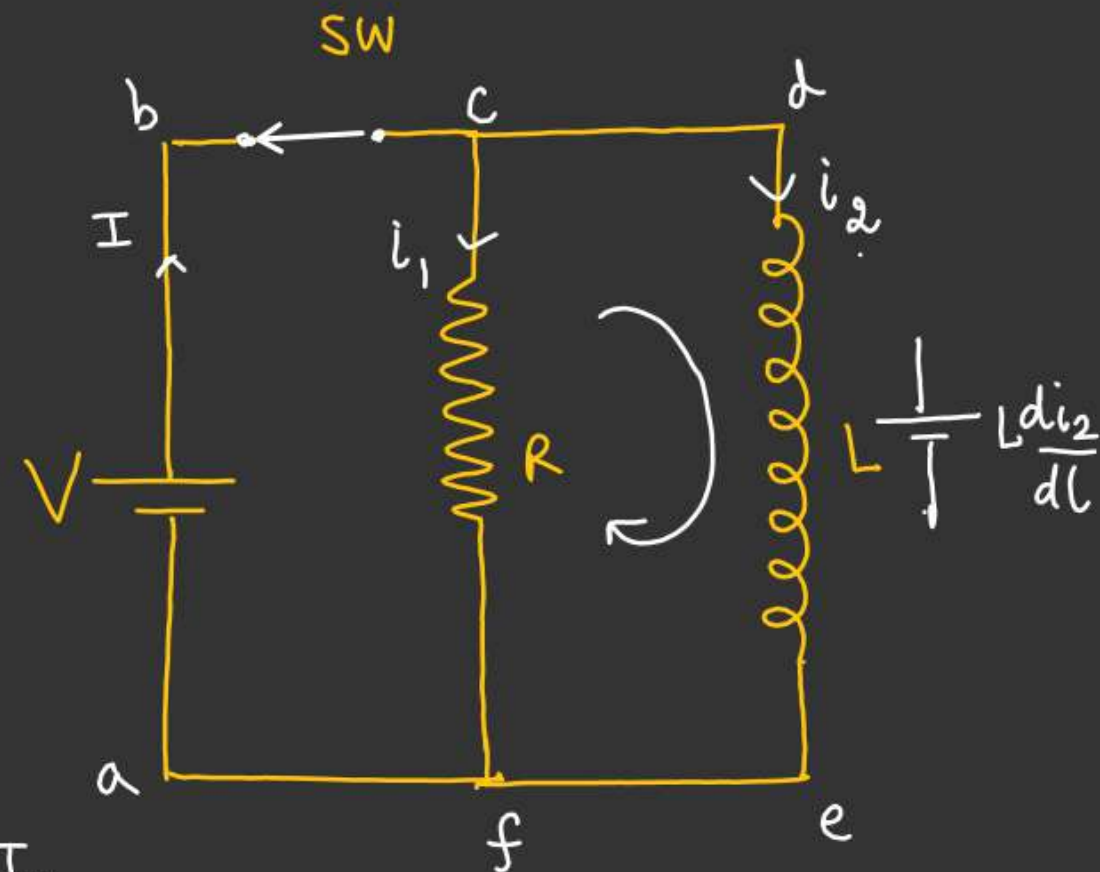

$$i_2 = I - i_1$$

$$i_2 = I - I e^{-\frac{R}{L} t}$$

$$i_2 = I (1 - e^{-\frac{R}{L} t})$$

$$i_2 = \frac{V}{R} (1 - e^{-\frac{R}{L} t})$$

Time when current in the inductor and resistor equal.

$$L_1 = L_2$$

$$\frac{V}{R} e^{-\frac{R}{L}t} = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$2 e^{-\frac{R}{L}t} = 1$$

$$e^{-\frac{R}{L}t} = \frac{1}{2}$$


$$-\frac{R}{L}t = \ln\left(\frac{1}{2}\right)$$

$$\neq \frac{R}{L}t = \neq \ln 2$$

$$t = \ln 2 \left(\frac{L}{R} \right)$$

$$t = (0.693) \frac{L}{R}$$

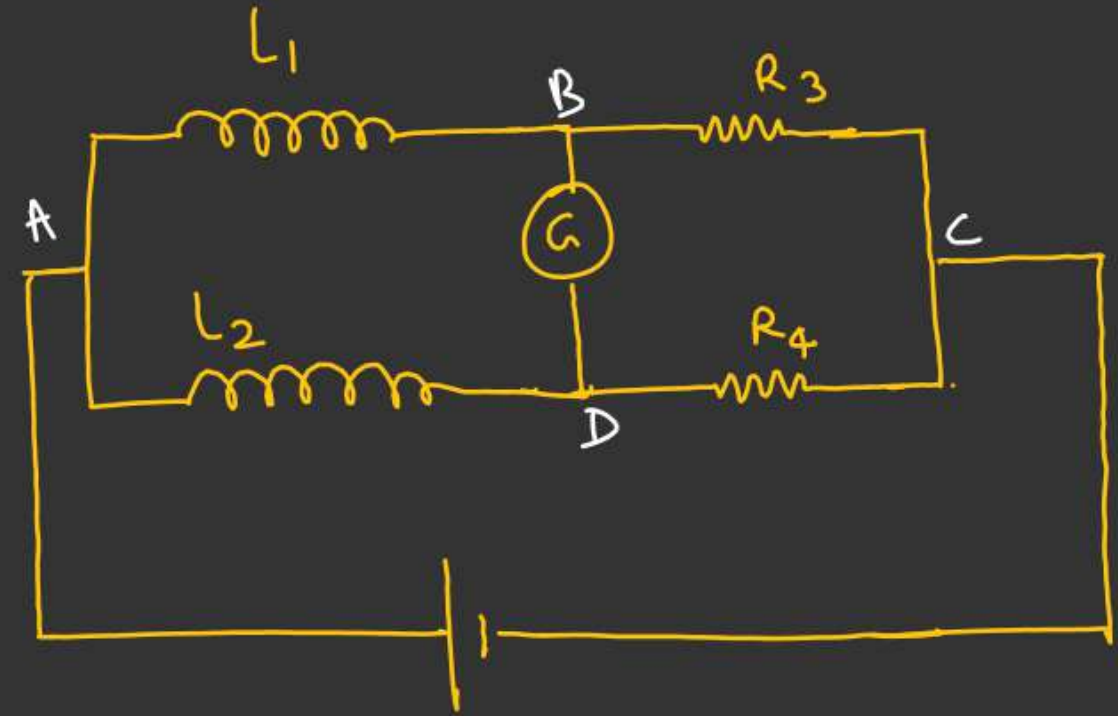Q. Q. L_1 and L_2 have resistance R_1 & R_2 respectively.
Find condition for Null deflection.



For Null deflection

$$V_B = V_D$$

$$V_{AB} = V_{AD}$$

$$L_1 \left(\frac{di_1}{dt} \right) + i_1 R_1 = L_2 \frac{di_2}{dt} + i_2 R_2$$

$$V_{BC} = V_{DC}$$

$$i_1 R_3 = i_2 R_4$$

$$R_3 \frac{di_1}{dt} = R_4 \left(\frac{di_2}{dt} \right)$$

$$L_1 \frac{R_4}{R_3} \left(\frac{di_2}{dt} \right) - L_2 \frac{di_2}{dt} = \left[i_2 R_2 - \left(\frac{L_2 R_4}{R_3} \right) \frac{di_1}{dt} \right] = \frac{R_4}{R_3} \left(\frac{di_2}{dt} \right)$$

$$\left(\frac{R_4 L_1}{R_3} - L_2 \right) \left(\frac{di_2}{dt} \right) = \left(R_2 - \frac{R_4 R_1}{R_3} \right) i_2$$

$$i_1 = \left(i_2 \frac{R_4}{R_3} \right)$$

$$At \rightarrow \infty$$


$$\rightarrow \frac{di_2}{dt} = 0, \quad i_2 = \text{Constant.}$$

$$i_2 = \frac{V}{R_2 + R_4}$$

$$\Rightarrow R_2 - \frac{R_4 R_1}{R_3} = 0$$

$$\Rightarrow \left(\frac{R_2}{R_1} = \frac{R_4}{R_3} \right) \quad \text{--- (2)}$$

Condition for Null deflection.

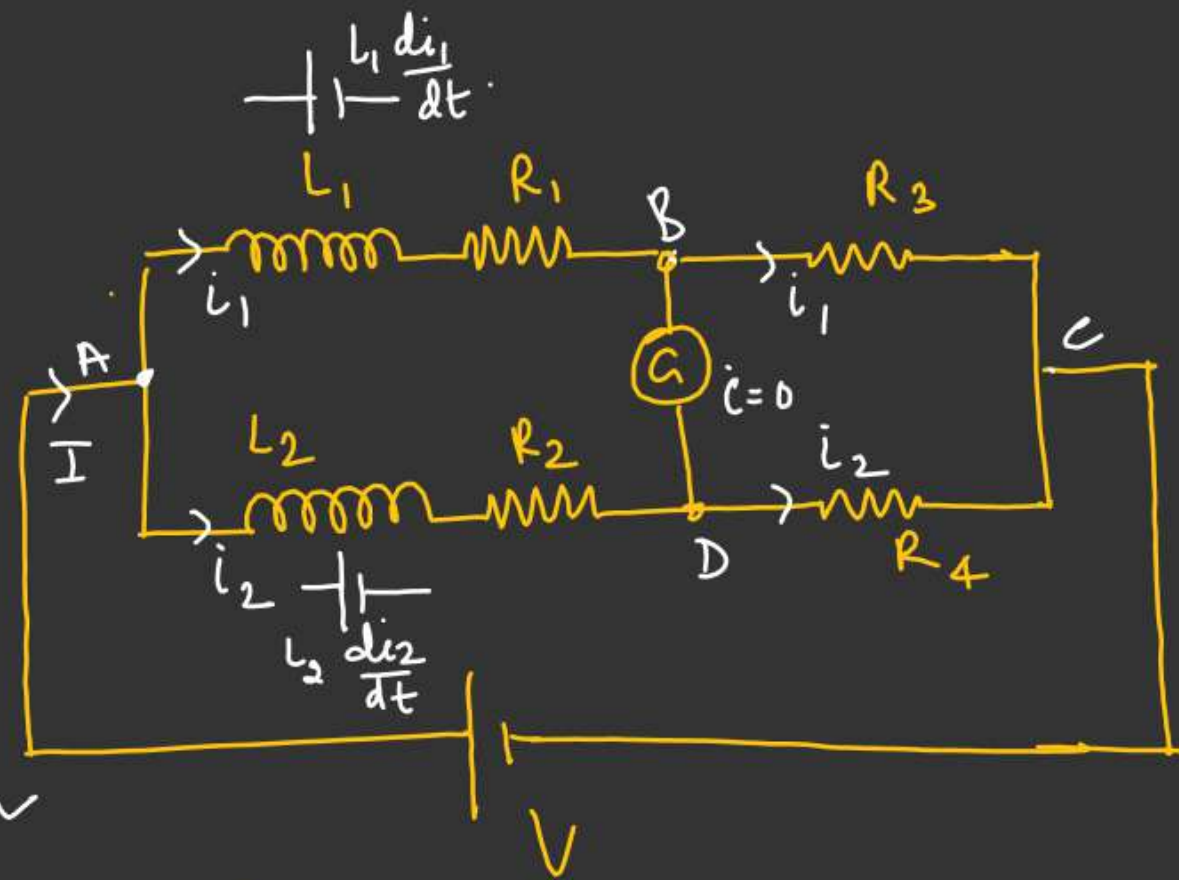

$$At \rightarrow 0, \quad i_2 = 0, \quad \frac{di_2}{dt} \neq 0$$

$$\frac{R_4 L_1}{R_3} - L_2 = 0$$

$$\frac{L_2}{L_1} = \frac{R_4}{R_3} \quad \text{--- (1)}$$

$$\frac{L_2}{L_1} = \frac{R_2}{R_1} = \frac{R_4}{R_3}$$


$$\frac{L_1}{L_2} = \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

SW is closed for a very long time.

At $t=0$, Switch is shifted from position 1 to 2.


Find Current as a function 2.

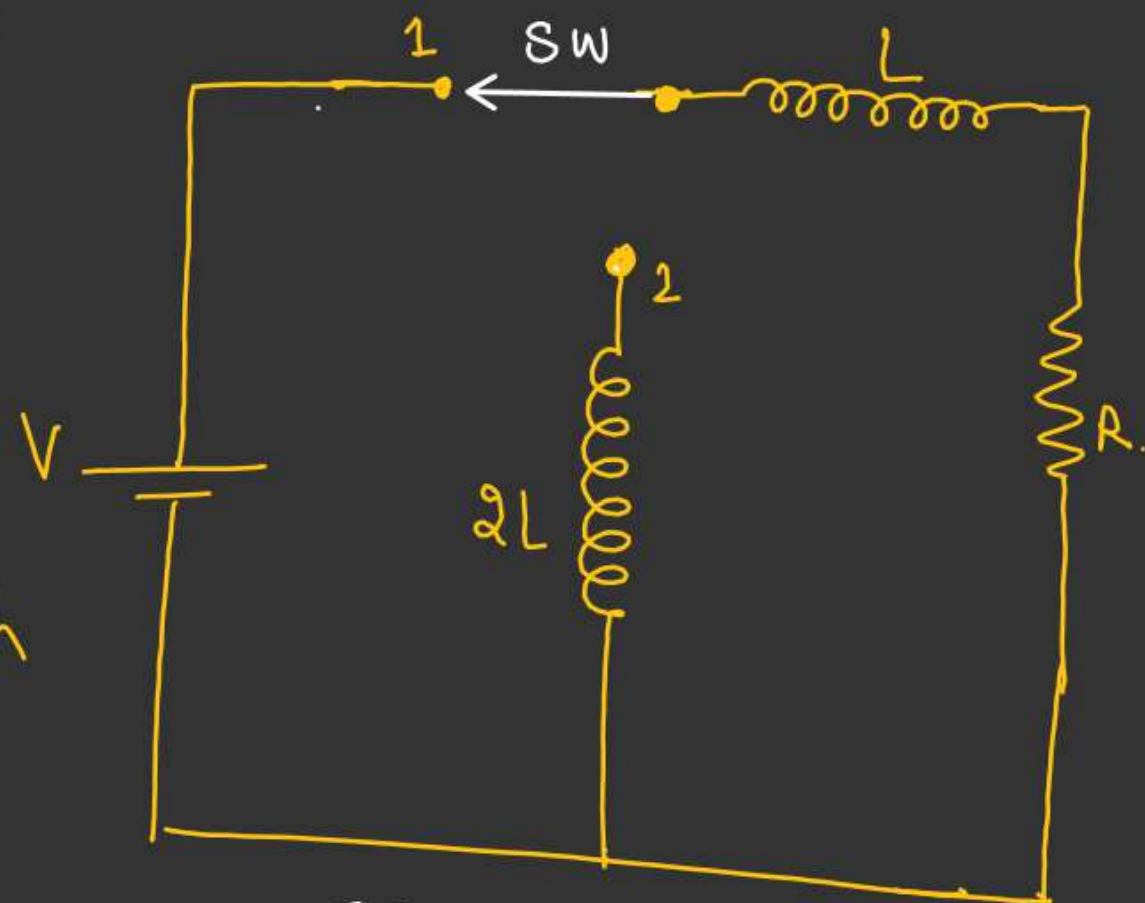Note:- When SW is shifted from position 1 to 2, Current in the ckt changes at $t=0$. flux just before shifting of switch will be same as just after shifting.



Steady State Current

$$I_0 = \left(\frac{V}{R} \right)$$

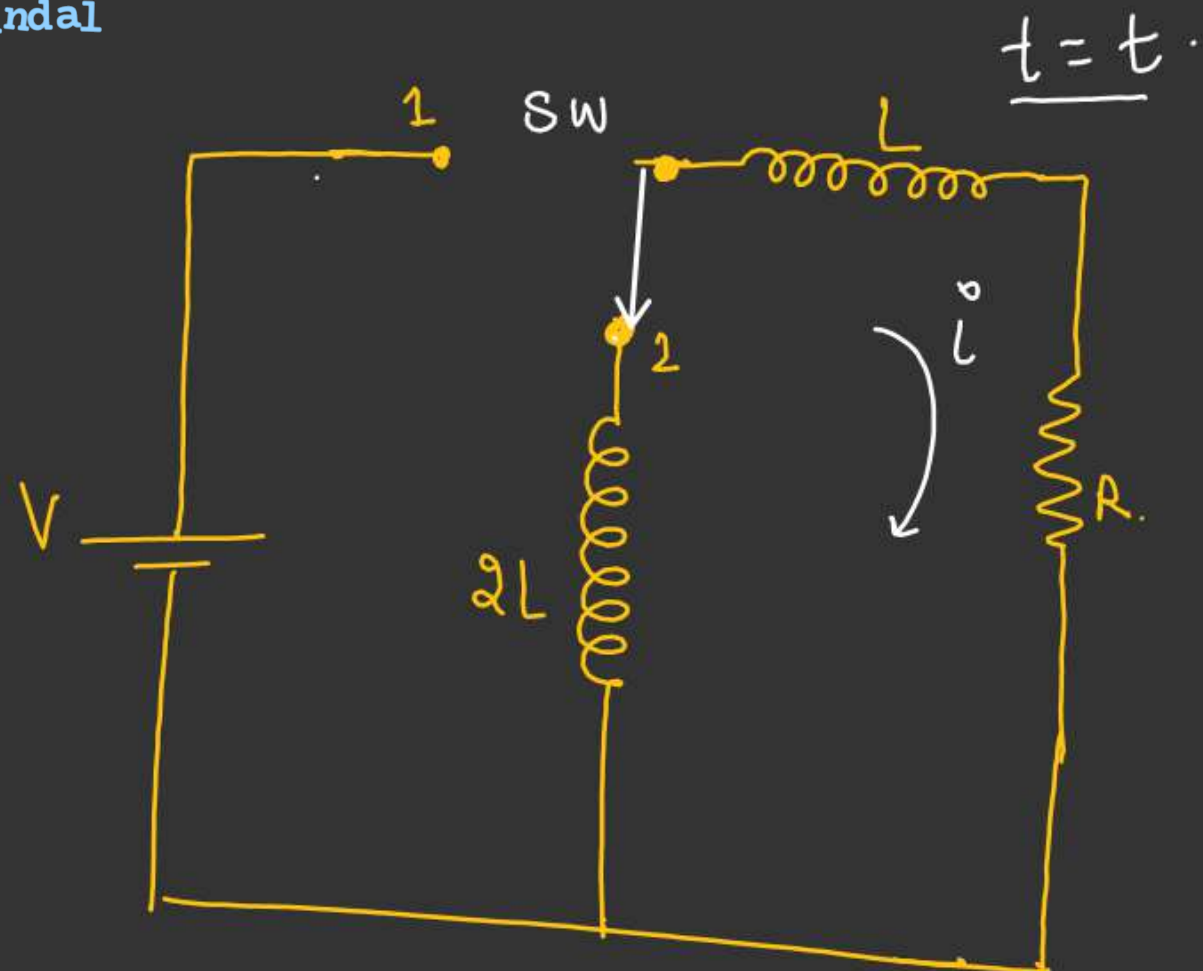


$$-3L \frac{di}{dt} = iR$$

$$\int_{\frac{i_0}{3}}^i \frac{di}{i} = -\frac{R}{3L} \int_0^t dt$$

$$\ln\left(\frac{i}{i_0/3}\right) = -\frac{R}{3L}t$$


$$i = \frac{i_0}{3} e^{-\frac{R}{3L}t}$$

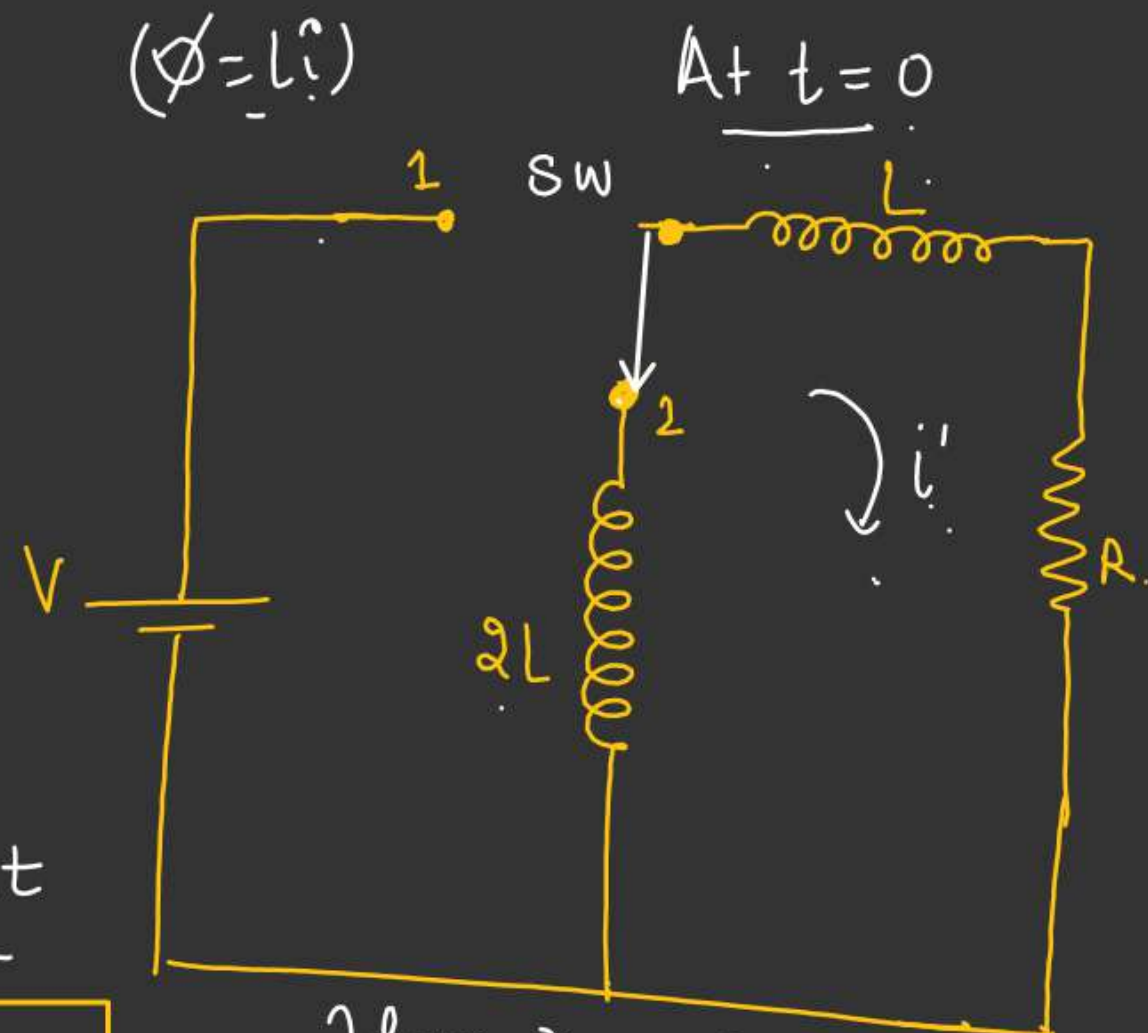

flux remain constant.
just before shifting of
switch to just after
shifting


$$Li_0 = 3L i' \Rightarrow i' = \left(\frac{i_0}{3}\right)$$

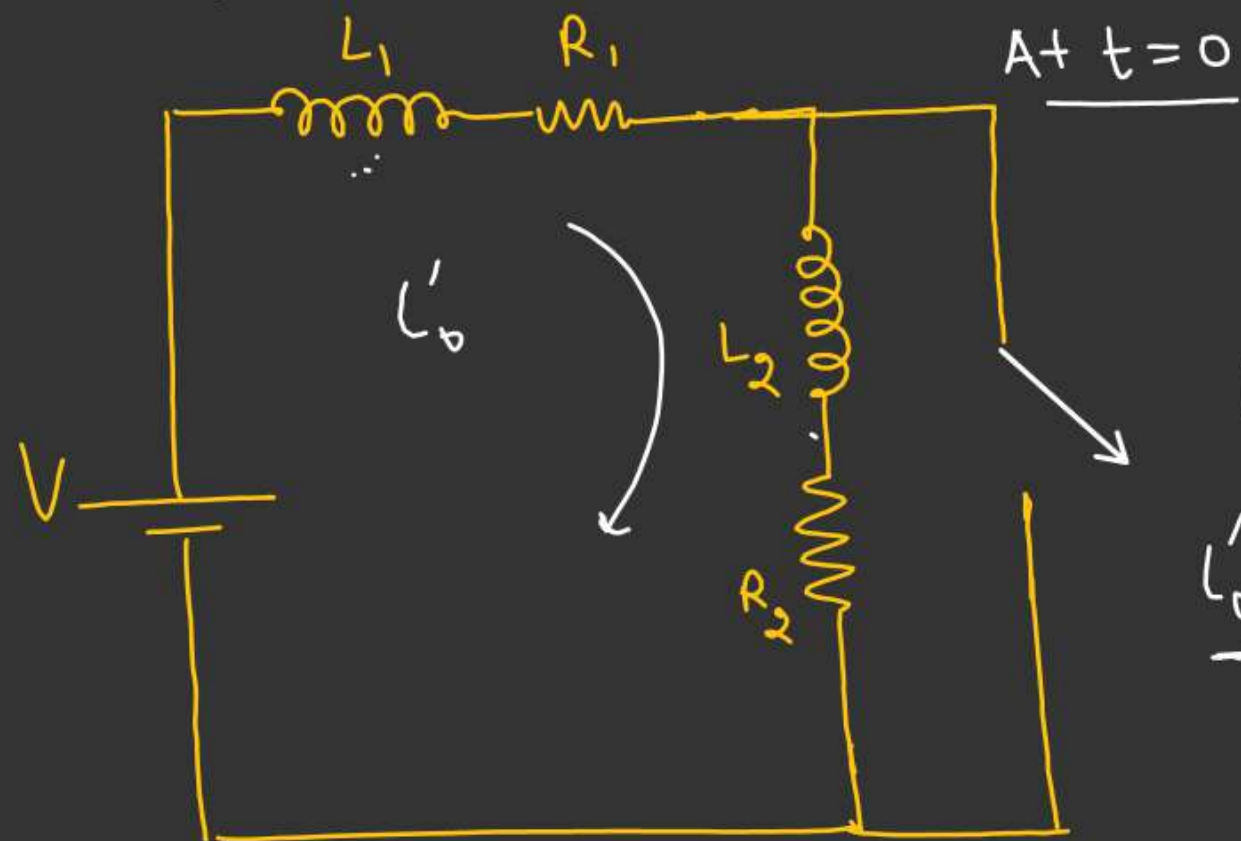
★★. SW closed for a very long time.
Find Current in the CKT as a function of time. At $t=0$ Switch is opened.



$$L_1 i_0 = (L_1 + L_2) i_0'$$
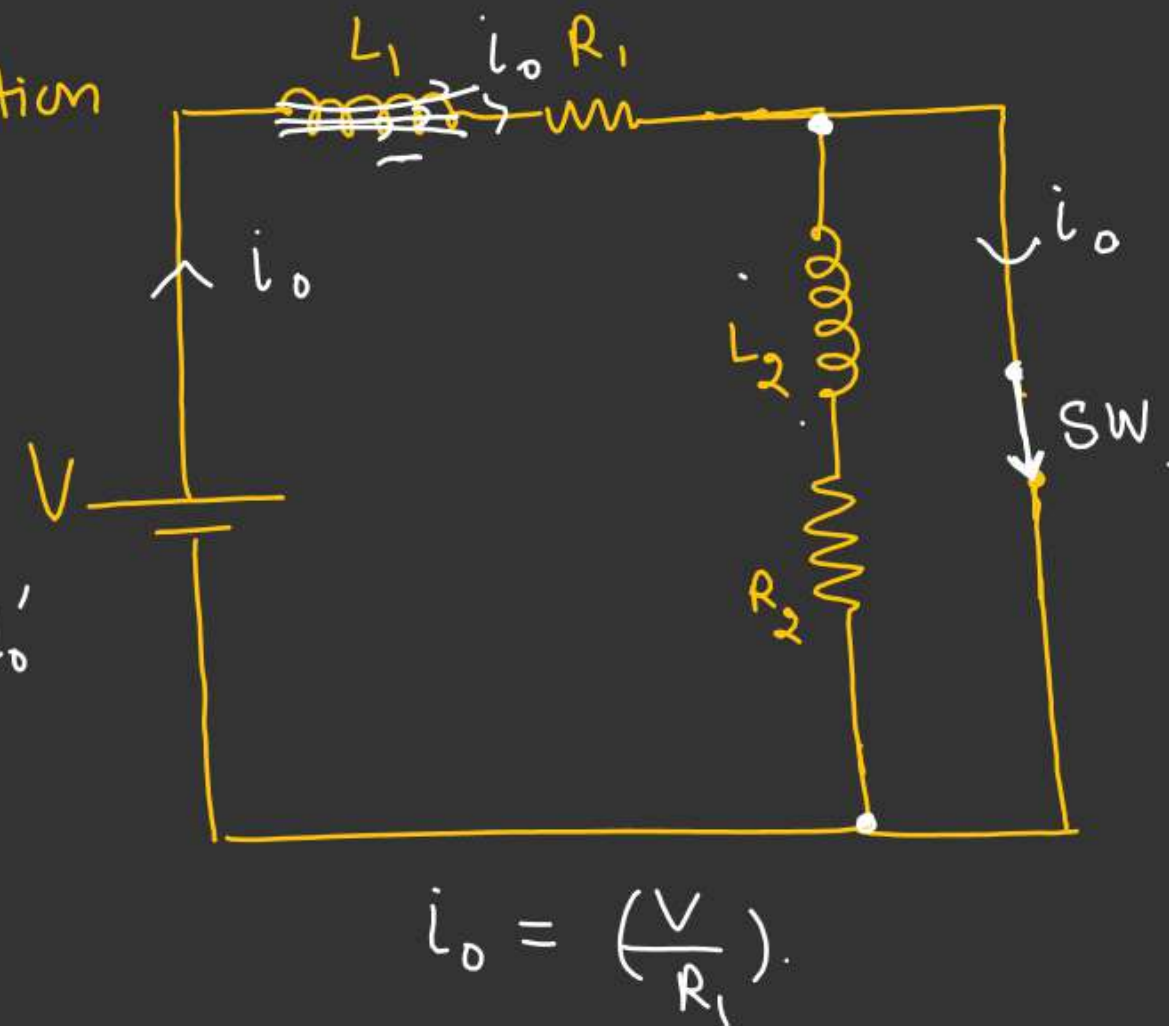
$$i_0' = \left(\frac{L_1}{L_1 + L_2} \right) i_0$$



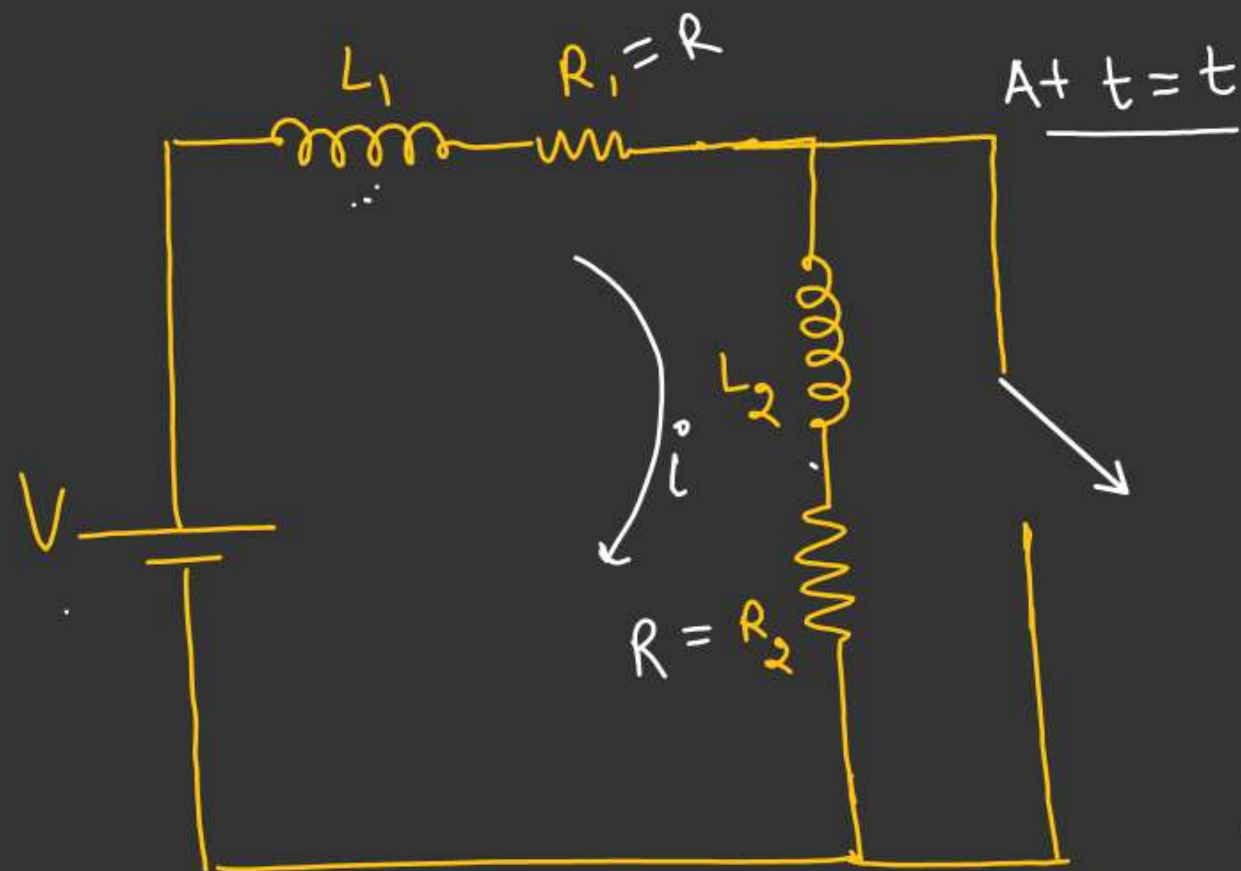

$$\text{put } i_0' = \frac{L_0 L_1}{L_1 + L_2}$$

$$i_0' = \frac{V}{R} \left(\frac{L_1}{L_1 + L_2} \right)$$

$$V - (L_1 + L_2) \frac{di}{dt} - i 2R = 0$$

$$V - 2Ri = (L_1 + L_2) \frac{di}{dt}$$

$$\int_{i_0'}^i \left(\frac{di}{V - 2Ri} \right) = \frac{1}{L_1 + L_2} \int_0^t dt$$

$$\ln \left(\frac{V - 2Ri}{V - 2Ri_0'} \right) = \frac{-2R}{L_1 + L_2} t$$

$$V - 2Ri = (V - 2Ri_0') e^{-\frac{2R}{L_1 + L_2} t}$$


\Downarrow

$$i = \frac{V}{2R} \left[1 - \frac{L_2 - L_1}{L_1 + L_2} e^{-\frac{2R}{L_1 + L_2} t} \right]$$

No Electrical resistance in the
Ckt.

Slider projected on Conducting
frictionless parallel rails
With velocity v_0 . at $t=0$.

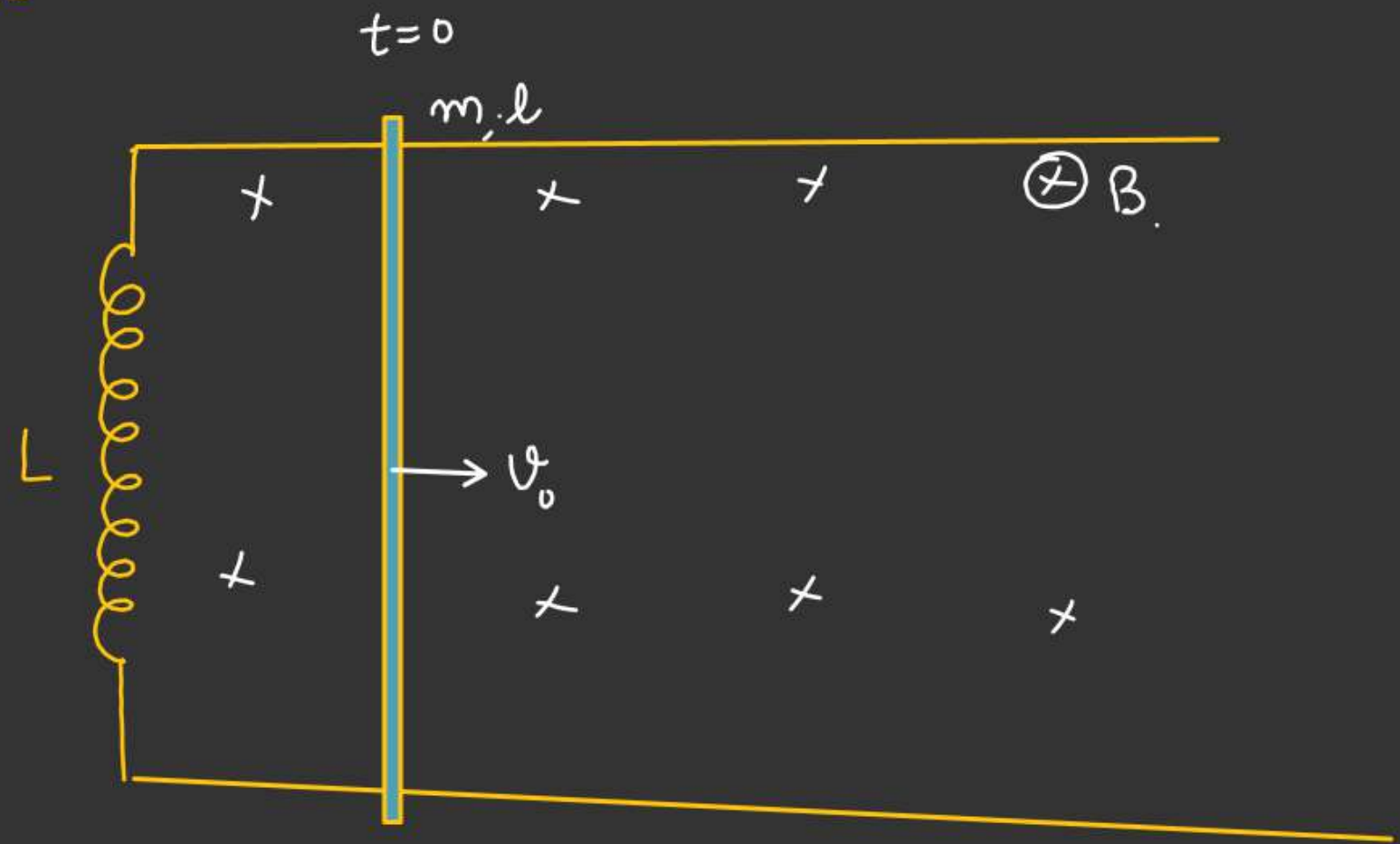Find a) Displacement of Slider
as a function of time.



$$Blv = L \frac{dI}{dt}$$

$$F_B = I l B$$

\Downarrow

$$a = \frac{F_B}{m}$$



$$a = \frac{Bl}{m} I$$

$$-\frac{dv}{dt} = \frac{Bl}{m} (I)$$

Again differentiating w.r.t time.

$$\frac{d^2 v}{dt^2} = -\frac{Bl}{m} \left(\frac{dI}{dt} \right)$$
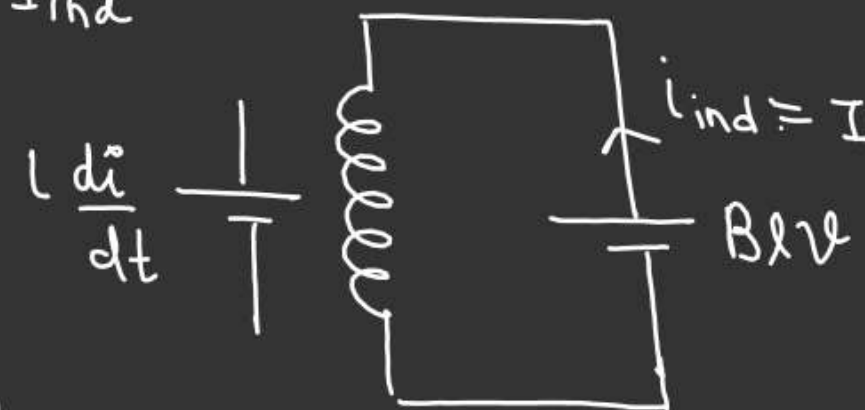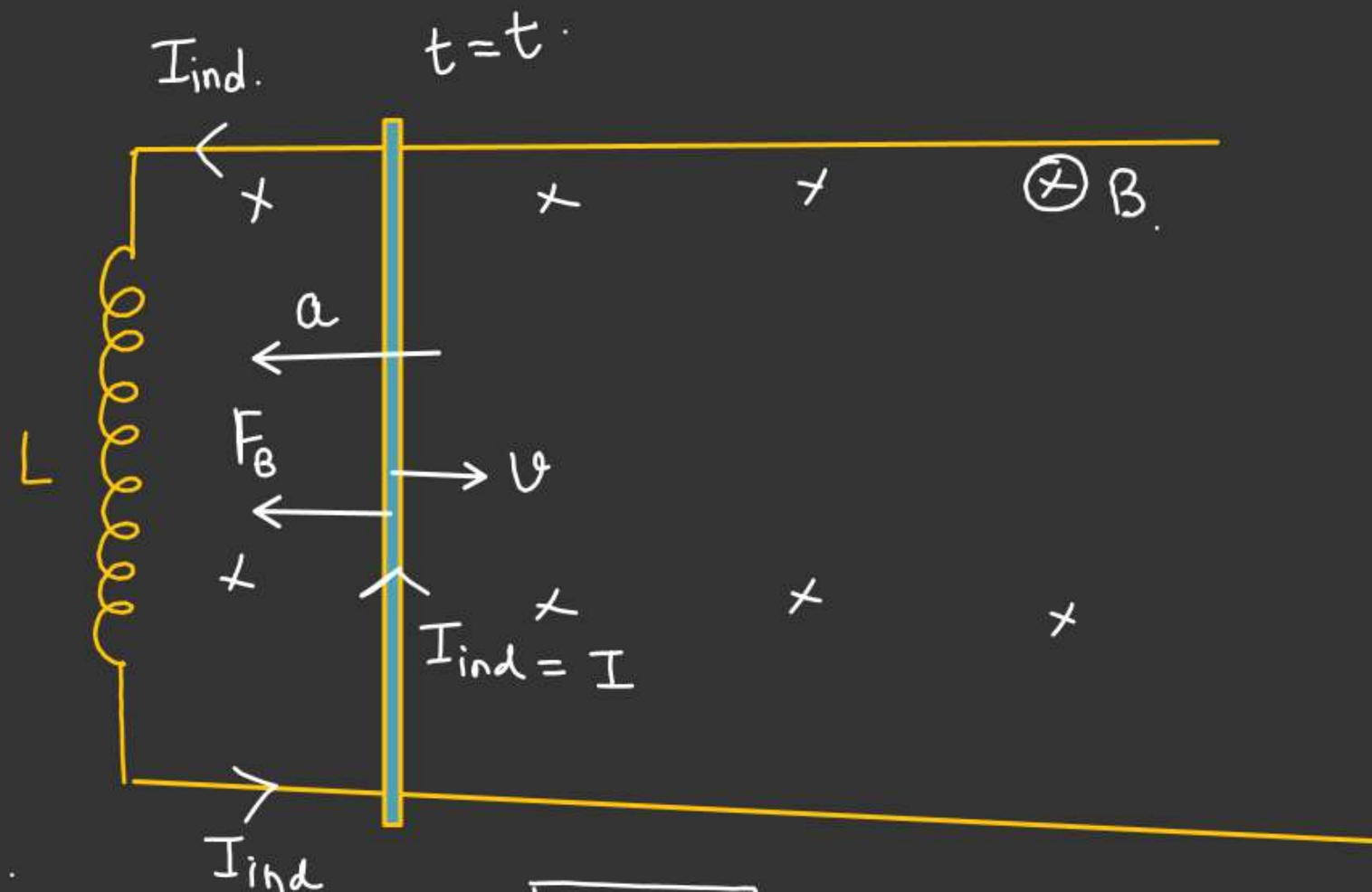
$$\frac{d^2 v}{dt^2} = -\frac{Bl}{m} \left(\frac{Blv}{L} \right) = -\left(\frac{B^2 l^2}{mL} \right) v$$



$$\frac{d^2 \psi}{dt^2} = - \frac{B^2 l^2}{mL} \psi$$

\Downarrow
 ω^2

$$\omega^2 = \frac{B^2 l^2}{mL}$$

$$\omega = \frac{Bl}{\sqrt{mL}}$$

$$\psi_{\max} = \psi_0$$

$$\psi_0 = A\omega$$

$$A = \frac{\psi_0}{\omega} = \frac{\psi_0}{Bl} \sqrt{mL}$$

\Downarrow
Amplitude

$$\psi = \psi_0 \sin(\omega t + \phi)$$

$$At t=0, \psi = \psi_0$$

$$\sin \phi = 1 \quad \phi = \pi/2$$

$$\psi = \psi_0 \sin(\omega t + \pi/2)$$

$$\psi = \underline{\psi_0} \cos \omega t$$

\Downarrow

$$\frac{dx}{dt} = \psi_0 \cos \omega t$$

$$\int_0^x dx = \psi_0 \int_0^t \cos \omega t \cdot dt$$

$$x = \frac{\psi_0}{\omega} [\sin \omega t]_0^t$$

$$x = \frac{\psi_0}{\omega} \sin \omega t$$

$$\underline{x = A \sin \omega t}$$

$$a = -\omega^2 x$$

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

\Downarrow

$$x = \underline{A} \sin(\omega t + \phi) \checkmark$$

$$(v_{\max} = A\omega)$$

H.W.: Slider is released from the frictionless vertical rails.
No Electrical resistance.

Find $x \rightarrow f(t)$.

