

DPP 7

1. when S is opened

$$V_c - V_a = \frac{18 \times 6}{6+3} = 12 \text{ V}$$

$$\therefore V_c = 18 \text{ V}$$

$$V_a = 6 \text{ V}$$



$$C_{eq} = 2 \mu\text{F}$$

$$q = CV = 18 \times 2 = 36 \mu\text{F}$$

$$V_c - V_b = \frac{36}{6} = 6 \text{ V}$$

$$V_b = V_c - 6 = 18 - 6 = 12 \text{ V}$$

$$V_a - V_b = -6 \text{ V ie } K_1 = 6$$

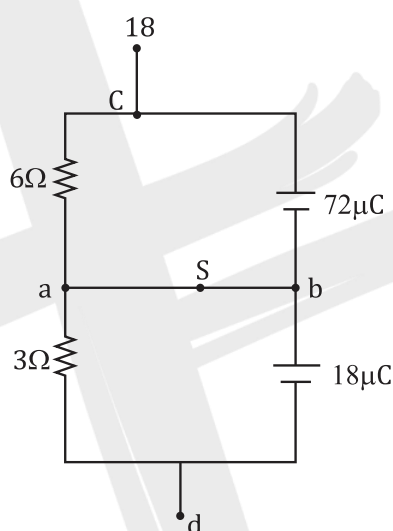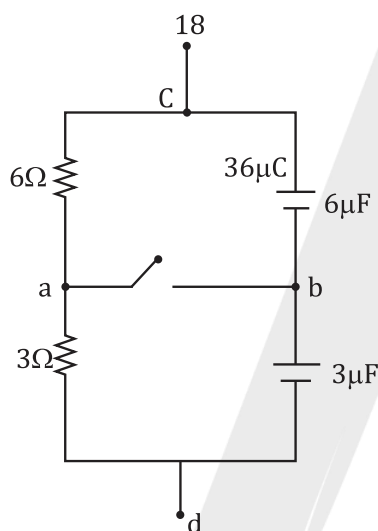

The potential difference across 6Ω resistor will be same as $6\mu\text{f}$ capacitor.

find potential of 'b' is 6 V

$$q'_1 = CV = 6 \times 12 = 72 \mu\text{C}$$

$$q'_2 = CV = 3 \times 6 = 18 \mu\text{C}.$$

charges flow after s is closed.

$$q_1 = 72 - 36 = 36 \mu\text{C}$$

$$q_2 = 36 - 18 = 18 \mu\text{C}$$


Charges flow through s after it is closed

$$\Rightarrow 36 + 18 = 54 \mu\text{C}$$

$$\text{ie } k_2 = 54$$

$$\text{so } k_1 + k_2 = 6 + 54 = 60$$

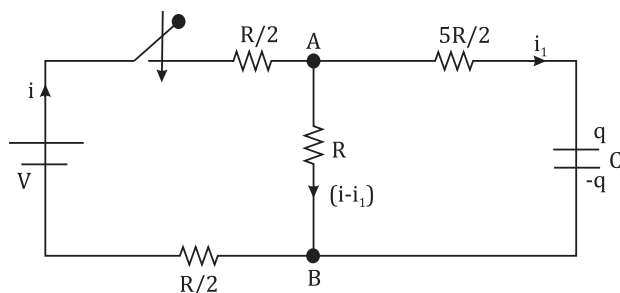2. When S is closed, let the current through the battery = i



at time 't' if charge on capacitor is q then

$$\frac{dq}{dt} = i_1 \quad \dots(i)$$

$$\begin{aligned} \text{By KVL } \Rightarrow V &= \frac{R}{2}i + R(i - i_1) + \frac{R}{2}i \\ &= 2Ri - Ri_1 \quad \dots(ii) \end{aligned}$$

$$\begin{aligned} \text{And } V &= \frac{iR}{2} + \frac{iR}{2} + \frac{5R}{2}i_1 + \frac{q}{C} \\ &= iR + \frac{5R}{2}i_1 + \frac{q}{C} \quad \dots(iii) \end{aligned}$$

$$\text{from eq}^n (2) \quad iR = \frac{V + i_1 R}{2} \quad \dots(A)$$

put (A) in (3).

$$\begin{aligned} V &= \frac{V}{2} + \frac{i_1 R}{2} + \frac{5Ri_1}{2} + \frac{q}{C} \\ \frac{V}{2} &= 3i_1 R + q/C \quad \dots(iv) \end{aligned}$$

$$\therefore i_1 = \frac{dq}{dt} \text{ put it in eq}^n(4)$$

$$\frac{V}{2} = 3R \frac{dq}{dt} + \frac{q}{C}$$

$$\int_0^t \frac{dt}{6RC} = \int_0^q \frac{dq}{Vc - 2q}$$

$$\frac{t}{6RC} = \frac{[\ln Vc - 2q]_0^q}{-2}$$

$$\frac{t}{6RC} = \frac{\ln \left[\frac{Vc - 2q}{Vc} \right]}{-2}$$

$$\frac{-t}{3RC} = \ln \left[\frac{Vc - 2q}{Vc} \right] \Rightarrow -t/3RC.$$

$$Vc - 2q = Vce$$

$$q = \frac{Vc}{2} (1 - e^{-t/3RC})$$

$$\therefore N = 3$$

$$3. \quad \therefore i_1 = \frac{dq}{dt} = \frac{vc}{2} \left[0 - e^{-t/3RC} \left(\frac{-1}{3RC} \right) \right]$$

$$i_1 = \frac{v}{2R} \left[\frac{e^{-t/3RC}}{3} \right]$$


$$\therefore i = \frac{v}{2R} + \frac{i_1}{2}$$

$$i - i_1 = \frac{v}{2R} - \frac{i_1}{2}$$

$$(1 - i_1) = \frac{v}{2R} \left[1 - \frac{e^{-t/3RC}}{6} \right]$$

$$2^K - 2 = 6 \Rightarrow K = 3$$

4.

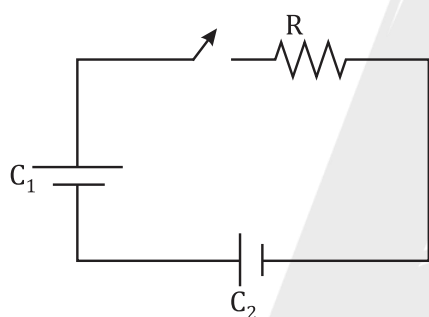

$$\text{Total charge} = q_0$$

$$q_2 = \frac{c_2}{c_1 + c_2} q_0$$

$$q_2(t) = q_2 (1 - e^{-t/Rc_{eq}})$$

$$Rc_{eq} = 80 \times \left[\frac{6\mu f \times 4\mu f}{10\mu F} \right]$$


$$Rc_{eq} = 80 \times \frac{24}{10} \mu = 192 \mu \text{ sec}$$

$$q_2(t = 192 \mu \text{ sec}) = \frac{c_2}{c_1 + c_2} q_0 \left[1 - e^{\frac{-192\mu}{192\mu}} \right]$$

$$= \frac{4\mu}{10\mu} \left(\frac{30e}{e-1} \right) \left[1 - \frac{1}{e} \right] = 12 \mu c$$

$$q_2(t = 192 \mu \text{ sec}) = 12 \mu c$$

5.

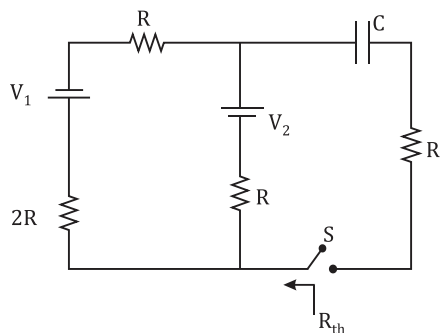

$$\frac{1}{R_{th}} = \frac{1}{3R} + \frac{1}{R}$$

$$R_{th} = \frac{3R}{4}$$

$$R_{eq} = \frac{3R}{4} + R = \frac{7R}{4}$$


$$\therefore \tau = \text{time constant} = RC.$$

$$\tau = \frac{7RC}{4}$$

6. When switch is closed, the energy stored in the capacitor will be dissipated through resistor.

$$\frac{Q^2}{2C} = 3.6 \times 10^{-3}.$$

$$Q = 120 \mu C$$

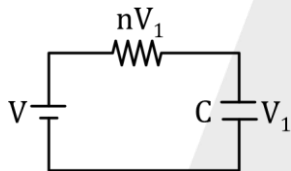

7.


$$nv_1 + v_1 = v \Rightarrow v_1 = \frac{v}{(n+1)}$$

$$v_1 = v[1 - e^{-t/RC}]$$

$$\frac{v}{n+1} = v[1 - e^{-t/RC}]$$

$$t = RC \ln \left[\frac{n+1}{n} \right]$$

8.

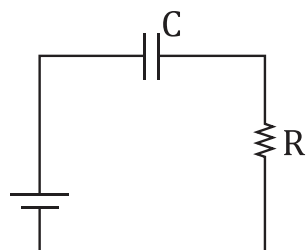

$$\therefore I = \frac{V}{R} e^{-t/RC}.$$

$$\text{Log } I = \log \frac{V}{R} - \frac{t}{RC}$$

$$y = c + mx$$

$$\therefore y = \log I, c = \log \frac{V}{R}$$

$$x = t \Rightarrow m = \frac{-1}{RC}$$

first slope is greater than second slope ie $\frac{1}{RC_1} > \frac{1}{RC_2}$

ie $C_1 < C_2 \Rightarrow$ capacitance increased.

9. charge on capacitor $q = q_{\max}(1 - e^{-t/RC})$ As the q_{\max} of the both curve is same so both capacitor will be charged to same charge.

curve 2 is taking more time to reach q_{\max} . ie $\tau_2 > \tau_1 \Rightarrow C_2 R_2 > C_1 R_1$

$\therefore q_{\max}$ is same for both curves

$$\therefore C_1 E_1 = C_2 E_2$$

$\therefore C_2$ and C_1 are different so E_2 and E_1 will be different

10. $\therefore \tau_2 > \tau_1 \Rightarrow C_2 R_2 > C_1 R_1$

$$\frac{R_1}{R_2} < \frac{C_2}{C_1}$$