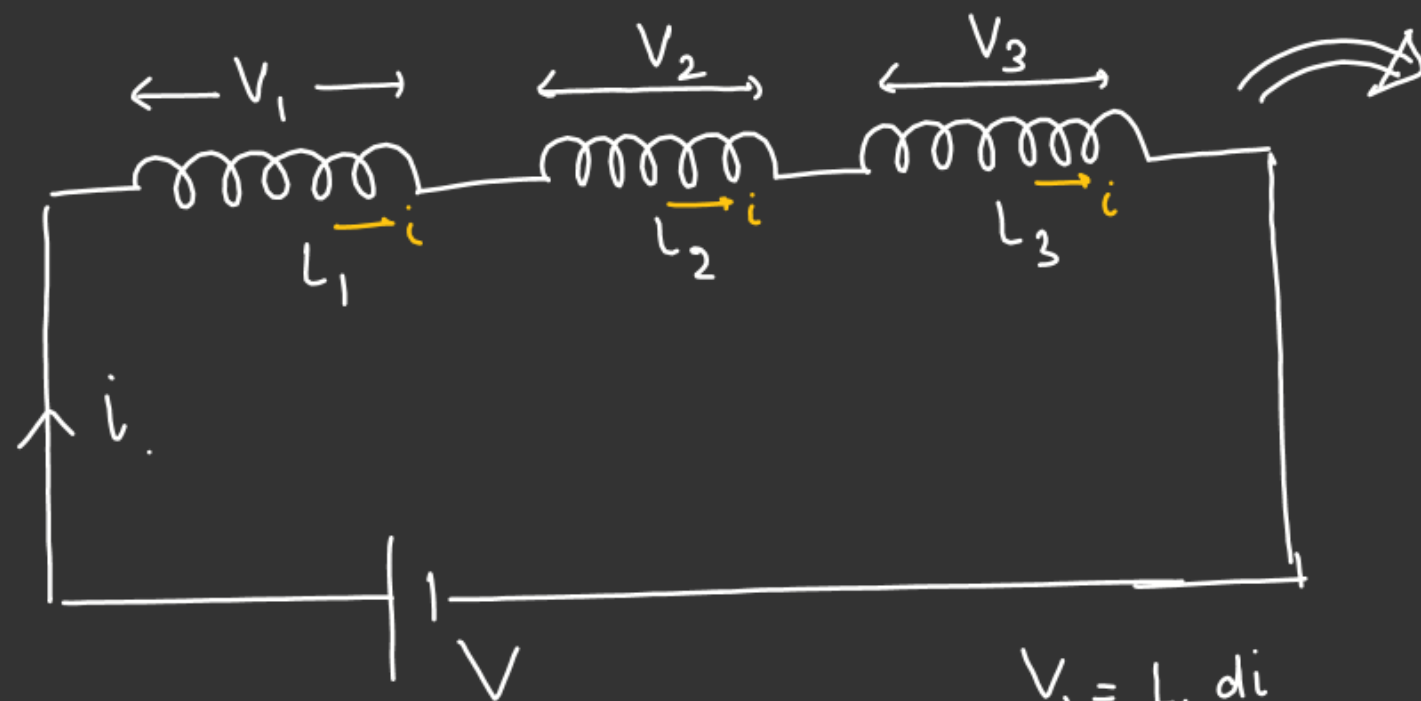


Series Combination of Inductor

$$V_1 = L_1 \frac{di}{dt}$$


$$V_2 = L_2 \frac{di}{dt}$$

$$V_3 = L_3 \frac{di}{dt}$$

$$V = V_1 + V_2 + V_3$$


$$L_{eq} \left(\frac{di}{dt} \right) = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$
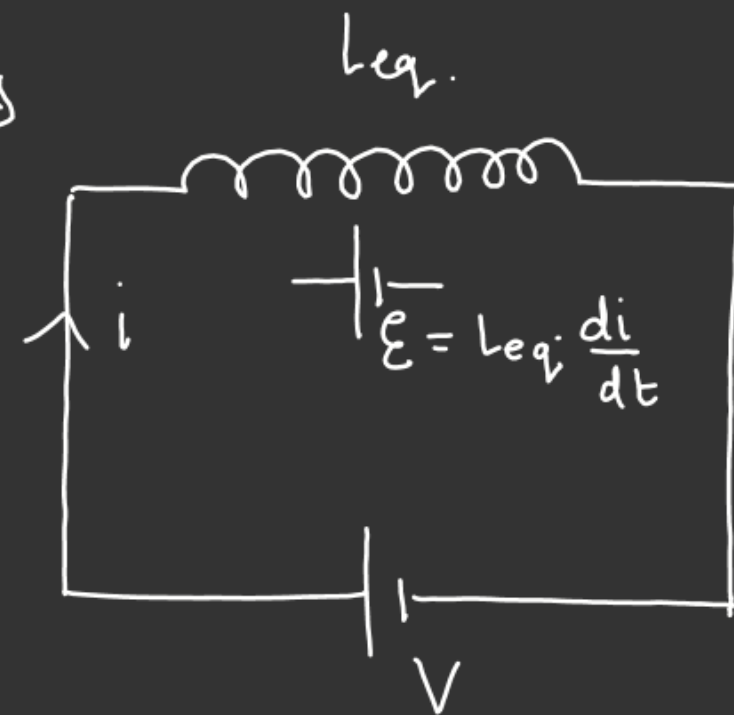
$$\underline{L_{eq} = (L_1 + L_2 + L_3)} \quad \checkmark$$



$$V = L_{eq} \frac{di}{dt}$$


24 Parallel Combination

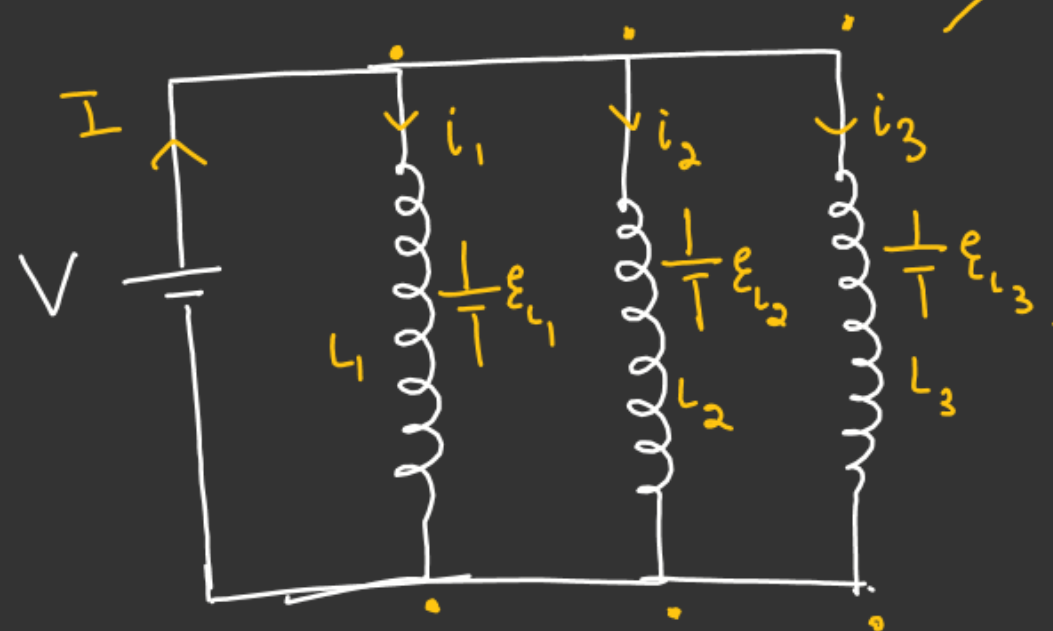

$$\mathcal{E}_{L_1} = L_1 \frac{d i_1}{dt}$$

$$\mathcal{E}_{L_2} = L_2 \frac{d i_2}{dt}$$
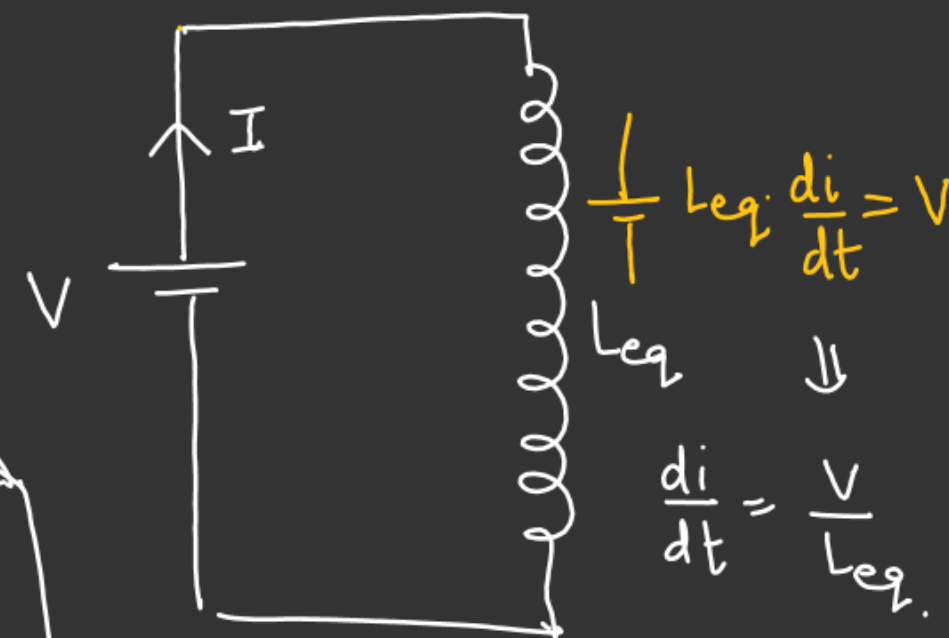
$$\mathcal{E}_{L_3} = L_3 \frac{d i_3}{dt}$$



$$\frac{d i}{dt} = \frac{V}{L_{eq}}$$

$$I = I_1 + I_2 + I_3$$

Differentiating both side w.r.t time

$$\frac{d I}{dt} = \frac{d I_1}{dt} + \frac{d I_2}{dt} + \frac{d I_3}{dt}$$

$$\frac{V}{L_{eq}} = \frac{V}{L_1} + \frac{V}{L_2} + \frac{V}{L_3}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\frac{d i_1}{dt} = \frac{\mathcal{E}_{L_1}}{L_1} = \frac{V}{L_1}$$

$$\frac{d i_2}{dt} = \frac{\mathcal{E}_{L_2}}{L_2} = \frac{V}{L_2}$$

$$\frac{d i_3}{dt} = \frac{\mathcal{E}_{L_3}}{L_3} = \frac{V}{L_3}$$

SS

General L-R CktGrowth of Current

$$I = I_0 (1 - e^{-t/\tau})$$

$I_0 \rightarrow$ [Maximum Current]
at ∞

Steady State Current
[At this inductor behave as zero resistance wire]


$$\tau = \left(\frac{L}{R_{eq}} \right)$$

$R_{eq} \rightarrow$ Across inductor

#

SW closed
at $t=0$

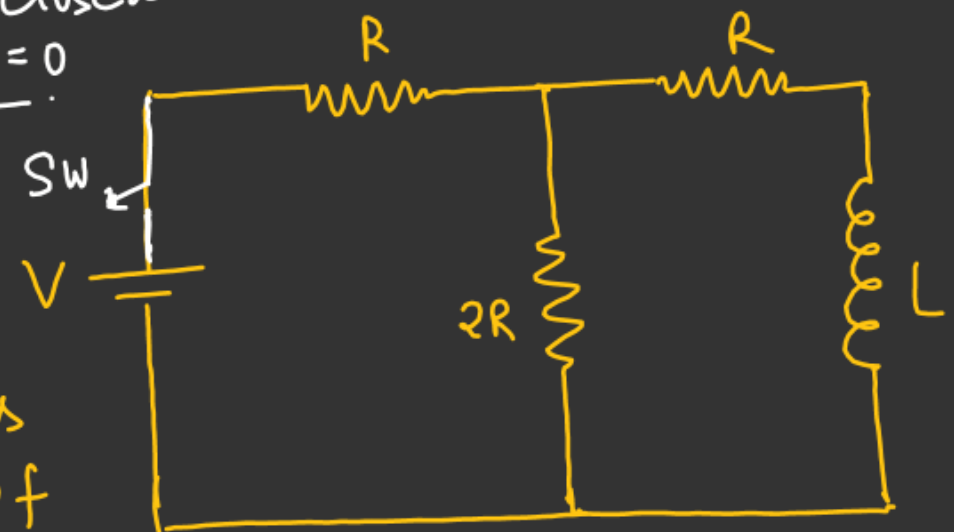a) Find Current in the inductor as a function of time.



b) Total Current in the Ckt as a function of time.

Solⁿ:-KVL in loop abcdefa $\vec{i} = i_1 + i_2$ — ①

$$V - iR - i_2R - L \frac{di_2}{dt} = 0$$

KVL in loop bcaeb

$$-i_2R - L \frac{di_2}{dt} + i_1 2R = 0$$


$$i_1(2R) = i_2R + L \frac{di_2}{dt}$$

$$\underline{i_1} = \frac{i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right) \text{ — ②}$$

From ① $i - i_2 = i_1$ put in ②

$$i - i_2 = \frac{i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right)$$
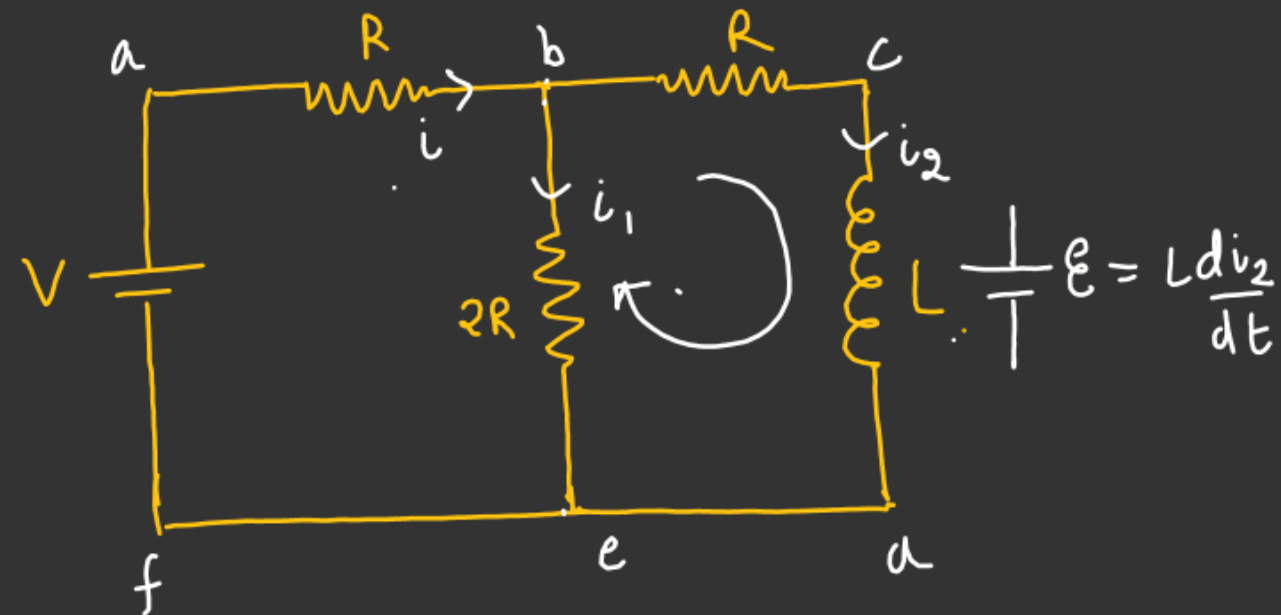
$$\underline{i} = \frac{3i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right)$$



$$V - \left(\frac{3i_2}{2} + \frac{L}{2R} \frac{di_2}{dt} \right) R - i_2R - L \frac{di_2}{dt} = 0$$

$$V - \frac{3i_2R}{2} - i_2R - \left(\frac{L}{2} + L \right) \frac{di_2}{dt} = 0$$

$$V - \frac{5i_2R}{2} - \frac{3L}{2} \frac{di_2}{dt} = 0$$

Solⁿ:-KVL in loop abcdefa $\vec{i} = i_1 + i_2$ — ①

$$V - iR - i_2R - L \frac{di_2}{dt} = 0$$

KVL in loop bcaeb

$$-i_2R - L \frac{di_2}{dt} + i_1 2R = 0$$


$$i_1(2R) = i_2R + L \frac{di_2}{dt}$$

$$\underline{i_1} = \frac{i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right) \text{ — ②}$$

From ① $i - i_2 = i_1$ put in ②

$$i - i_2 = \frac{i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right)$$
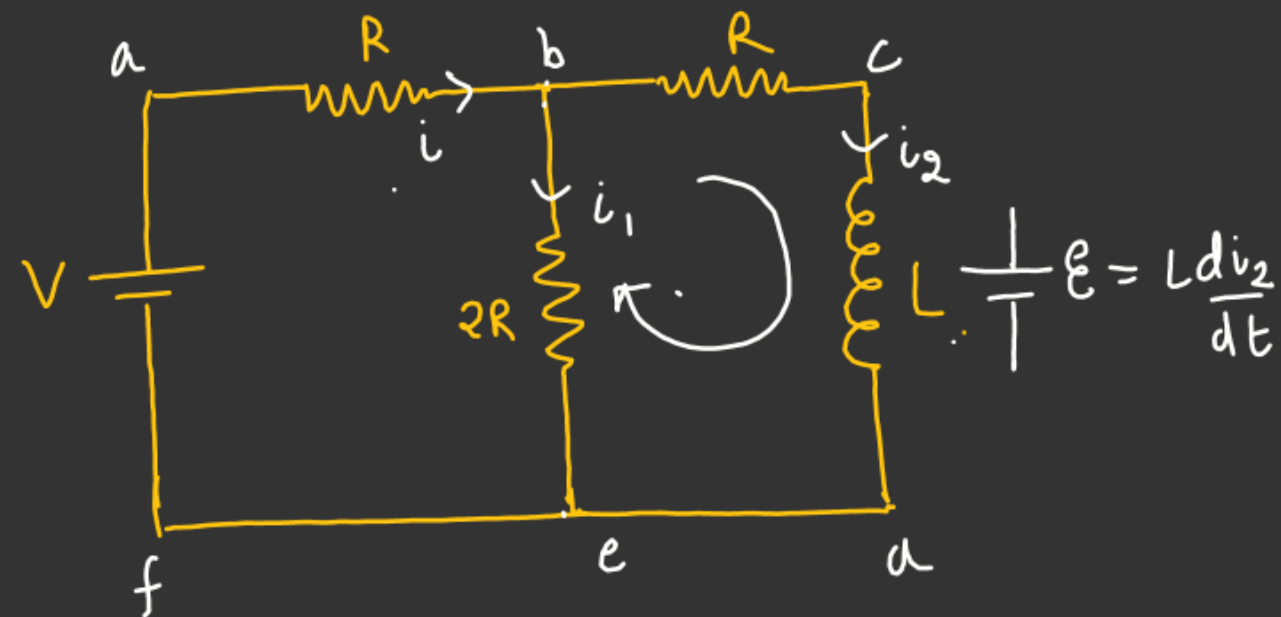
$$\underline{i} = \frac{3i_2}{2} + \frac{L}{2R} \left(\frac{di_2}{dt} \right)$$



$$V - \left(\frac{3i_2}{2} + \frac{L}{2R} \frac{di_2}{dt} \right) R - i_2R - L \frac{di_2}{dt} = 0$$

$$V - \frac{3i_2R}{2} - i_2R - \left(\frac{L}{2} + L \right) \frac{di_2}{dt} = 0$$

$$V - \frac{5i_2R}{2} - \frac{3L}{2} \frac{di_2}{dt} = 0$$

$$(2V - 5Ri_2) = 3L \frac{di_2}{dt}$$

$$\begin{aligned}
 (2V - 5Ri_2) &= 3L \frac{di_2}{dt} \\
 \int_0^{i_2} \frac{di_2}{(2V - 5Ri_2)} &= \frac{1}{3L} \int_0^t dt \\
 \frac{\ln(2V - 5Ri_2) \Big|_0^{i_2}}{-5R} &= \frac{1}{3L} t \\
 \ln\left(\frac{2V - 5Ri_2}{2V}\right) &= -\frac{5R}{3L} t \\
 2V - 5Ri_2 &= 2V e^{-\frac{5R}{3L} t}
 \end{aligned}$$

$$2V(1 - e^{-\frac{5R}{3L} t}) = 5Ri_2$$

$$i_2 = \frac{2V}{5R} (1 - e^{-\frac{5R}{3L} t})$$

$$i = i_0 (1 - e^{-t/\tau})$$

$(i_0)_{\max}$ in inductor (At the time of Steady state)


$$= \frac{2V}{5R}$$

$$\tau = \left(\frac{3L}{5R}\right) \checkmark$$


Time Constant

M-2.Find T

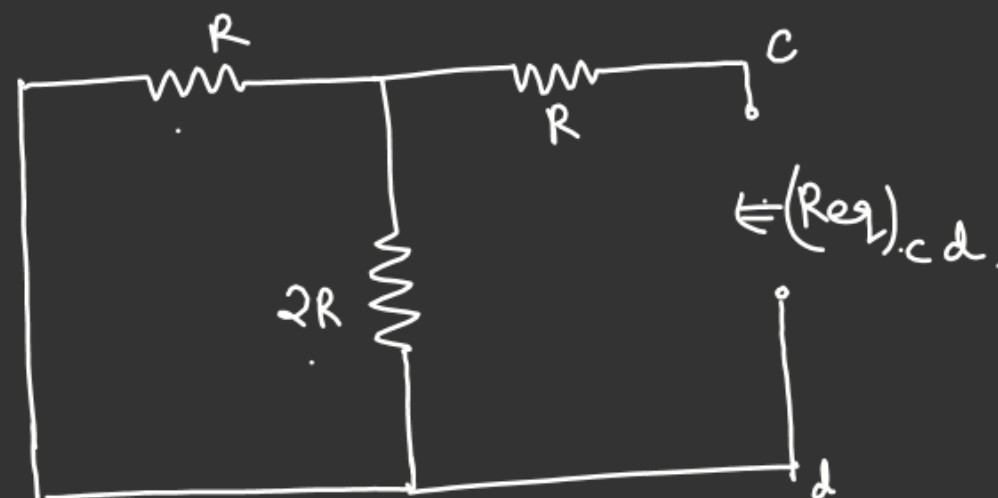- i) Req across inductor.
for this short the battery.


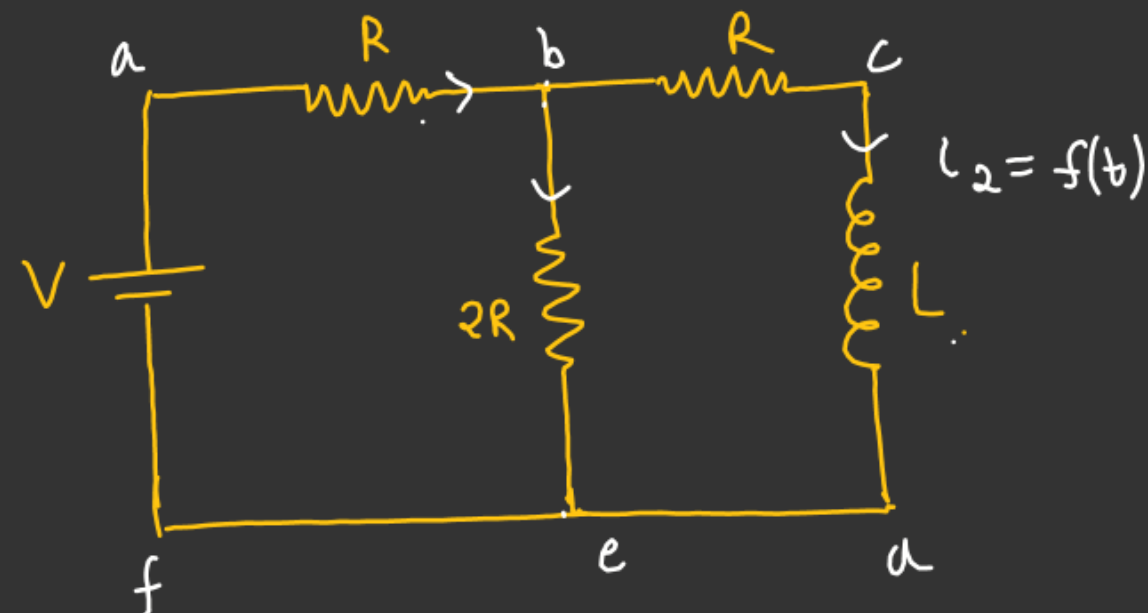
$$\begin{aligned}
 (R_{eq})_{c-d} &= \frac{R \cdot 2R}{R + 2R} + R \\
 &= \frac{2R}{3} + R \\
 &= \left(\frac{5R}{3}\right)
 \end{aligned}$$



$$T_{ckt} = \frac{L}{(R_{eq})_{across L}}$$

$$T_{ckt} = \frac{L}{\frac{5R}{3}} = \left(\frac{3L}{5R}\right) \underline{Ans}$$

M-2, $i_2 = f(t)$ ✓

$(i_2)_{\max}$ at the time of Steady State.

At that time inductor behave as a zero resistance wire.

K-V.L in loop
abcdefa

$$V - IR - (i_2)_{\max} R = 0$$

$$(i_2)_{\max} R = V - IR$$

$$= \left(V - \frac{3V}{5} \right) = \left(\frac{2V}{5} \right)$$

$$(i_2)_{\max} = \left(\frac{2V}{5R} \right)$$

$$R_{eq} = \frac{2R \cdot R}{2R + R} + R$$



$$R_{eq} = \frac{2R}{3} + R$$

$$= \left(\frac{5R}{3} \right)$$

$$I = \frac{V}{\left(\frac{5R}{3} \right)} = \left(\frac{3V}{5R} \right)$$

$$i_2 = \frac{2V}{5R} \left(1 - e^{-\frac{t5R}{3L}} \right)$$

Ans ✓

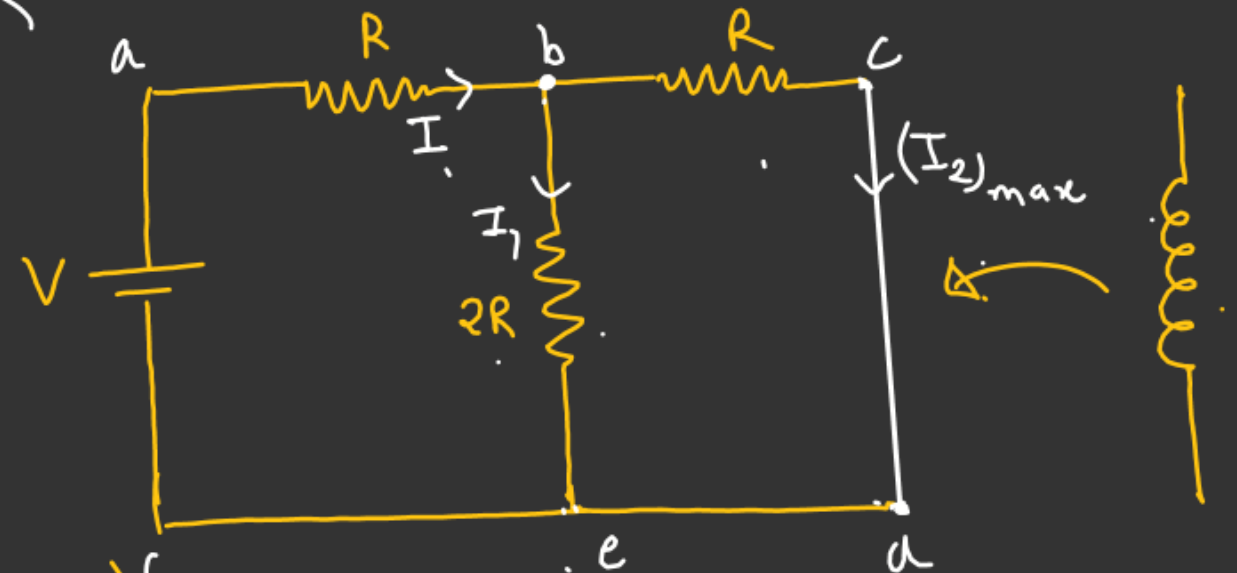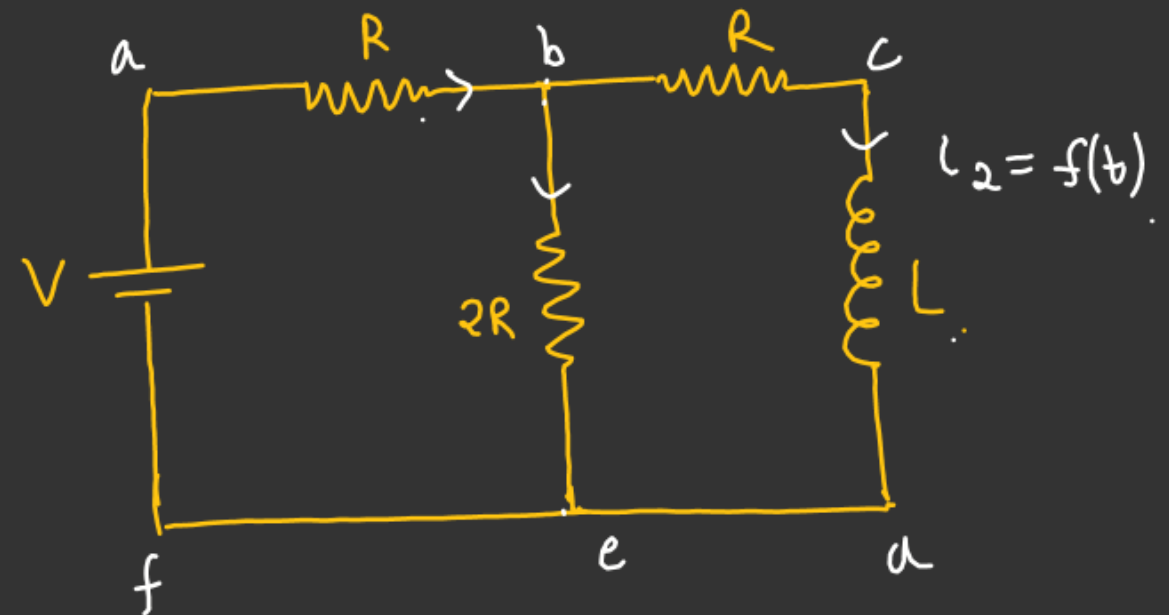

Q. Q.

$$V = 12 \text{ volt.}$$

$$R = 2 \Omega.$$

$$L = 400 \text{ mH.}$$


Switch is closed at $t=0$.

a) potential drop across L as a function of time.

b) After steady achieved, SW again opened.

i) find current in resistor just after SW is reopened.

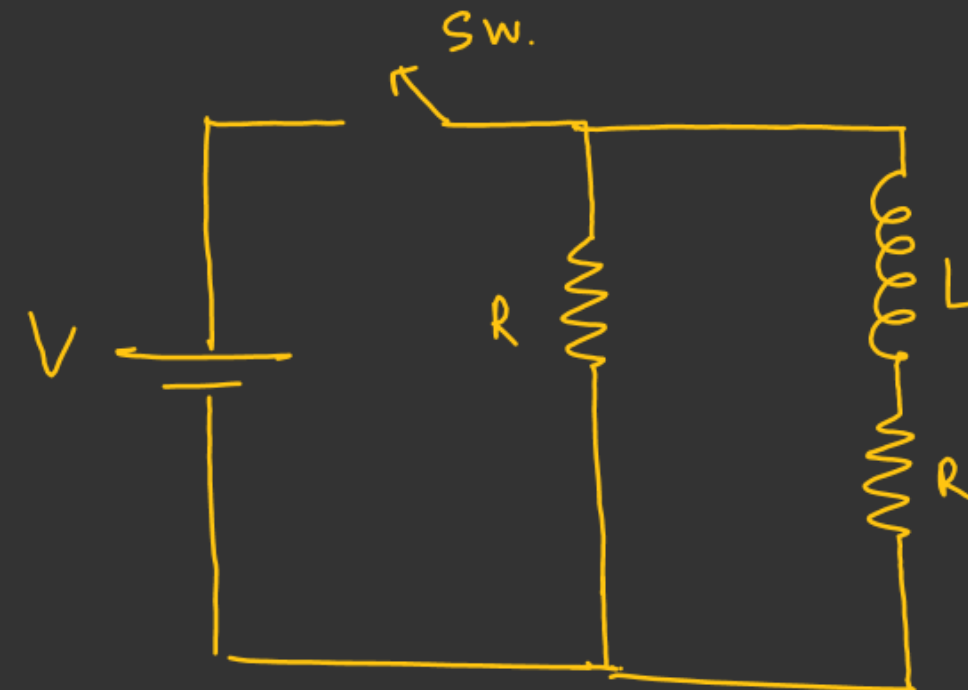ii) find current in resistor as a function of time after SW reopened.



Q. Q.


$$V = 12 \text{ Volt.}$$

$$R = 2 \Omega.$$

$$L = 400 \text{ mH.}$$

a) $\mathcal{E}_L = f(t).$

$$\tau = ??$$

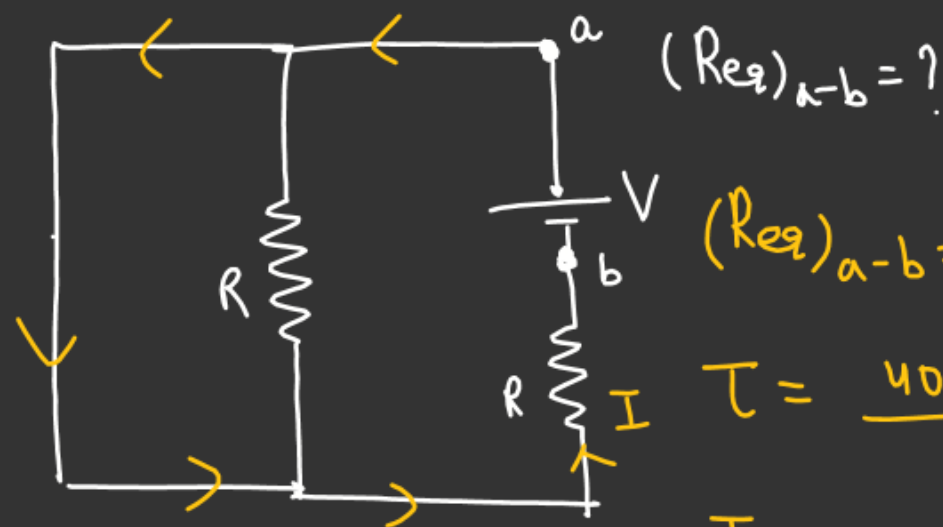

$$(R_{eq})_{a-b} = R$$



$$\tau = \frac{400 \times 10^{-3}}{2}$$

$$\tau = \frac{2}{10} = \frac{1}{5} = 0.2 \text{ sec.}$$

Current in the inductor $\leftarrow i_L = 6(1 - e^{-5t})$ as a function of time

i_{max} in the inductor

Inductor behave as zero resistance wire.

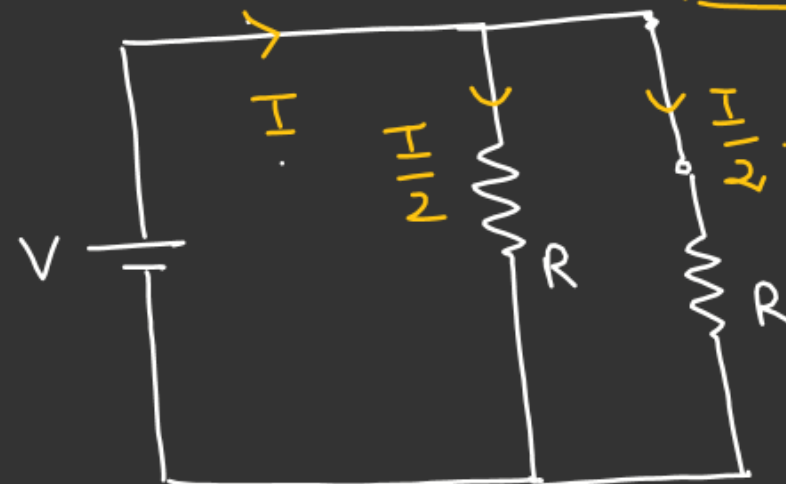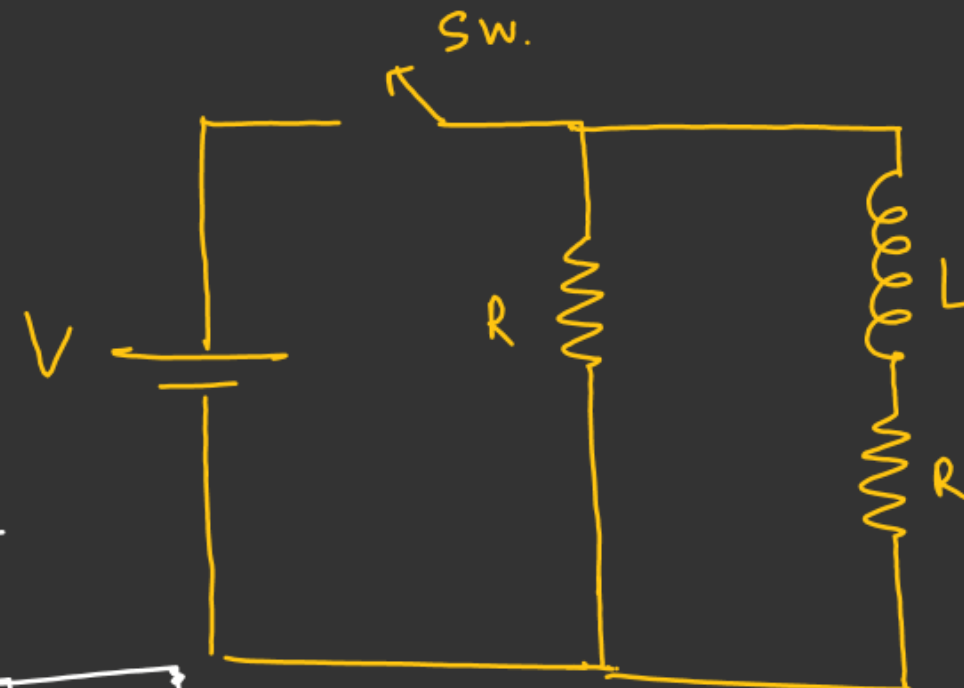

$$I = \frac{V}{R_{\text{eq}}} = \frac{12}{2} = 6 \text{ A.}$$

i_{max} in the inductor = 6 Amp. ✓

$$i_L = 6(1 - e^{-5t})$$

$$\mathcal{E}_L = -L \frac{d(i_L)}{dt}$$

$$\mathcal{E}_L = -L \left[-6 \frac{d}{dt}(e^{-5t}) \right]$$

$$\mathcal{E}_L = +6L (e^{-5t})(-5)$$

$$\mathcal{E}_L = -30L (e^{-5t})$$

$$\mathcal{E}_L = -30 \times 400 \times 10^{-3} \cdot e^{-5t}$$

$$\mathcal{E}_L = -12 e^{-5t}$$



$$\underline{|\mathcal{E}_L| = (12 e^{-5t})} \checkmark$$

- Imp
- b) After steady achieved, SW again opened.
- find Current in resistor just after SW is reopened. ✓
 - find Current in resistor as a function of time after SW reopened.

Note:- Inductor has a property of inertia
 So, just after SW open. the state
 of inductor is same as just before
 the SW opened.

$$R_1 = 0, R_2 = 6 \text{ Amp.}$$

At the time
 of steady state

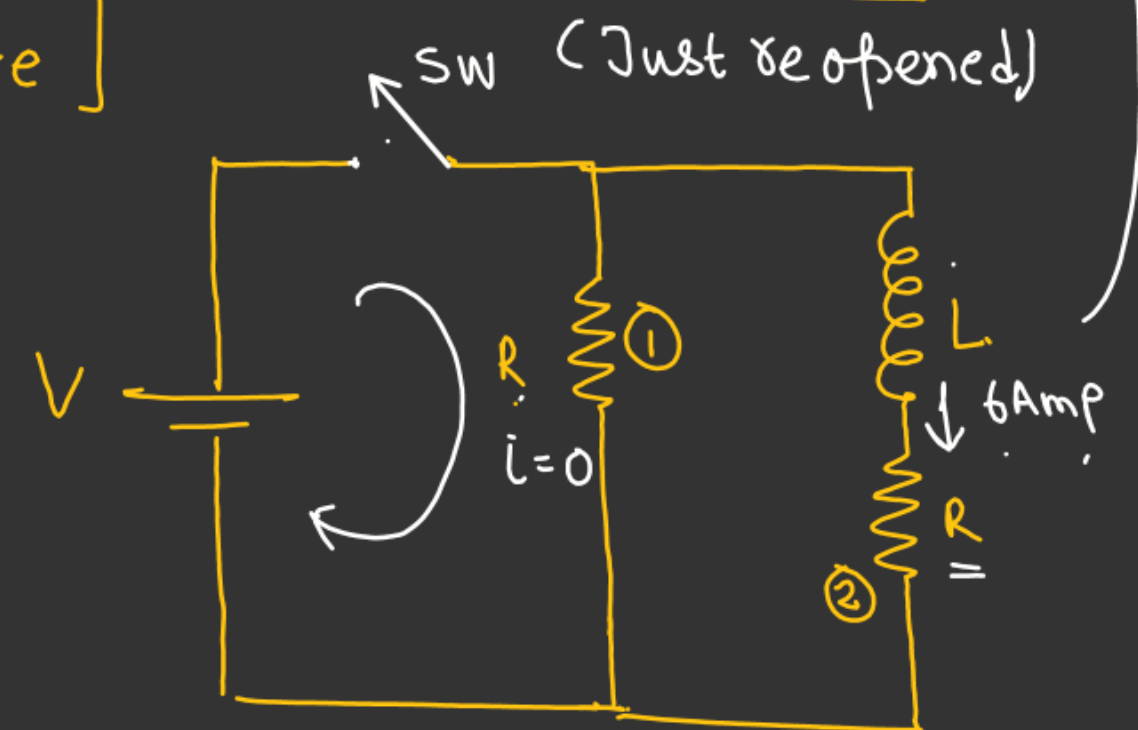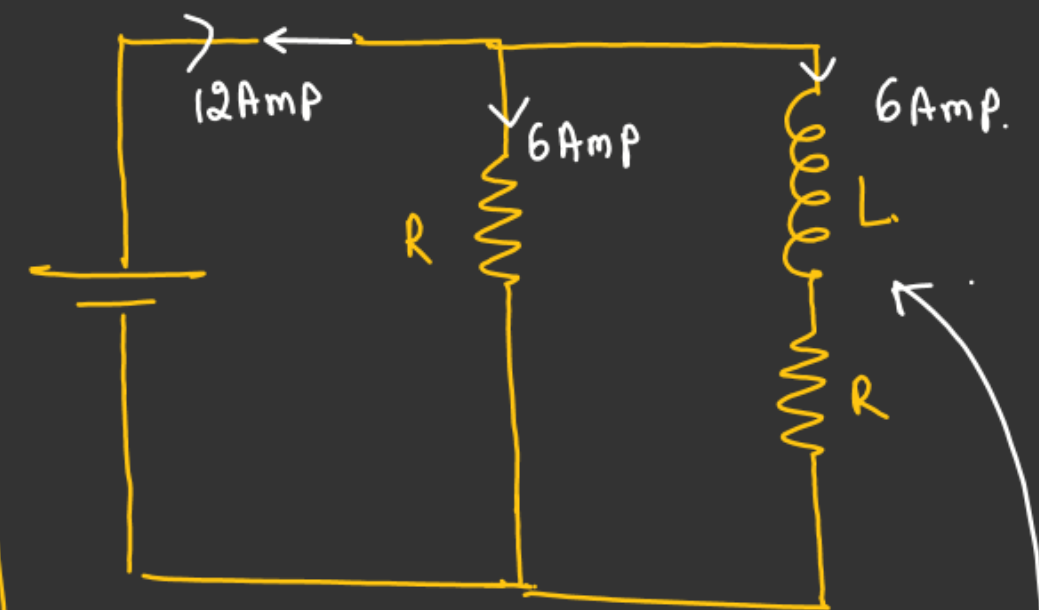

(b) (ii) For decay of current

$$i = i_0 e^{-t/\tau} \checkmark$$

i_0 = Current just after SW is reopend.

$$i_0 = 6 \text{ Amp.}$$

$$\tau = \frac{L}{2R} =$$

$$\frac{400 \times 10^{-3}}{2 \times 2} = \left(\frac{1}{10}\right)$$

$$i = 6 e^{-10t}$$

