
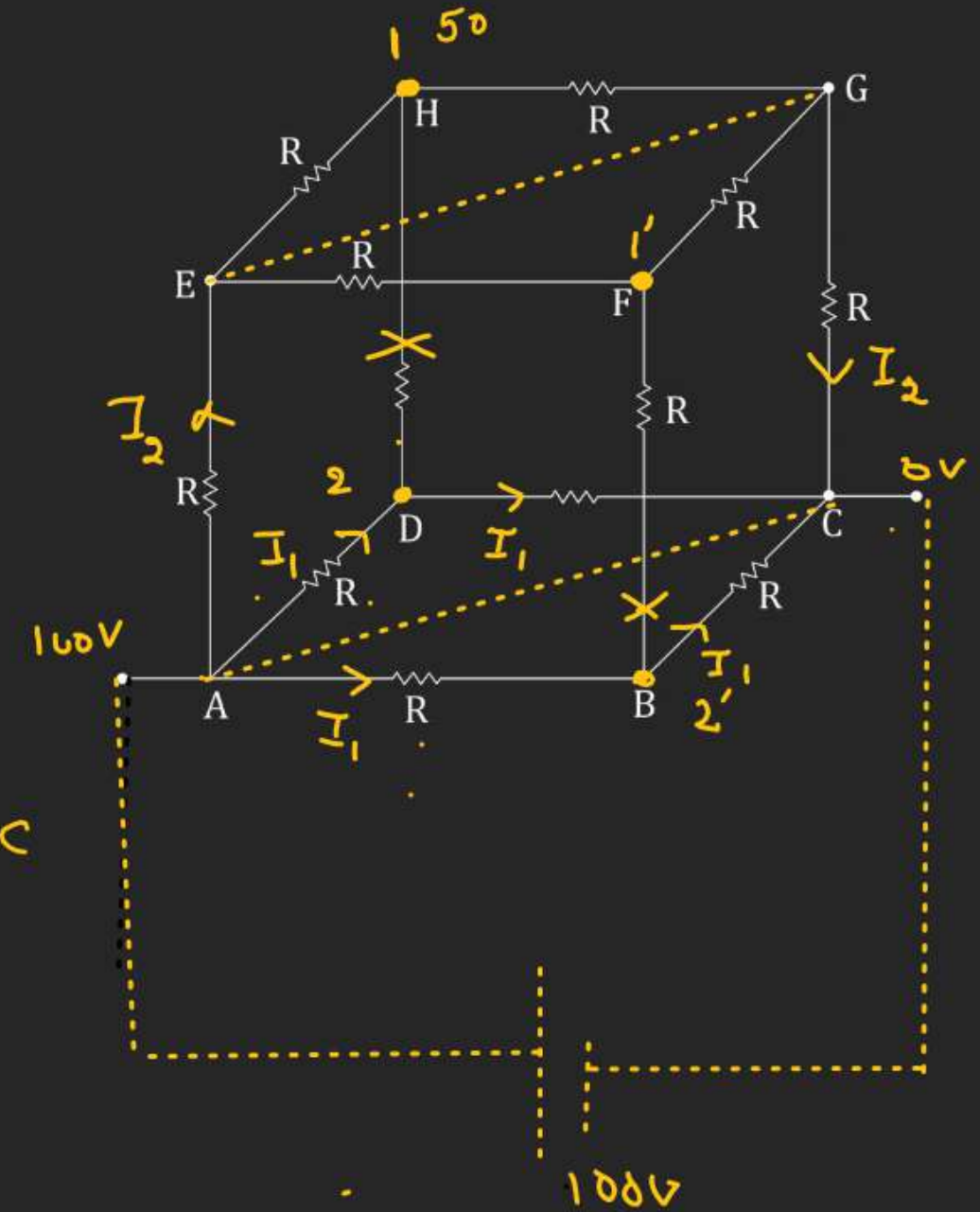
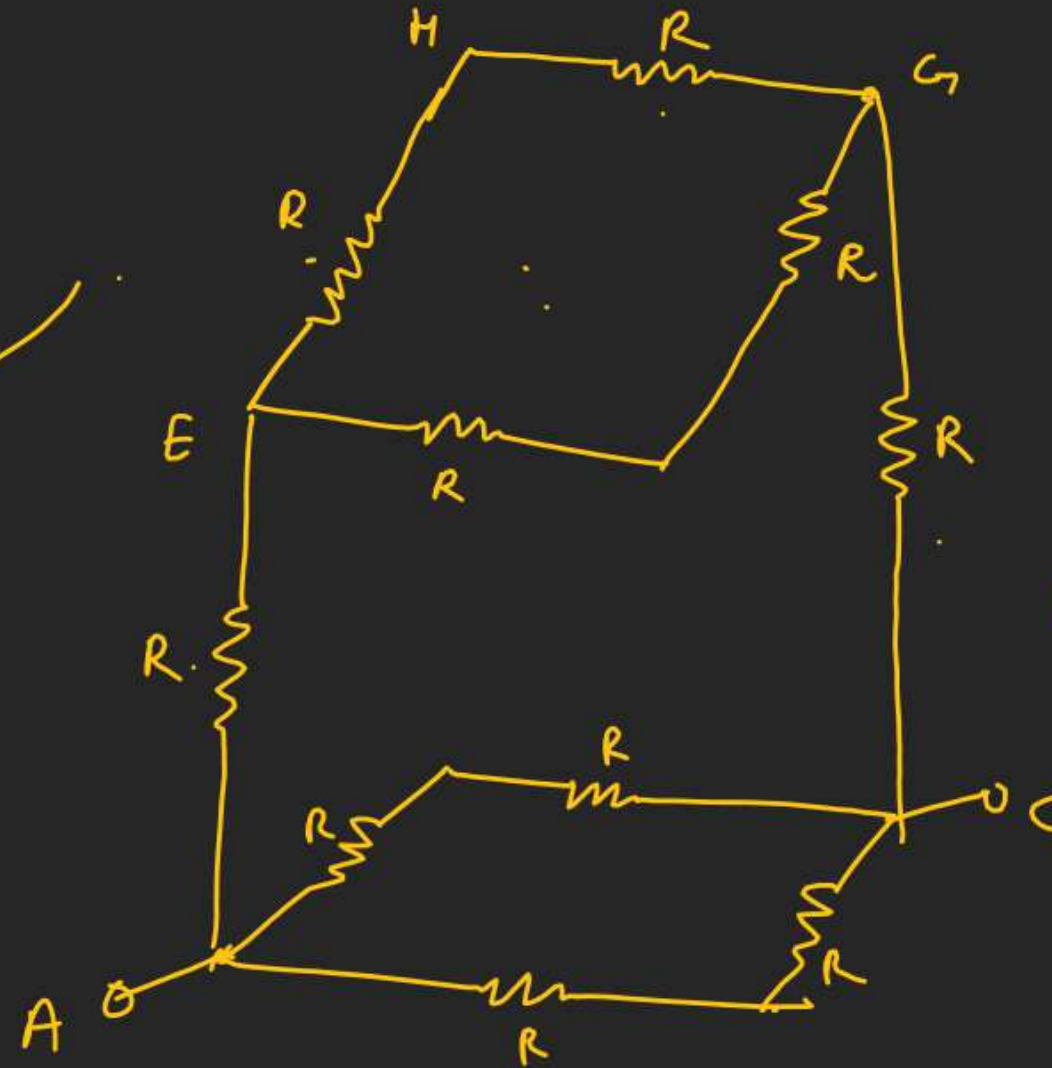


# CURRENT ELECTRICITY
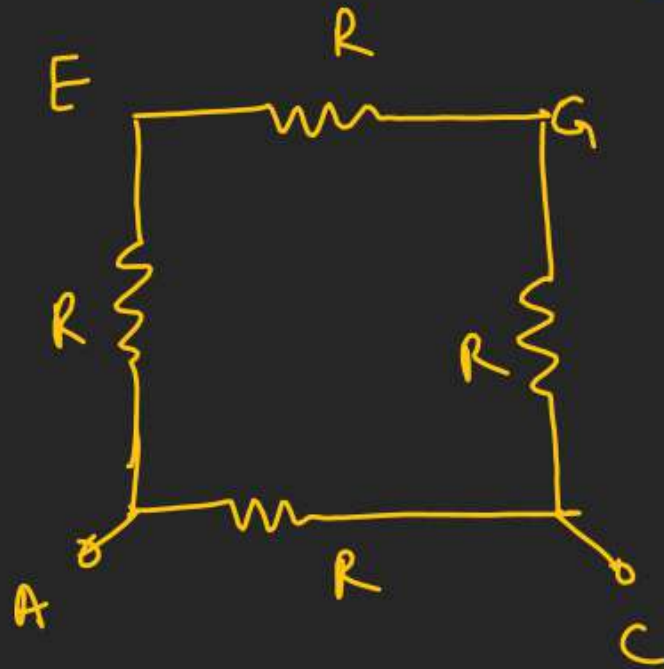
## Equivalent resistance by symmetry

$$(R_{eq})_{AB} = \frac{3R \cdot R}{3R + R} = \frac{(3R)}{4} \checkmark$$



$$V = I R_{eq} \Rightarrow R_{eq} = \frac{V}{I} = \left( \frac{100}{I} \right)$$

**Q.8** Find the equivalent resistance across the terminals A and B in the circuit shown in figure. Each resistance in circuit is R.

(Req) about edge??

For Node F

$$\frac{x-y}{R} + \frac{x-0}{R} + \frac{x-(100-x)}{R} = 0$$

$$4x - y = 100 \quad \text{--- (I)}$$

$$4x - \frac{6x}{5} = 100$$

$$14x = 500$$

$$x = \frac{500}{14} = \left( \frac{250}{7} \right) \text{ Volt}$$

For Node G

$$\frac{y-(100-y)}{R} + \frac{2(y-x)}{R} = 0$$

$$4y - 2x = 100 \quad \text{--- (II)}$$

$$4y - 2x = 4x - y$$

$$5y = 6x$$

$$y = \left( \frac{6x}{5} \right)$$


A+B

$$\frac{100-0}{R} + \left( \frac{x-0}{R} \right) \times 2 = I$$

$$\frac{100}{R} + \frac{2}{R} \times \frac{250}{7} = I$$

$$\frac{100}{R} + \frac{500}{7R} = I \Rightarrow \frac{100}{R} \left( 1 + \frac{5}{7} \right) = I \quad V$$
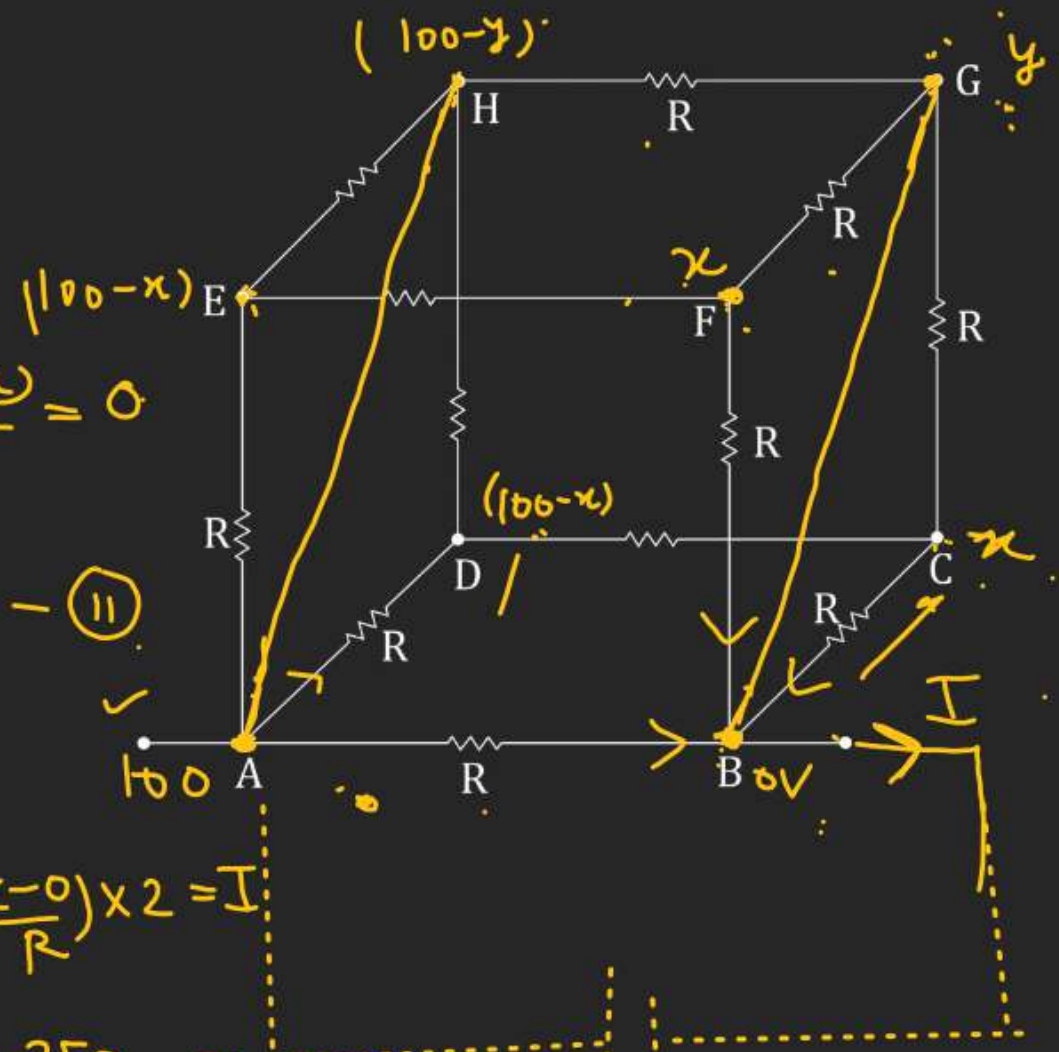
$$R_{eq} \leftarrow \left( \frac{100}{I} \right) = \left( \frac{7R}{12} \right) \quad \checkmark$$






## Equivalent resistance by symmetry

Case of infinite ladder

#

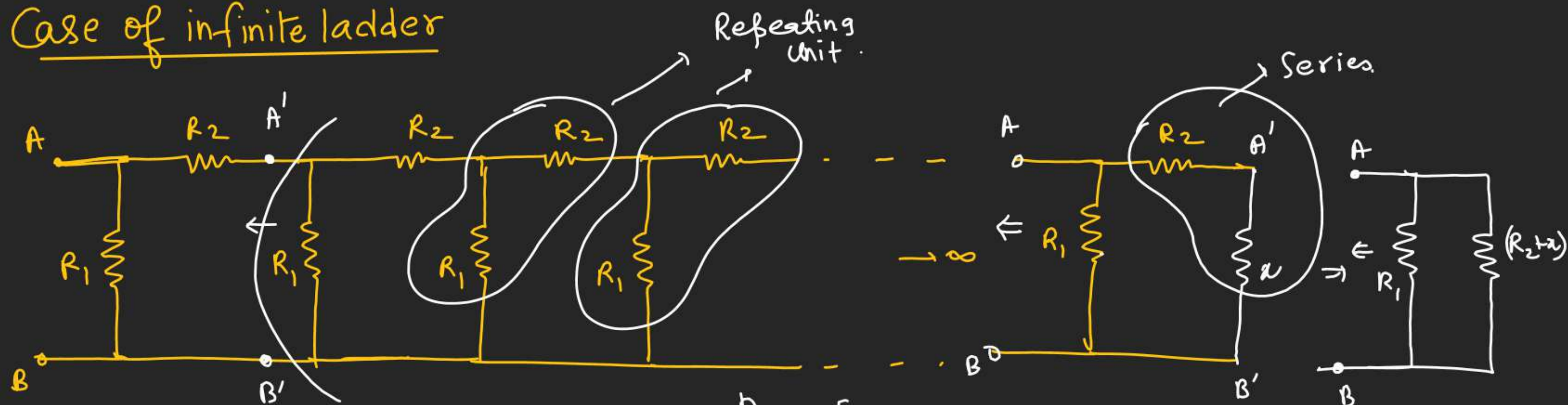

Since ladder is infinite

$$\text{So, } (R_{eq})_{A-B} = (R_{eq})_{A'B'} = x$$

$$R_{AB} \rightarrow [x = \frac{R_1(R_2+x)}{R_1+R_2+x}]$$

$$x(R_1+R_2)+x^2 = R_1R_2+R_1x$$

$$x^2 + R_2x - R_1R_2 = 0$$


$$x = \frac{-R_2 \pm \sqrt{R_2^2 + 4R_1R_2}}{2}$$

$$x = \frac{-R_2 + \sqrt{R_2^2 + 4R_1R_2}}{2}$$

$$x = \frac{R_2}{2} \left[ -1 + \sqrt{1 + \frac{4R_1}{R_2}} \right]$$

## Equivalent resistance by symmetry

#

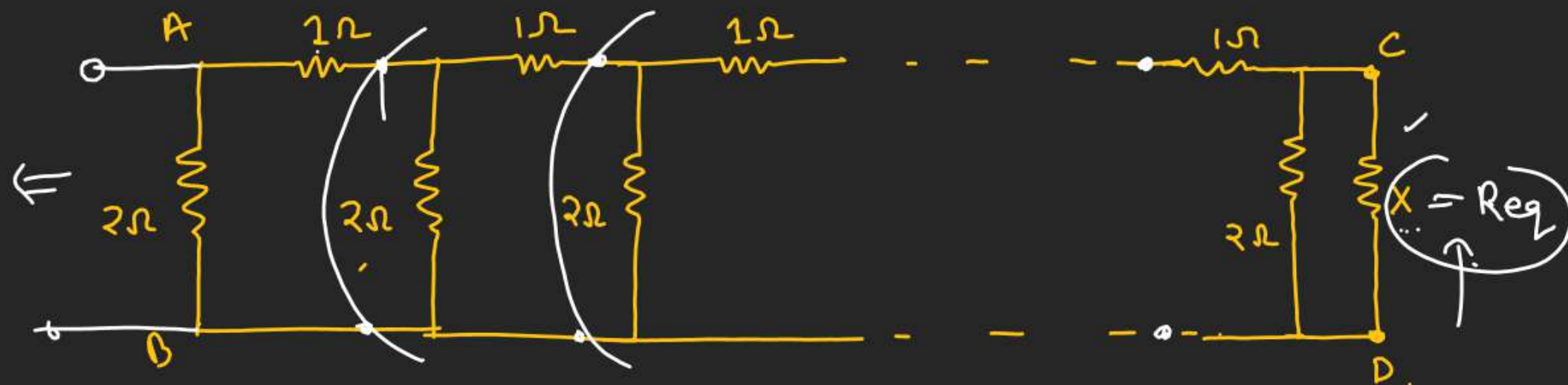

Find the value of 'x' so that Equivalent resistance of the Ckt is independent of the no of repeating sequence of the Ckt.

$$\Rightarrow x = (R_{eq}) = 1\Omega \checkmark$$



$$\frac{(1+x)2}{1+x+2} = x$$


$$2+2x = x(3+x)$$

$$2+2x = 3x+x^2$$

$$x^2 + x - 2 = 0$$




## Equivalent resistance by symmetry

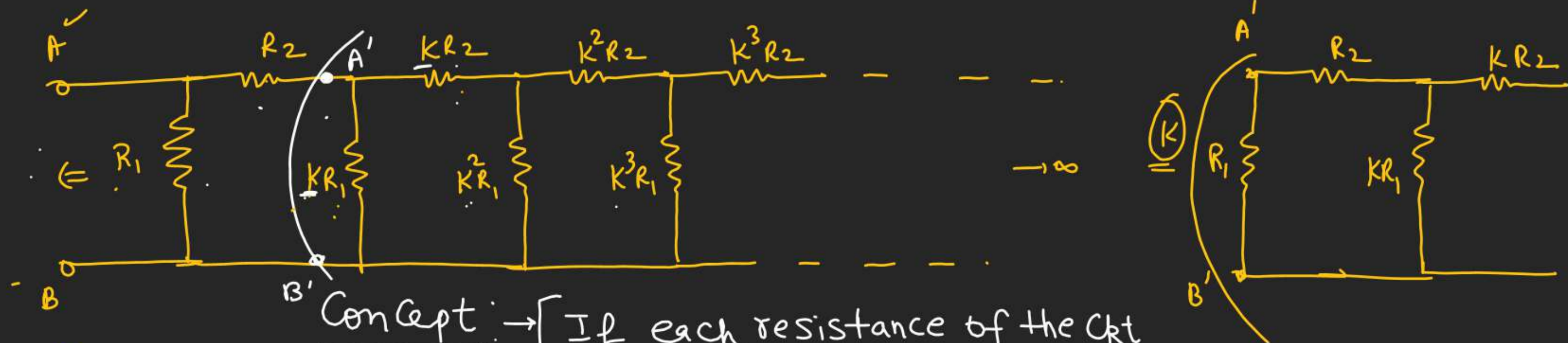

Concept → If each resistance of the Ckt is multiply by a constant 'k' then Equivalent resistance of the Ckt is also become 'k' times.

$$(R_{eq})_{AB} = ??$$
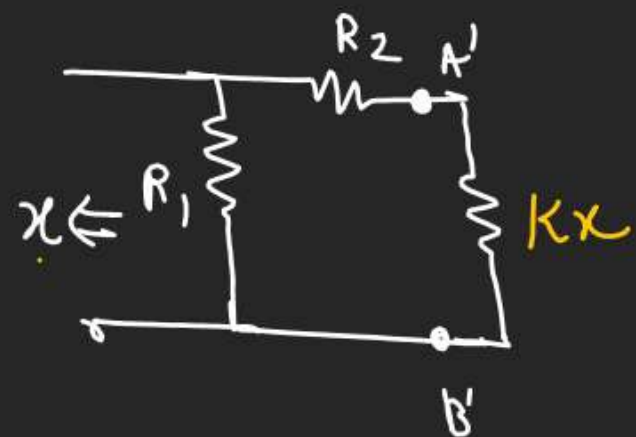
$$\begin{cases} (R_{eq})_{AB} = x \\ (R_{eq})_{A'B'} = Kx \end{cases}$$




$$x = \frac{(R_2 + Kx)R_1}{R_1 + R_2 + Kx}$$

Solve for  $K = \frac{1}{2}$  (given)

# CURRENT ELECTRICITY

## Equivalent resistance by symmetry

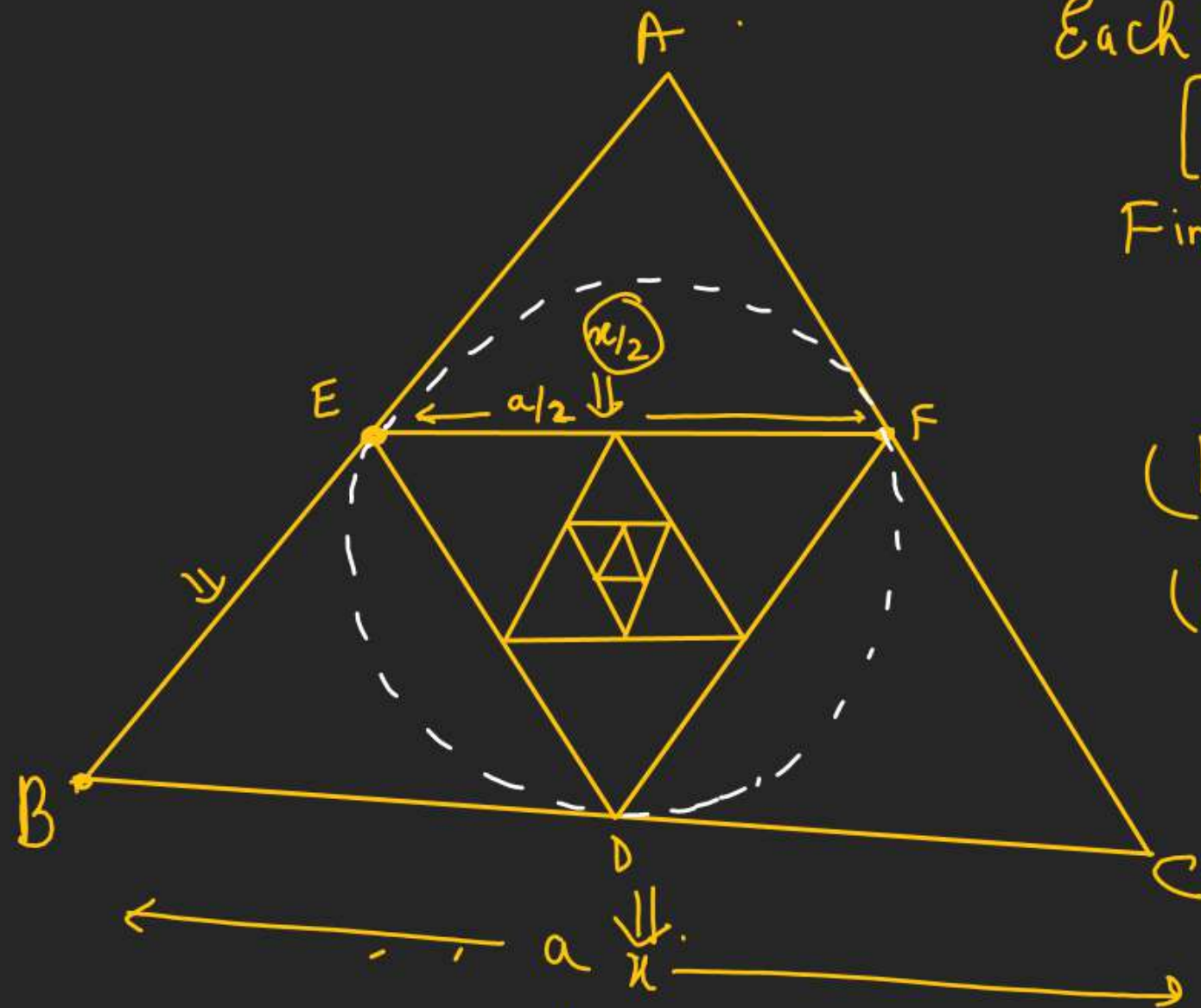

Each Side of the Successive triangle decreases by  $\frac{1}{2}$ .

$\triangle ABC \rightarrow$  Side length  $\rightarrow a$

$\triangle DEF \rightarrow$  Side length  $\rightarrow \frac{a}{2}$


Find Equivalent resistance about BC of the network.

$BC \rightarrow x$

$BD = DC = BE = CF = EA = AF = \frac{x}{2}$

$$(R_{eq})_{BC} = x$$


$$(R_{eq})_{EF} = \frac{x}{2}$$

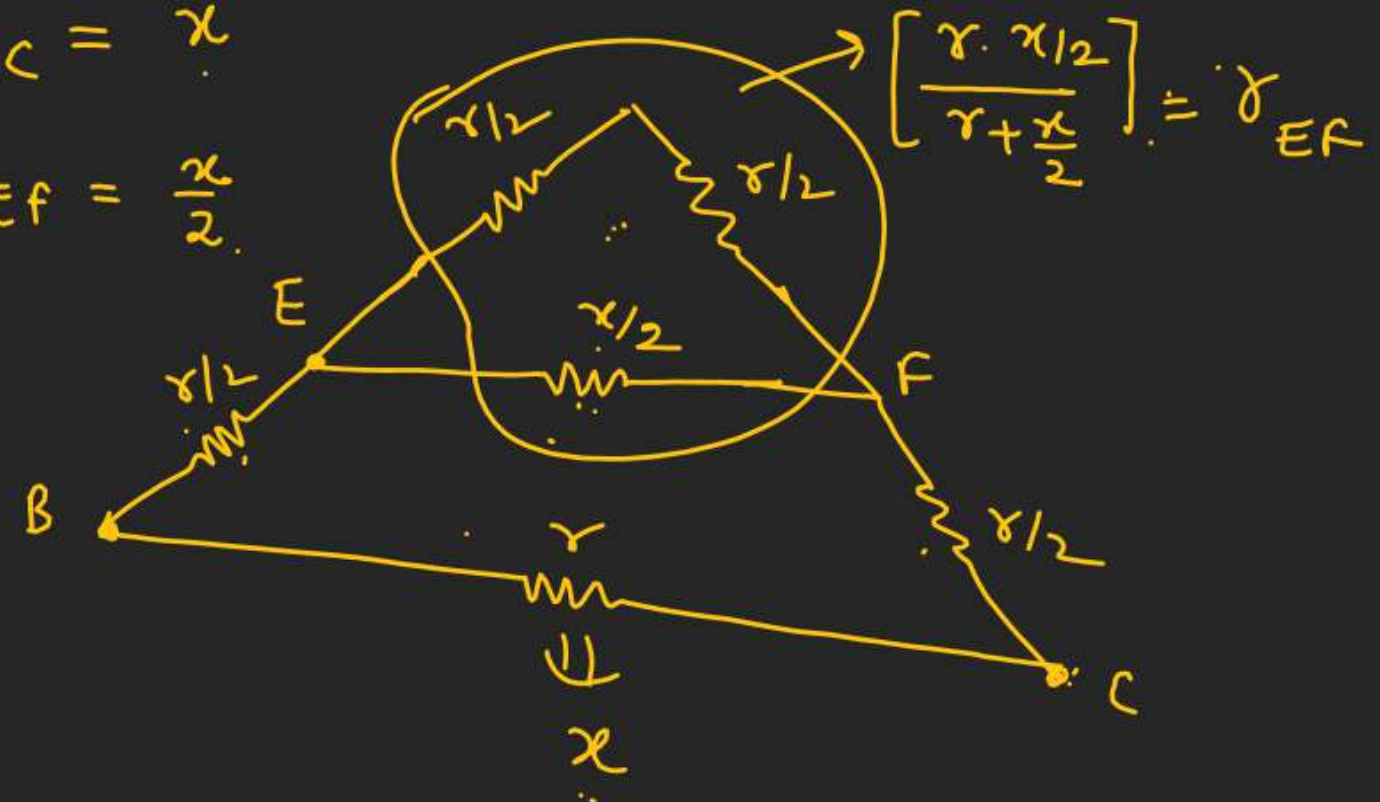

$$\left[ \frac{x \cdot \frac{x}{2}}{x + \frac{x}{2}} \right] = x_{EF}$$



## Equivalent resistance by symmetry

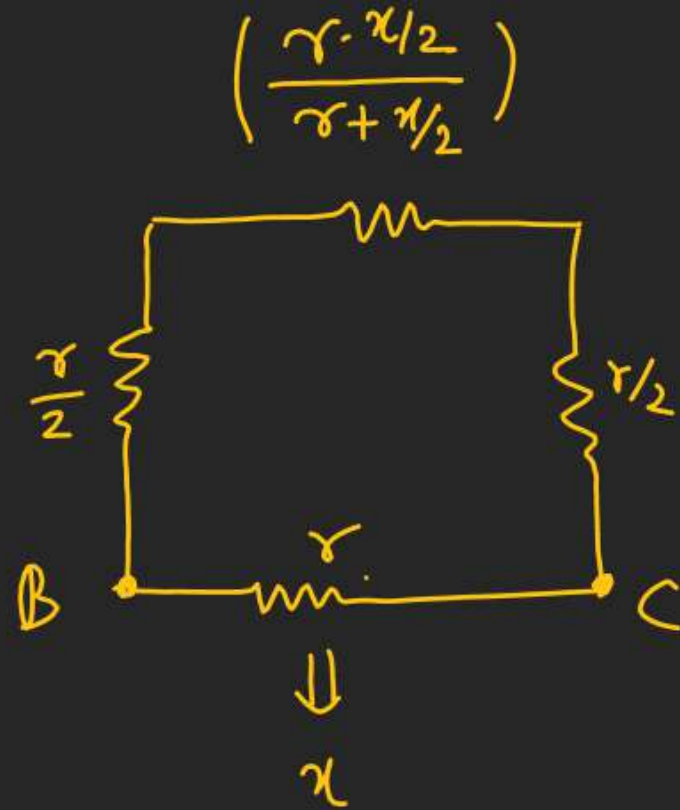

$$\Rightarrow \frac{\left[ \left[ \frac{r \cdot (x/2)}{r + \frac{x}{2}} \right] + r \right] r}{\left[ \frac{(r \cdot x/2)}{(r + x/2)} + r + r \right]} = x$$

Each wire has resistance 'r'.  
Find  $(R_{eq})_{AB} = ??$

