

## CURRENT ELECTRICITY


★★

$$\mathcal{E}_{eq} = \left[ \frac{\sum_{i=1}^n \mathcal{E}_i / r_i}{\sum_{i=1}^n \frac{1}{r_i}} \right]$$

If all the Cells are identical. having emf ' $\mathcal{E}$ ' and internal resistance ' $r$ '

$$\mathcal{E}_{eq} = \left( \frac{\frac{\mathcal{E}}{r} + \frac{\mathcal{E}}{r} + \dots + \frac{\mathcal{E}}{r}}{\frac{1}{r} + \frac{1}{r} + \dots + \frac{1}{r}} \right) \Rightarrow (\mathcal{E}_{eq} = \mathcal{E})$$
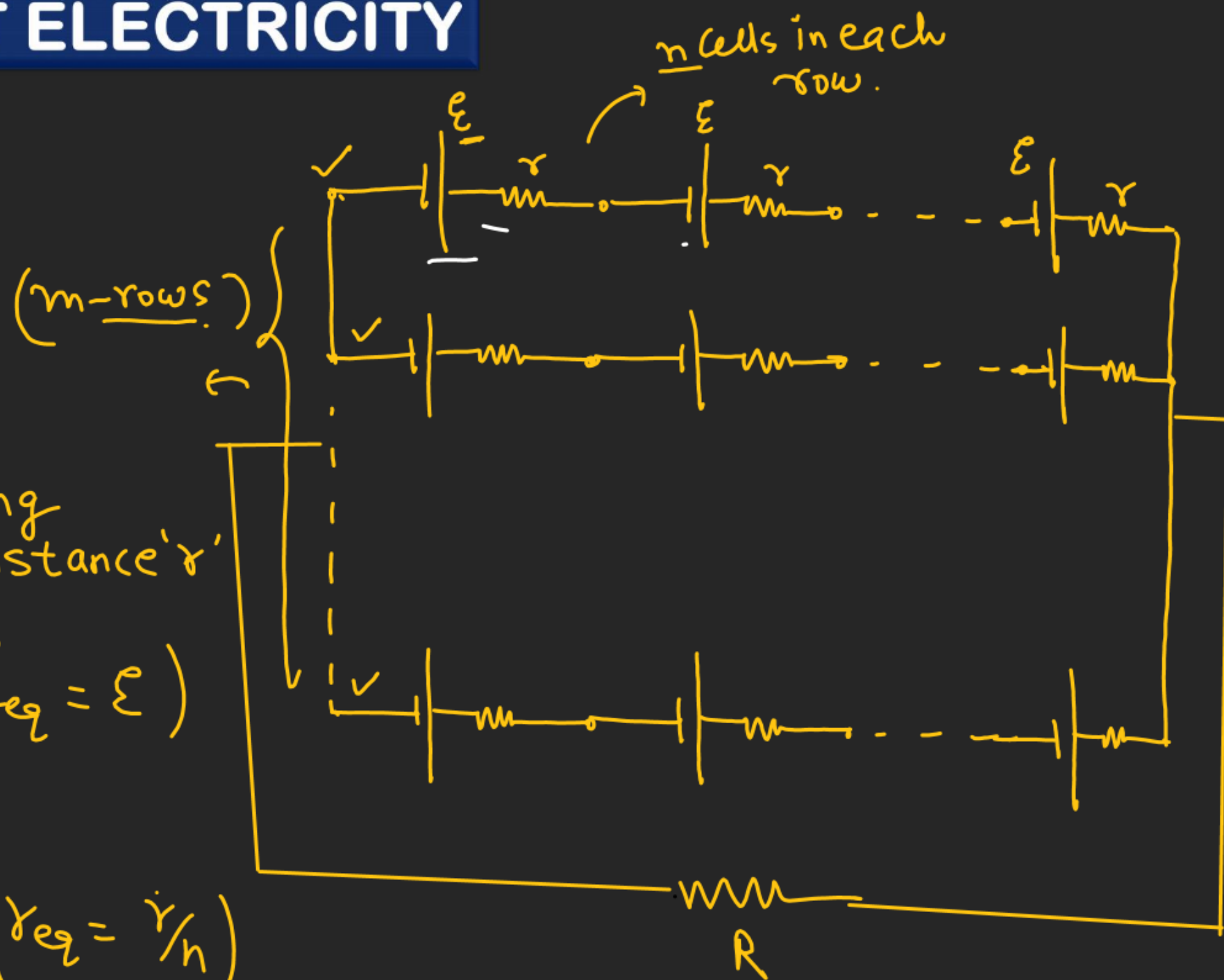
$$\frac{1}{r_{eq}} = \left( \frac{1}{r} + \frac{1}{r} + \dots + \frac{1}{r} \right) = \frac{n}{r} \Rightarrow (r_{eq} = r/n)$$



Q4.


Power:-

↳ It is rate of change of heat dissipated across the resistor w.r.t time

$$H = \underbrace{P}_{P=c} t = I^2 R t = \frac{V^2}{R} t$$

$$P = \left( \frac{dH}{dt} \right) \quad H = \text{heat dissipated}$$

↓  
inst.

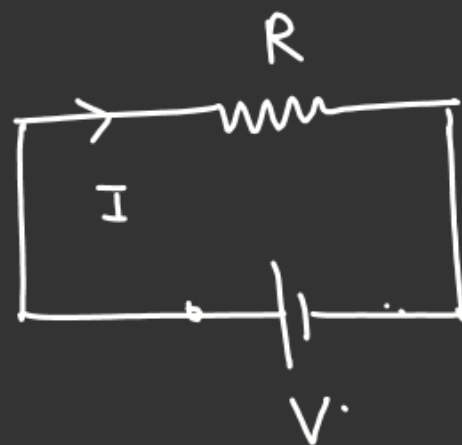

$$V = IR$$

$$P = I^2 R = \frac{V^2}{R}$$

$$(P_{avg}) = \left( \frac{\int_0^t P dt}{\int_0^t dt} \right)$$


$\int_0^t P dt = \text{Total heat in time 0 to } t$

# A Current flowing across the resistor is linearly decreases to zero from  $t=0$  to  $t=t_0$ .

If 'q' be the total charge flow in the interval  $t=0$  to  $t=t_0$ . Find total heat dissipated.

if R be the resistance of resistor.

Sol<sup>n</sup>

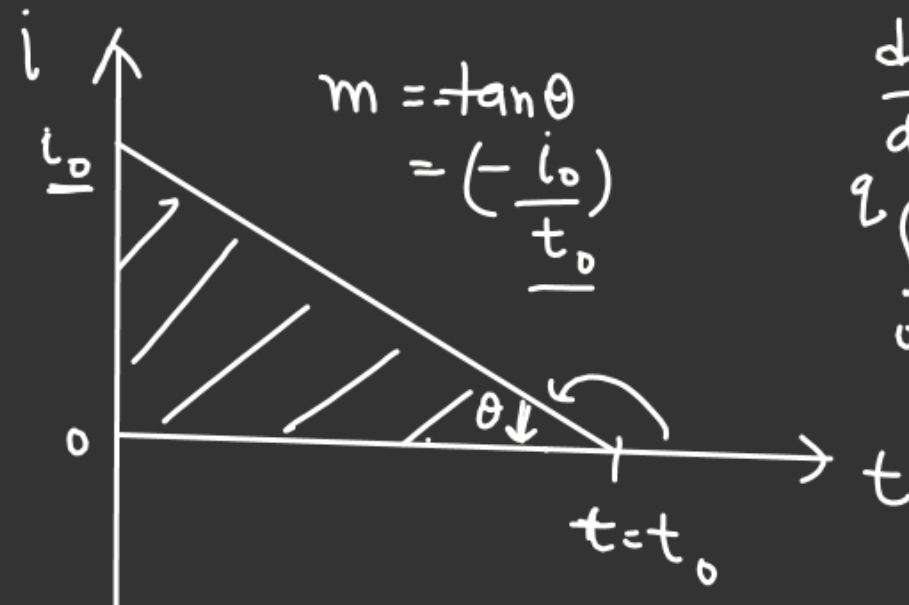

$$\frac{dq}{dt} = i$$

$$\int_0^{t_0} dq = \int_0^{t_0} i dt$$

Area under  $i$  vs  $t$  graph.

$$q = \frac{1}{2} t_0 \cdot i_0$$

$$i_0 = \left( \frac{2q}{t_0} \right) \leftarrow$$

$$i \rightarrow f(t)$$

$$i = \left( -\frac{i_0}{t_0} \right) t + i_0$$

$$P = i^2 R$$

$$P = \left[ i_0 - \left( \frac{i_0}{t_0} \right) t \right]^2 R$$

$$\frac{dH}{dt} = \left( i_0 - \left( \frac{i_0}{t_0} \right) t \right)^2 R$$

$$\frac{dH}{dt} = \left( l_0 - \left( \frac{l_0}{t_0} \right) t \right)^2 R$$

$$\int_0^{t_0} dH = R \int_0^{t_0} \left[ \left( l_0 - \left( \frac{l_0}{t_0} \right) t \right)^2 \right] dt$$

$$H = R \int_0^{t_0} \left( l_0^2 + \frac{l_0^2}{t_0^2} t^2 - 2 \frac{l_0^2}{t_0} t \right) dt$$


$$H = R \left[ l_0^2 \int_0^{t_0} dt + \frac{l_0^2}{t_0^2} \int_0^{t_0} t^2 dt - 2 \frac{l_0^2}{t_0} \int_0^{t_0} t dt \right]$$

$$H = R \left[ l_0^2 t_0 + \frac{l_0^2}{t_0^2} \times \frac{t_0^3}{3} - \cancel{\frac{2l_0^2}{t_0}} \times \cancel{\frac{t_0^2}{2}} \right]$$

$$H = R \left[ \cancel{l_0^2 t_0} + \frac{l_0^2 t_0}{3} - \cancel{l_0^2 t_0} \right]$$

$$H = \left( \frac{l_0^2 t_0 R}{3} \right) = \left( \frac{2q}{t_0} \right)^2 \times \frac{t_0 R}{3}$$
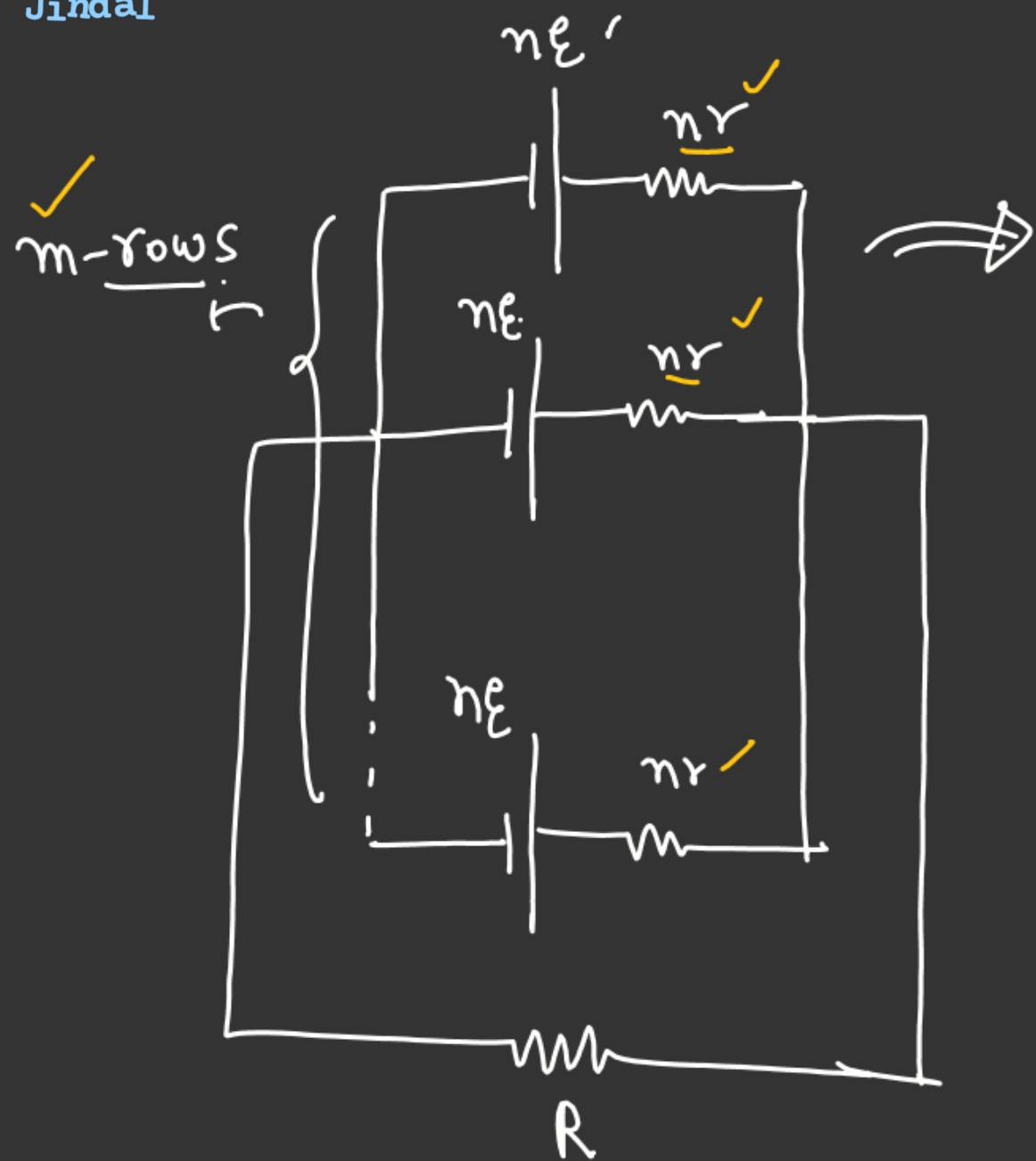
$$H = \left( \frac{4q^2 R}{3t_0} \right) \checkmark$$



$R \rightarrow$  (Load resistance)

$$I = \left( \frac{n\mathcal{E}}{R + \frac{nr}{m}} \right)$$


$$\frac{1}{r_{eq}} = \left( \frac{1}{nr} + \frac{1}{nr} + \dots + \frac{1}{nr} \right)$$

$\Downarrow$   
 $m\text{-times.}$

$$\frac{1}{r_{eq}} = \left( m \times \frac{1}{nr} \right)$$

$$r_{eq} = \left( \frac{nr}{m} \right)$$

⑧

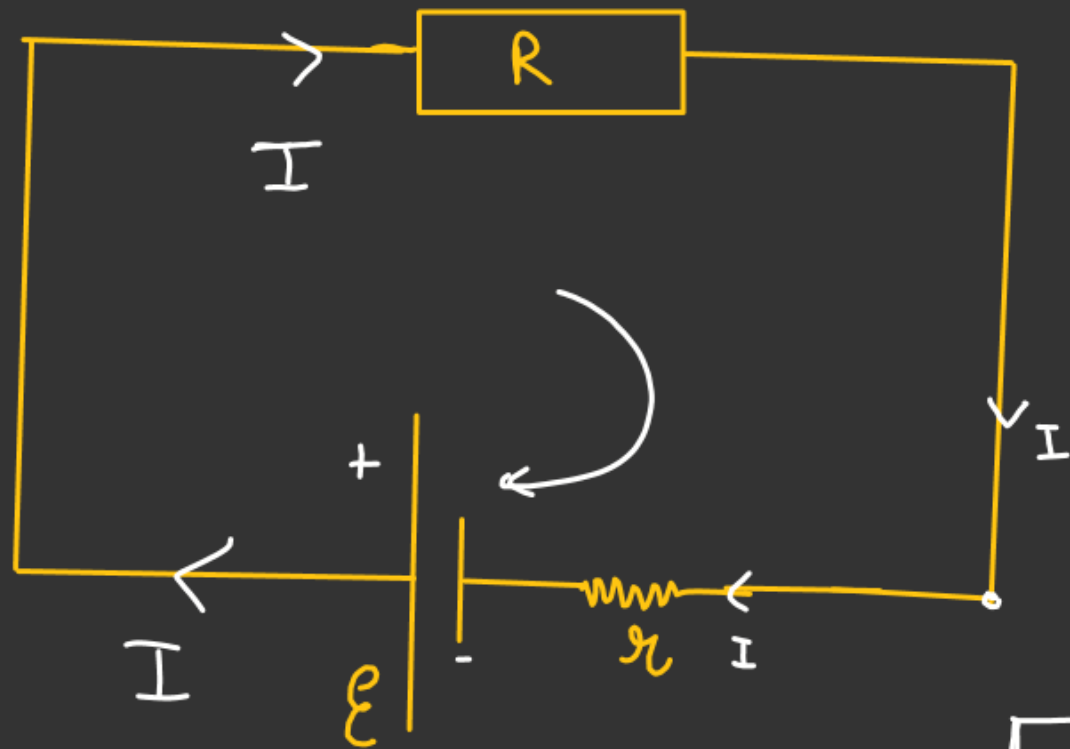Maximum power transfer theorem

$$-Ir + \varepsilon - IR = 0$$

$$I(R+r) = \varepsilon$$

$$I = \left( \frac{\varepsilon}{R+r} \right)$$

$$I = \left( \frac{\varepsilon}{R+r} \right)$$

$$P = I^2 R$$

$$P = \frac{\varepsilon^2 R}{(R+r)^2}$$

For P to be maximum  
Value of R = ??

$$\boxed{\frac{dP}{dR} = 0}$$

$$\varepsilon^2 \frac{d}{dR} \left[ \frac{R}{(R+r)^2} \right] = 0$$

$$\frac{\varepsilon^2 \left[ (R+r)^2 \frac{d(R)}{dR} - R \frac{d(R+r)^2}{dR} \right]}{((R+r)^2)^2} = 0$$

$$(R+r)^2(1) - R \{ 2(R+r) \} \frac{d(R+r)}{dR} = 0$$

$$(R+r)^2 - 2R(R+r) = 0$$

$$R+r = 2R$$

$$\boxed{R=r} \leftarrow$$




\*\*

[According to maximum power transfer theorem if load resistance is equal to internal resistance of battery then maximum power transferred].

⇒ Steps of maximum power transfer theorem

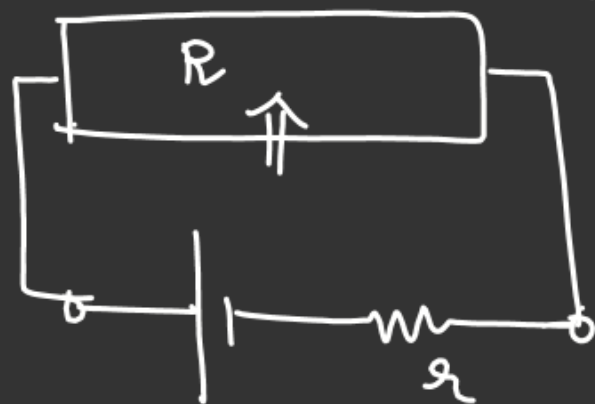- ① Find the equivalent resistance across the terminals of the battery.




$$\Rightarrow (R=r)$$

$$R = \frac{32}{8} \quad \Leftarrow \quad r = \frac{8R}{3}$$


Find  $R$  for (maximum power)

↓  
(For total ckt)

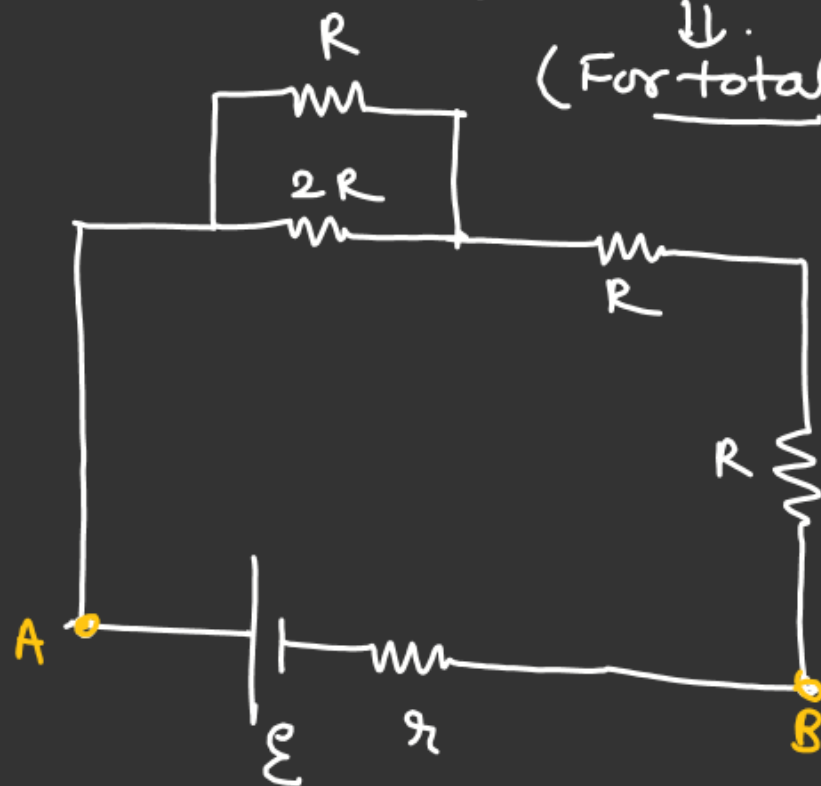

$$\Downarrow \quad (R_{eq})_{AB} = \left( \frac{R \cdot 2R}{R+2R} \right) + 2R = \frac{2R}{3} + 2R = \left( \frac{8R}{3} \right) \checkmark$$

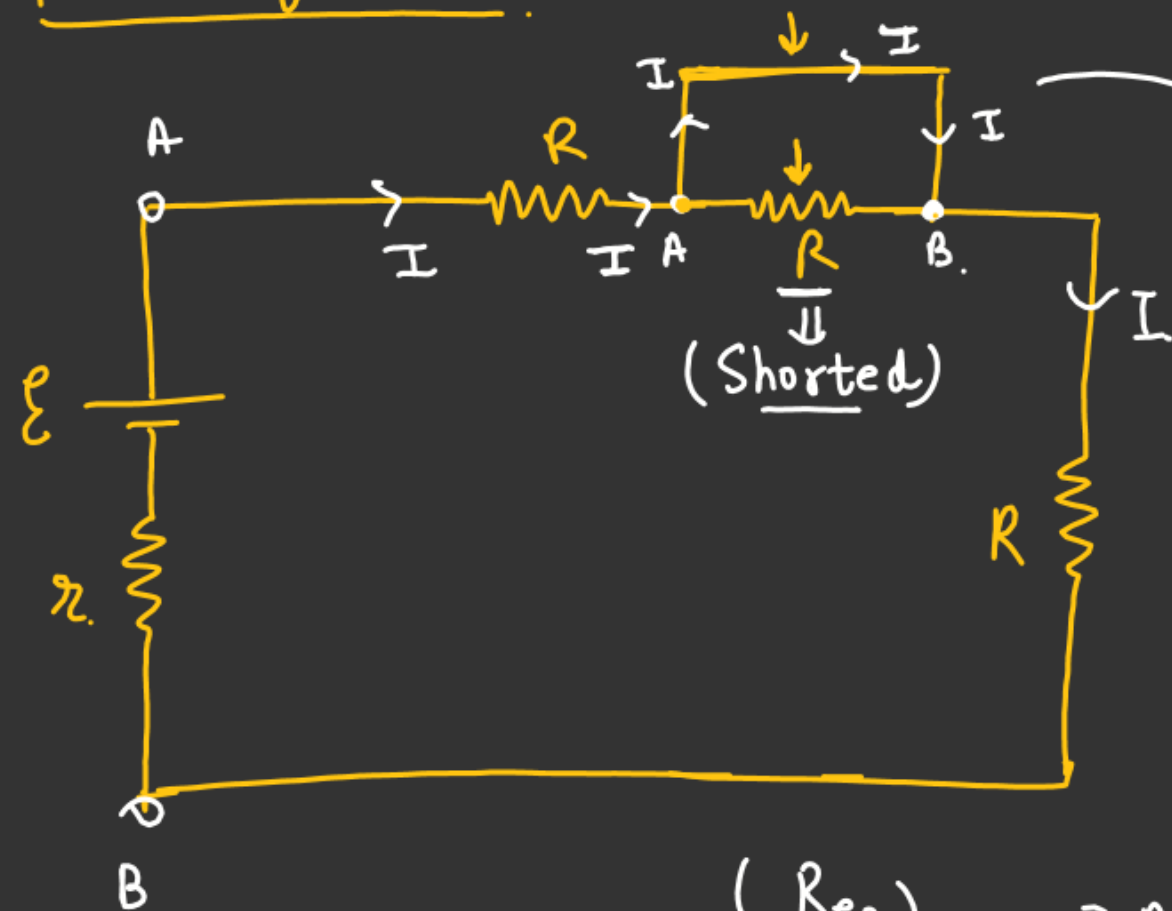Q. Find 'R' for  $P_{\max}$ . (Zero resistance wire).



( $R_{eq}$ )<sub>A-B</sub> =  $2R$ .  
For  $P_{\max}$

( $R_{eq}$ )<sub>A-B</sub> =  $r$ .


$2R = r$

$R = r/2$  ✓

Shorting:-

→ Current always prefer zero resistance path.

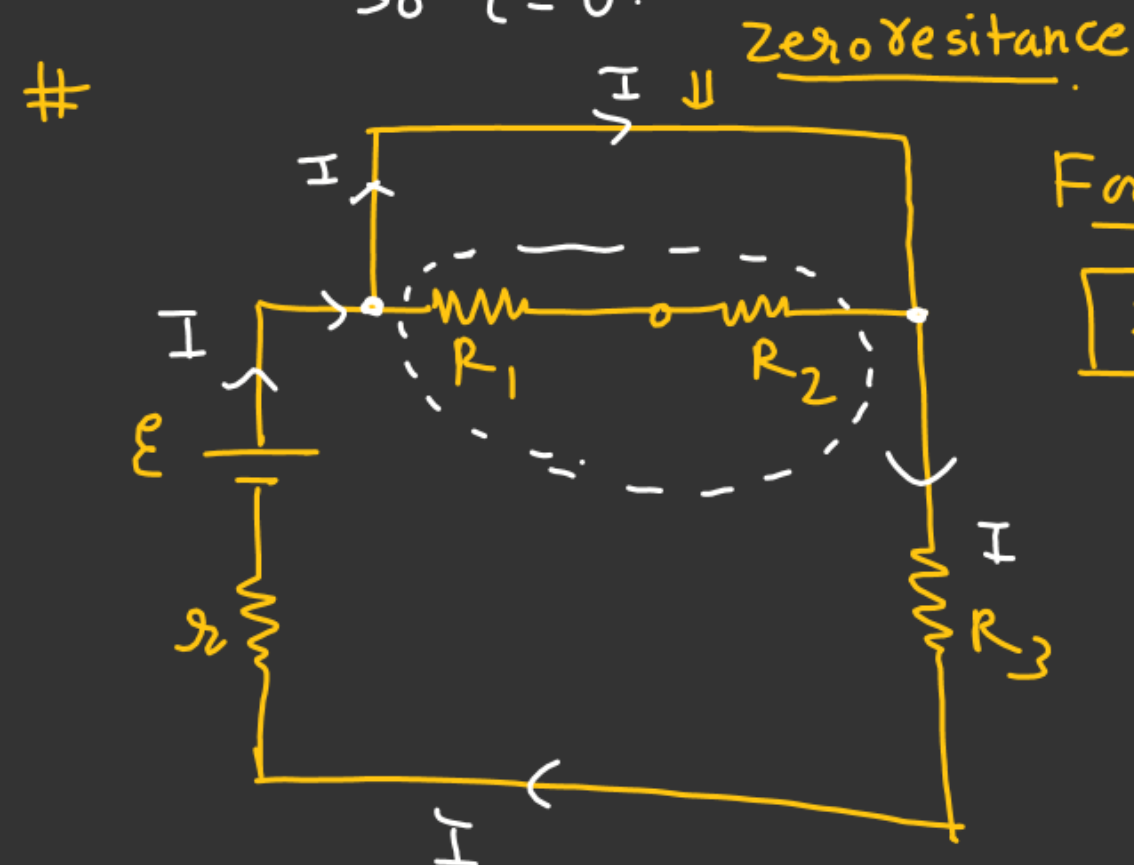→ ( $V_A = V_B$ ) ⇒ i.e. no potential difference across the resistor.  
So  $i = 0$ .




For  $P_{\max}$

$r = R_3$  ✓



#

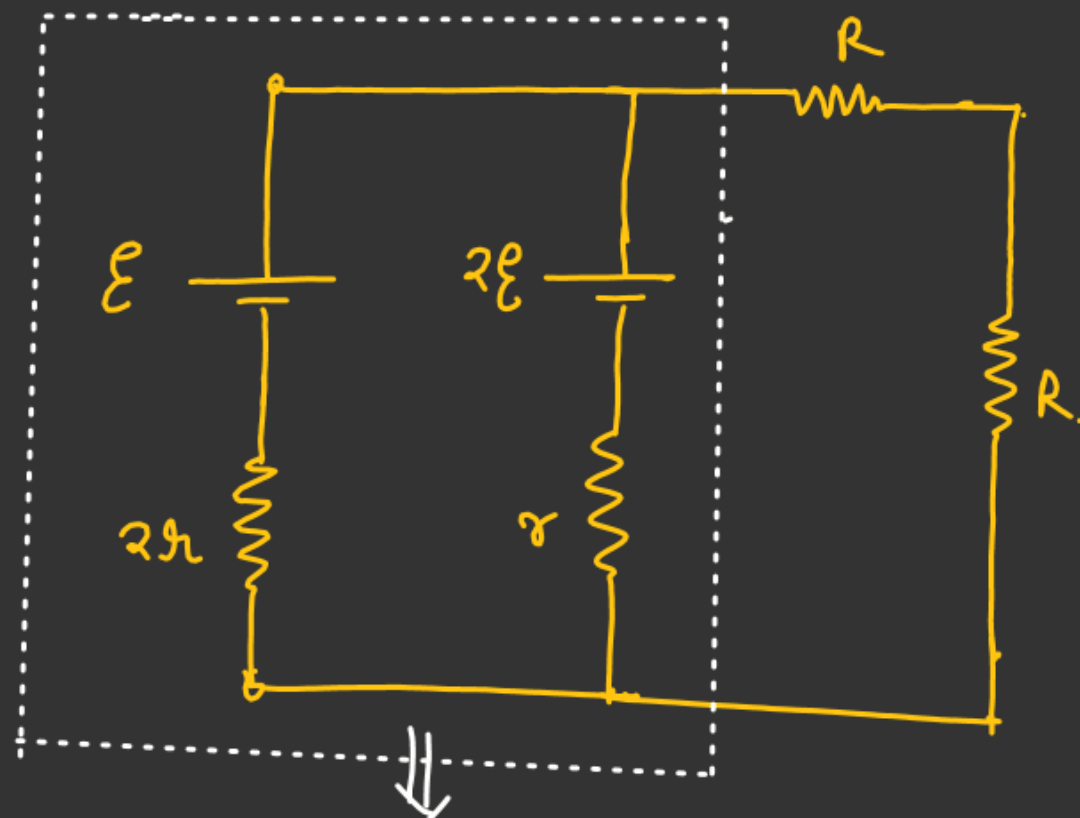
Find 'R' for  $P_{\max} = ??$ 

$$\mathcal{E}_{eq} = \left( \frac{\frac{\varepsilon}{2r} + \frac{2\varepsilon}{r}}{\frac{1}{2r} + \frac{1}{r}} \right) = \frac{\frac{5\varepsilon}{2r}}{\left( \frac{3}{2r} \right)} = \left( \frac{5\varepsilon}{3} \right)$$

$$\frac{1}{r_{eq}} = \frac{1}{2r} + \frac{1}{r}$$

$$\frac{1}{r_{eq}} = \frac{1+2}{2r} = \frac{3}{2r}$$

$$r_{eq} = \left( \frac{2r}{3} \right)$$

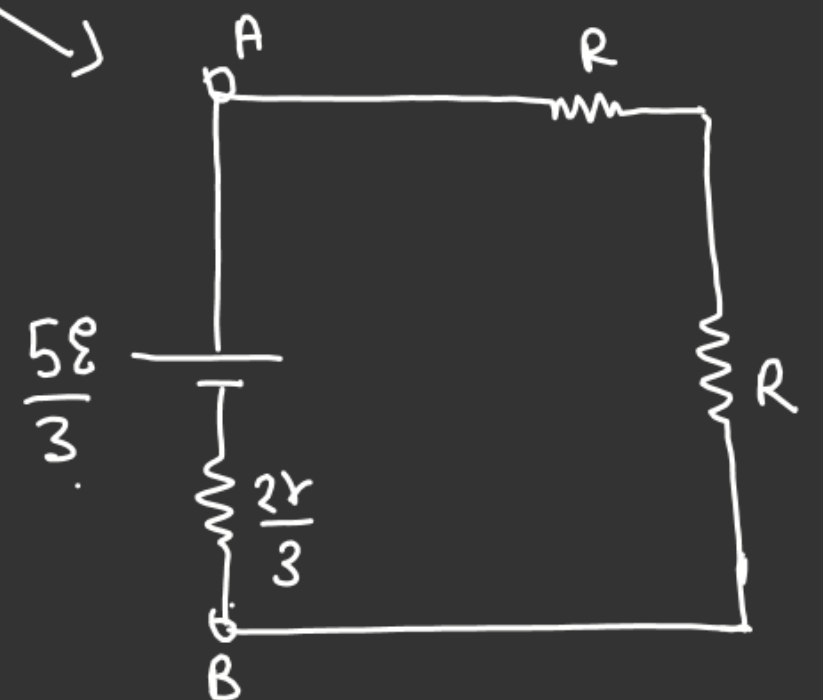

$$(R_{eq})_{AB} = 2R$$

For  $P_{\max}$

$$2R = \frac{2r}{3}$$

$$R = \frac{r}{3}$$


Q.1 A battery of internal resistance  $4\Omega$  is connected to the network of resistances as shown in the figure. In order that the maximum power can be delivered to the network, the value of  $R$  in  $\Omega$  should be

(A)  $4/9$

(B) 2

(C)  $8/3$

(D) 18

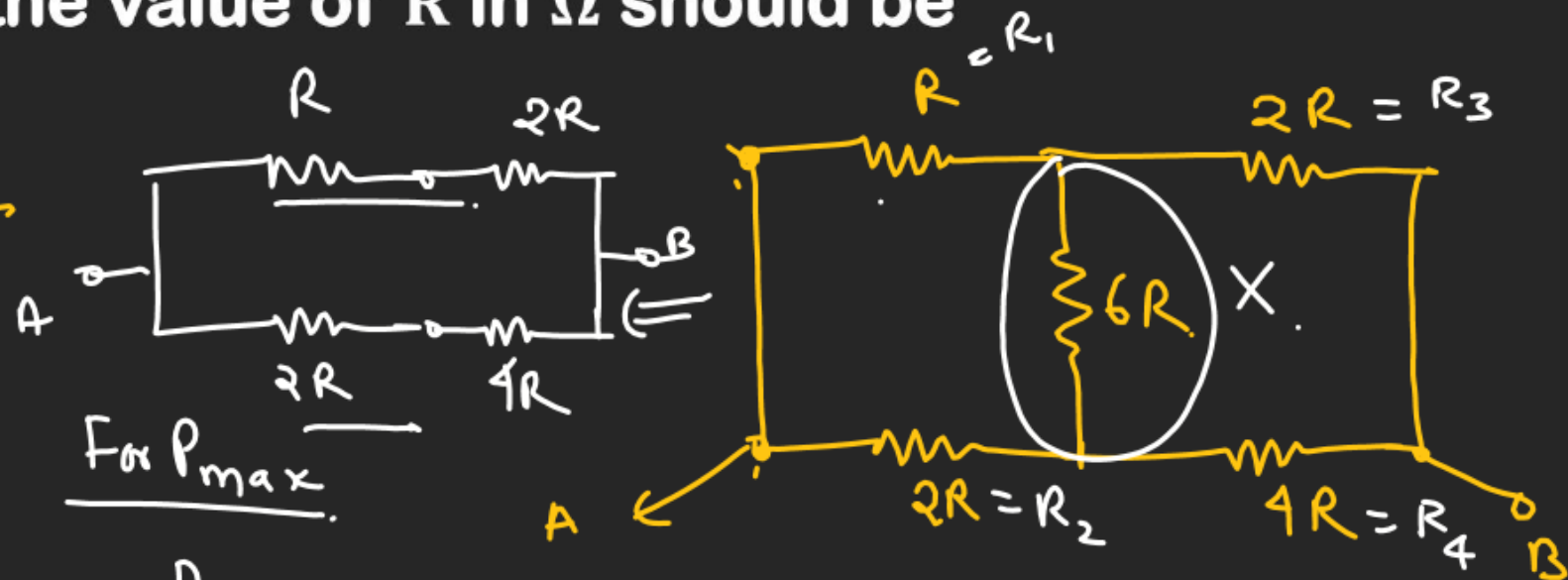


$$(R_{eq})_{A-B} = 4$$

$$2R = 4$$

$$R = 2$$


$$\frac{R_1}{R_2} = \frac{1}{2} \quad \frac{R_3}{R_4} = \frac{1}{2}$$
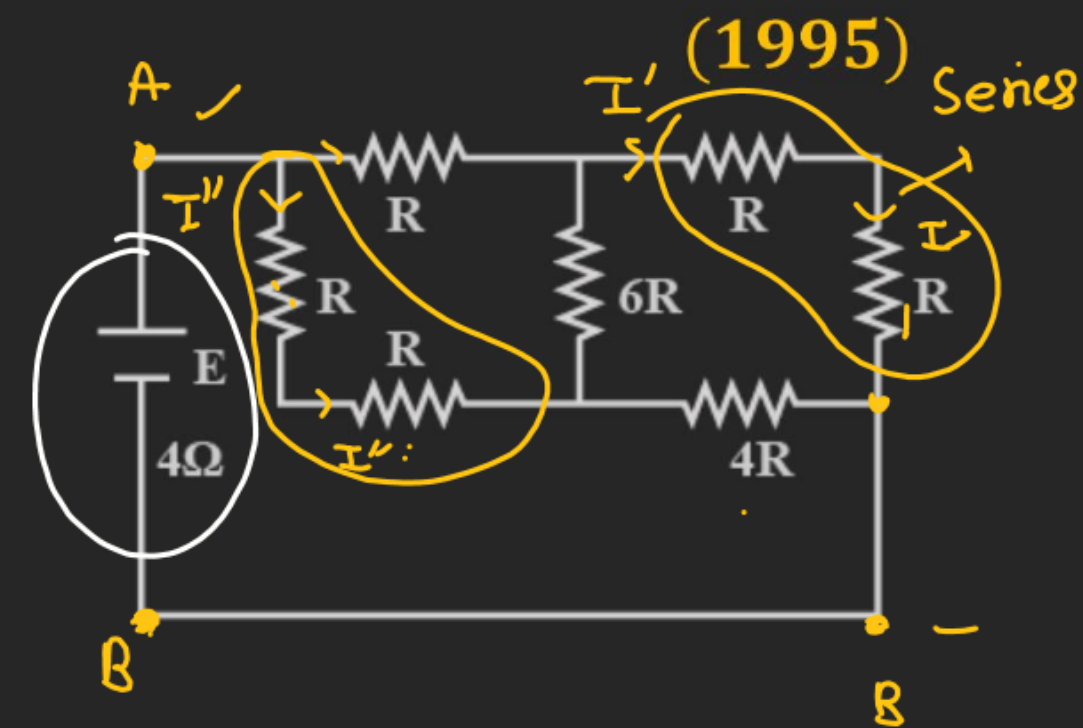
$$(R_{eq})_{A-B} = \frac{(3R)(6R)}{(3R+6R)} = \frac{18R^2}{9R} = 2R$$



**Q.2** Three resistance of equal value are arranged in the different combinations as shown below. Arrange them in increasing order of power dissipation.


*H.W*

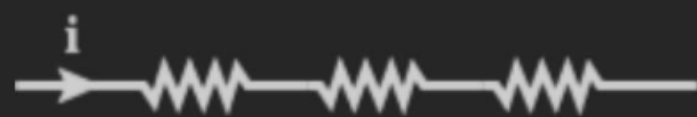


(I)



(II)

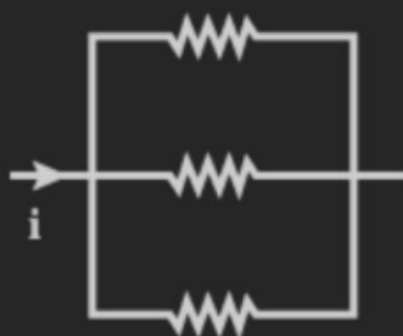

(III)

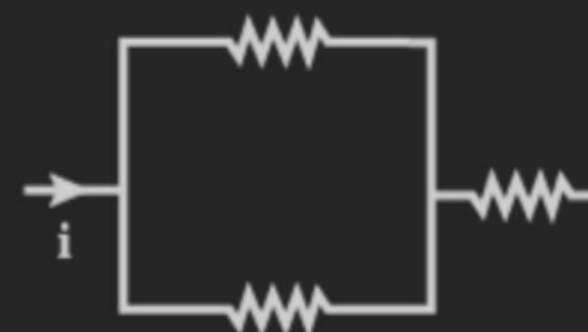


(IV)

Q.3 Six identical resistors are connected as shown in the figure. The equivalent resistance will be (2004)

H.W

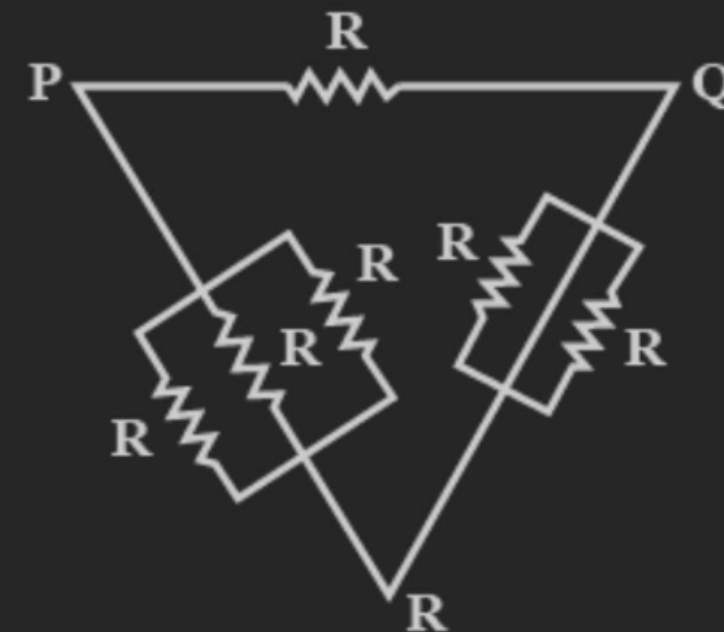- (A) maximum between P and R
- (B) maximum between Q and R
- (C) maximum between P and Q
- (D) all are equal.








**Q.4** Figure shows three resistor configurations  $R_1$  and  $R_2$  and  $R_3$  connected to 3 V battery. If the power dissipated by the configuration  $R_1$ ,  $R_2$  and  $R_3$  is  $P_1$ ,  $P_2$  and  $P_3$  respectively, then **(2008)**

(A)  $P_1 > P_2 > P_3$

(B)  $P_1 > P_3 > P_2$


(C)  $P_2 > P_1 > P_3$

(D)  $P_3 > P_2 > P_1$

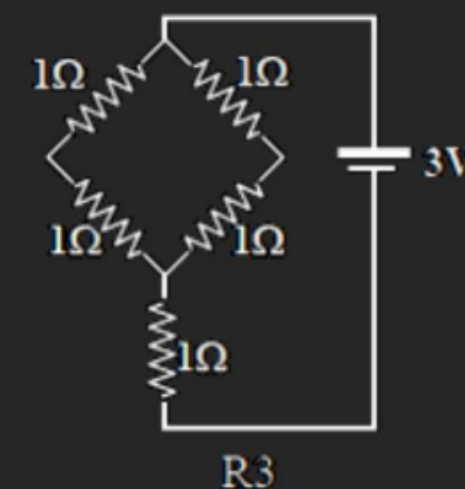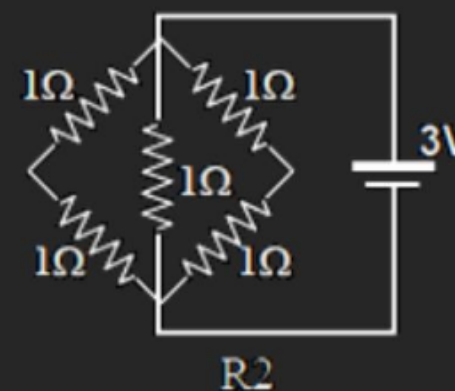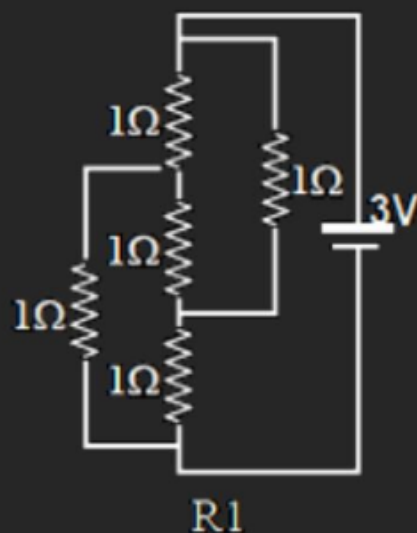

**Q.5** In circuit-1 and circuit-2 shown in the figures,  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$  and  $R_3 = 3\Omega$ .  $P_1$  and  $P_2$  are the power dissipations in circuit-1 and circuit-2 when the switches  $S_1$  and  $S_2$  are in open conditions, respectively.  $Q_1$  and  $Q_2$  are the power dissipations in circuit-1 and circuit-2 when the switches  $S_1$  and  $S_2$  are in closed conditions, respectively. Which of the following statement(s) is(are) correct?

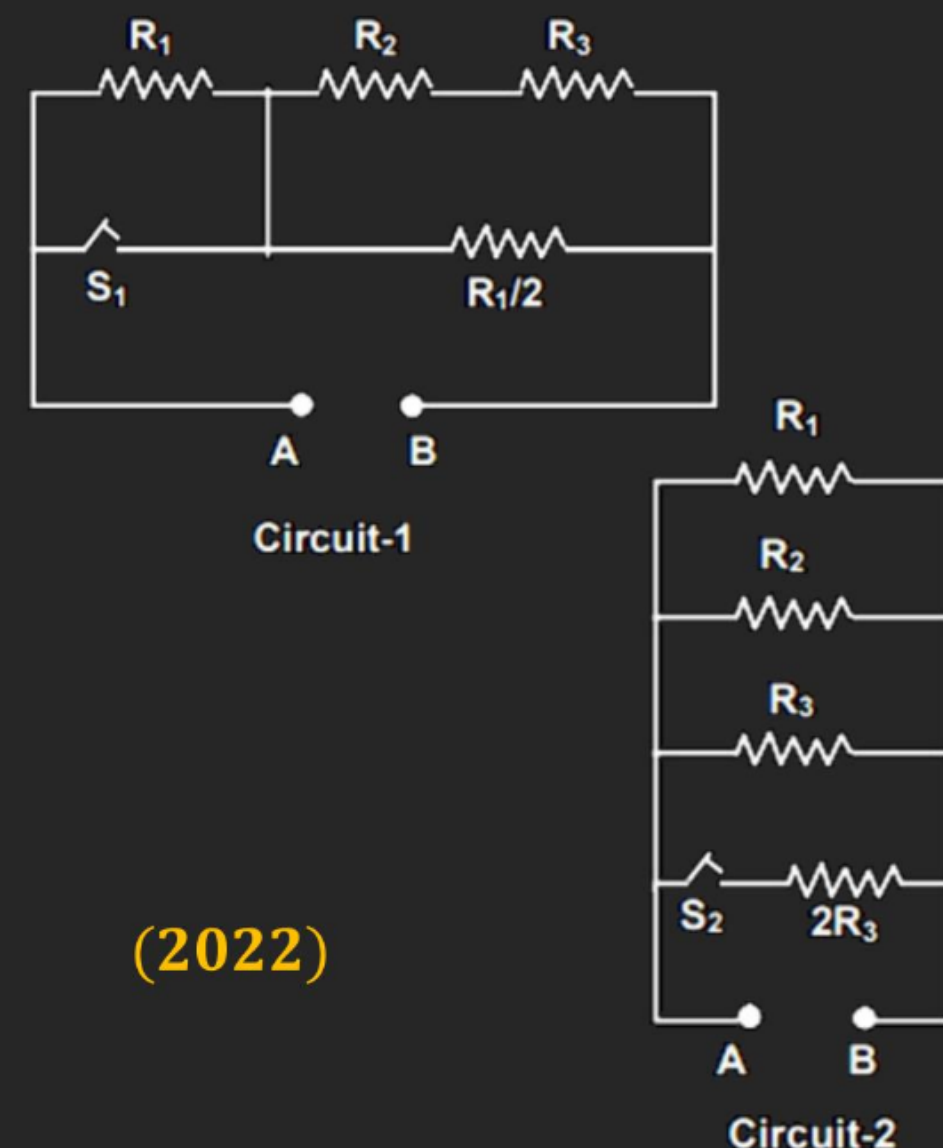- (A) When a voltage source of 6 V is connected across A and B in both circuits,  $P_1 < P_2$ .
- (B) When a constant current source of 2 amp is connected across A and B in both circuits,  $P_1 > P_2$
- (C) When a voltage source of 6 V is connected across A and B in Circuit-1,  $Q_1 > P_1$ .
- (D) When a constant current source of 2 amp is connected across A and B in both circuits,  $Q_2 < Q_1$ .



(2022)