


Link to View Video Solution:  [Click Here](#)

1.  $\lambda = 960 \text{ m}; C = 256 \mu\text{F}$

At resonance,  $\omega_0 = \frac{1}{\sqrt{LC}}$

Squaring both sides,  $\frac{4\pi^2 c^2}{\lambda^2} = \frac{1}{LC}$

$$\Rightarrow \frac{4 \times 10 \times (3 \times 10^8)^2}{(960)^2} = \frac{1}{L \times 2.56 \times 10^{-6}}$$

$$\Rightarrow L = 10 \times 10^{-8} \text{ H}$$

2.  $R = 5 \Omega, L = 20 \text{ mH}$

$C = 0.5 \mu\text{F}; V_{\text{rms}} = 250 \text{ V}$


At resonance,  $I_{\text{rms}} = \frac{V_{\text{rms}}}{R}$  as  $R = Z$

$$\text{Power} = \frac{V_{\text{rms}}^2}{R} = \frac{250 \times 250}{5} = 125 \times 10^2 \text{ W}$$

3.  $\omega = 300 \text{ rad s}^{-1}; \phi = 45^\circ$

$C = \frac{1}{x} \times 10^{-3} \text{ F}; L = 30 \text{ mH}, R = 1 \Omega$

When current leads

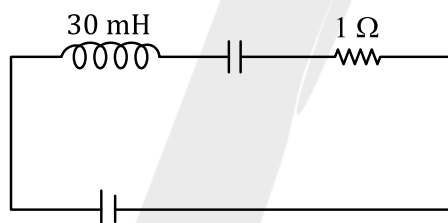

$$\tan \phi = \frac{X_C - X_L}{R}; R = X_C - X_L$$

$$1 = \frac{1}{\omega C} - \omega L; 1 = \frac{1}{300C} - 30 \times 10^{-3} \times 300$$

$$\Rightarrow C = \frac{1}{3} \times 10^{-3} \text{ F}$$

4. Given:  $L = 100 \text{ mH},$

$C = 100 \mu\text{F}, R = 10 \Omega, V = 220 \text{ V}, f = 50 \text{ Hz}$

$$X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 100 \times 10^{-3} = 31.4 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 100 \times 10^{-6}} = 31.85 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Link to View Video Solution: [Click Here](#)

$$Z = \sqrt{10^2 + (31.85 - 31.4)^2} = 10\Omega$$

$$\text{So, } i = \frac{V}{Z} = \frac{220}{10} = 22 \text{ A}$$

5. Here,  $\omega = 100 \text{ rad/s}$ ,  $L = 0.5 \text{ H}$ ,

$$C = 100 \mu\text{F}, V = 20 \text{ V}$$

$$\therefore X_L = \omega L = 100 \times 0.5 = 50\Omega$$


$$X_C = \frac{1}{\omega C} = \frac{1}{100 \times 100 \times 10^{-6}} = 100\Omega$$

Impedance across capacitor,

$$Z_1 = \sqrt{R^2 + X_C^2} = \sqrt{(100)^2 + (100)^2}$$

$$Z_1 = 100\sqrt{2}\Omega \therefore I_1 = \frac{20}{100\sqrt{2}} = \frac{1}{5\sqrt{2}} \text{ A}$$

Voltage across  $100\Omega$

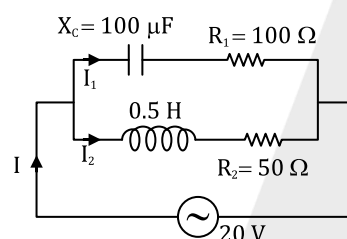

$$V = I_1 = 100 = \frac{1}{5\sqrt{2}} \times 100 = 10\sqrt{2} \text{ V}$$

Impedance across inductance,

$$Z_2 = \sqrt{R^2 + (X_L)^2} = \sqrt{(50)^2 + (50)^2}$$

$$Z_2 = 50\sqrt{2}\Omega \therefore \frac{20}{50\sqrt{2}} = \frac{2}{5\sqrt{2}} = \frac{\sqrt{2}}{5}$$

$$\text{Now voltage across } 50\Omega = \frac{\sqrt{2}}{5} \times 50 = 10\sqrt{2}$$


$$I_1 = \frac{1}{5\sqrt{2}} \text{ A at } 45^\circ \text{ leading}$$

$$I_2 = \frac{\sqrt{2}}{5} \text{ A at } 45^\circ \text{ leading}$$

$\therefore$  Current through circuit

$$I_{\text{net}} = \sqrt{I_1^2 + I_2^2} = 0.3 \text{ A}$$

6. (A)


Link to View Video Solution:  [Click Here](#)

7. Since power factor has to be made 1.

$\therefore$  Effective capacitance should be increased thus connecting in parallel.

$$\therefore \cos \phi = 1 \therefore \phi = 0$$

$$I\omega L = \frac{I}{\omega(C + C')}$$

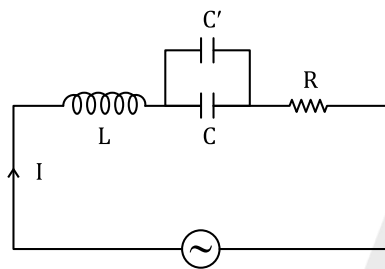

$$\text{or } C + C' = \frac{1}{\omega^2 L} \therefore C' = \frac{1}{\omega^2 L} - C$$

$$\therefore C' = \frac{1 - \omega^2 LC}{\omega^2 L} \text{ in parallel}$$

8. For current  $I_1$ ,

$$\tan \phi = \frac{X_L}{R_1} = \frac{\omega L}{R_1} = \frac{100 \times \frac{\sqrt{3}}{10}}{10} = \sqrt{3}$$

$$\phi = 60^\circ; V \text{ leads } I_1$$

For current  $I_2$ ,

$$\tan \phi' = \frac{X_C}{R_2} = \frac{1}{\omega C R_2} = \frac{1}{100 \times \frac{\sqrt{3}}{2} \times 10^{-6} \times 20}$$

$$= \frac{1000}{\sqrt{3}} \cdot \phi' \simeq 90^\circ; V \text{ lags } I_2.$$

The required phase difference between  $I_1$  and  $I_2$  is,  $\phi + \phi' = 60^\circ + 90^\circ = 150^\circ$


\* None of the given options is correct.

9. Given:  $R = 100 \Omega$ ,  $C = 2 \mu\text{F}$ ,

$$L = 80\text{mH}$$

$$\text{Quality factor, } Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{100} \sqrt{\frac{80 \times 10^{-3}}{2 \times 10^{-6}}}$$

$$Q = \frac{1}{10^2} \times \frac{1}{10^{-2}} \sqrt{4} = 2$$

Link to View Video Solution:  [Click Here](#)

10. For series LR circuit, power factor is,  $\cos\phi = \frac{R}{\sqrt{R^2 + X_L^2}}$

When  $X_L = R$ , power factor,


$$P_1 = \frac{R}{\sqrt{R^2 + R^2}} = \frac{1}{\sqrt{2}}$$

For a series LCR circuit, power factor is,

$$\cos\phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

When  $X_L = X_C$ , power factor,  $P_1 = \frac{R}{\sqrt{R^2}}$
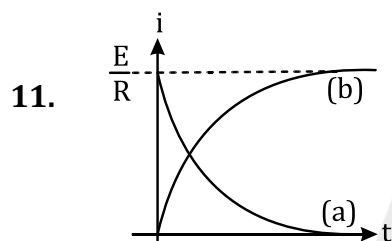
$$\therefore P_2 = 1; \therefore \frac{P_1}{P_2} = \frac{1}{\sqrt{2}}$$



For RC circuit,  $i = \frac{E}{R} e^{-t/RC}$

For RL circuit,  $i = \frac{E}{R} (e^{-t(R/L)})$