

## (\*) Growth of Current in R.C Ckt

Initially Capacitor is uncharged

At  $t=0$ , SW is closed. ✓

When SW Closed:-

When SW closed, Charging of Capacitor start.



At  $t=t$ , let, Charge on the Capacitor is  $q$ .

During Charging of Capacitor

$$I = (+dq/dt)$$

K.V.L.

$$V - \frac{q}{C} - IR = 0$$

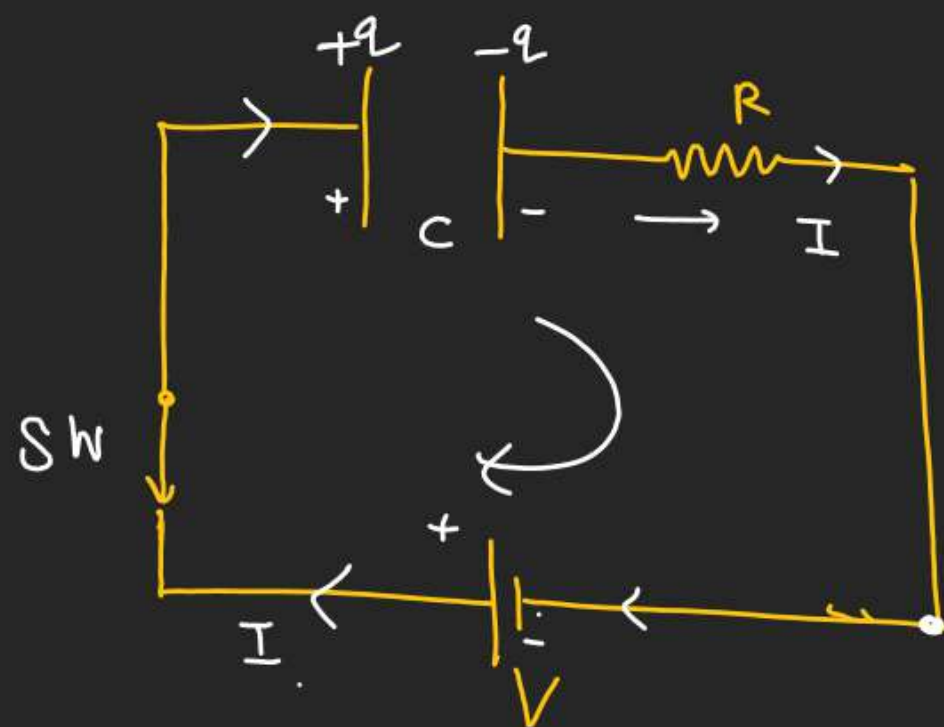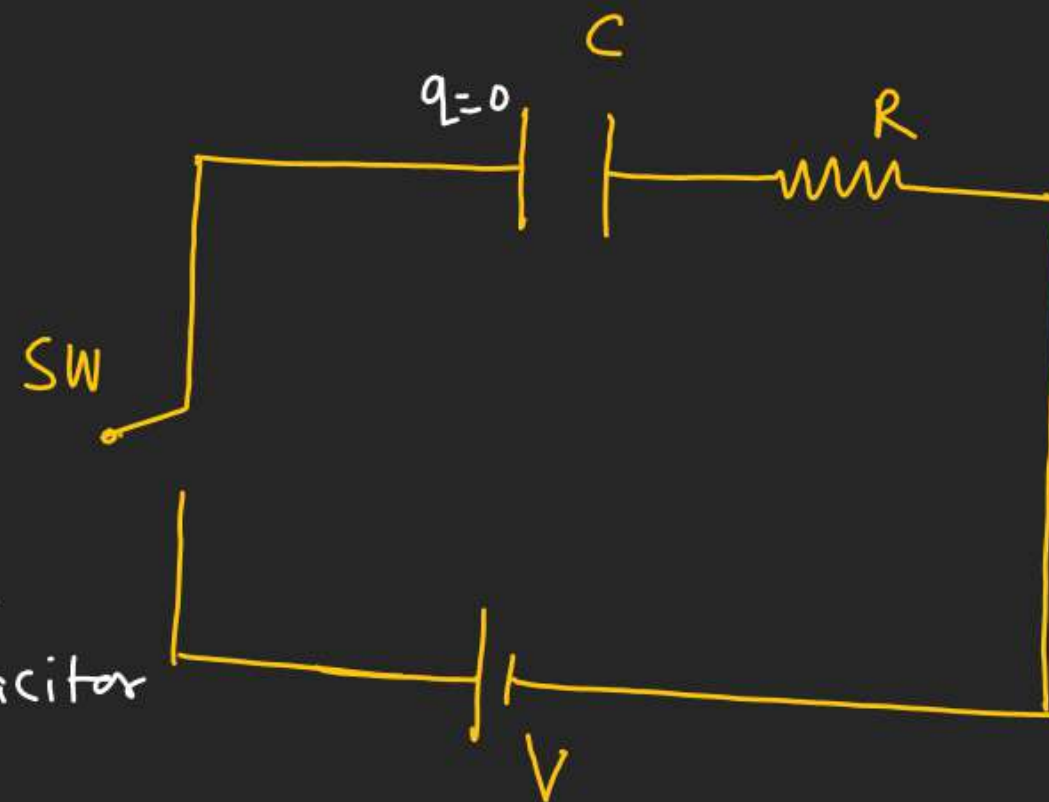

# CURRENT ELECTRICITY

$$V - \frac{q}{C} - iR = 0$$

$$V - \frac{q}{C} = iR$$

$$CV - q = RC \left( \frac{dq}{dt} \right)$$

$$(CV - q) = RC \left( \frac{dq}{dt} \right)$$

$$\int_0^q \frac{dq}{CV - q} = \frac{1}{RC} \int_0^t dt$$

$\begin{matrix} \downarrow & \downarrow & \downarrow \\ a & (-1) & x \\ & \downarrow & b \end{matrix}$

$$\ln \left[ \frac{CV - q}{CV} \right]_0^q = -\frac{t}{RC}$$

$$\ln [CV - q] - \ln [CV] = -\frac{t}{RC}$$

$$\ln \left[ \frac{CV - q}{CV} \right] = -\frac{t}{RC}$$

$$\frac{CV - q}{CV} = e^{-t/RC}$$

$$CV - q = CV e^{-t/RC}$$

$$q = CV (1 - e^{-t/RC})$$

$q_{\max} = CV$  at  $t \rightarrow \infty$   
[At  $t=0$ ,  $q=0$ ]

$$\int \frac{dx}{a+bx} = \frac{\ln(a+bx)}{b}$$

$\hookrightarrow a \& b \text{ Constant}$



## CURRENT ELECTRICITY

RC ckt Time Constant of RC ckt.

$$q = q_0 (1 - e^{-t/\tau})$$

$$\tau = RC$$

$$q_0 = CV$$

(Maximum charge on the Capacitor)

Time Constant of R-C Ckt.

$$q = \lim_{t \rightarrow \infty} q_0 (1 - e^{-t/\tau}) = q = q_0$$

At  $t = \tau$ 


$$q = q_0 (1 - e^{-\tau/\tau})$$

$$q = q_0 (1 - \frac{1}{e})$$

$$q = 0.63 q_0$$

$$[e^{-\infty/\tau} \rightarrow e^{-\infty} \rightarrow \frac{1}{e^{\infty}} \rightarrow 0]$$

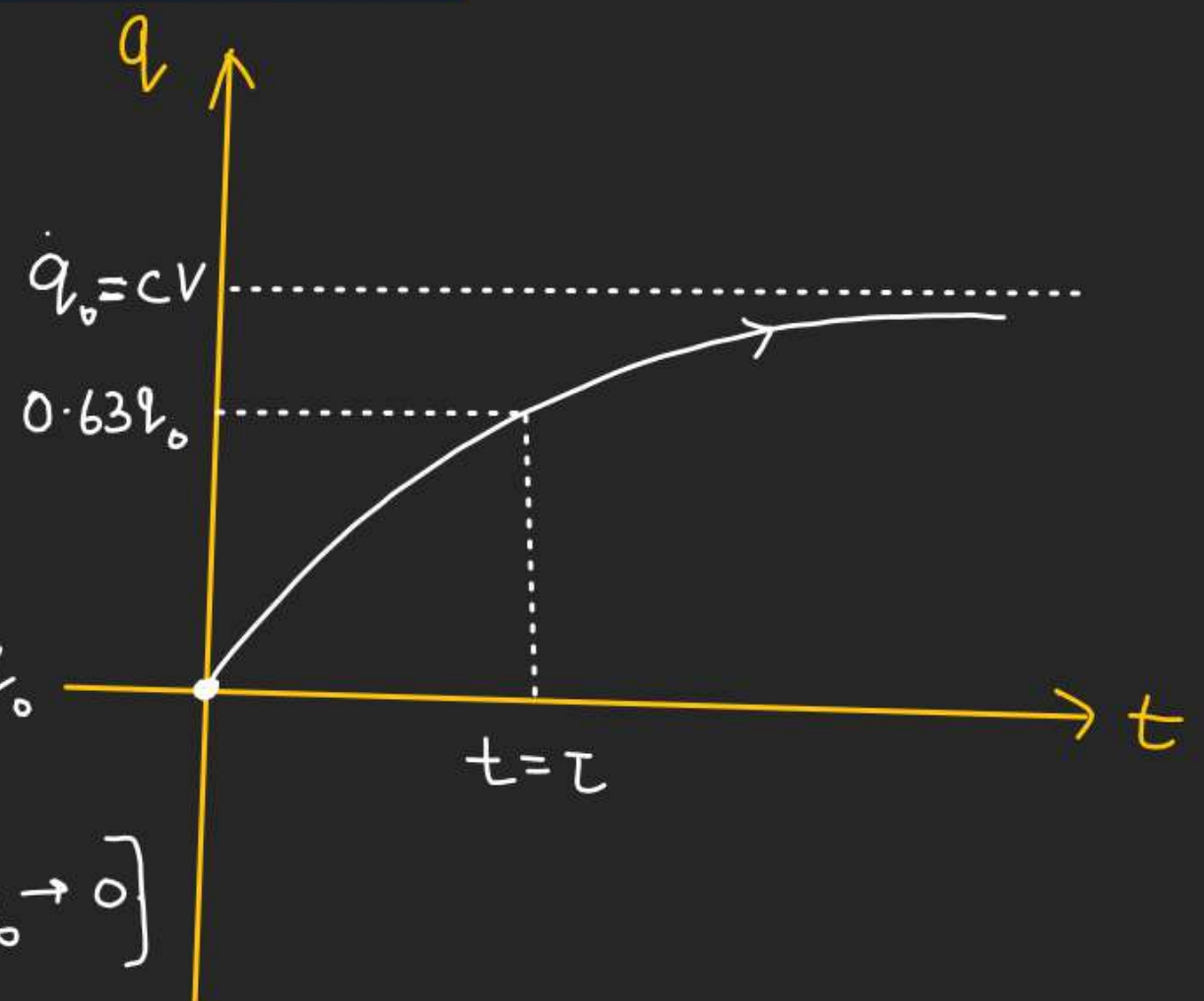Def<sup>n</sup> ( $\tau$ )  $\rightarrow$  It is time when Capacitor is charged to 63% of its maximum value



## CURRENT ELECTRICITY

$$I = f(t)$$

$$q = q_0(1 - e^{-t/\tau})$$

$$\tau = RC$$

$$q_0 = CV$$

$$\frac{d}{dx}(e^{\alpha x}) = \alpha e^{\alpha x}$$

$\alpha = \text{Constant}$

For Charging

$$I = \left(+\frac{dq}{dt}\right)$$

$$I = q_0 \frac{d}{dt}(1 - e^{-t/\tau})$$

$$I = q_0 \left[ -\frac{d}{dt}(e^{-t/\tau}) \right]$$

$$I = q_0 \left[ (-1) \left( -\frac{1}{\tau} \right) (e^{-t/\tau}) \right]$$


$$I = \frac{q_0}{\tau} (e^{-t/\tau})$$

$$I = \frac{CV}{RC} (e^{-t/\tau})$$

$$I = \left(\frac{V}{R}\right) e^{-t/\tau}$$



$$\frac{V}{R} = q_0$$

$$I = I_0 e^{-t/\tau} **$$

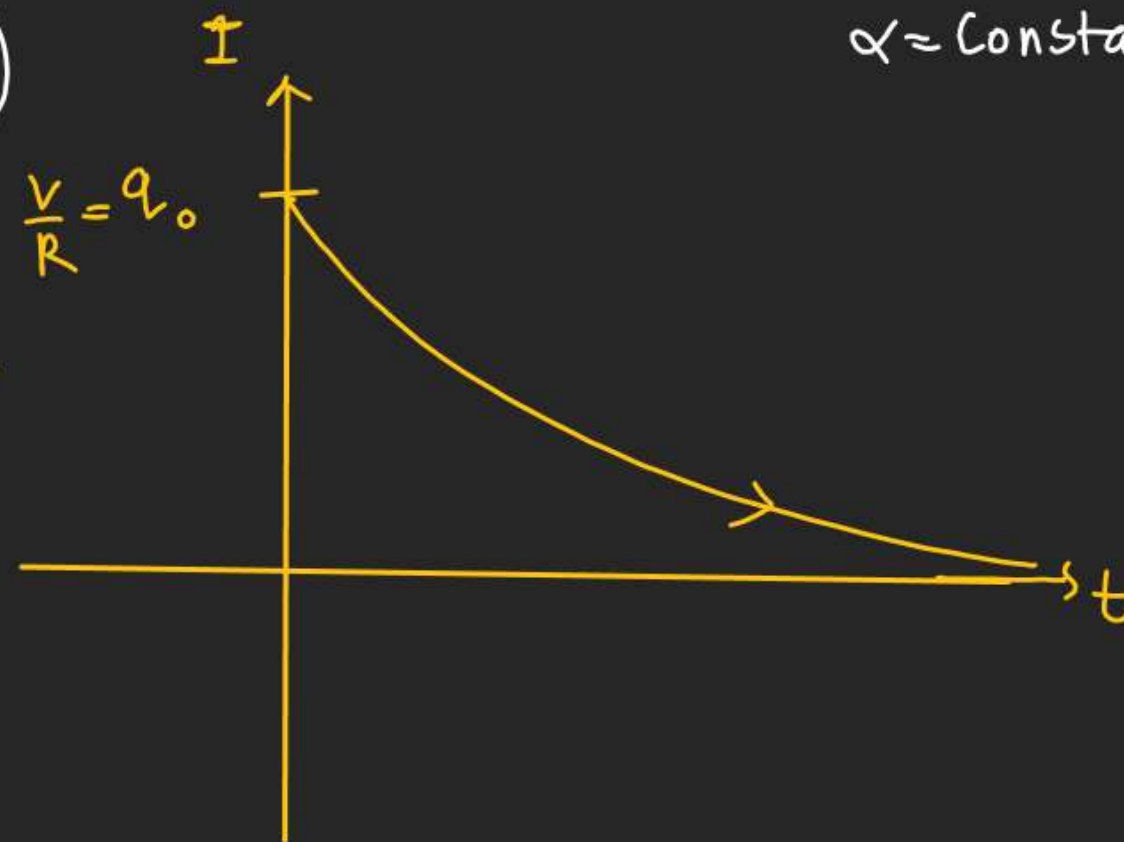

(★) Discharging of Capacitor! →

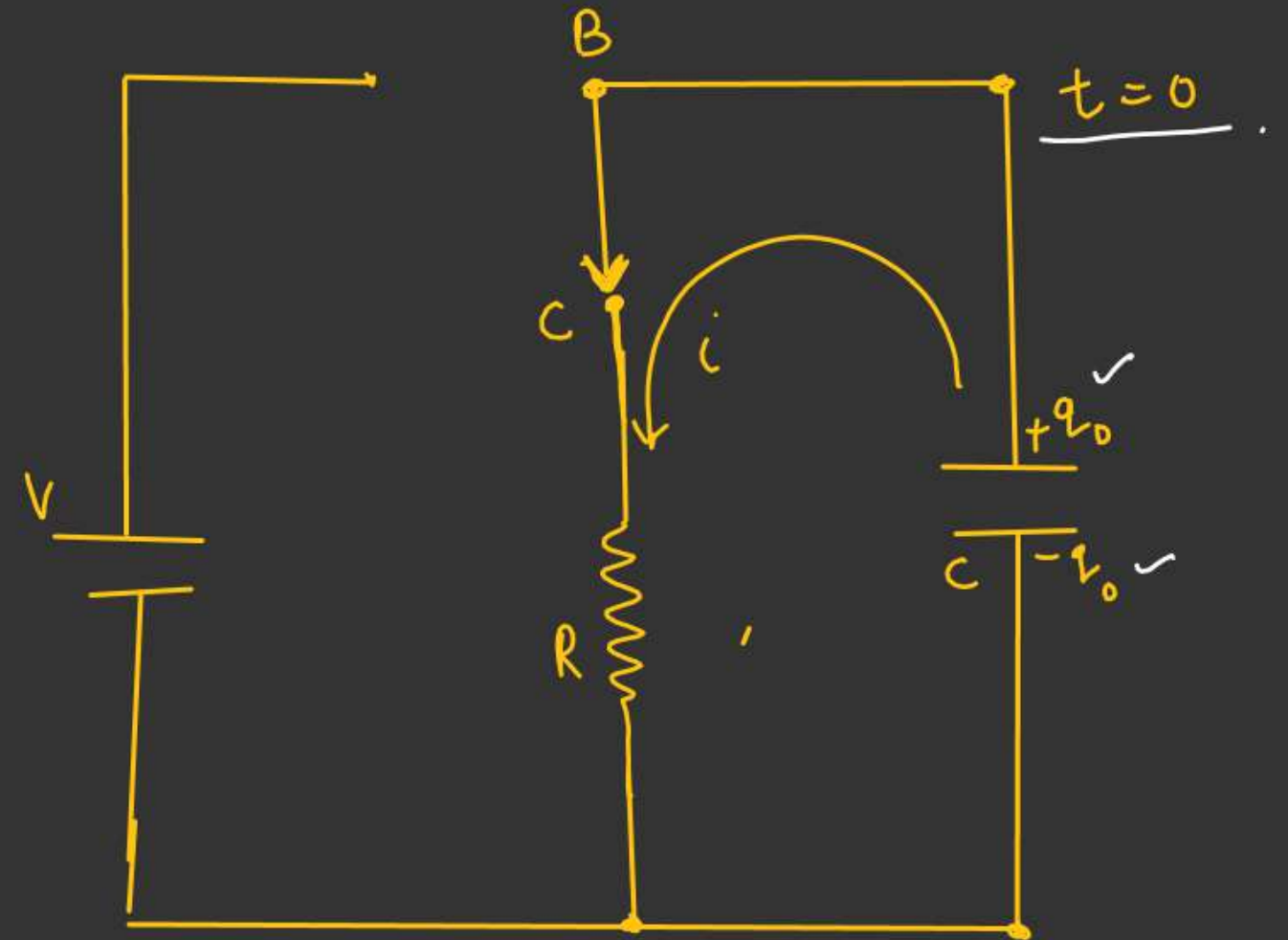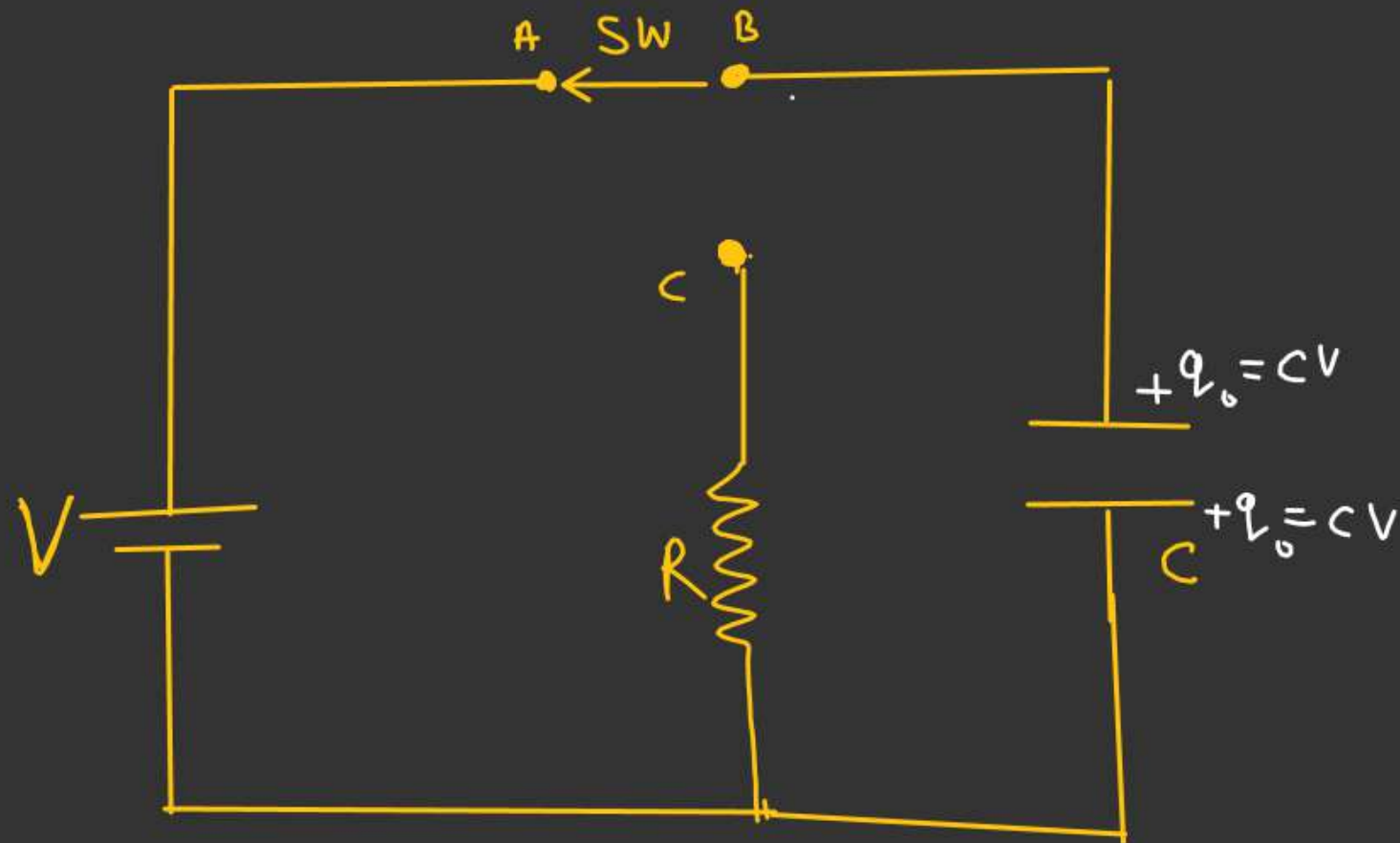SW Closed for a very long time.  
i.e Capacitor become fully charged.  
let, at,  $t=0$ , SW moved from A to C.





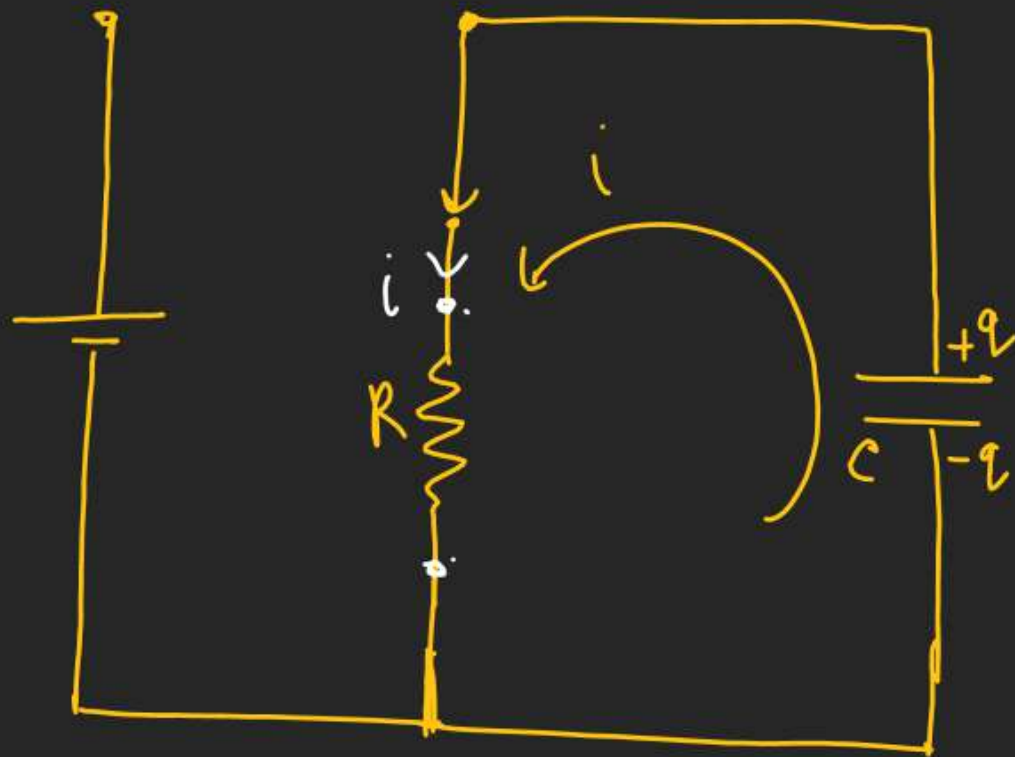
## CURRENT ELECTRICITY

$$\int \frac{dx}{x} = \ln(x)$$

let, at any time  $t=t$ , Charge on the Capacitor be  $q$ .



K.V.L

$$\frac{q}{C} - iR = 0$$

$$\frac{q}{C} = iR$$

$$i = -\frac{dq}{dt}$$

During discharging  
 $q$  decreases w.r.t  
 time

$$\frac{q}{RC} = -\frac{dq}{dt}$$

$$\int_{q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$

$$\ln[q]_{q_0}^q = -\frac{t}{RC}$$

$$\ln(q/q_0) = -\frac{t}{RC}$$

$$q = q_0 e^{-t/RC}$$


$$RC = \tau$$

## CURRENT ELECTRICITY

$$q = q_0 e^{-t/\tau}$$

$q \rightarrow$  (present value on the Capacitor)

$$\tau = RC$$

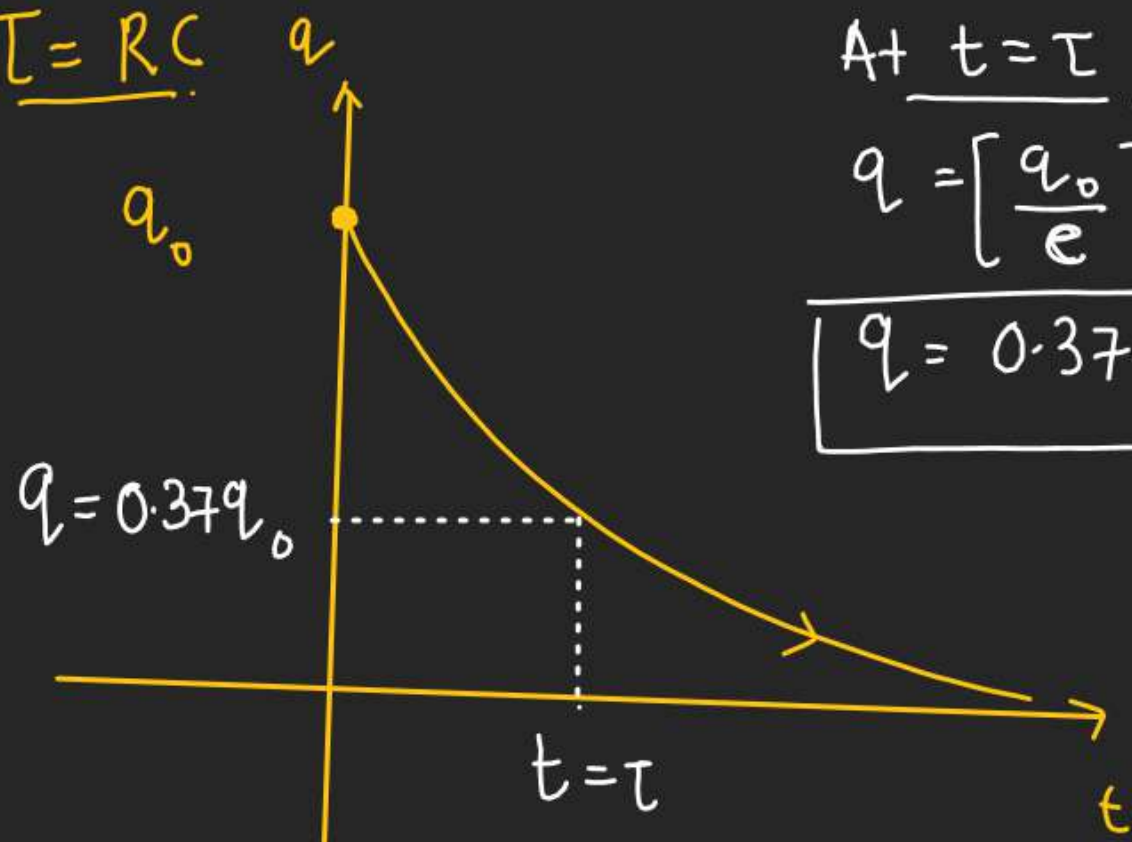

At  $t = \tau \rightarrow$  [Time when Capacitor discharge to 63%]  
 $q = \left[ \frac{q_0}{e} \right]$


$$q = 0.37q_0$$

$$I = -\left(\frac{dq}{dt}\right)$$


$$I = -q_0 \frac{d}{dt}(e^{-t/\tau})$$

$$I = \frac{q_0}{\tau} e^{-t/\tau}$$


$$I = \frac{V}{R} e^{-t/\tau}$$

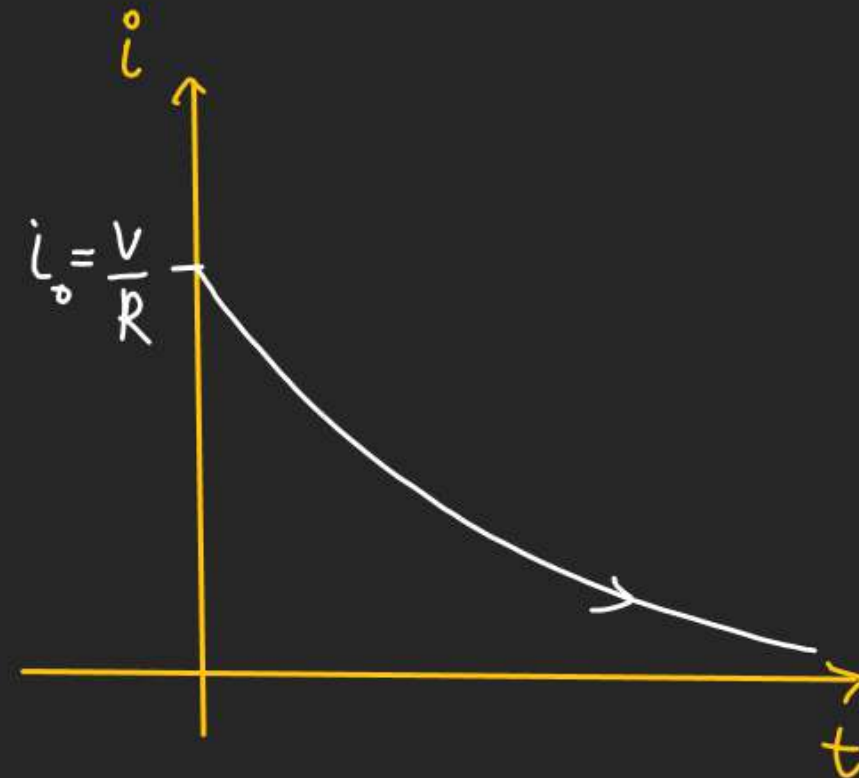

AA.

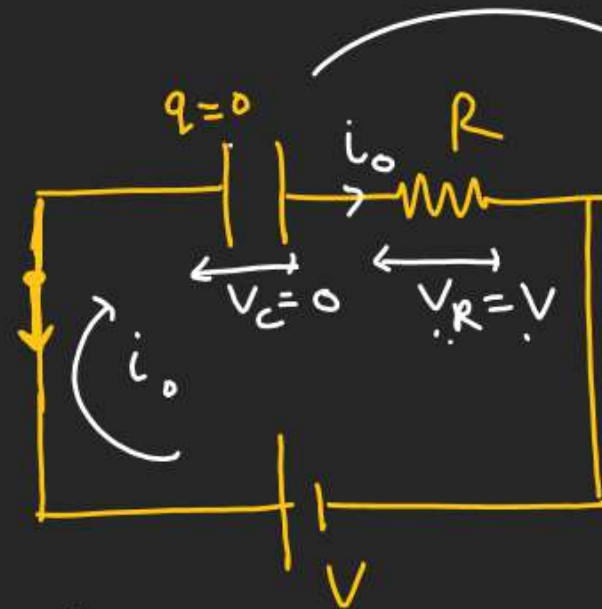Behaviour of Capacitor in R-C Ckt:-At  $t = 0$ 

Capacitor can be replaced by a zero resistance wire.

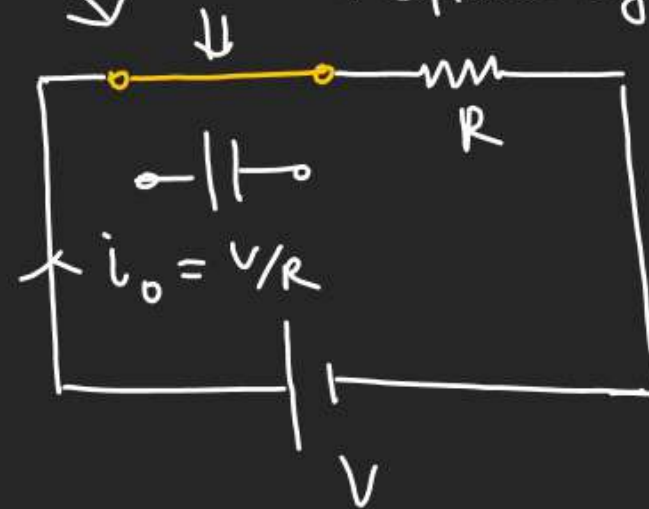At  $t = t$ 

$$q = q_0(1 - e^{-t/\tau})$$

$$i = i_0 e^{-t/\tau} = \left( \frac{V}{R} e^{-t/\tau} \right), \quad V_C = 0$$

At  $t = 0$ 

$$\boxed{i = i_0} \quad (i_0 = \frac{V}{R})$$



## Behaviour of Capacitor at $[t \rightarrow \infty]$

- $[t \rightarrow \infty] \Rightarrow$  very long time.  
 $\Rightarrow$  Capacitor fully charged.  
 $\Rightarrow$  [Steady State of Capacitor]

$$\left[ \begin{array}{l} q = q_0 (1 - e^{-t/\tau}) \\ i = I_0 e^{-t/\tau} \end{array} \right]$$


At  $t \rightarrow \infty$  (Steady state)

$$q = q_0 = \boxed{CV}$$

$t \rightarrow \infty$

$$i = I_0 e^{-\infty/\tau} = \frac{I_0}{e^\infty} = \frac{I_0}{\infty} \rightarrow 0$$

$$\boxed{i \rightarrow 0}$$

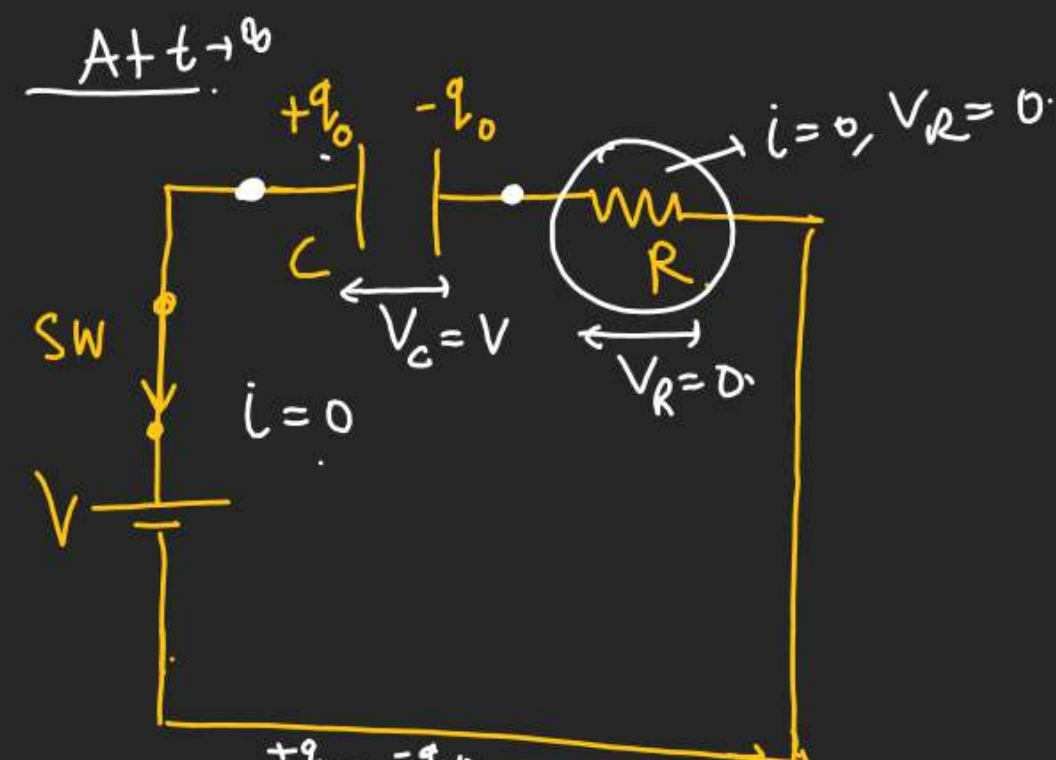

$\Rightarrow$  Capacitor behave as open ckt

