

Link to View Video Solution: [Click Here](#)

1. Initially $c_{eq} = \frac{4}{3} \mu F$
 $(q_{flow})_{battery} = \frac{4}{3} \times 24 \mu C$
 $= 32 \mu C$

When switch is closed

$$C_{eq} = \frac{3 \times 3}{6} = \frac{3}{2}$$

q_{flow} through battery

$$= \frac{3}{2} \times 24 = 36 \mu C$$

$$Q = CV$$


$$\Rightarrow \frac{q_1}{1} = \frac{36 - q_1}{2}$$

$$\Rightarrow 2q_1 = 36 - q_1$$

$$3q_1 = 36$$

$$q_1 = 12 \mu C$$


2. Initially

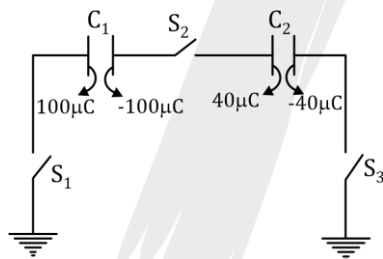

Sum of charge on negative plate of C_1 & +ive plate of C_2 is constant

$$= -100 + 40 = -60 \mu C$$



After closing the switch

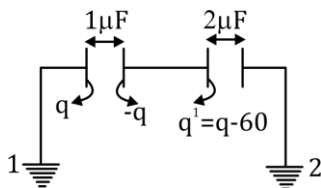

$$q' - q = -60$$

$$q' = q - 60$$
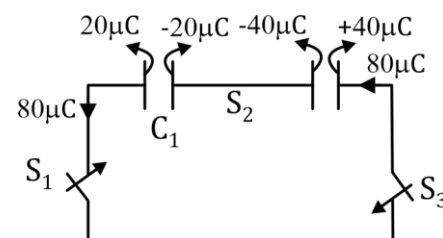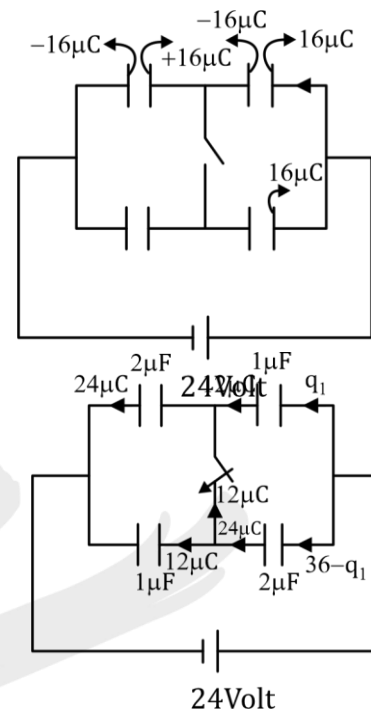
$$V_1 - \frac{q}{1} - \frac{(q-60)}{2} = V_2$$




Link to View Video Solution: [Click Here](#)

$$q + \frac{(q-60)}{2} = 0 \Rightarrow 2q + q - 60 = 0$$

$$q = 60$$

$$q = 20\mu\text{C}$$

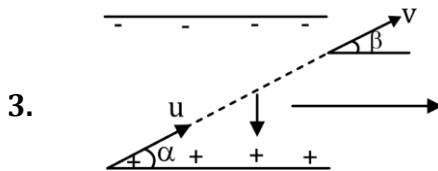


uniform electric field which produce constant acceleration downward.

$$\Rightarrow u \cos \alpha = v \cos \beta$$

$$v = u \left(\frac{\cos \alpha}{\cos \beta} \right)$$

$$\frac{k_i}{k_f} = \frac{\frac{1}{2} m u^2}{\frac{1}{2} m v^2 \left(\frac{\cos \alpha}{\cos \beta} \right)^2}$$
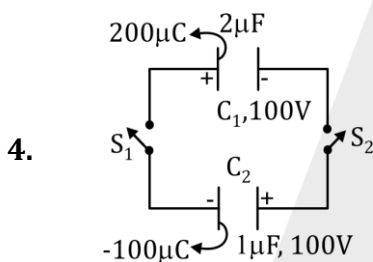
$$\frac{k_i}{k_f} = \left(\frac{\cos \beta}{\cos \alpha} \right)^2$$



$$\Rightarrow U_i = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

$$= \frac{1}{2} \times 3 \times 100^2 = 1.5 \times 10^4 \mu\text{J}$$


Link to View Video Solution: [Click Here](#)

\Rightarrow Finally

Sum of charge on +ive plate of C_1 & negative plate of C_2 = Constant

$$q_1 + q_2 = 200 - 100$$
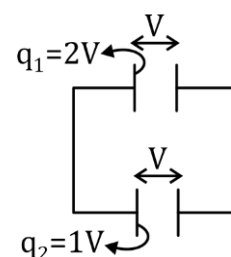
$$3V = 100 \Rightarrow V = \frac{100}{3}$$




$$U_f = \frac{1}{2} c_1 v_f^2 + \frac{1}{2} c_2 V_f^2$$

$$= \frac{1}{2} \times 3 \times \left(\frac{100}{3}\right)^2 = \frac{1.5 \times 10^4}{9} \mu\text{J}$$

$$\frac{U_f}{U_i} = \frac{1}{9}$$

5.

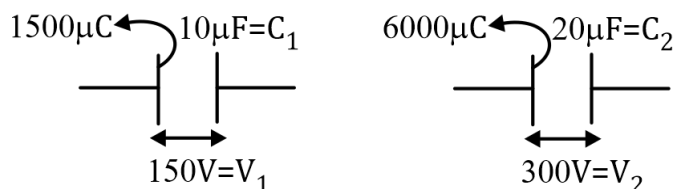

$$U_i = \frac{1}{2} c_1 V_1^2 + \frac{1}{2} c_2 V_2^2$$

$$U_i = \left[\frac{1}{2} \times 10 \times (150)^2 + \frac{1}{2} \times 20 \times (300)^2 \right] \mu\text{J}$$

$$30V = (1500 + 6000)$$


$$V = \frac{7500}{30} = 250 \text{ volt}$$

$$U_f = \frac{1}{2} (c_1 + c_2) V^2$$


$$\Delta H = V_f - V_i$$

6.

when Sw₁ closed & Sw₂ open

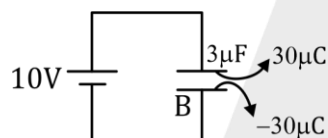

When Sw₁ open & Sw₂ closed.

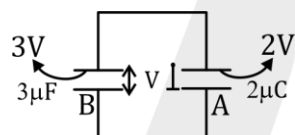


$$3V + 2V = 30$$

$$V = 6 \text{ Volt}$$

$$\Rightarrow q_A = 12 \mu\text{C}$$

$$q_B = 18 \mu\text{C}$$

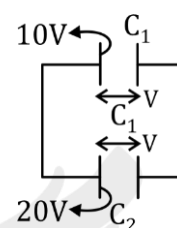

Link to View Video Solution: [Click Here](#)


7.

To determine the value of x.

$$\Rightarrow 6(x - 0) + 2(x - 10) + 4(x - 20) = 0$$


$$x = \frac{25}{3} \text{ Volt}$$
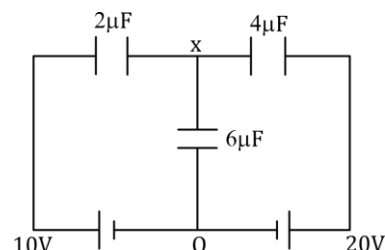
$$\Rightarrow q_{6\mu\text{F}} = 6 \times \frac{25}{3} = 50 \mu\text{C}$$




8.

Initially

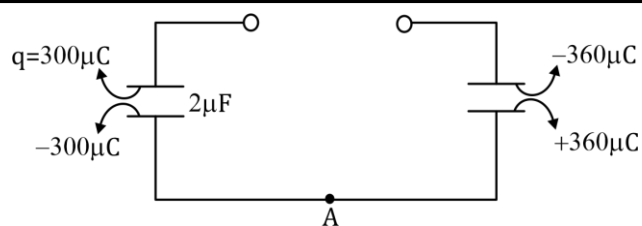

Finally

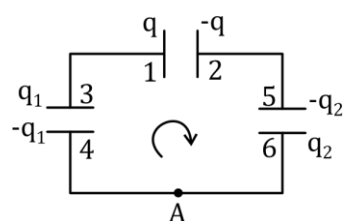

⇒ Plate 1 & 3 are isolated.

$$q + q_1 = 300 \mu\text{C} \quad \text{--- (i)}$$

Plate 4 & 5 are isolated.

$$-q_1 + q_2 = -300 + 360$$

$$-q_1 + q_2 = 60 \quad \text{--- (ii)}$$

Plate (2) & (6) are isolated

$$-q - q_2 = -360$$

$$q + q_2 = 360 \quad \text{--- (iii)}$$

$$\text{Using } \frac{-q}{1.5} + \frac{q_2}{3} + \frac{q_1}{2} = 0$$

$$q = 180 \mu\text{C} = q_1 = 120 \mu\text{C}, q_2 = 180 \mu\text{C}$$

Link to View Video Solution: [Click Here](#)

(Physics)

CAPACITOR

9. $C_{eq} = \frac{2 \times 3}{5} = \frac{6}{5} \mu F$

$Q = CV = \frac{6}{5} \times 120 = 6 \times 24$

$Q = 144 \mu C$

When switch is closed

charged on $3 \mu C = 180 \mu C$


charged on $2 \mu C = 120 \mu C$

Initially charge on $2 \mu C = 144$

charge flow through

$S_3 = (144 - 120) + (180 - 144)$

$= 24 + 36 = 60 \mu C$

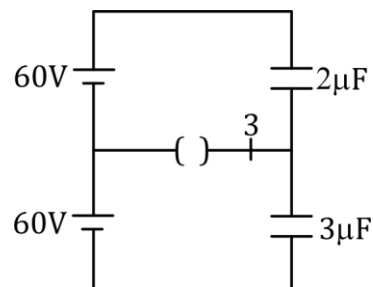

10.

