

## Nodal method

## CAPACITOR

$$q = C \Delta V$$


Q.1 In the circuit shown in Fig. determine charge on each capacitor.

$$2(x-20) + (x-0)4 + [(x+10)-0]2 = 0$$

Charge on Capacitor-1:  $8x - 20 = 0$   
 $x = \frac{20}{8} = \left(\frac{5}{2} \text{ Volt}\right)$

Charge on Capacitor-2:  $2(x-20)$

Charge on Capacitor-3:  $[(x+10)-0]2$

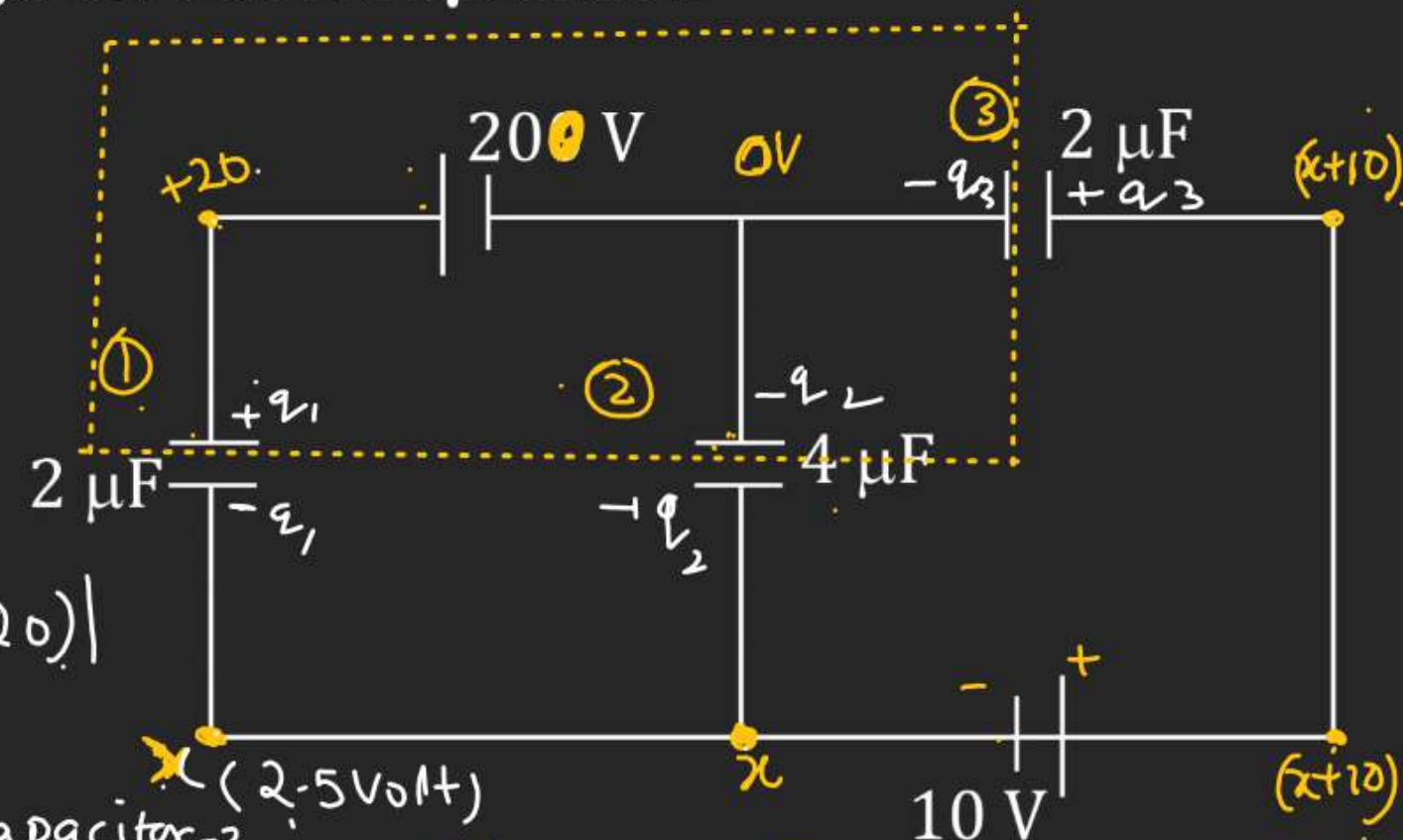

$$[\text{Initial Charge} = 0]$$

At steady state = (final charge)

$$0 = \text{Initial Charge} = \left[ \sum_{i=1}^n q_i \right]$$

$$= |2(2.5-20)|$$

$$= 35\mu C$$

Charge on Capacitor-2

$$= (2.5 \times 4)$$

$$= (10\mu C)$$

Charge on Capacitor-3

$$= (x+10) \times 2$$

$$= (12.5) \times 2$$

$$= 25\mu C$$


## Nodal method

## CAPACITOR

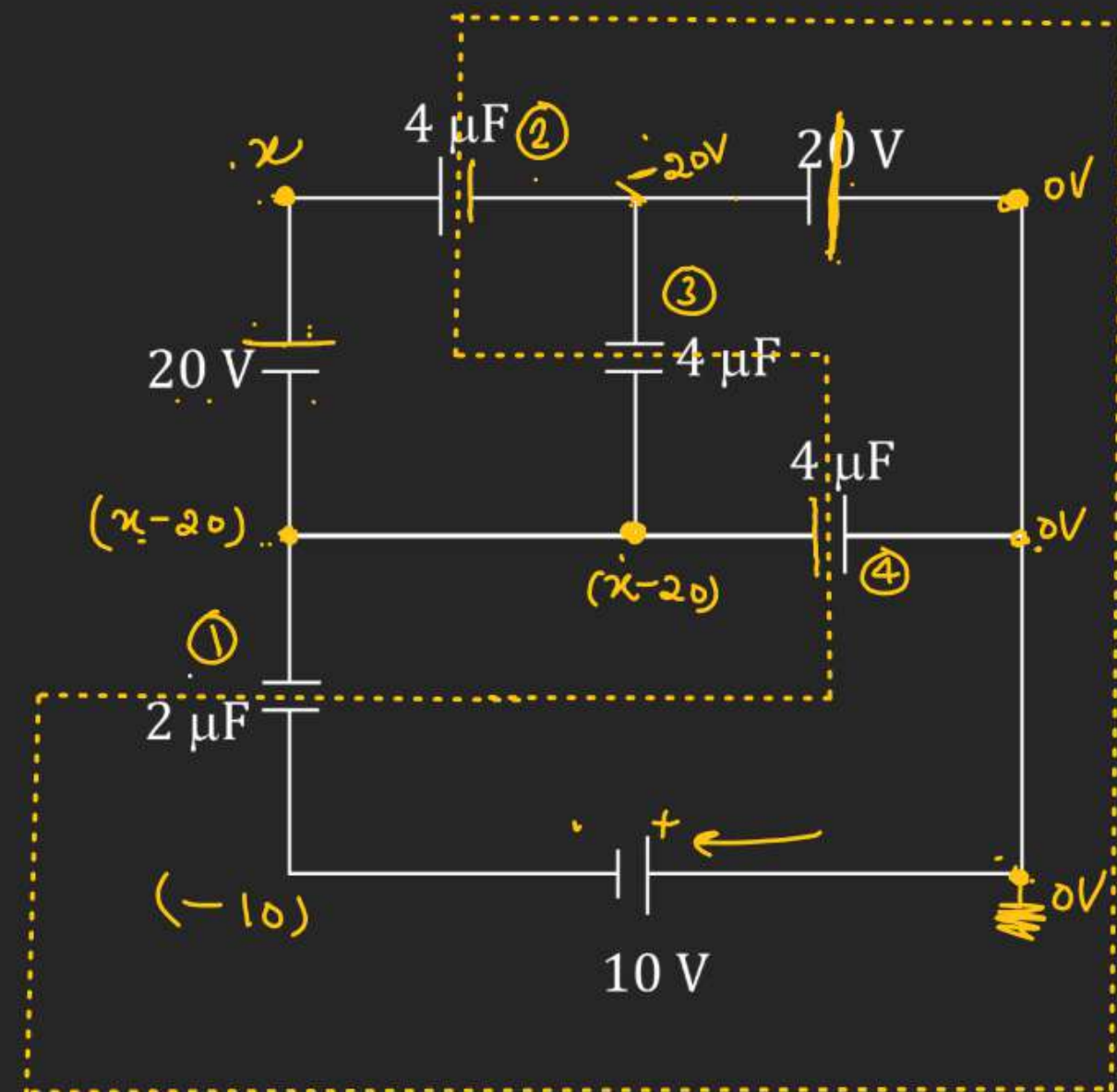Q.2 Find charge on all the capacitors in circuit:

$$\underbrace{\left[ (x-20) - (-10) \right] 2}_{q_1} + \underbrace{\left[ (x-(-20)) \right] \times 4}_{\Rightarrow q_2} + \underbrace{\left[ (x-20) - (-20) \right] 4}_{\Rightarrow q_3} + \underbrace{(x-20) 4}_{\Rightarrow q_4} = 0$$

$$x = \left( \frac{10}{7} \right) \text{ volt. Ans}$$





## Nodal method

## CAPACITOR

M-2

$$\begin{aligned} & \xrightarrow{q_1} \quad \quad \quad \xrightarrow{q_2} \\ & \underline{3(x-0) + (x-200) \times 6 = 0} \\ & 3x + 6x - 1200 = 0 \\ & 9x = 1200 \\ & \underline{x = \frac{1200}{9} = \frac{400}{3} \text{ Volt}} \end{aligned}$$

$$q_1 = 3 \times \frac{400}{3} = 400 \mu\text{C}$$

$$q_2 = \left( \frac{400}{3} - 200 \right) \times 6$$

$$= -\frac{200}{3} \times 6$$

$$= -400 \mu\text{C}$$

For plate (3) & (4)


$$6(y-0) + (y-200) \times 3 = 0$$

$$6y + 3y - 600 = 0$$

$$9y = 600$$

$$y = \frac{600}{9} = \left( \frac{200}{3} \right) \text{ Volt}$$
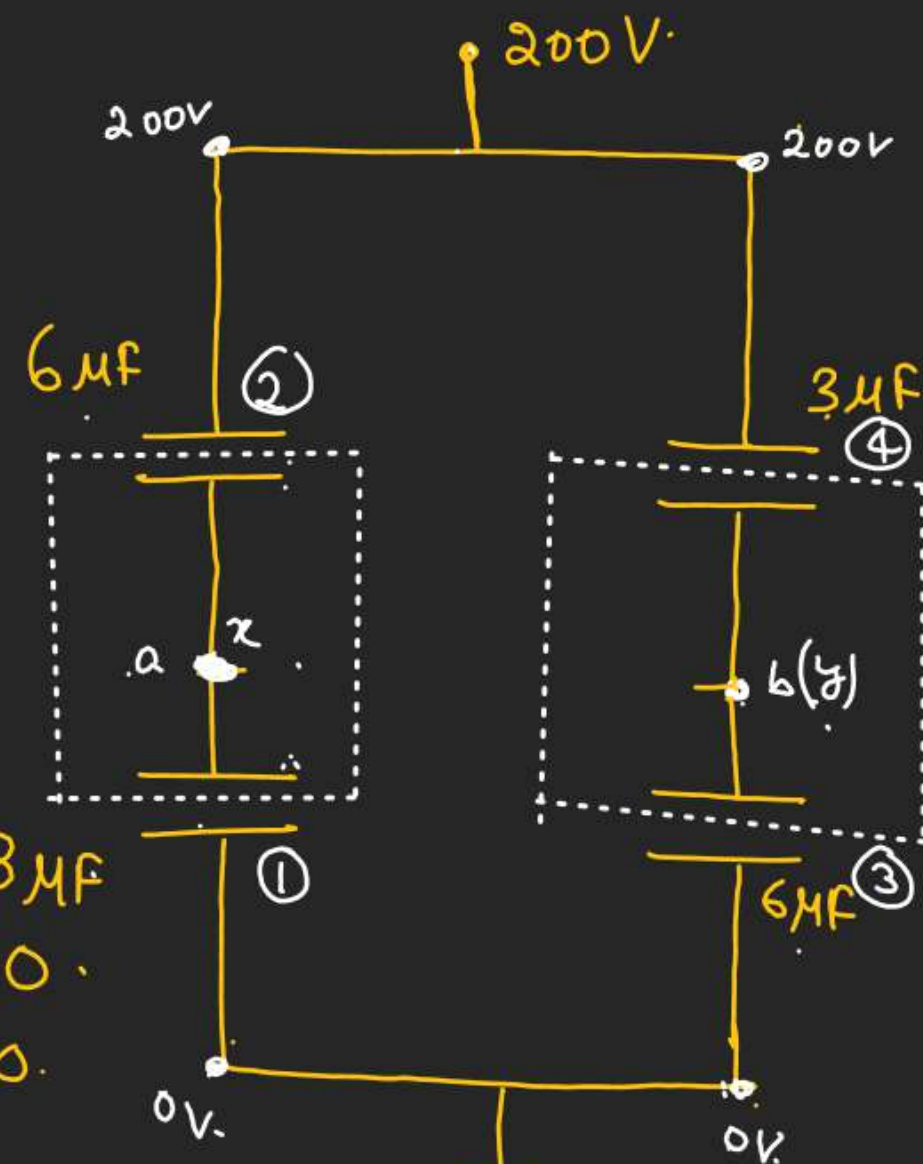
$$x - y = \frac{400}{3} - \frac{200}{3} = \left( \frac{200}{3} \right) \text{ Volt}$$



## Nodal method


## CAPACITOR

Q.3 Fig. shows a capacitive circuit, with a switch  $S_w$ .

(a) What is potential difference between a and b when switch is open ?

(b) What is potential of b after switch is closed ?

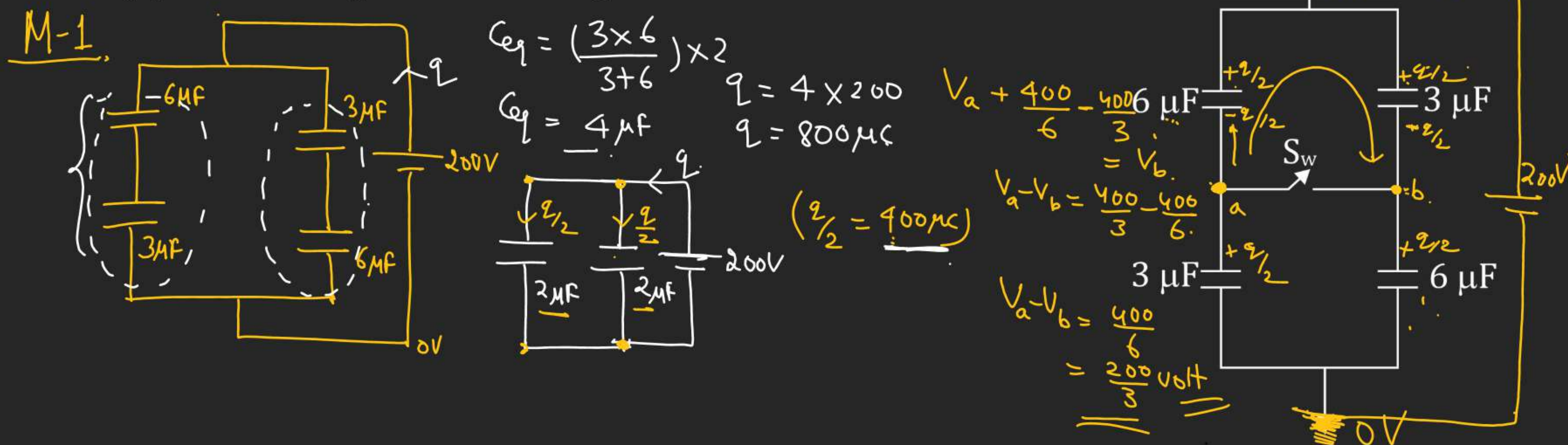(c) What charge flows through switch when it is closed?





## Nodal method

## CAPACITOR

Q.5 Find the potential difference between point A and B in the circuit shown in figure.

For loop-2

$$(5y) + (y-20) \times 10$$


$$+ [(y+20) - 20] \times 10$$

$$+ [(y+20) - 30] \times 5 = 0$$

For loop-1

$$(x-30) \times 10 + (x-10) \times 5 + [(x-20) - 10] \times 10$$
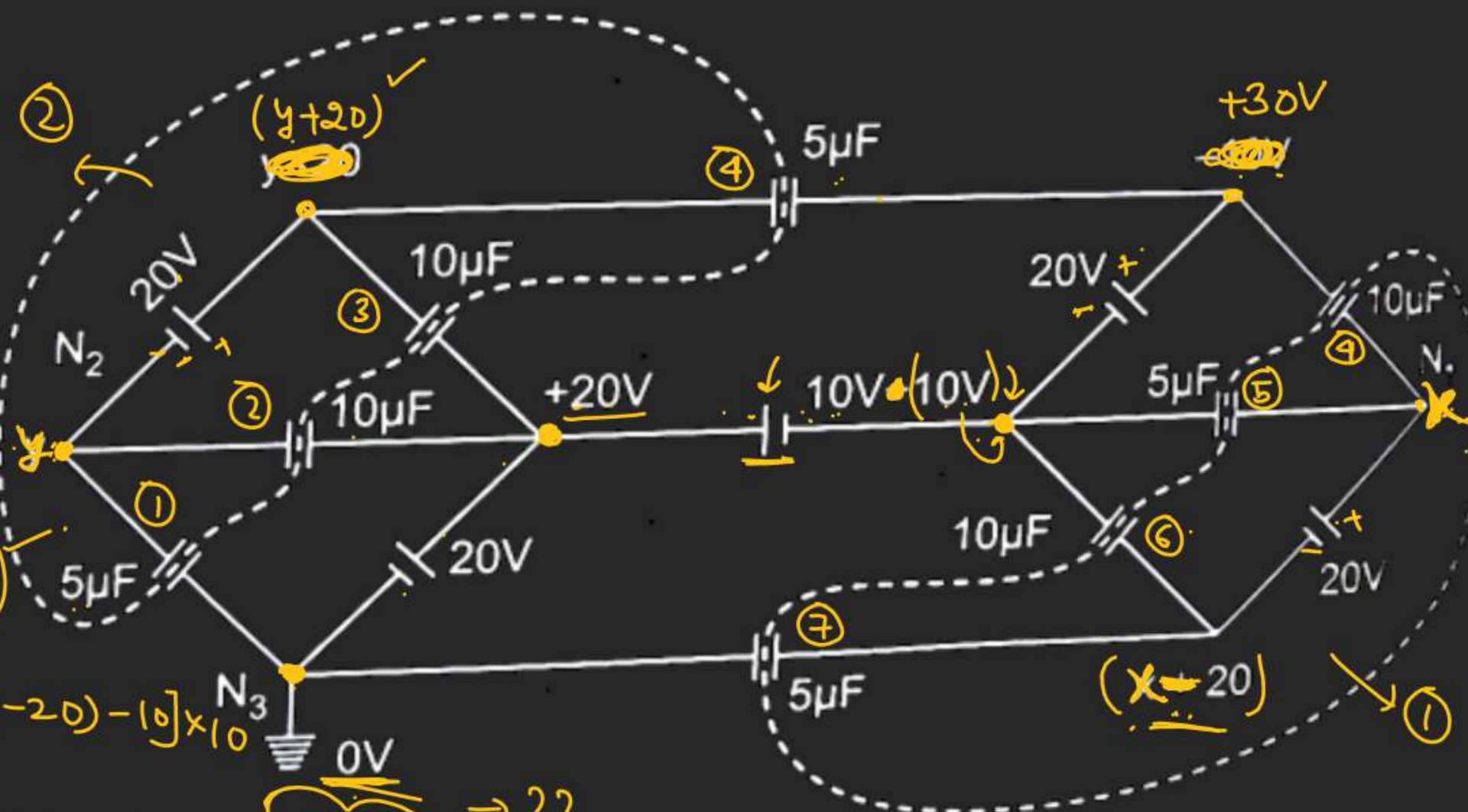
$$+ [(x-20) - 0] \times 5 = 0 \Rightarrow x = 25 \text{ Volt}$$





(★) Diagonal Symmetry = ??

$$[(V-x)-V]C_1 + (V-x)C_2 + (V-2x)C_3 = 0$$

$$(-xC_1 - xC_2 - 2xC_3) + VC_2 + VC_3 = 0$$
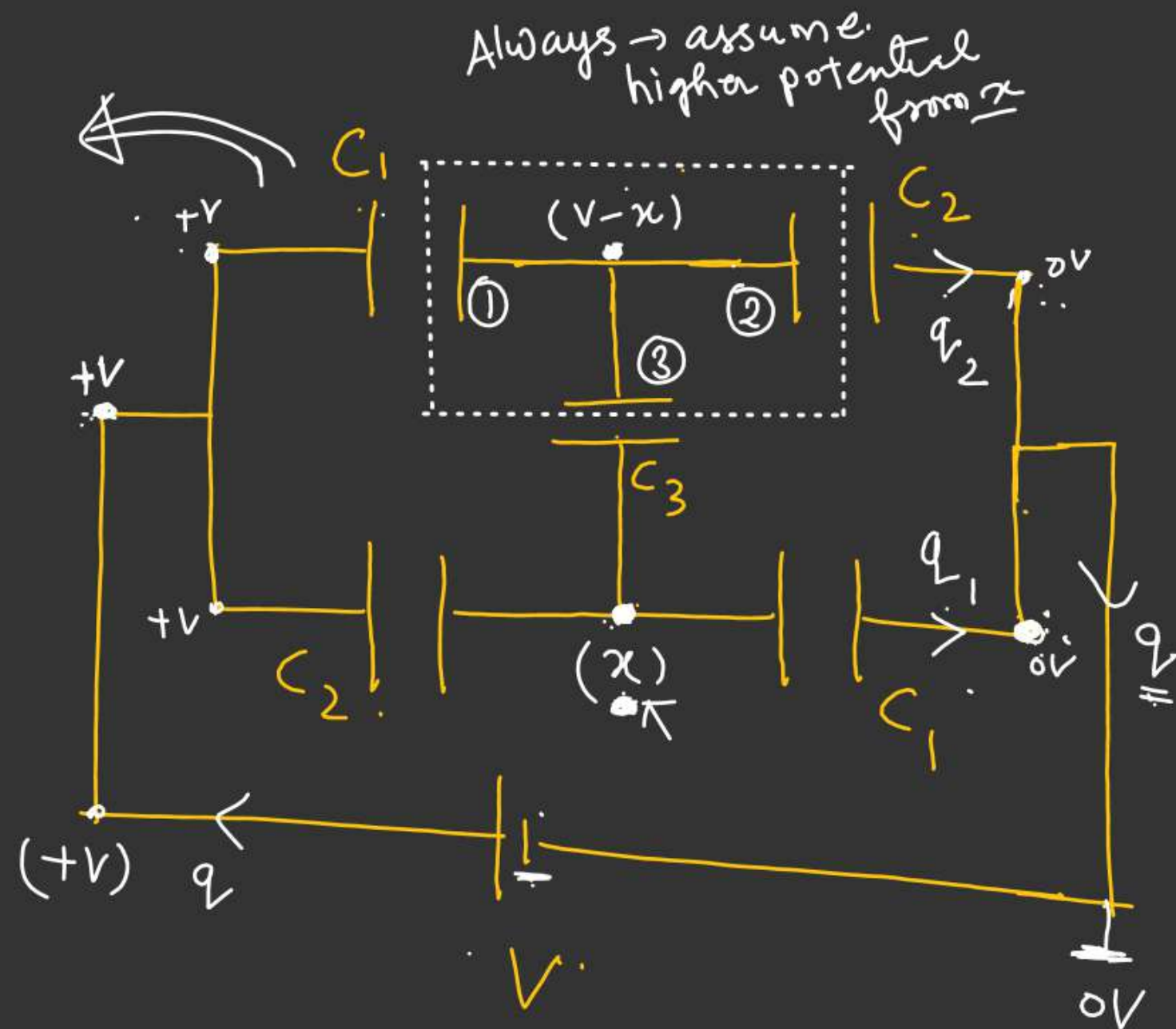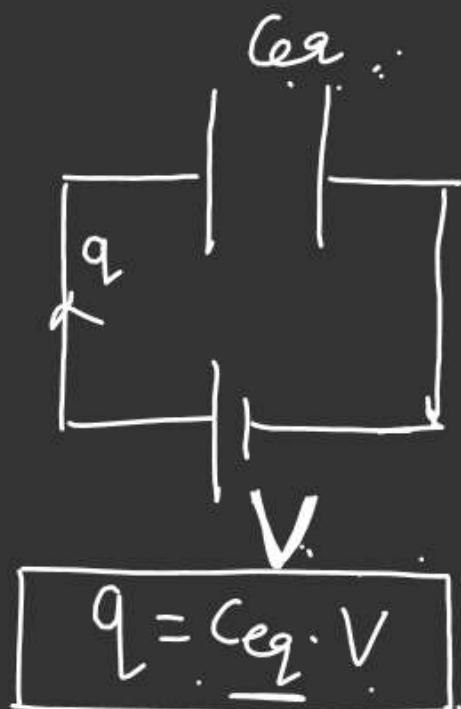
$$x = \left[ \frac{V(C_2 + C_3)}{C_1 + C_2 + 2C_3} \right]$$





## Nodal method

## CAPACITOR

$$q = q_1 + q_2$$

$$q = xC_1 + (V-x)C_2$$

$$q = x(C_1 - C_2) + VC_2$$

$$q = \left[ \frac{V(C_2 + C_3)}{C_1 + C_2 + 2C_3} \right] (C_1 - C_2) + VC_2$$

$$q = \left[ \frac{(C_2 + C_3)(C_1 - C_2)}{C_1 + C_2 + 2C_3} + C_2 \right] V$$

$$q = \left[ \frac{C_1 C_2 - C_2^2 + C_3 C_1 - C_2 C_3}{C_1 + C_2 + 2C_3} + C_2 \right] V$$

$$q = \left[ \frac{C_1 C_2 - \cancel{C_2^2} + \underline{C_3 C_1} - C_2 C_3 + \underline{C_1 C_2} + \cancel{C_2^2} + 2C_2 C_3}{C_1 + C_2 + 2C_3} \right] V$$

$$q = \left[ \frac{2C_1 C_2 + \underline{C_2 C_3} + \underline{C_3 C_1}}{C_1 + C_2 + 2C_3} \right] V$$

$$q = C_{eq} V$$

H.W.

## CAPACITOR

**Q.7** A capacitor of capacitance  $C_1 = 1.0\mu\text{F}$  withstands the maximum voltage  $V_1 = 6.0\text{kV}$  while a capacitor of capacitance  $C_2 = 2.0\mu\text{F}$ , the maximum voltage  $V_2 = 4.0\text{kV}$ . What voltage will the system of these two capacitors withstand if they are connected in series?