

CURRENT ELECTRICITY

Battery :-

- Combination of many cells.
- It act's as a external agent in the ckt.
- It works in two mode:-
 - ① Charging mode.
 - ② DisCharging mode.

$$i = \frac{dq}{dt}$$

DisCharging mode




$$\text{Wk done by battery} = (qV_b)$$

Charging mode

(Current flow from ckt to battery)

Work done on the battery.

$$= -(qV_b)$$

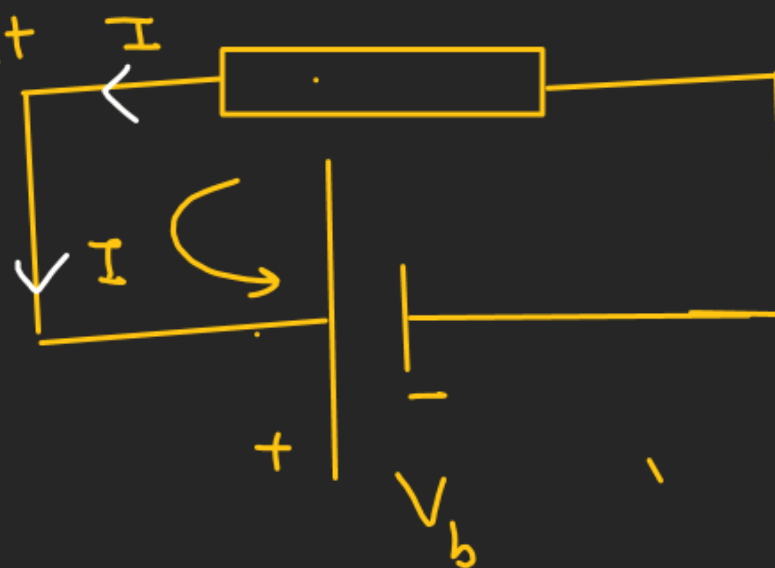


CURRENT ELECTRICITY

Battery

Ideal battery

↳ Internal resistance neglected.

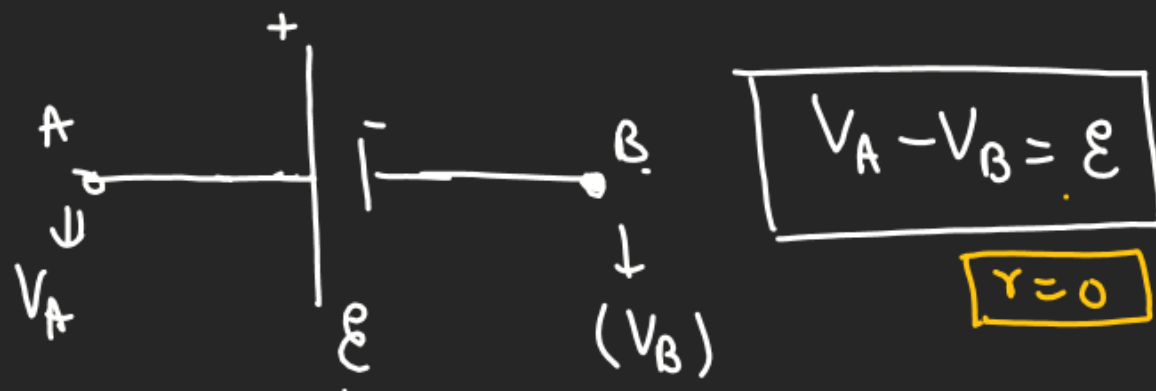
↳ E.M.f → [Electromotive force] is equal to terminal potential drop.



Non-Ideal battery


↳ (Internal resistance) not zero.

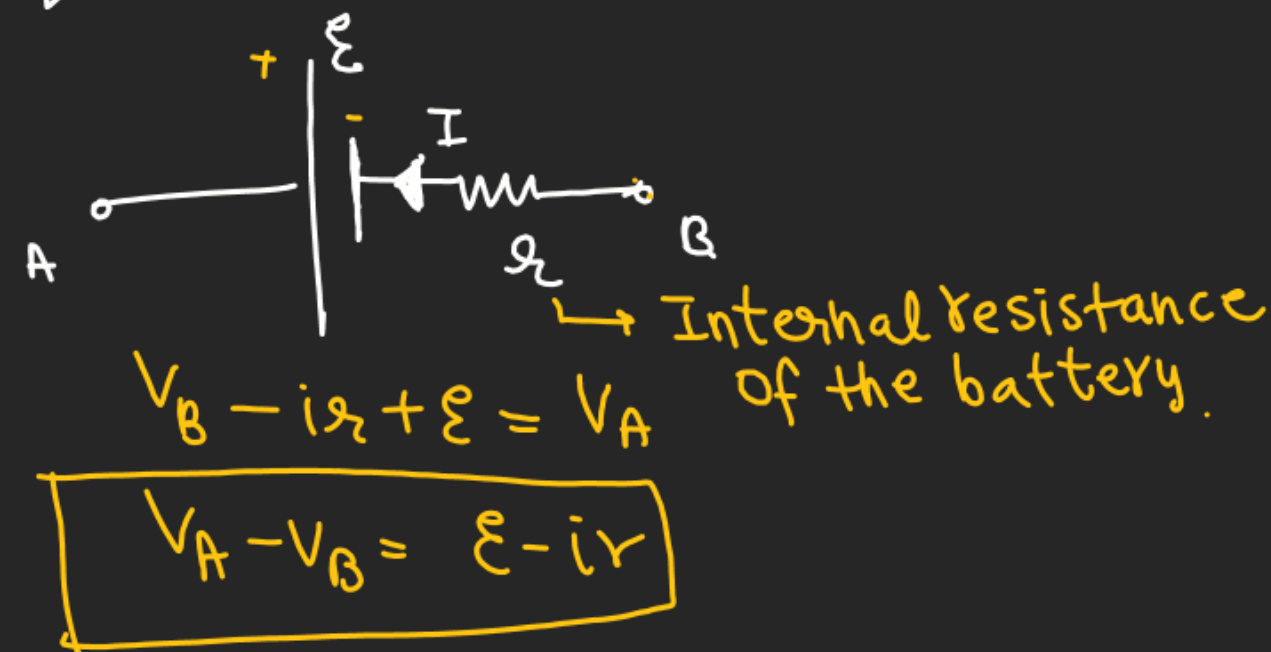↳ Terminal potential drop not equal to E.M.f.




QA

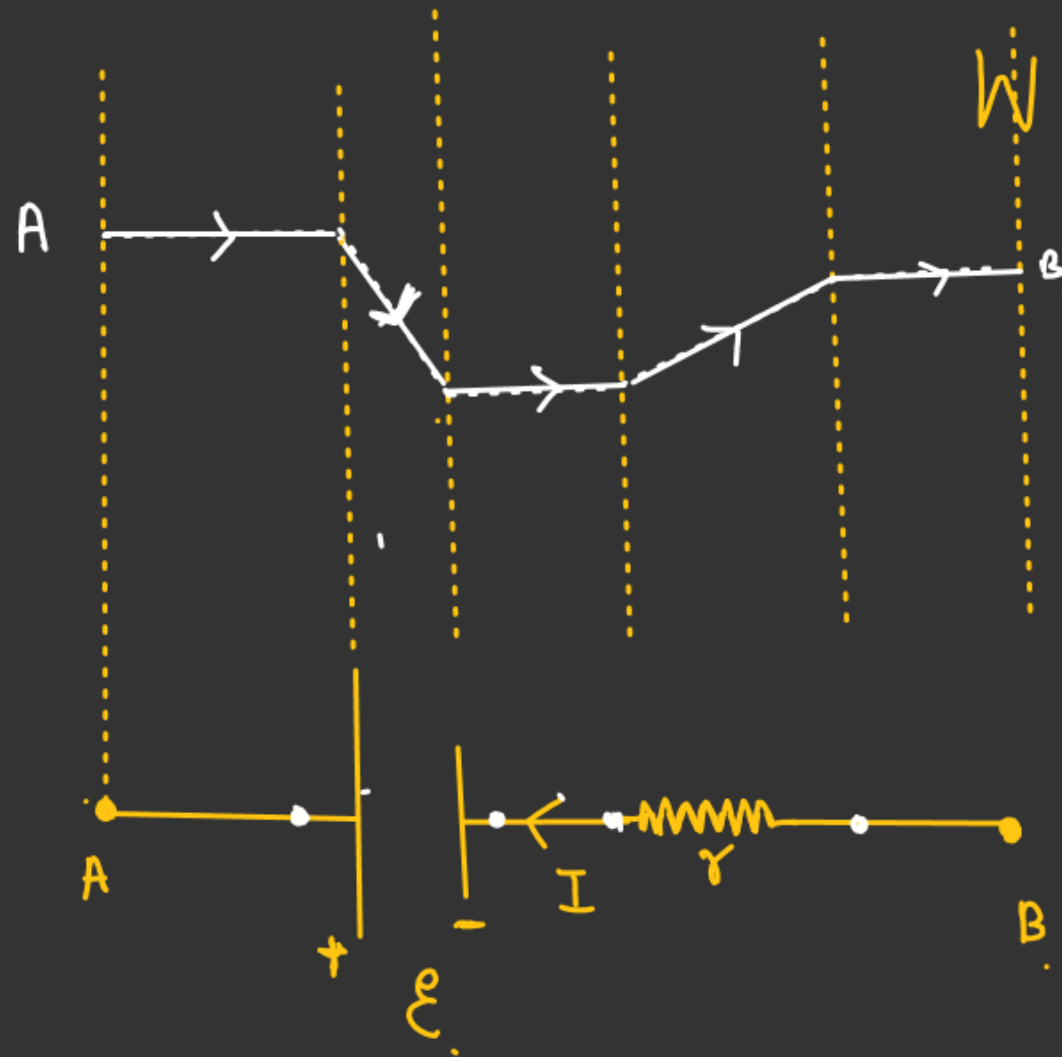E.M.f :- $\left(\frac{\text{Work done}}{q} \right) = \left(\frac{W}{q} \right)$



$W \rightarrow$ Work done in moving the cations and anions on the respective electrode

Charging mode :-

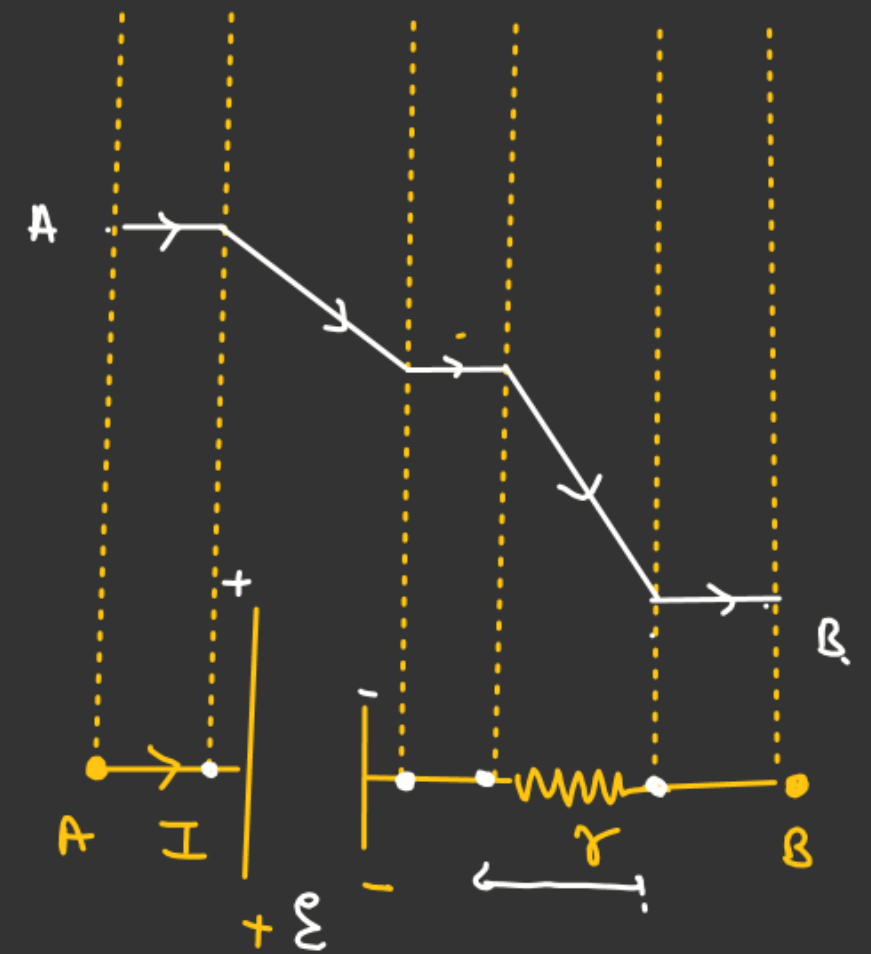


$$V_A - \varepsilon - ir = 0$$

⇒ Combination of battery

Series Combination

⇒ Current in all the battery must be same.

\mathcal{E}_{eq} in Series Combination

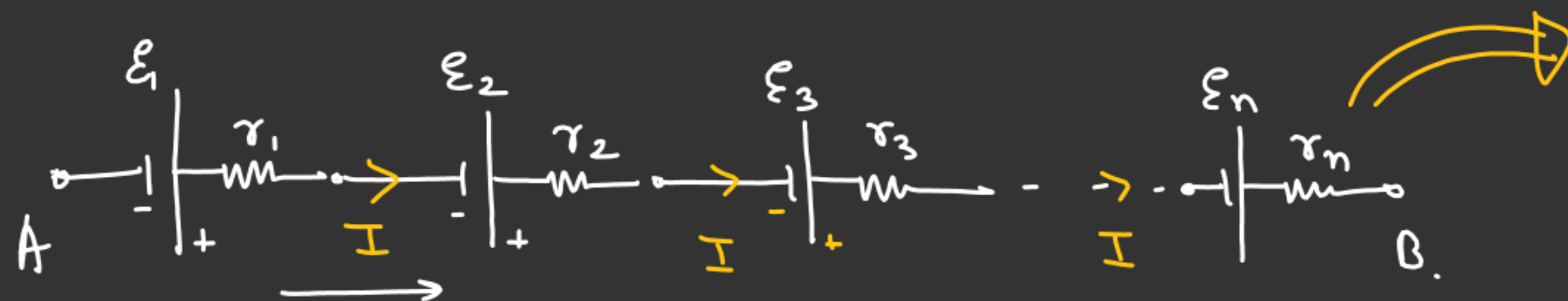

$$V_A + \mathcal{E}_1 - I r_1 + \mathcal{E}_2 - I r_2 - \dots + \mathcal{E}_n - I r_n = V_B$$

$$V_B - V_A = (\mathcal{E}_1 + \mathcal{E}_2 - \dots + \mathcal{E}_n) - I (r_1 + r_2 - \dots + r_n) \quad (1)$$

$$V_A + \mathcal{E}_{eq} - I r_{eq} = V_B$$


$$V_B - V_A = (\mathcal{E}_{eq} - I r_{eq}) \quad (2)$$

- * Total no of Cells = n .
 m cells of opposite polarity.
 \mathcal{E} = Emf of each cells.
 r = Internal resistance.

$$\mathcal{E}_{eq} = [(n-m)\mathcal{E} - m\mathcal{E}]$$


$$r_{eq} = nr$$
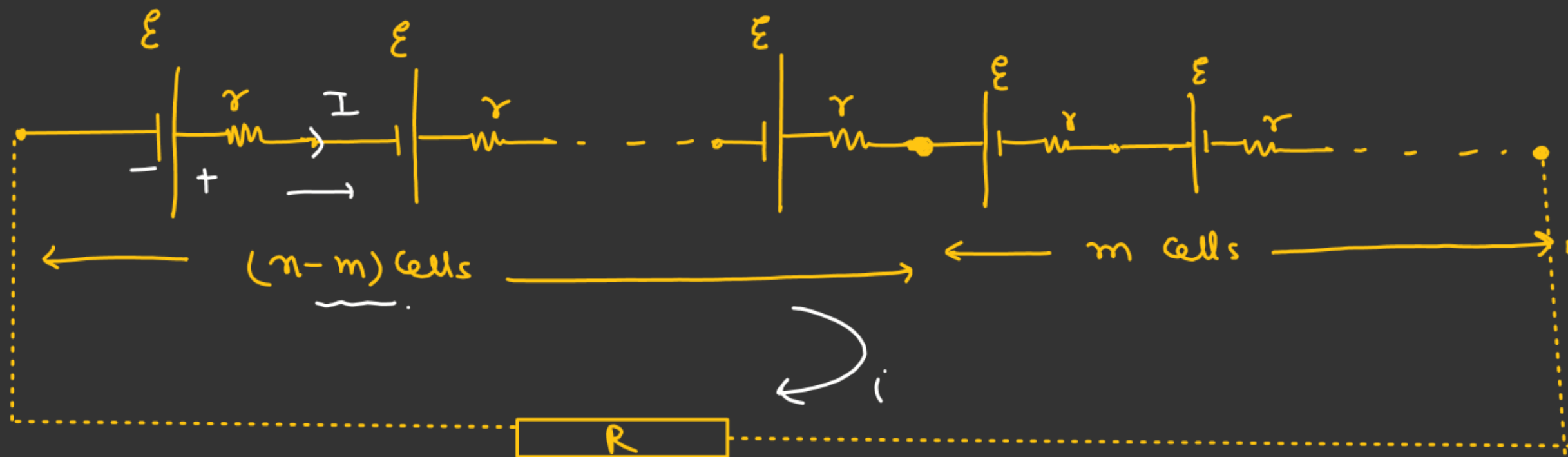
$$I = \frac{\mathcal{E}[n-2m]}{(nr+R)} \checkmark$$



CURRENT ELECTRICITY

Parallel Combination of battery:-

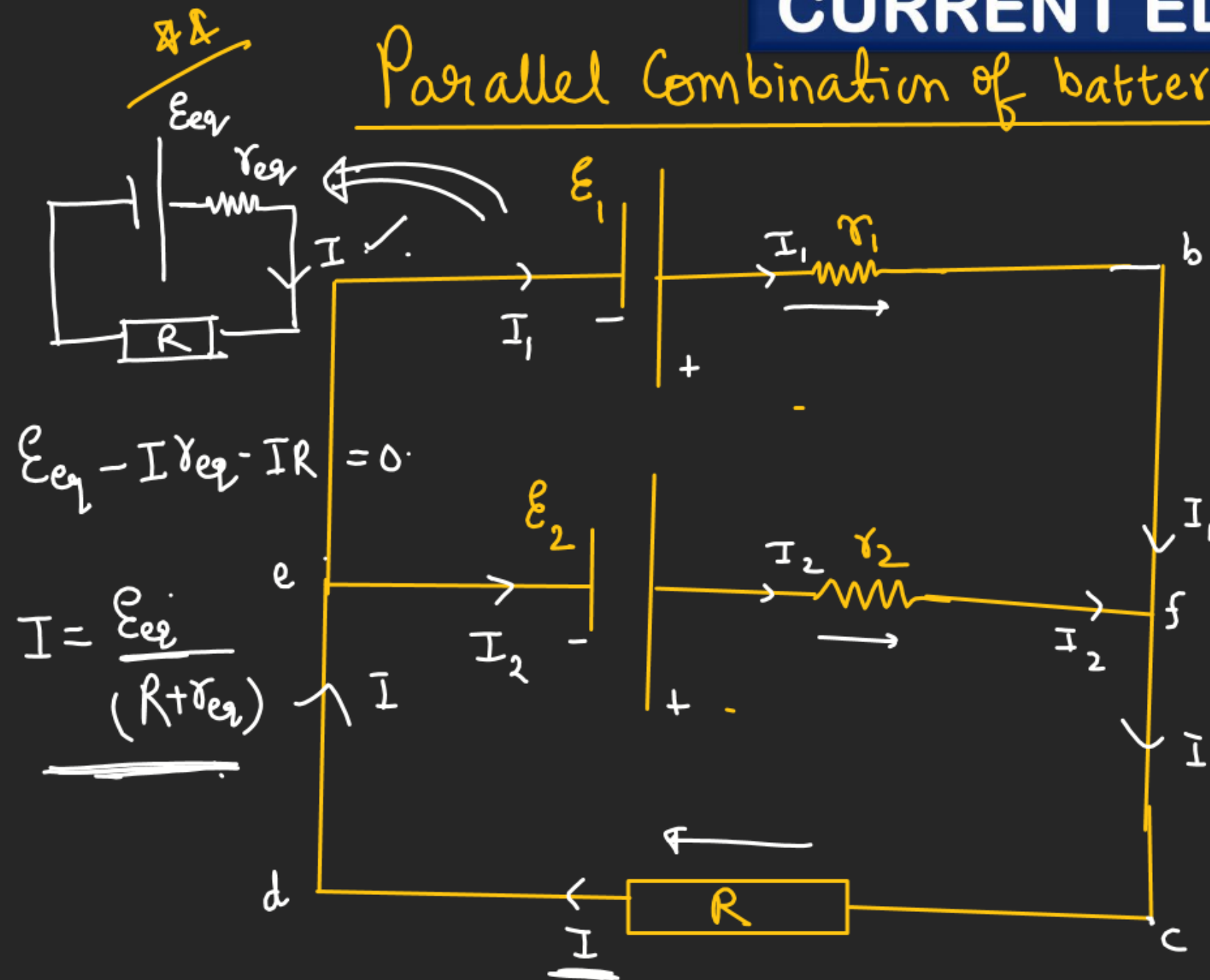

K.V.L in loop $a b c d a$:-

$$\epsilon_1 - I_1 r_1 - IR = 0$$

$$I_1 = \frac{(\epsilon_1 - IR)}{r_1}$$

K.V.L in loop $c d e f c$

$$\epsilon_2 - I_2 r_2 - IR = 0$$

$$I_2 = \frac{(\epsilon_2 - IR)}{r_2}$$

$$I = I_1 + I_2$$

$$I = \left(\frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2} \right) - IR \left(\frac{1}{r_1} + \frac{1}{r_2} \right)$$

$$I \left[1 + R \left(\frac{1}{r_1} + \frac{1}{r_2} \right) \right] = \left(\frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2} \right)$$

CURRENT ELECTRICITY

$$I = \left[\frac{\mathcal{E}_1/r_1 + \mathcal{E}_2/r_2}{1 + R \left(\frac{1}{r_1} + \frac{1}{r_2} \right)} \right]$$

$$I = \frac{\mathcal{E}_1/r_1 + \mathcal{E}_2/r_2}{\left(\frac{1}{r_1} + \frac{1}{r_2} \right) \left[\frac{1}{\left(\frac{1}{r_1} + \frac{1}{r_2} \right)} + R \right]}$$

$$I = \frac{\left(\frac{\mathcal{E}_1/r_1 + \mathcal{E}_2/r_2}{1/r_1 + 1/r_2} \right)}{\left(R + \frac{1}{\left(1/r_1 + 1/r_2 \right)} \right)}$$

$$I = \left(\frac{\mathcal{E}_{eq}}{r_{eq} + R} \right)$$

For n-battery

$$\mathcal{E}_{eq} = \frac{\sum_{i=1}^n \frac{\mathcal{E}_i}{r_i}}{\sum_{i=1}^n \frac{1}{r_i}}$$


$$\mathcal{E}_{eq} = \frac{\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2}}{1/r_1 + 1/r_2}$$

$$r_{eq} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2}} = \left(\frac{r_1 r_2}{r_1 + r_2} \right)$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$$

CURRENT ELECTRICITY

#

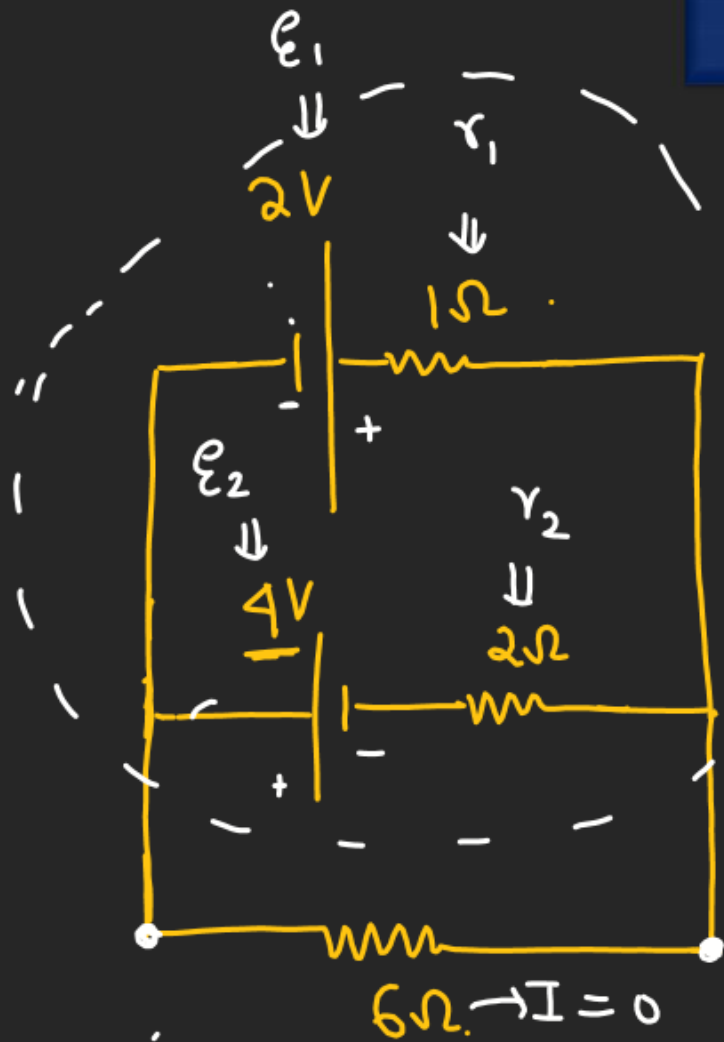


Find Current in 6Ω .

$$\mathcal{E}_{eq} = \frac{\left(-\frac{2}{1} + \frac{4}{2}\right)}{\left(1 + \frac{1}{2}\right)}$$

$$\boxed{\mathcal{E}_{eq} = 0}$$

#

Find Current in $R = ?$.

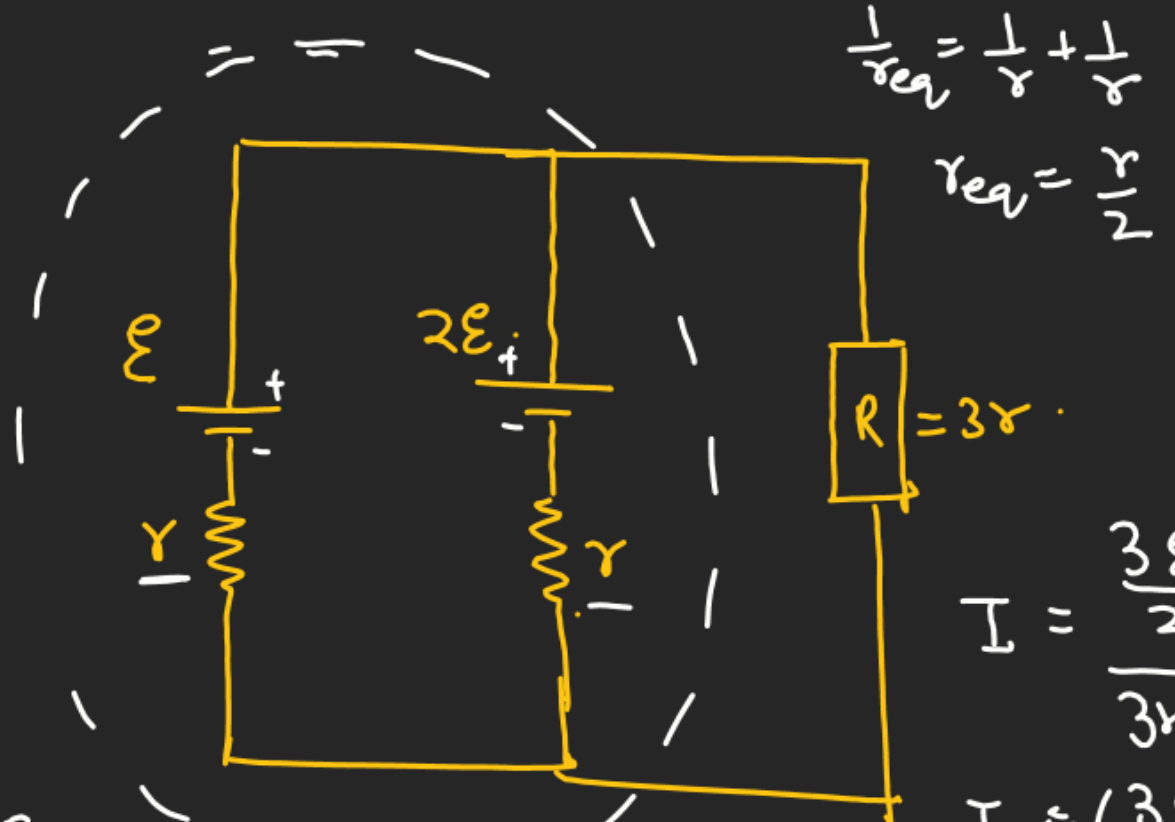

$$\frac{1}{r_{eq}} = \frac{1}{r} + \frac{1}{r}$$

$$r_{eq} = \frac{r}{2}$$

$$I = \frac{\frac{3\varepsilon}{2}}{3r + \frac{r}{2}}$$

$$I = \left(\frac{3\varepsilon}{7r}\right)$$

$$\mathcal{E}_{eq} = \frac{\frac{\varepsilon}{r} + \frac{2\varepsilon}{r}}{\frac{1}{r} + \frac{1}{r}}$$

$$\mathcal{E}_{eq} = \frac{3\varepsilon/r}{2/r} = \left(\frac{3\varepsilon}{2}\right)$$

