


DPP 2


SOLUTION

Link to View Video Solution:  [Click Here](#)

$$1. \quad E_{\text{net}} = \frac{\frac{\epsilon_1 + \epsilon_2 + \epsilon_3}{r_1 + r_2 + r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}}$$

$$= \frac{\frac{2 + 4 + 6}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{12}{3} = 4 \text{ volt}$$

Potential of $V_0 = 4 \text{ volt}$

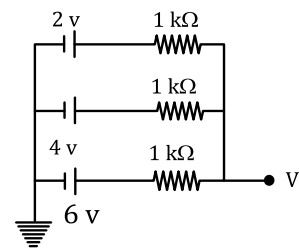

$$2. \quad \epsilon_{\text{net}} = \epsilon_1 + \epsilon_2$$

$$R_{\text{net}} = r_1 + r_2 + R$$

$$I = \frac{\epsilon_1 + \epsilon_2}{r_1 + r_2 + R}$$

$$\epsilon_1 - Ir_1 = 0$$

$$\epsilon_1 - \left(\frac{\epsilon_1 + \epsilon_2}{r_1 + r_2 + R} \right) r_1 = 0$$


$$\epsilon_1 = \epsilon_2 = \epsilon \text{ given}$$

$$\epsilon - \frac{2\epsilon r_1}{r_1 + r_2 + R} = 0$$

$$1 = \frac{2r_1}{r_1 + r_2 + R}$$

$$r_1 + r_2 + R = 2r_1$$

$$\frac{r_1 = r_2 + R}{R = r_1 - r_2}$$

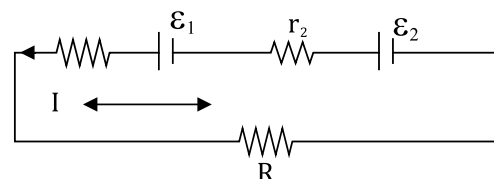

$$3. \quad \epsilon_{\text{net}} = \epsilon_1 + \epsilon_2$$

$$R_{\text{net}} = r_1 + r_2 + R$$

$$I = \frac{\epsilon_1 + \epsilon_2}{r_1 + r_2 + R}$$

$$\epsilon_1 - Ir_1 = 0$$

$$\epsilon_1 - \left(\frac{\epsilon_1 + \epsilon_2}{r_1 + r_2 + R} \right) r_1 = 0$$

$$\epsilon_1 = \epsilon_2 = \epsilon \text{ given}$$

$$\epsilon - \frac{2\epsilon r_1}{r_1 + r_2 + R} = 0$$

$$1 = \frac{2r_1}{r_1 + r_2 + R}$$


$$r_1 + r_2 + R = 2r_1$$

Link to View Video Solution: [Click Here](#)

$$\frac{r_1 = r_2 + R}{R = r_1 - r_2}$$

Only one value of R exist for which potential difference across battery having internal resistance r_1 is zero.

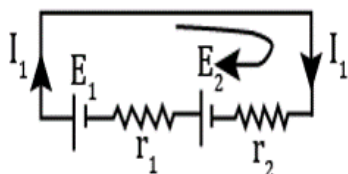4. The correct option is $AE_1 = \frac{I_1 + I_2}{I_1 - I_2} E_2$



Using kirchhoff's loop law, we get:

$$-I_1 r_2 + E_2 - I_1 r_1 + E_1 = 0$$

$$\frac{E_1 + E_2}{r_1 + r_2} = I_1 \dots (1)$$



Again using kirchhoff's loop law:


$$E_1 - I_2 r_1 - E_2 - I_2 r_2 = 0$$

$$\frac{(E_1 - E_2)}{r_1 + r_2} = I_2 \dots (2)$$

From equation (1) and (2):

$$\frac{E_1 + E_2}{E_1 - E_2} = \frac{I_1}{I_2} \Rightarrow E_1 = \frac{(I_1 + I_2)}{I_1 - I_2} E_2$$


5. first in series connection

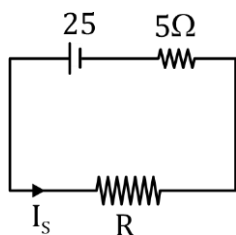

$$I_s = \frac{25}{5 + R}$$

In parallel connection

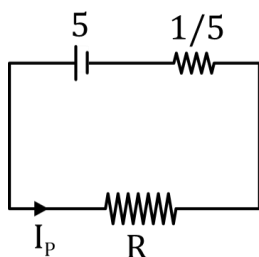Link to View Video Solution: [Click Here](#)



$$I_p = \frac{5}{R + 1/5}$$


$$I_p = I_s \Rightarrow \frac{25}{5+R} = \frac{5}{\frac{5R+1}{5}}$$

$$5R + 1 = 5 + R$$

$$4R = 4$$

$$R = 1\Omega$$

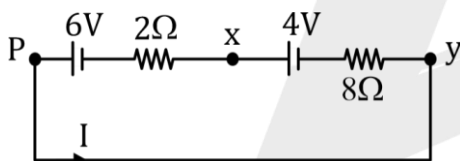6. $\epsilon_{\text{net}} = 6 - 4 = 2 \text{ volt } [-4 \text{ V}]$



$$I = \frac{2}{10} = 0.2 \text{ Amp}$$

$$V_x + 4 + 8 \times 0.2 = V_y$$


$$V_x - V_y = -5.6 \text{ volt}$$

$$V_y - V_x = 5.6 \text{ volt}$$

7. $V_A + 1 + 2 - 2 = V_B$


$$V_A - V_B = -1 \text{ volt}$$

$$V_B - V_A = 1 \text{ volt}$$

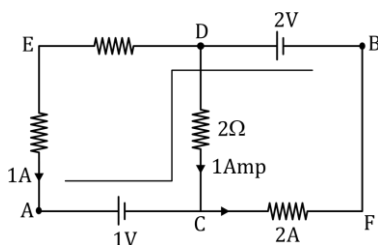

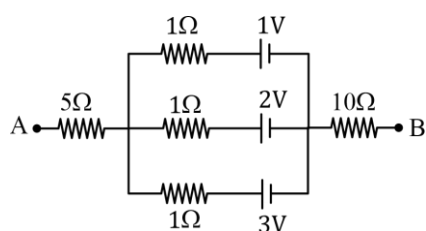
8. $\epsilon_{\text{net}} = \frac{1/1 + 2/1 + 3/1}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{6}{3} = 2 \text{ volt}$

Link to View Video Solution: [Click Here](#)



$$\Rightarrow \frac{1}{r_{eq}} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1}$$


$$r_{eq} = \frac{1}{3} \Omega$$

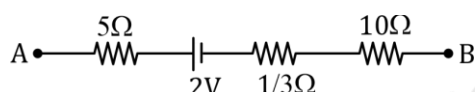

$$v_A - 2 = v_B \quad i=0$$


$$v_A - v_B = 2 \text{ volt}$$

9.

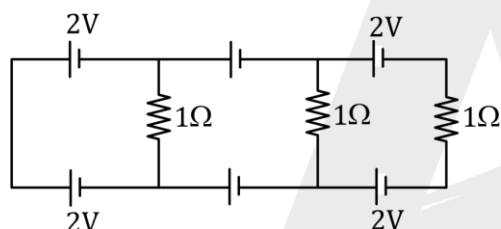

0.

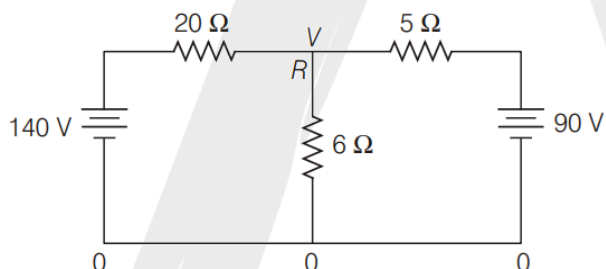10. The given figure can be represented as



From the above figure, it can be clearly seen that the voltage across point R is assumed as V .

Therefore, applying Kirchhoff's current law at point R , we can write

$$\frac{V-0}{6} + \frac{V-90}{5} + \frac{V-140}{20} = 0$$

$$\Rightarrow \frac{V}{6} + \frac{V-90}{5} + \frac{V-140}{20} = 0$$

$$\Rightarrow \frac{10V + 12V - 1080 + 3V - 420}{60} = 0$$

$$\Rightarrow 25V = 1500 \Rightarrow V = 60V$$

Therefore, current through 6Ω resistor is

$$I = \frac{V}{R} = \frac{60}{6} = 10A$$