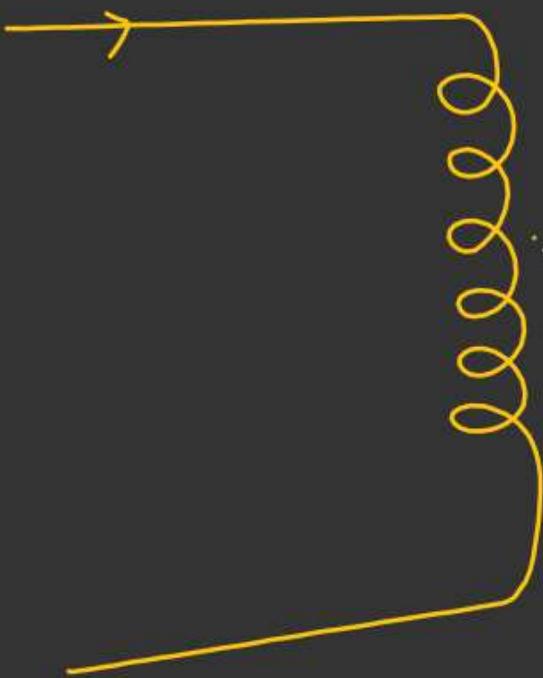


~~Δ&~~L-R Circ $i \rightarrow \frac{di}{dt}$  increasing

$$\frac{1}{T} |\mathcal{E}_L| = L \frac{di}{dt}$$

 $i \rightarrow \frac{di}{dt}$  (decreasing)


$$\frac{1}{T} |\mathcal{E}_L| = L \frac{di}{dt}$$

$$\phi_{self} = L i$$


$$\mathcal{E}_{self} = - \frac{d\phi_{self}}{dt} = -L \frac{di}{dt}$$

L-R Ckt  Growth of Current  
At  $t=0$ , SW closed, let at  $t=t$

current in the Ckt is

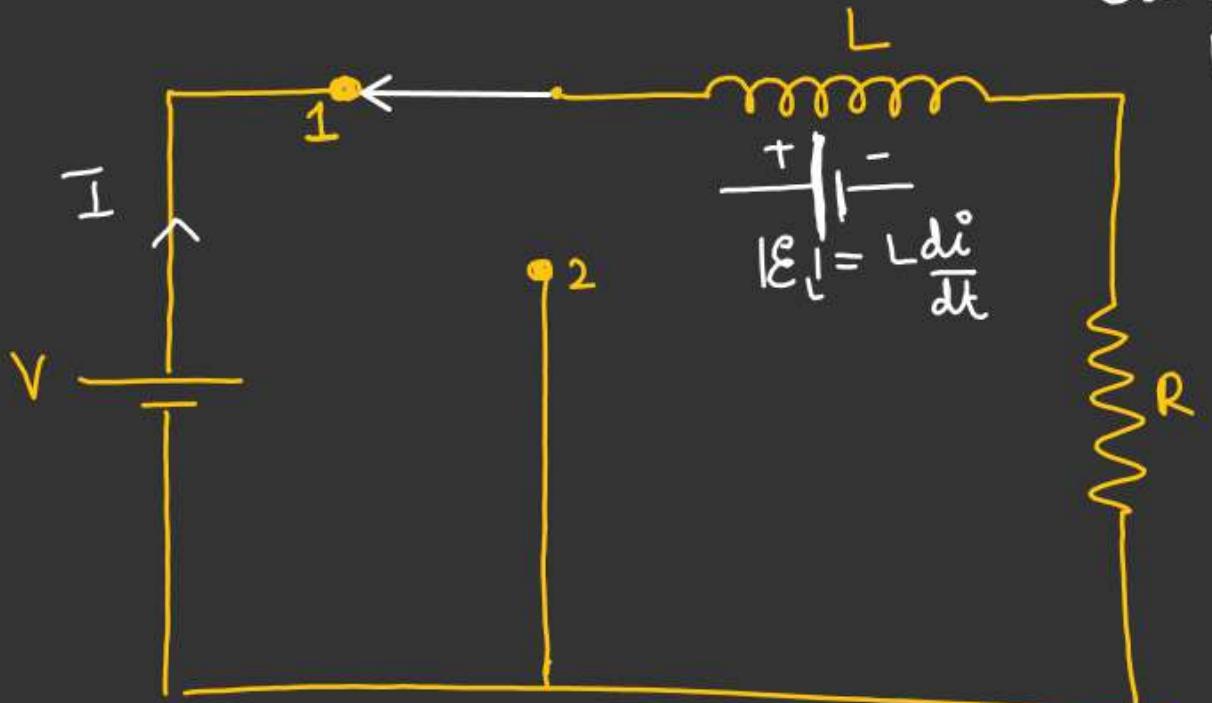

$$|E_L| = L \frac{di}{dt}$$

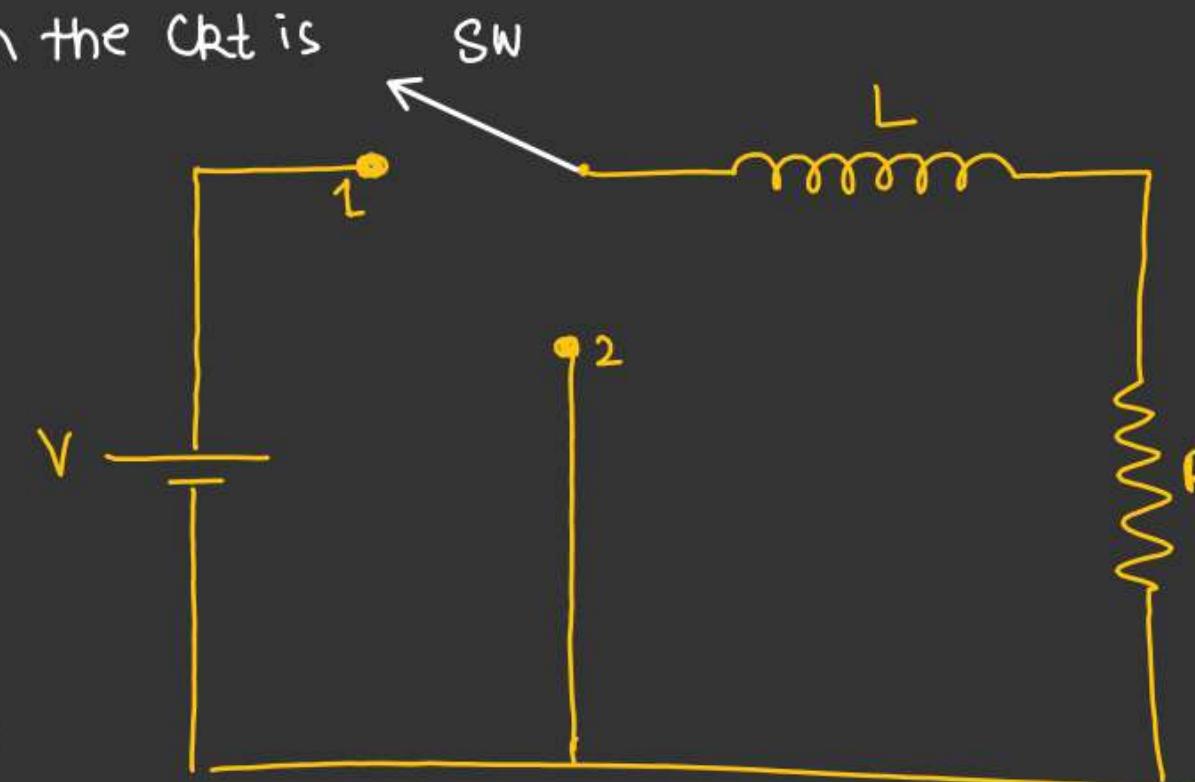

$\frac{K-V \cdot L}{V - L \frac{di}{dt} - iR} \quad (\text{At } t=t)$

$$V - L \frac{di}{dt} - iR = 0$$

$$(V - iR) = L \frac{di}{dt}$$

$$\int_0^i \frac{di}{V - iR} = \frac{1}{L} \int_0^t dt$$

$$\frac{\ln(V - iR)}{-R} \Big|_0^i = \frac{1}{L} t$$

$$\ln \left[ \frac{V - iR}{V} \right] = -\frac{R}{L} t$$

$$V - iR = V e^{-\frac{R}{L} t}$$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L} t})$$

$$i = \frac{V}{R} (1 - e^{-t/\tau})$$

$$\frac{1}{\tau} = \frac{R}{L}$$

$$\tau = \frac{L}{R}$$

Time constant of L-R Ckt

Rate of Change of  $i$

$$\frac{di}{dt} = -\frac{V}{R} e^{(-t/\tau)} \cdot \left( -\frac{1}{\tau} \right)$$

$$\frac{di}{dt} = \frac{V}{R\tau} e^{(-t/\tau)}$$

$$\frac{di}{dt} = \frac{V}{L} (e^{-t/\tau})$$

Inductor behave  
as a open ckt


At  $t = 0$

$$L \left( \frac{di}{dt} \right) = V e^{-t/\tau}$$

$$\mathcal{E}_{self} = V e^{-t/\tau}$$

At  $t = 0$ ,

$$(\mathcal{E}_{self})_{max} = V$$

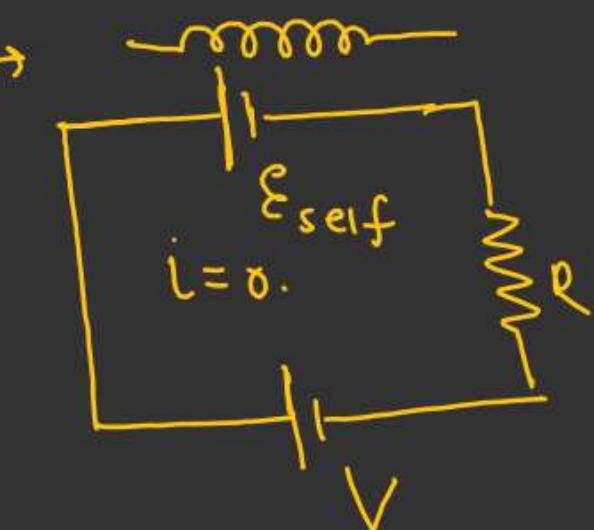


$$i = \frac{V}{R} (1 - e^{-t/\tau})$$

$i_{\max} = \left(\frac{V}{R}\right)$   $\rightarrow$  At  $t \rightarrow \infty$   
i.e very long time.

$$\mathcal{E}_{\text{self}} = V e^{-t/\tau}$$

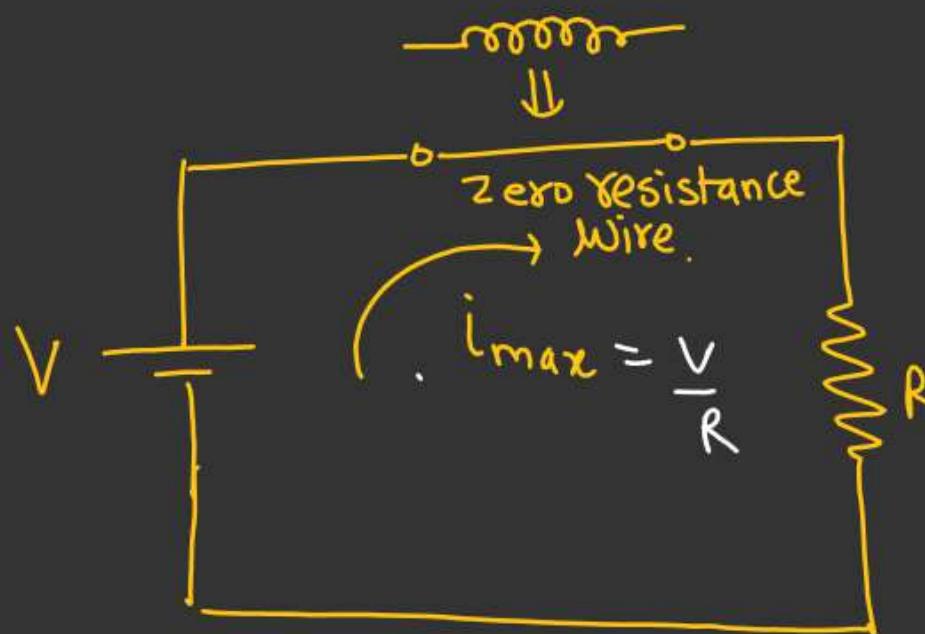At  $t \rightarrow \infty$  }  $\Rightarrow$  After very long  
 $\mathcal{E}_{\text{self}} = 0$  time inductor behave  
as a zero resistance  
wire.



$$\overset{\circ}{i} = \frac{V}{R} (1 - e^{-t/\tau}) \quad (\tau = L/R)$$

~~Q~~: Heat dissipated across resistance

$$V_R = \overset{\circ}{i} R = V (1 - e^{-t/\tau})$$

$$P = I^2 R.$$

$$E_{self} = L \frac{di}{dt} = (V e^{-t/\tau})$$

~~Q~~: Charge flow as a function of time.

$$\overset{Q}{\rightarrow} \frac{dq}{dt} = \frac{V}{R} (1 - e^{-t/\tau})$$

$$\int_0^t dq = \frac{V}{R} \int_0^t (1 - e^{-t/\tau}) dt$$

$$\frac{dH}{dt} = \frac{V^2}{R} (1 - e^{-t/\tau})^2$$

$$\int_0^H dH = \frac{V^2}{R} \int_0^t (1 - e^{-t/\tau})^2 dt$$

$$\Downarrow H = ??$$

~~RR~~: Avg power in L-R Ckt.

$$P_{\text{inst}} = \frac{V^2}{R} = \frac{V^2}{R^2} (1 - e^{-t/\tau})^2 \times R$$

$$P_{\text{inst}} = \frac{V^2}{R} (1 - e^{-t/\tau})^2$$

$$\overline{P}_{\text{avg}} = \frac{\int_0^t P \cdot dt}{\int_0^t dt}$$

Ex:- Avg power in one time constant.

$$\overline{P}_{\text{avg}} = \left( \frac{V^2}{R} \right) \frac{\int_0^\tau (1 - e^{-t/\tau})^2 dt}{\int_0^\tau dt}$$

$$\overline{P}_{\text{avg}} = \frac{V^2}{\tau R} \left[ \int_0^\tau (1 + e^{-2t/\tau} - 2e^{-t/\tau}) dt \right]$$

$$\overline{P}_{\text{avg}} = \frac{V^2}{\tau R} \left[ \int_0^\tau dt + \int_0^\tau e^{-2t/\tau} dt - 2 \int_0^\tau e^{-t/\tau} dt \right]$$

$$\overline{P}_{\text{avg}} = \frac{V^2}{\tau R} \left[ \tau + \left[ \frac{e^{-2t/\tau}}{-2/\tau} \right]_0^\tau - 2 \left[ \frac{e^{-t/\tau}}{-1/\tau} \right]_0^\tau \right]$$

??

Time Constant of L-R Ckt.

In terms of growth of Current.


$$I = \frac{V}{R} (1 - e^{-t/\tau})$$

$$A + t = \tau$$

$$I = \frac{V}{R} (1 - e^{-1}) = \left( \frac{V}{R} \right) \left( 1 - \frac{1}{e} \right)$$



$$I = 63\% \text{ of } I_{max}$$

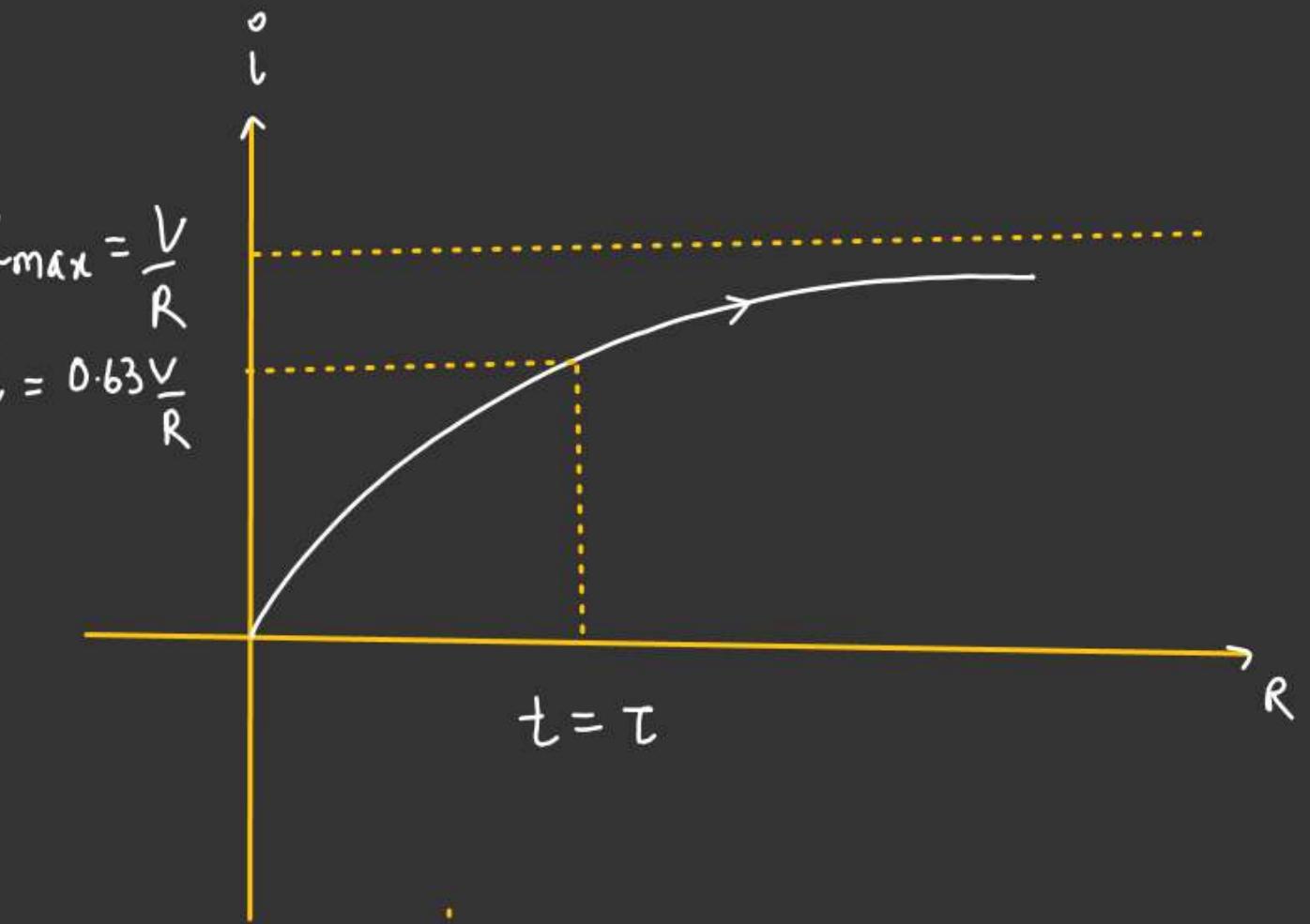↓  
 Time when Current build-up  
 in the Ckt is 63% of its maximum  
 Value






## Decay of Current

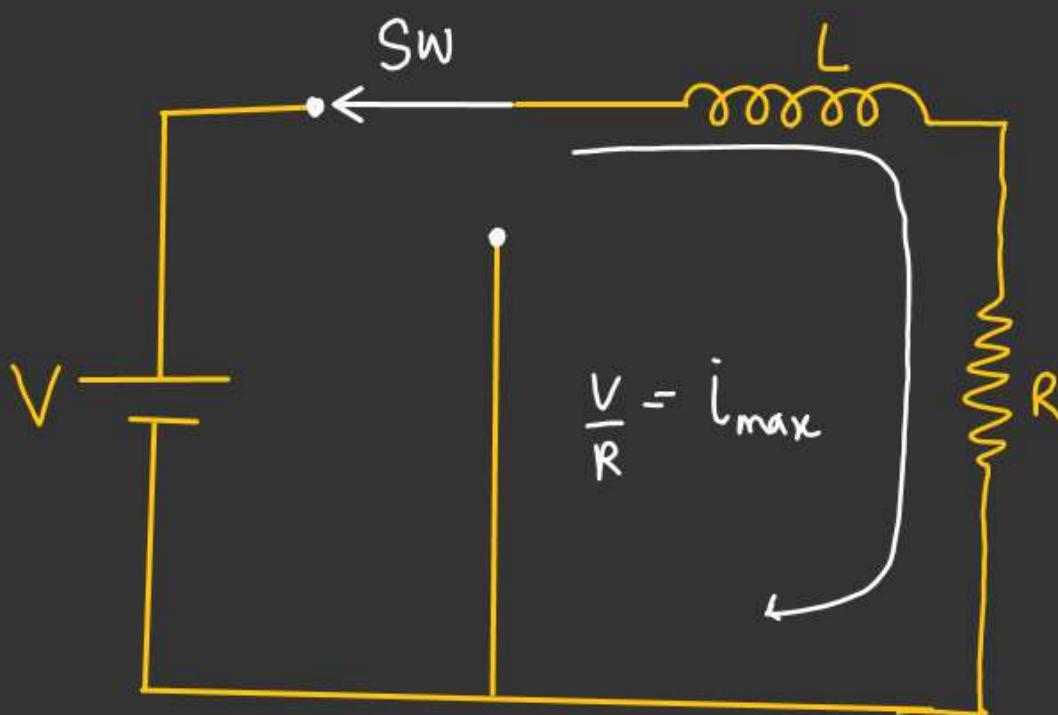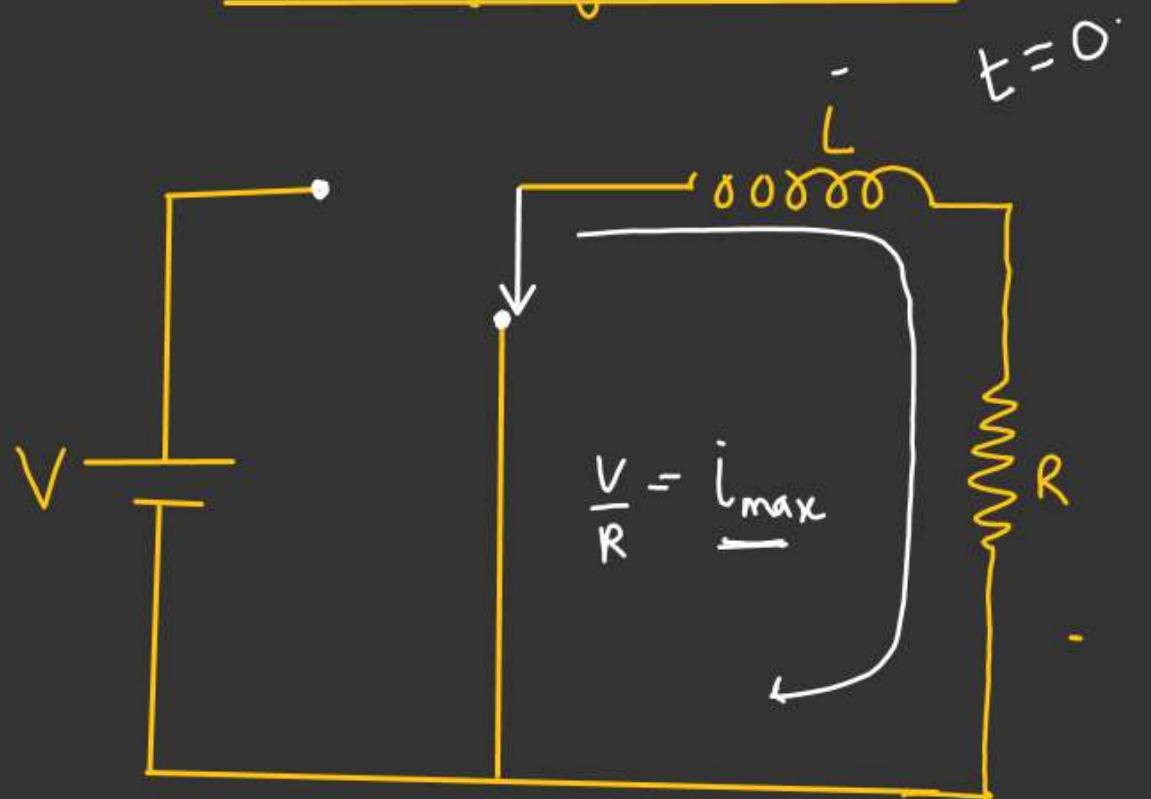

~~xx~~

## Decay of Current

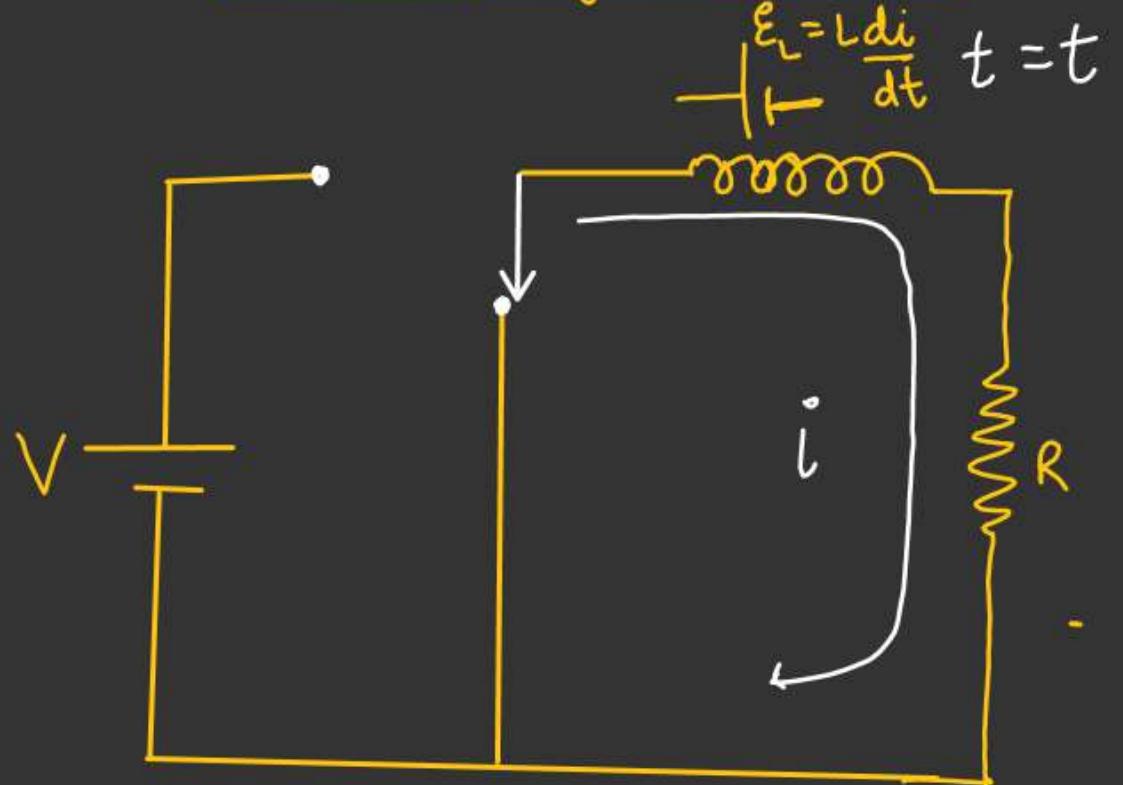

$$\text{---} \int \frac{e_L}{t} = L \frac{di}{dt} \quad t = t$$

K.V.L.

$$-L \frac{di}{dt} - iR = 0$$

$$-L \frac{di}{dt} = iR$$

$$-\int \frac{di}{i} = \frac{R}{L} \int dt$$

$$-\ln \left( \frac{i}{i_{\max}} \right) = \frac{R}{L} t$$

present value in  
the Ckt.  $\rightarrow$

$$i = i_{\max} e^{-R/L t}$$

$$i = \frac{V}{R} e^{-t/\tau}$$

Decay of  
Current in  
 $L-R$  Ckt


$\tau$ . ( Decay of  
Current ) .

At  $t = \tau$ .

$$I = \frac{V}{R} \left( \frac{1}{e} \right)$$

$$I = 0.37 \left( \frac{V}{R} \right) = 0.37 I_{\max}$$

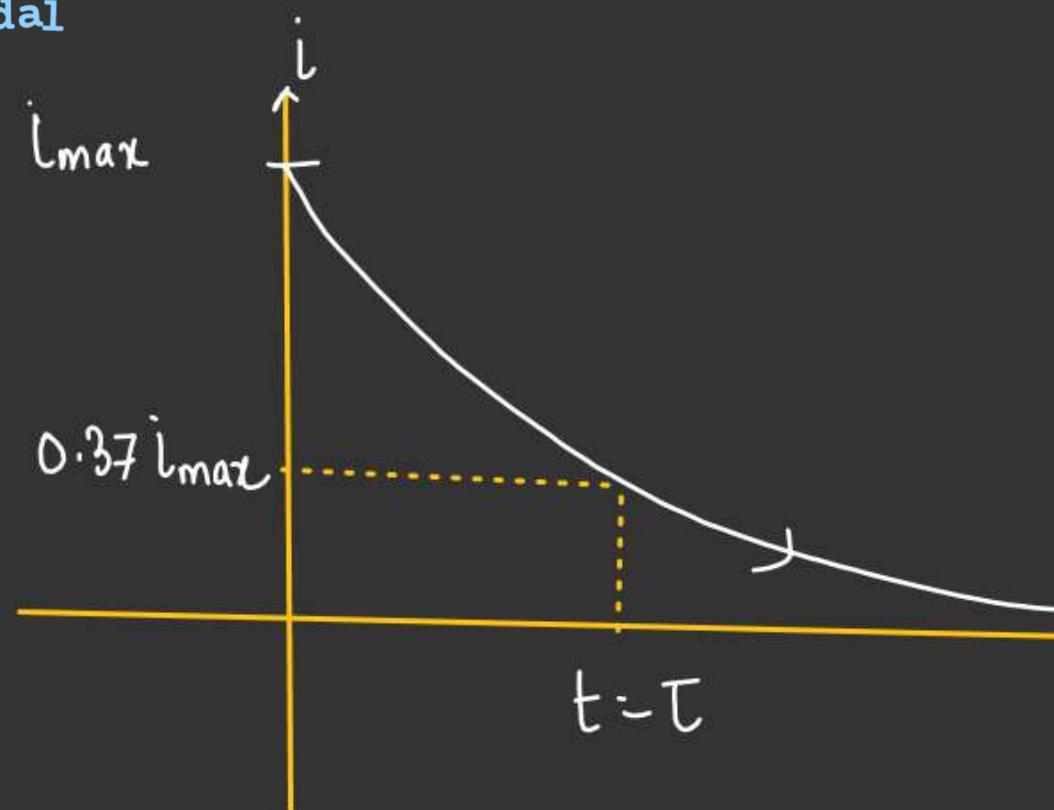Time when 63% of  
current has been  
decayed. or 37% of  
current present.



$$\text{Ans: } i = \frac{V}{R} e^{-t/\tau}$$

Charge flow

$$\frac{dq}{dt} = \frac{V}{R} e^{-t/\tau}$$

$$\int_0^t dq = \frac{V}{R} \int_0^t e^{-t/\tau} dt$$

Heat dissipation

$$P = i^2 R$$

$$\frac{dH}{dt} = \frac{V^2}{R} e^{-2t/\tau}$$

$$\int_0^t dH = \frac{V^2}{R} \int_0^t e^{-2t/\tau} dt$$

Avg. power

$$P_{avg} = \frac{\int_0^t P dt}{\int_0^t dt}$$

$$P_{avg} = \frac{\int_0^t i^2 R dt}{\int_0^t dt}$$