

✖✖

## L-C-R Series




graph

At the time of  
Resonance ( $Z_{\min} = R$ )

$$I_{\max} = I_0 = \left( \frac{\mathcal{E}_0}{R} \right)$$

$$I = \frac{\mathcal{E}}{|Z|} \sin(\omega t + \phi)$$

$$|Z| = \sqrt{R^2 + \left| \omega L - \frac{1}{\omega C} \right|^2}$$

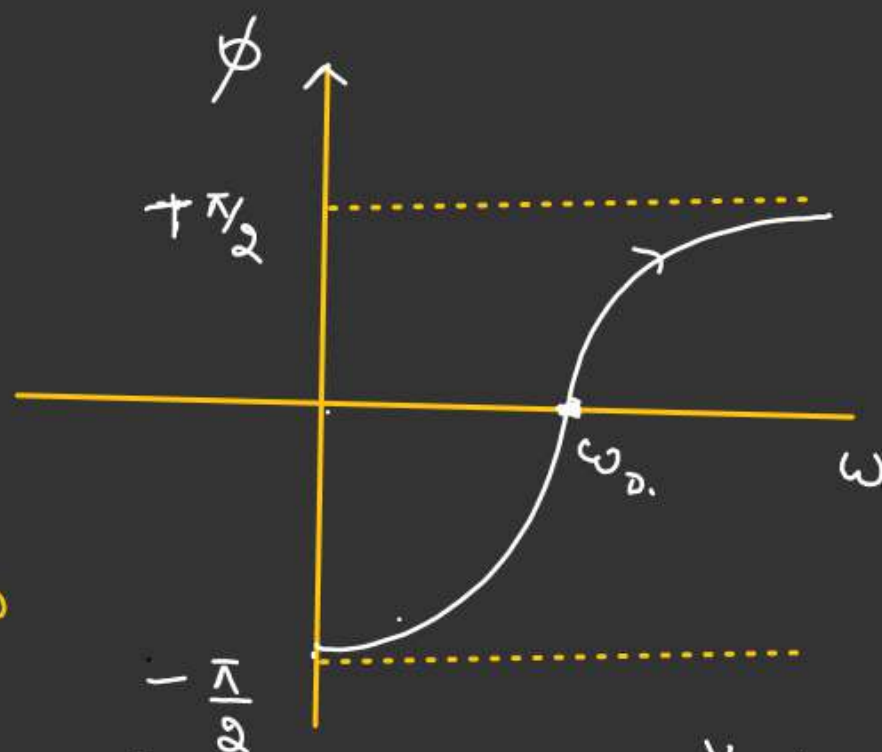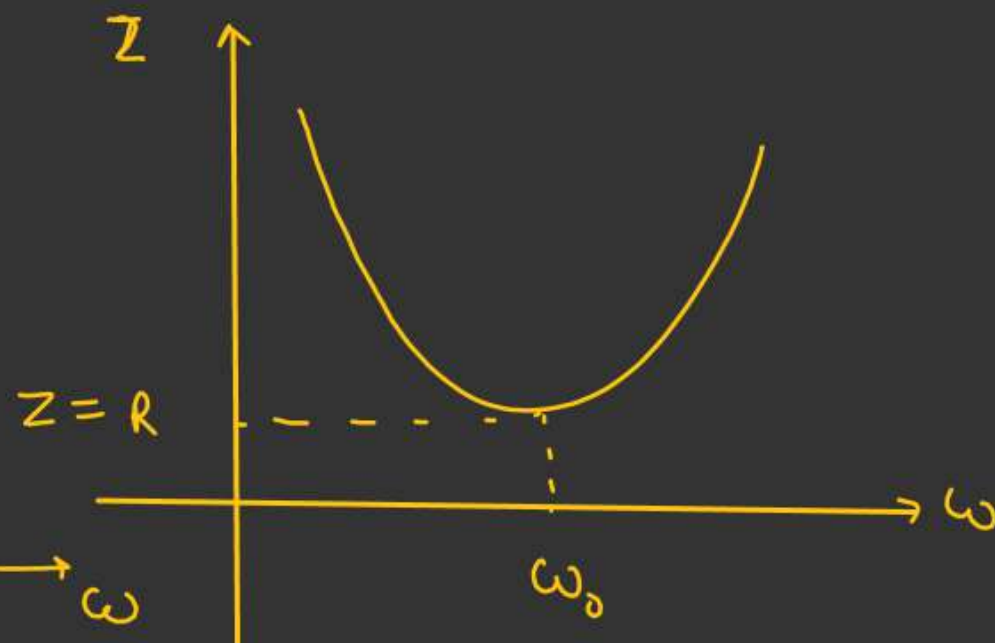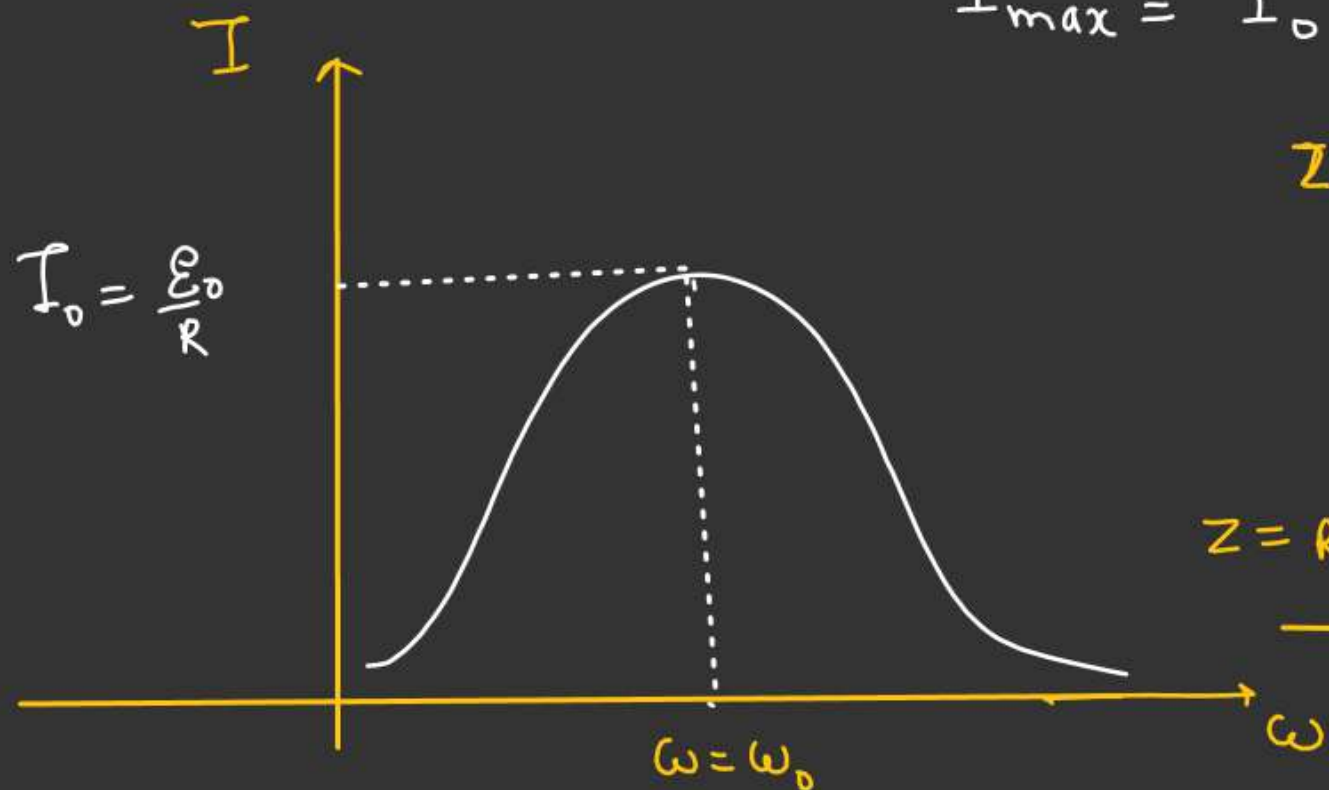

$$\tan \phi = \left| \frac{\omega L - \frac{1}{\omega C}}{R} \right|$$



# Quality Factor [JEE MAINS]

↳ gives the Idea about Sharpness of I vs  $\omega$  curve at the time of resonance.

↳  $Q = \left( \frac{\text{Voltage across L or C}}{\text{Maximum applied voltage}} \right)$

$$Q = \frac{IX_L}{IR}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{X_L}{R} = \frac{\omega_0 L}{R}$$

★ ★

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

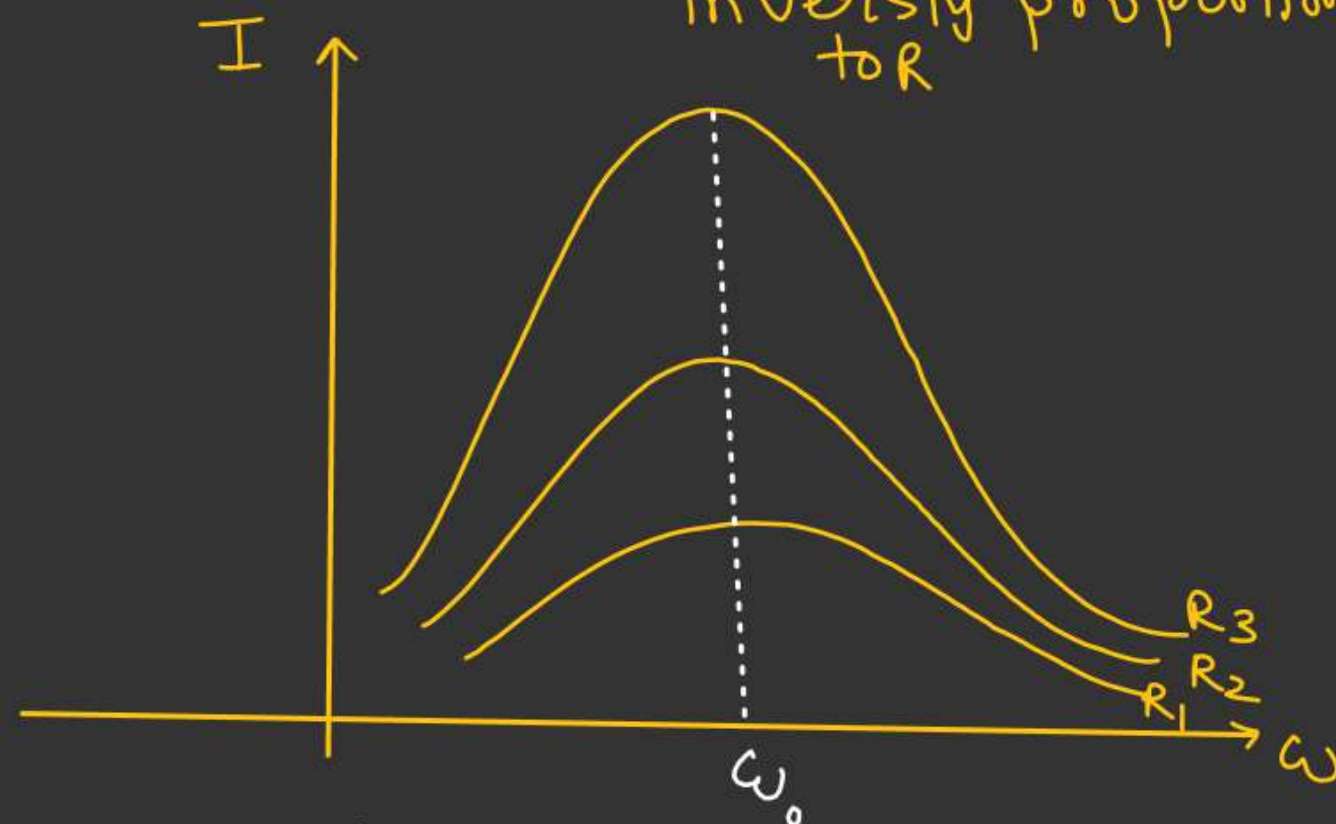$Q \propto \frac{1}{R} \Rightarrow$  Sharpness of the Curve is inversely proportional to R



$\Rightarrow \underline{R_3 < R_2 < R_1}$  ✓

Another way to defined Quality factor

$$Q = \frac{2\pi \left[ \begin{array}{l} \text{Maximum Energy} \\ \text{Stored in a inductor or Capacitor} \end{array} \right]}{\text{Energy loss per Cycle.}}$$

$$U_{\max} = \frac{1}{2} L I_0^2$$

$$P_{\text{avg}} = I_{\text{rms}}^2 R = \left( \frac{I_0}{\sqrt{2}} \right)^2 R$$

$$E = \left( \frac{I_0^2 R}{2} \right) T$$

$$Q = \frac{2\pi}{T} \left( \frac{\frac{1}{2} L I_0^2}{\frac{I_0^2 R}{2}} \right)$$

$$Q = \frac{\omega_0 L}{R}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$



Ex. 1

## Bandwidth of L-C-R Series Ckt

Let,  $I$  be the Current in L-C-R Series Ckt for which power dissipation is half of the maximum power dissipated.

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}}$$

$$P_{\max} = I_0^2 R$$


$$I^2 R = \frac{I_0^2 R}{2}$$

$$I = \left(\frac{I_0}{\sqrt{2}}\right) = \left(\frac{\mathcal{E}_0}{R\sqrt{2}}\right)$$

$$\frac{\mathcal{E}_0}{R\sqrt{2}} = \frac{\mathcal{E}_0}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}}$$

$$R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2 = 2R^2$$
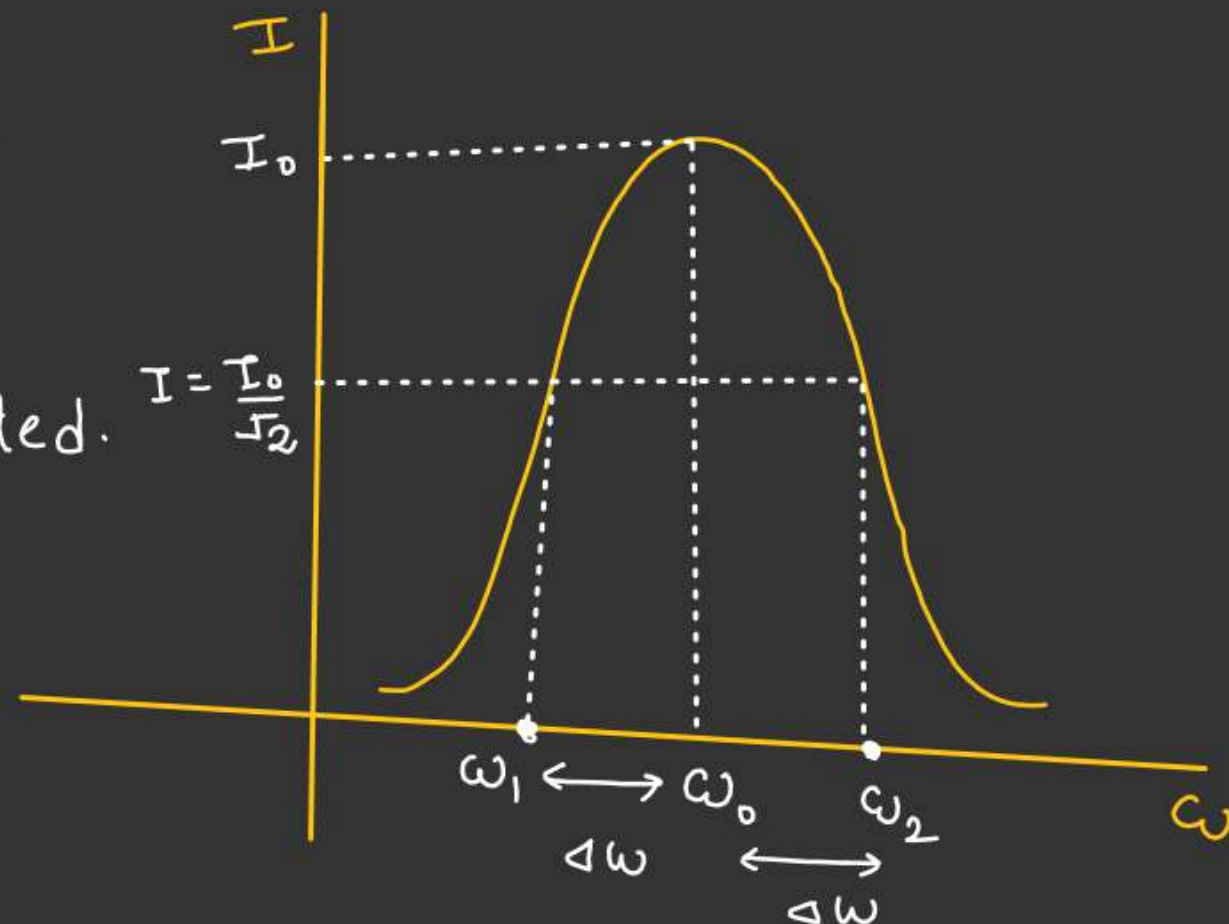
$$\left(\frac{1}{\omega C} - \omega L\right)^2 = R^2$$



$$\omega_2 - \omega_1 = (2\Delta\omega)$$

$$\left(\frac{1}{\omega C} - \omega L\right)^2 = R^2$$

$$\frac{1}{\omega C} - \omega L = \pm R$$

$$1 - \omega^2(LC) = \pm RC\omega$$

$$(LC)\omega^2 \pm (RC)\omega - 1 = 0$$

$\omega$

$$\omega = \frac{\mp RC + \sqrt{R^2 C^2 + 4LC}}{2LC}$$

$$\checkmark \omega_1 = \frac{-RC + \sqrt{R^2 C^2 + 4LC}}{2LC}, \quad \omega_2 = \frac{RC + \sqrt{R^2 C^2 + 4LC}}{2LC}$$

$$\omega_2 - \omega_1 = \Delta\omega = \frac{2RC}{2LC}$$

$$\omega_2 - \omega_1 = 2\Delta\omega = \frac{R}{L}$$

Bandwidth directly proportional to  $R$

$$\omega_1 \omega_2 = \frac{1}{LC}$$

Relation b/w Quality factor and bandwidth

$$Q = \left( \frac{\omega_0}{2\Delta\omega} \right)$$

$$\omega_2 - \omega_1 = R/L \checkmark$$

$$\left( \underline{Q_0} = \frac{\omega_0 R}{L} \right)$$

~~Q~~

$$Q = \left( \frac{\omega_0}{\omega_2 - \omega_1} \right)$$

[Quality factor is inversely  
proportional to bandwidth]



# ALTERNATING CURRENT

**Q.1** A series R – C combination is connected to an AC voltage of angular frequency  $\omega = 500 \text{ radian/s}$ . If the impedance of the R – C circuit is  $R\sqrt{1.25}$ , the time constant (in millisecond) of the circuit is (2011)

Sol<sup>n</sup> :-



$$R^2 + \frac{1}{\omega^2 C^2} = Z^2$$

$$R^2 + \frac{1}{\omega^2 C^2} = R^2 (1.25)$$

$$\frac{1}{\omega^2 C^2} = 0.25 R^2$$

$$C^2 = \frac{1}{\omega^2 \times 0.25 R^2} \quad \checkmark$$
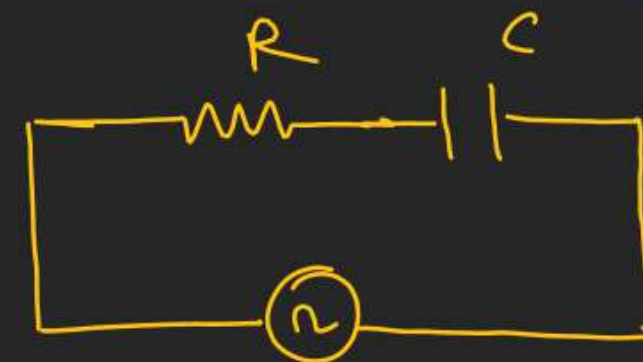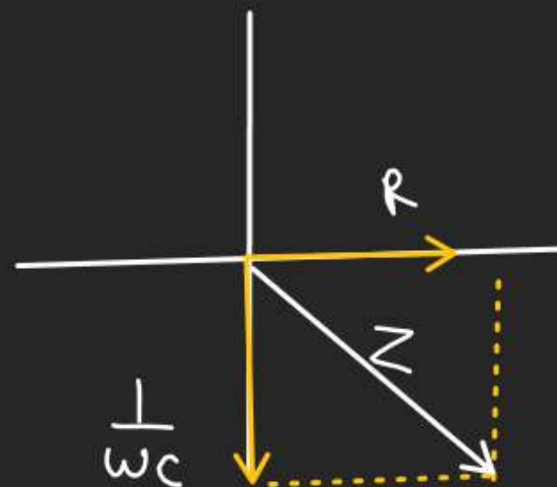
$$C = \frac{1}{\omega \times 0.5 \times R} = \frac{1}{500 \times 0.5 \times R}$$



$$\Rightarrow T = RC = \frac{1}{25} \times 10^{-1}$$

$$= 0.04 \times 10^{-1}$$

$$= 4 \times 10^{-3}$$

(4) Ans

# ALTERNATING CURRENT

**Q.2** In a circuit, a metal filament lamp is connected in series with a capacitor of capacitance  $C \mu\text{F}$  across a  $200 \text{ V}, 50 \text{ Hz}$  supply. The power consumed by the lamp is  $500 \text{ W}$  while the voltage drop across it is  $100 \text{ V}$ . Assume that there is no inductive load in the circuit. Take rms values of the voltages. The magnitude of the phase-angle (in degrees) between the current and the supply voltage is  $\phi$ . Assume  $\pi\sqrt{3} \approx 5$ .

1. The value of  $C$  is \_\_\_\_\_  $\mu\text{F}$

2. The value of  $\phi$  is \_\_\_\_\_

(2021)



$$P_R = \frac{V^2}{R}$$

$$R = \frac{V^2}{P_R} = \frac{10^4}{5 \times 10^2}$$

$$R = 0.2 \times 10^2$$

$$R = \underline{20 \Omega} \checkmark$$

$$\tan 60^\circ = \frac{X_C}{R}$$

$$\downarrow$$

$$20\sqrt{3} = X_C = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega \times 20 \times \sqrt{3}} = \frac{1}{100\pi \times 20 \times \sqrt{3}} = \frac{1}{5 \times 2 \times 10^3}$$


$$= 10^{-4} = 100 \times 10^{-6} = 100 \mu F$$

$$\tan \phi = \frac{V_C}{V_R}$$

$$\tan \phi = \frac{\sqrt{3} \times 10^2}{10^2}$$

$$\boxed{\phi = 60^\circ}$$

$$P_R = 500 \text{ Watt}$$

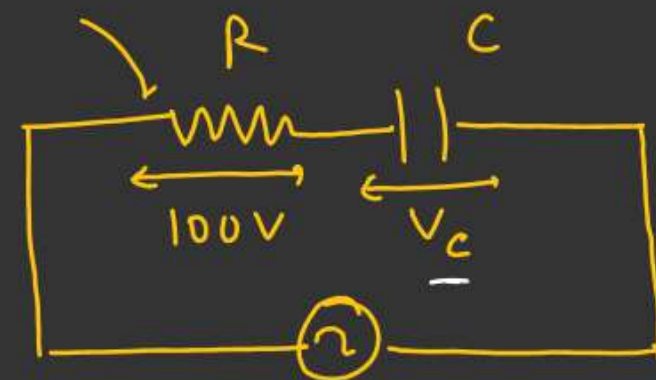


$$200V, 50Hz = f$$

$$\omega = 2\pi f$$

$$= 2\pi \times 50$$

$$= \underline{100\pi}$$

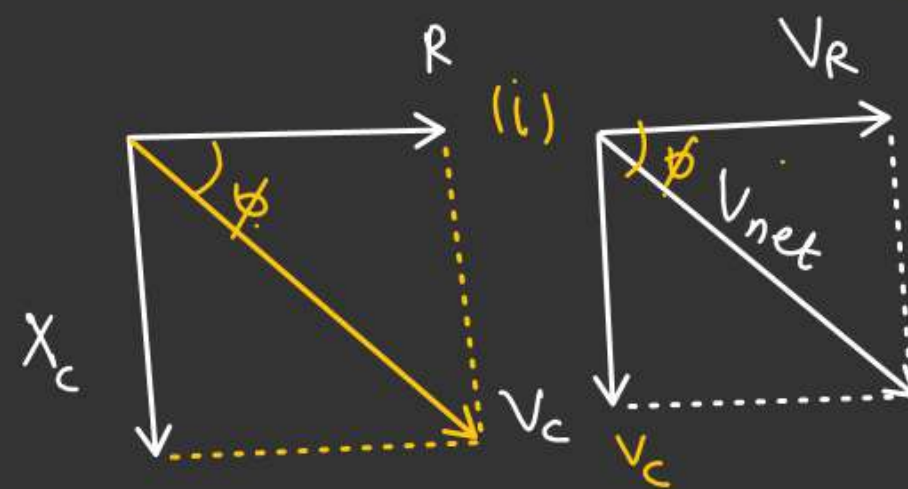

$$\underline{\tan \phi = \left( \frac{X_C}{R} \right)}$$

$$V_{net}^2 = V_R^2 + V_C^2$$

$$(200)^2 = (100)^2 + V_C^2$$

$$V_C^2 = (4 \times 10^4 - 1 \times 10^4)$$

$$V_C^2 = 3 \times 10^4$$

$$V_C = \sqrt{3} \times 10^2$$


**ALTERNATING CURRENT***H.W.*

**Q.3** Consider an LC circuit, with inductance  $L = 0.1\text{H}$  and capacitance  $C = 10^{-3}\text{ F}$ , kept on a plane. The area of the circuit is  $1\text{ m}^2$ . It is placed in a constant magnetic field of strength  $B_0$  which is perpendicular to the plane of the circuit. At time  $t = 0$ , the magnetic field strength starts increasing linearly as  $B = B_0 + \beta t$  with  $\beta = 0.04\text{ T s}^{-1}$ . The maximum magnitude of the current in the circuit is \_\_\_\_\_ mA. **(2022)**

# ALTERNATING CURRENT

H.W.

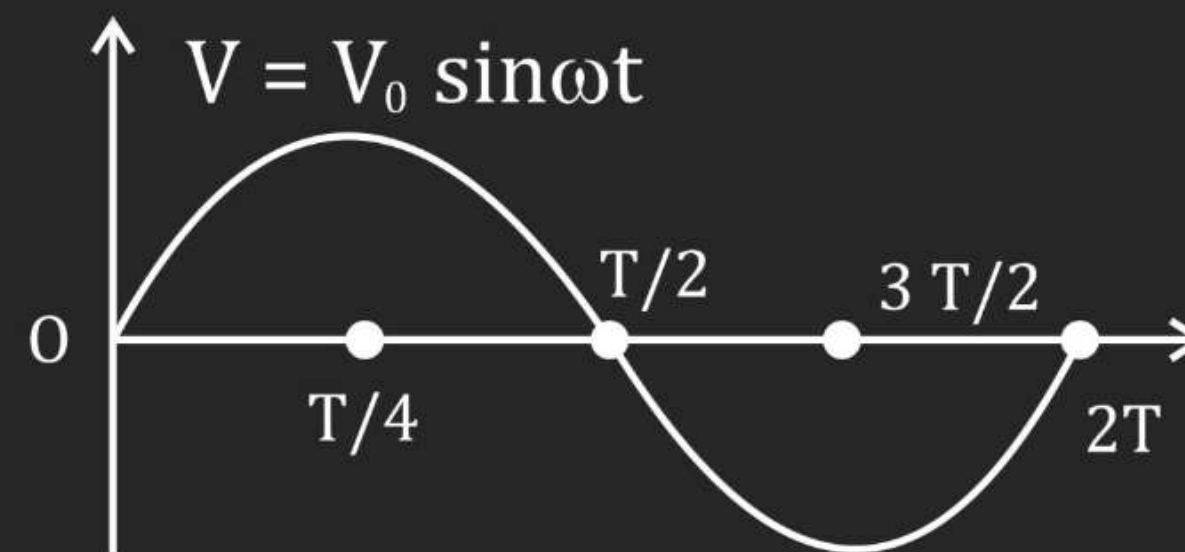- Q.4** In a series L – R circuit ( $L = 35\text{mH}$  and  $R = 11\Omega$ ), a variable emf source ( $V = V_0 \sin \omega t$ ) of  $V_{\text{rms}} = 220\text{ V}$  and frequency  $50\text{ Hz}$  is applied. Find the current amplitude in the circuit and phase of current with respect to voltage. Draw current-time graph on given graph ( $\pi = 22/7$ ). **(2004)**





**ALTERNATING CURRENT**

H.W.

**Q.5** The instantaneous voltages at three terminals marked X, Y and Z are given by

$$V_X = V_0 \sin \omega t,$$

$$V_Y = V_0 \sin \left( \omega t + \frac{2\pi}{3} \right) \text{ and } V_Z = V_0 \sin \left( \omega t + \frac{4\pi}{3} \right)$$

An ideal voltmeter is configured to read rms value of the potential difference between its terminals. It is connected between points X and Y and then between Y and Z. The reading(s) of the voltmeter will be

(A) independent of the choice of the two terminals

(B)  $V_{XY}^{\text{rms}} = V_0$


(C)  $V_{YZ}^{\text{rms}} = V_0 \sqrt{\frac{1}{2}}$

(D)  $V_{XY}^{\text{rms}} = V_0 \sqrt{\frac{3}{2}}$

**ALTERNATING CURRENT**

H.W.

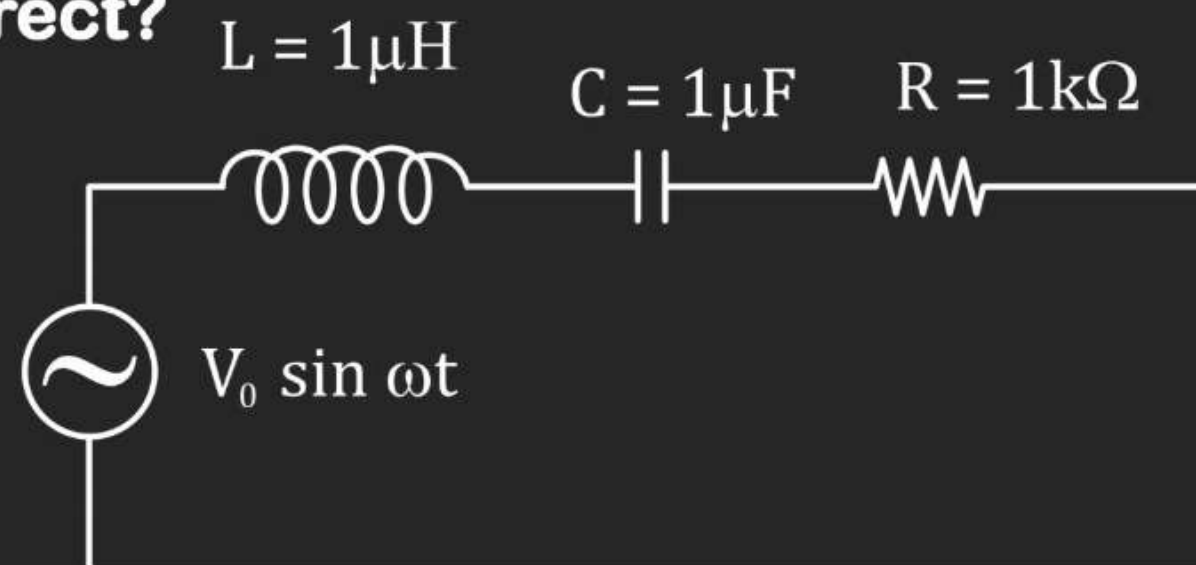**Q.6** In the circuit shown,  $L = 1\mu\text{H}$ ,  $C = 1\mu\text{F}$  and  $R = 1\text{k}\Omega$ . They are connected in series with an a.c. source  $V = V_0 \sin \omega t$  as shown. Which of the following options is/are correct? **(2017)**



- (A) At  $\omega \sim 0$  the current flowing through the circuit becomes nearly zero
- (B) The frequency at which the current will be in phase with the voltage is independent of  $R$
- (C) The current will be in phase with the voltage if  $\omega = 10^4 \text{rads}^{-1}$ .
- (D) At  $\omega \gg 10^6 \text{rads}^{-1}$ , the circuit behaves like a capacitor.



# ALTERNATING CURRENT

H-W

**Q.7** At time  $t = 0$ , terminal A in the circuit shown in the figure is connected to B by a key and an alternating current  $I(t) = I_0 \cos(\omega t)$ , with  $I_0 = 1 \text{ A}$  and  $\omega = 500 \text{ rad s}^{-1}$  starts flowing in it with the initial direction shown in the figure. At  $t = \frac{7\pi}{6\omega}$ , the key is switched from B to D. Now onwards only A and D are connected. A total charge  $Q$  flows from the battery to charge the capacitor fully. If  $C = 20 \mu\text{F}$ ,  $R = 10 \Omega$  and the battery is ideal with emf of  $50 \text{ V}$ , identify the correct statement(s). **(2014)**

**(A)** Magnitude of the maximum charge on the capacitor

before  $t = \frac{7\pi}{6\omega}$  is  $1 \times 10^{-3} \text{ C}$ .


**(B)** The current in the left part of the circuit

just before  $t = \frac{7\pi}{6\omega}$  is clockwise.

**(C)** Immediately after A is connected to D,

the current in  $R$  is  $10 \text{ A}$ .

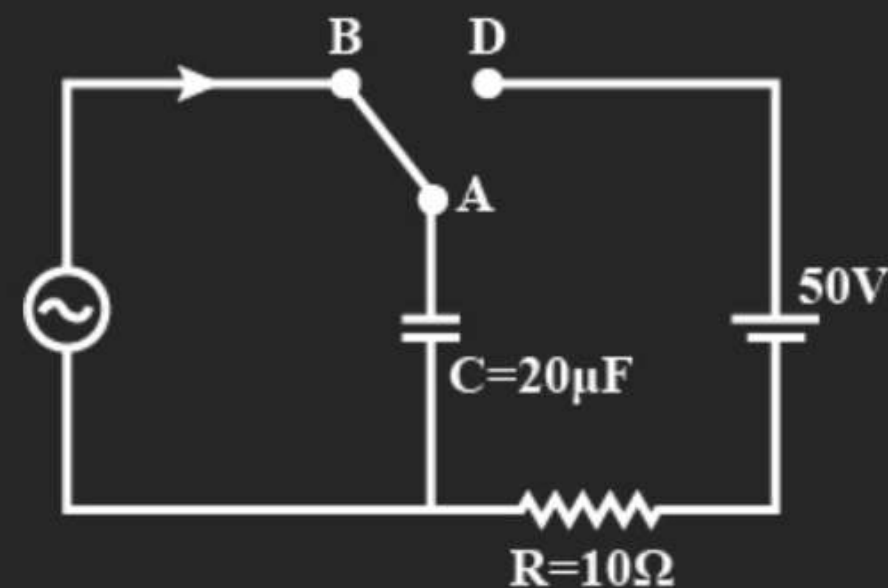**(D)**  $Q = 2 \times 10^{-3} \text{ C}$ .






# ALTERNATING CURRENT

HW

**Q.8** In the given circuit, the AC source has  $\omega = 100 \text{ rad/s}$ . Considering the inductor and capacitor to be ideal, the correct choice(s) is/are **(2012)**

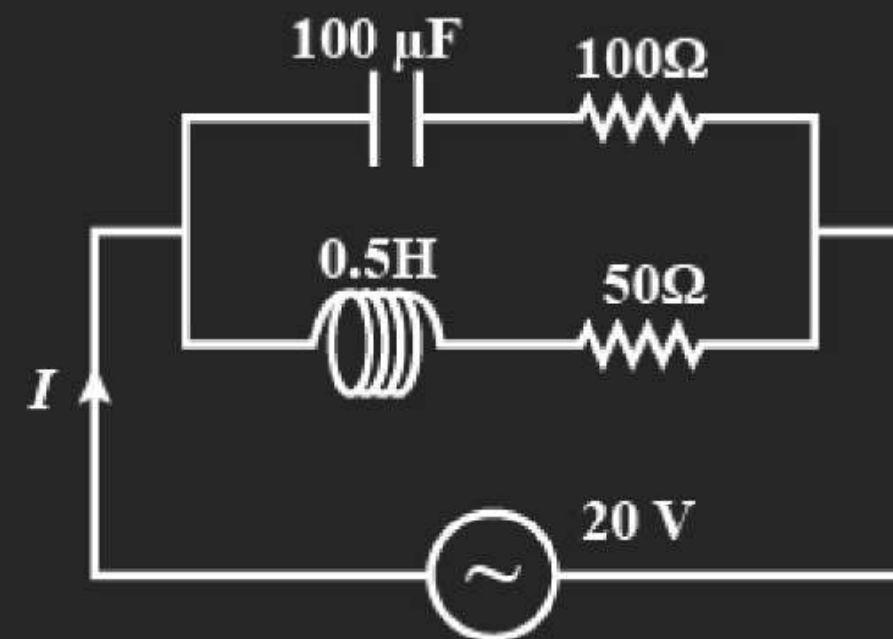- (A) the current through the circuit,  $I$  is  $0.3 \text{ A}$ .
- (B) the current through the circuit,  $I$  is  $0.3\sqrt{2} \text{ A}$ .
- (C) the voltage across  $100\Omega$  resistor =  $10\sqrt{2} \text{ V}$ .
- (D) the voltage across  $50\Omega$  resistor =  $10 \text{ V}$ .



# ALTERNATING CURRENT

H.W.

**Q.9** When an AC source of emf  $\varepsilon = E_0 \sin(100t)$  is connected across a circuit, the phase difference between the emf  $e$  and the current  $i$  in the circuit is observed to be  $\pi/4$ , as shown in the diagram. If the circuit consists possibly only of  $R - C$  or  $R - L$  or  $L - C$  in series, find the relationship between the two elements.

- (A)  $R = 1\text{k}\Omega, C = 10\mu\text{F}$
- (B)  $R = 1\text{k}\Omega, C = 1\mu\text{F}$
- (C)  $R = 1\text{k}\Omega, L = 10\text{H}$
- (D)  $R = 1\text{k}\Omega, L = 1\text{H}.$

