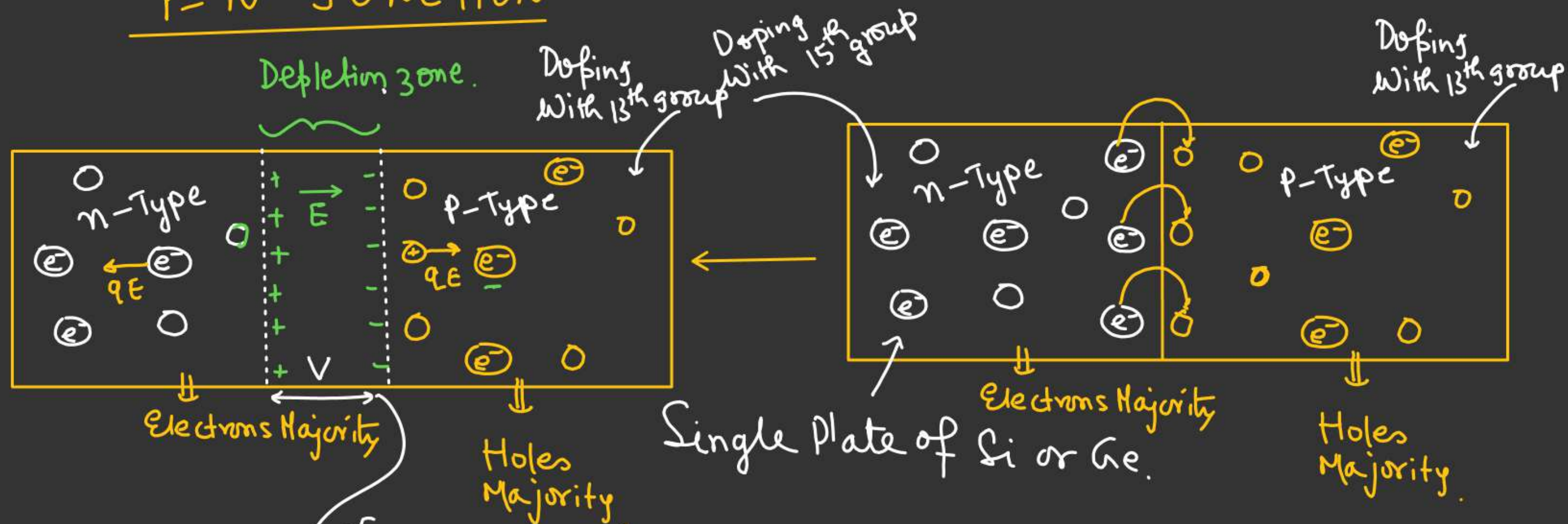



P-N JUNCTION



Due to barrier potential further diffusion process will suppress.



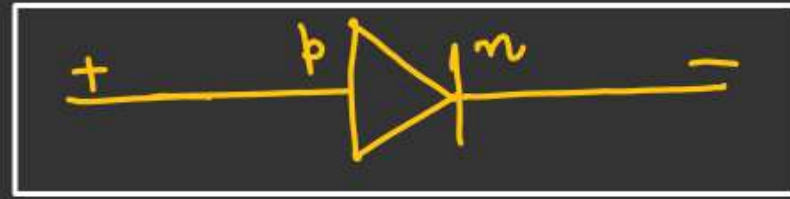
Diode \rightarrow p-n junction as a diode.



(Direction of Current)

Biasing of P-N junction

Forward biasing

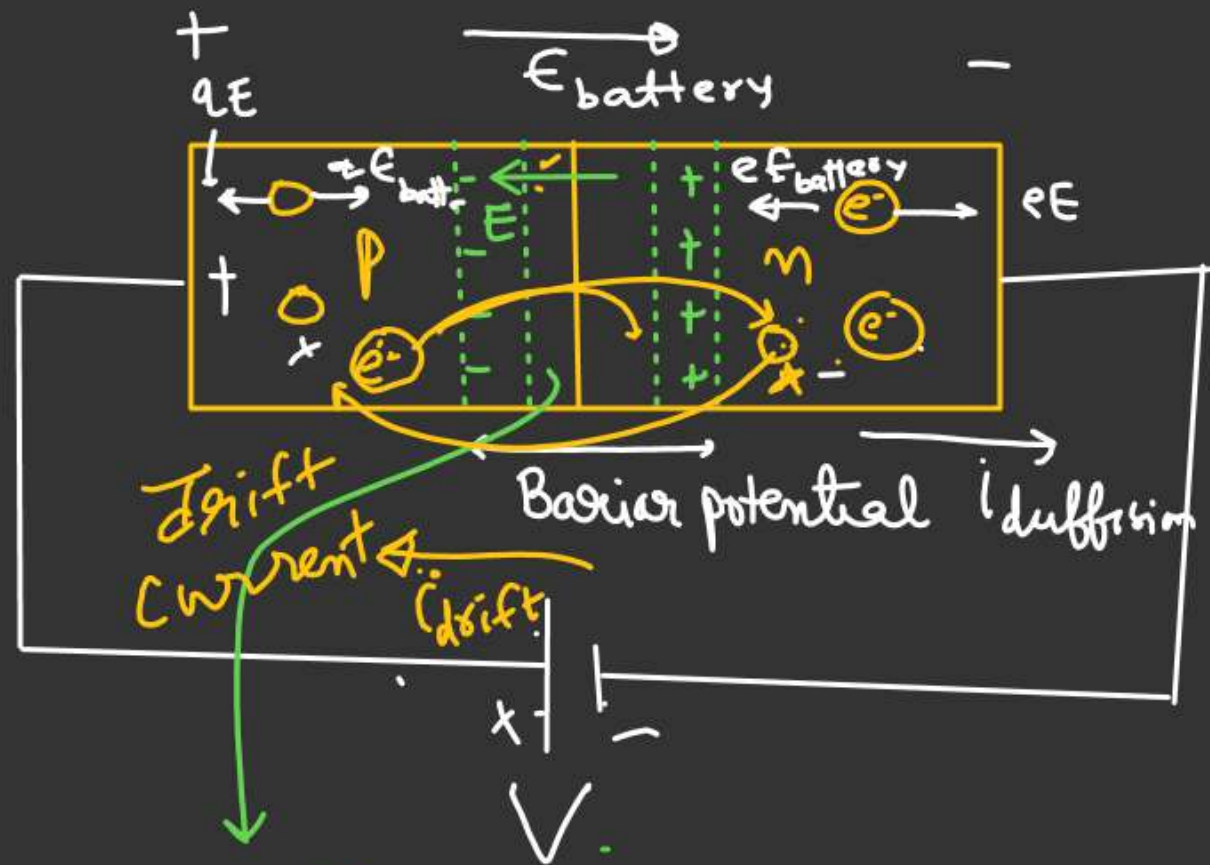


→ Diffusion Current :-


→ Drift Current :-

↳ Due to Minority Charge Carriers. which are drifted by barrier potential Electric field.


- ① Barrier potential decreases.
↳ Diffusion start
- ② Offer very low resistance.

Reverse biasing

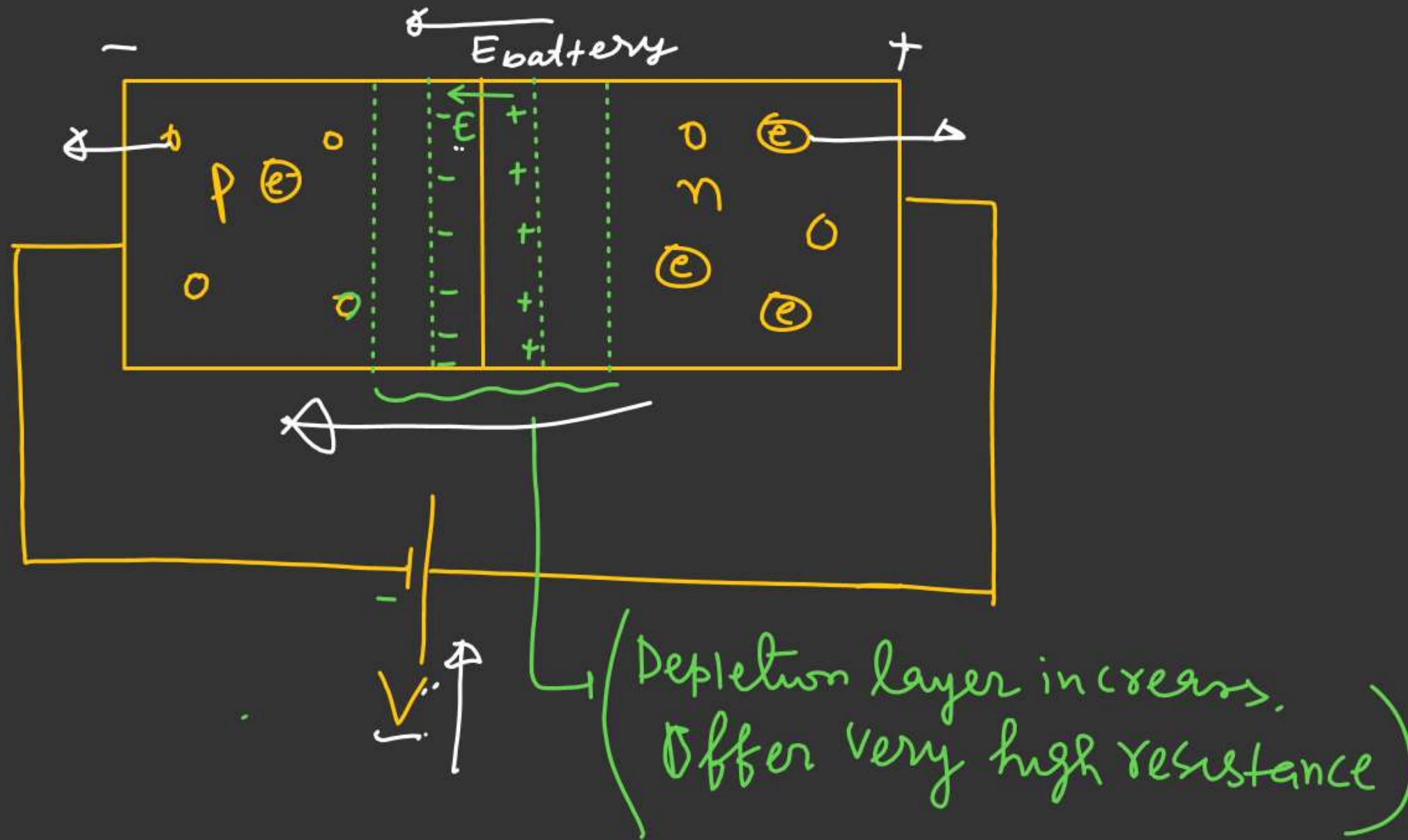

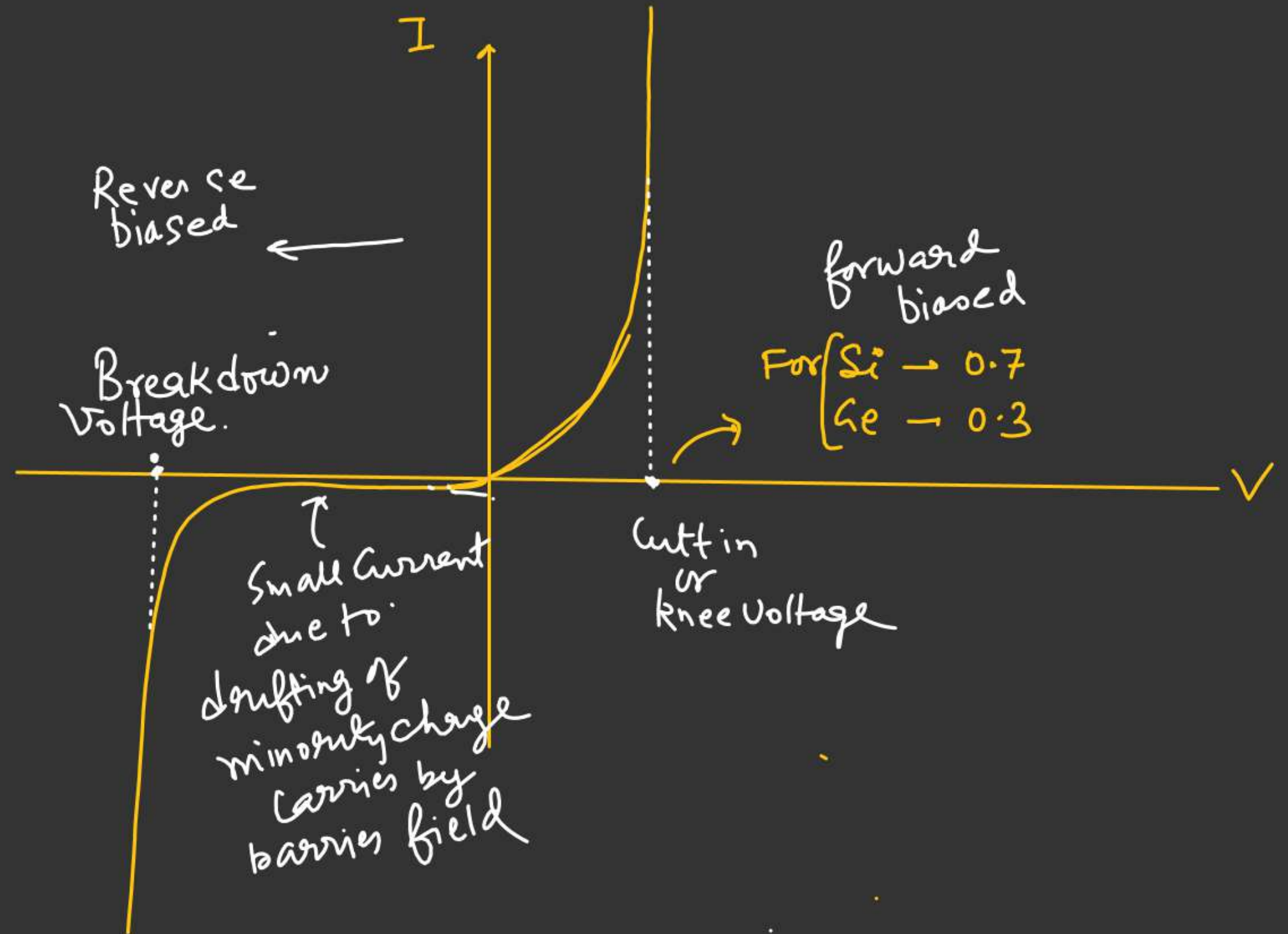


Diode → p-n junction as a diode.

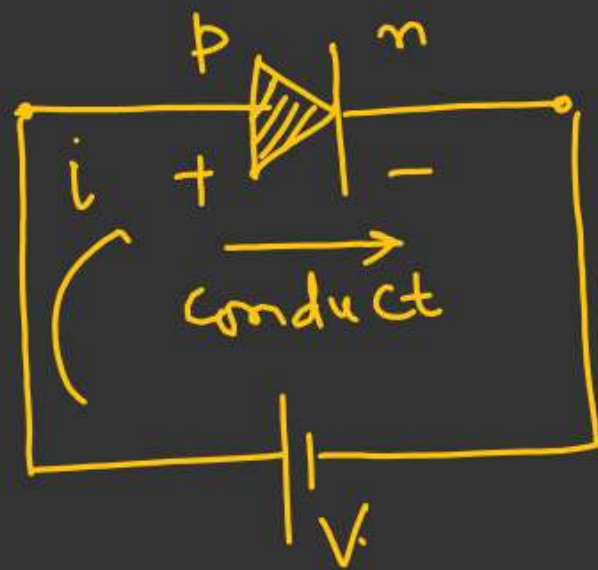


↳ Diode will Conduct in forward biasing.

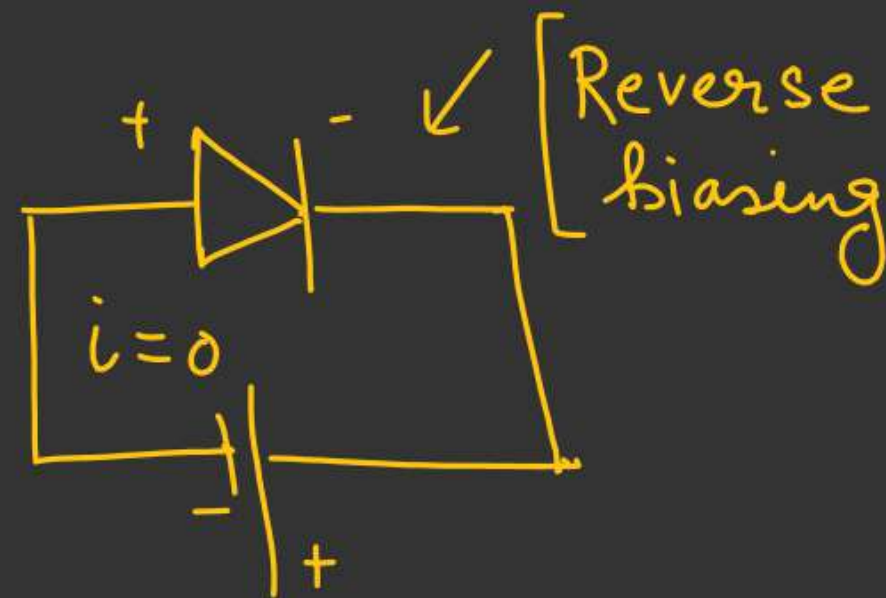↳ Not Conduct i.e open ckt in reverse biasing.



Diode as a half wave rectifier

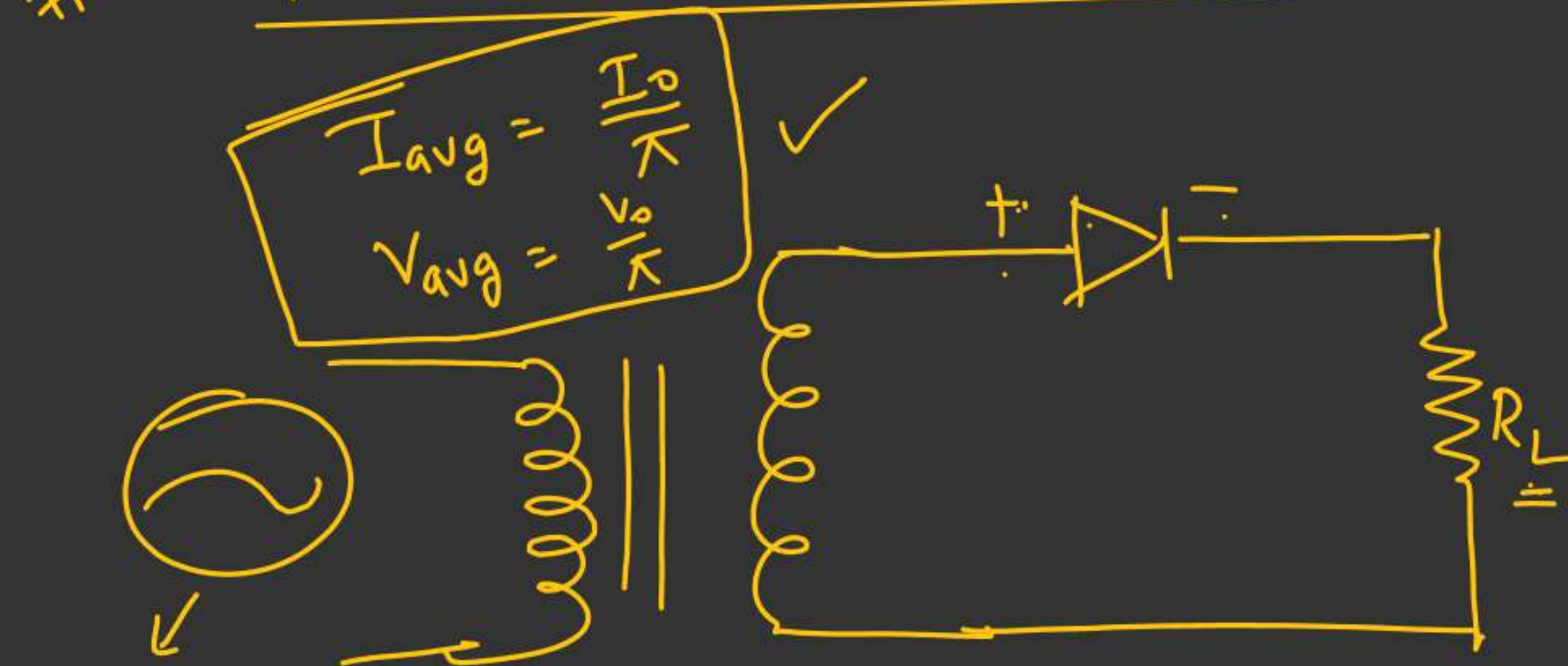

Input Signal

Input Signal

AC \rightarrow Flu

$$I = I_o \sin \omega t$$

$$I_{avg} = \frac{\int_0^{\pi} I_o \sin \omega t dt}{\int_0^{\pi} dt} = \left(\frac{I_o}{K} \right)$$


For +ve half signal

\hookrightarrow Diode in forward biasing Mode \rightarrow Conduct

For -ve half signal


\hookrightarrow Diode in reverse biasing Mode \rightarrow Not Conduct

Output Signal \rightarrow

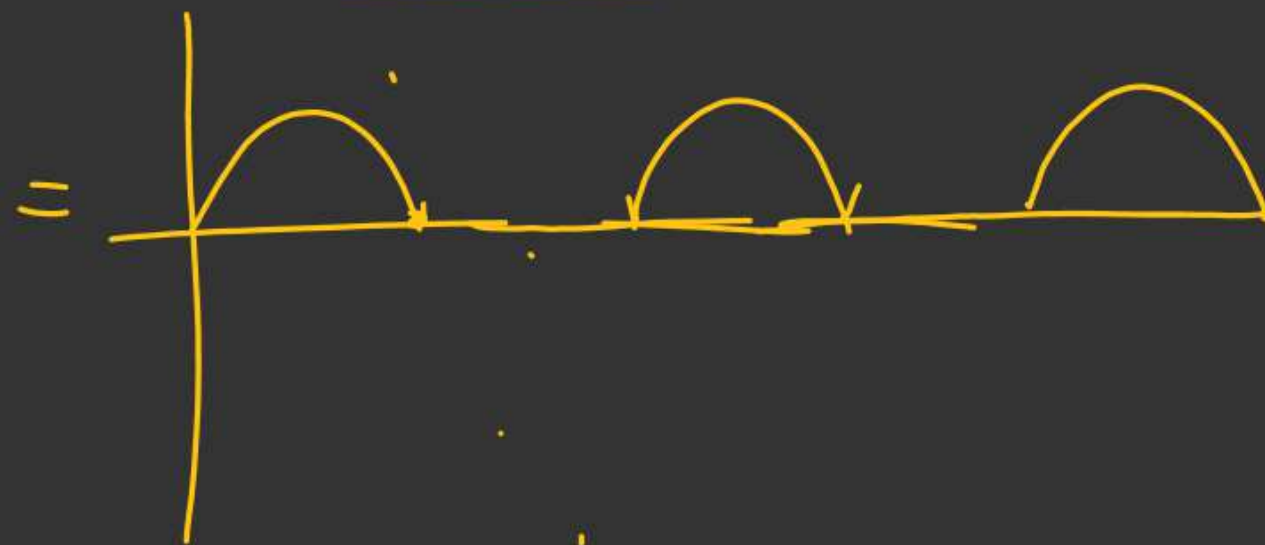


Full Wave Rectifier

Center tap transformer.

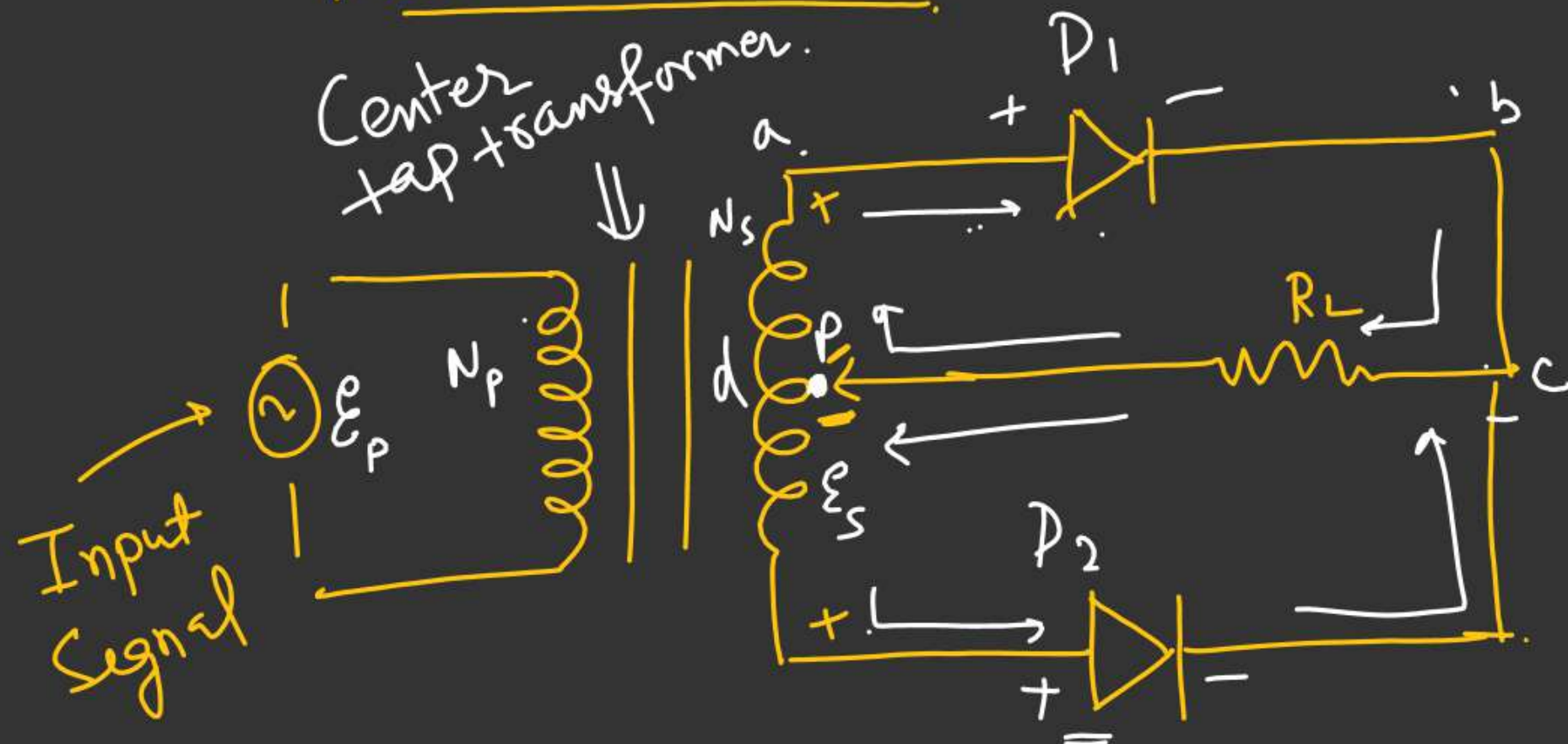


$$\frac{E_p}{E_s} = \frac{N_p}{N_s} \quad \checkmark$$

$$E_s = \frac{N_s}{N_p} \times E_p$$

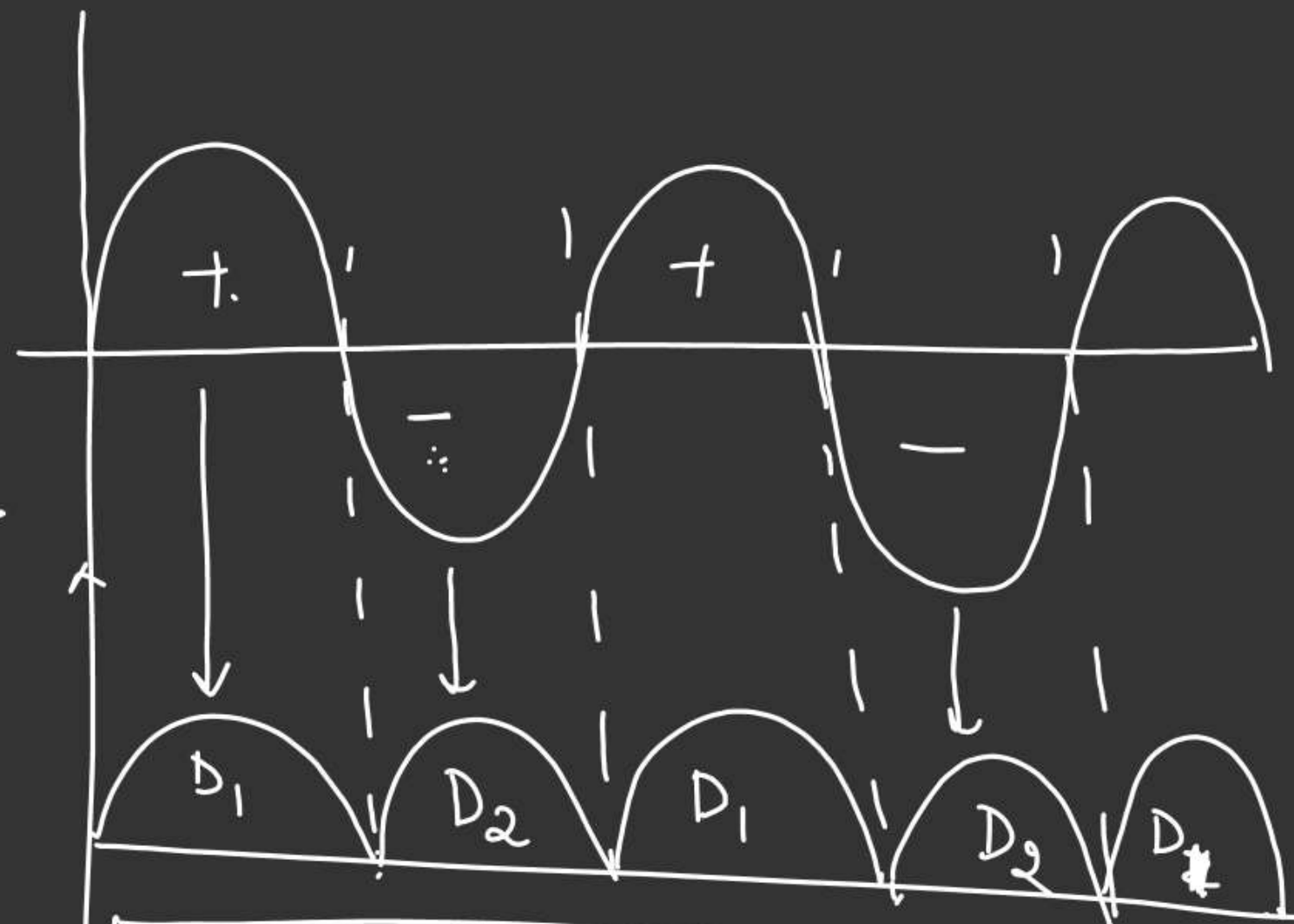



$$V_{avg} = \frac{2V_o}{\pi}, \quad I_{avg} = \frac{2I_o}{\pi}$$

Zener Diode

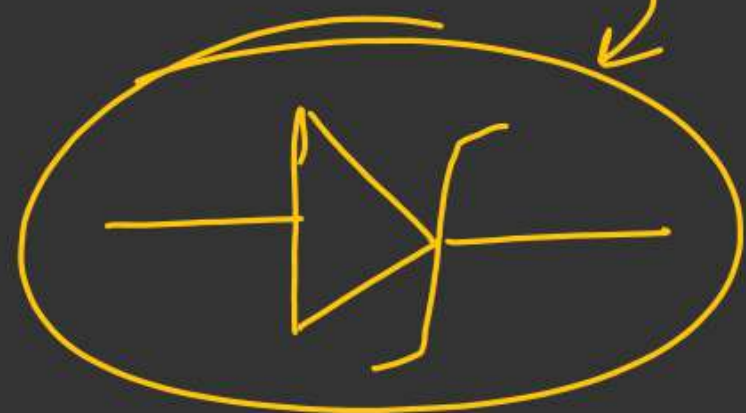

① Zener diode work in reverse biasing mode.

In reverse biasing mode.

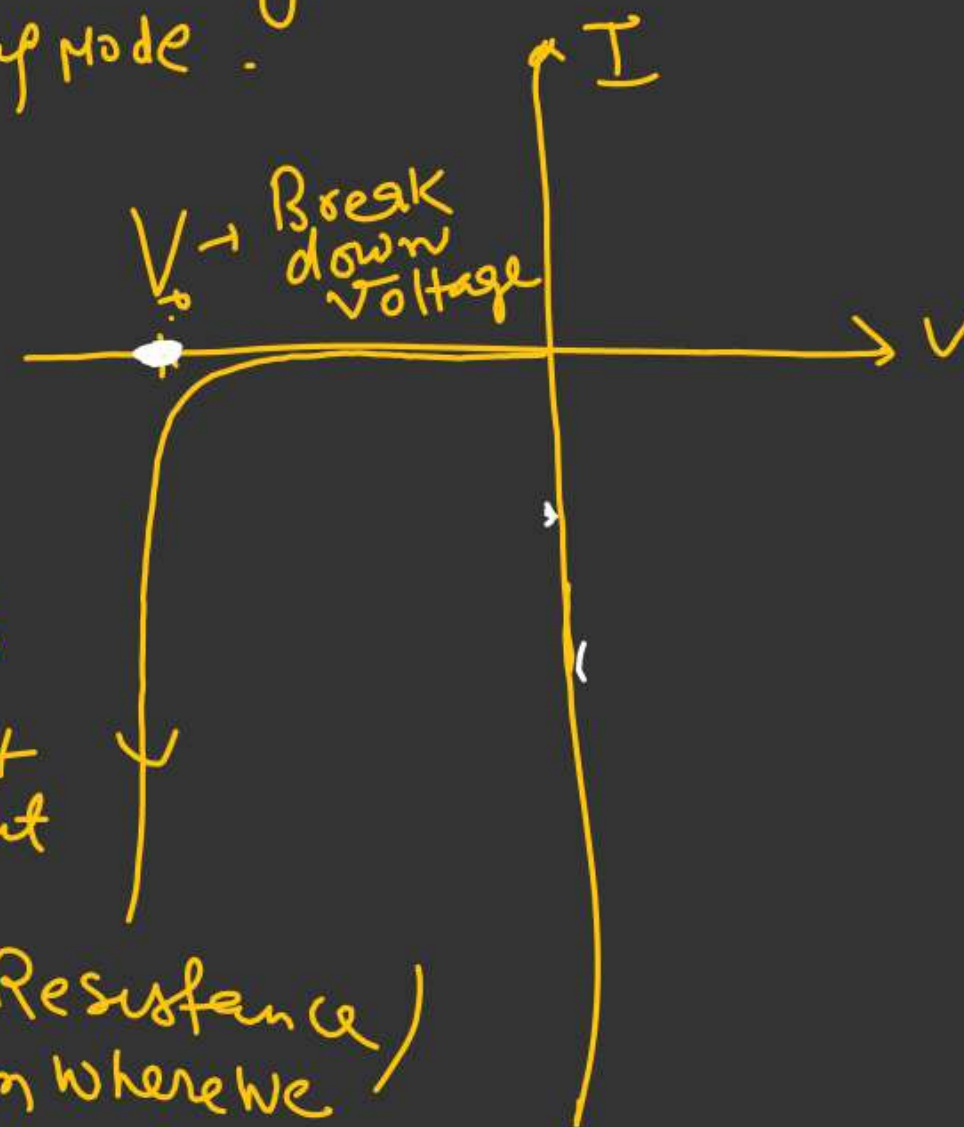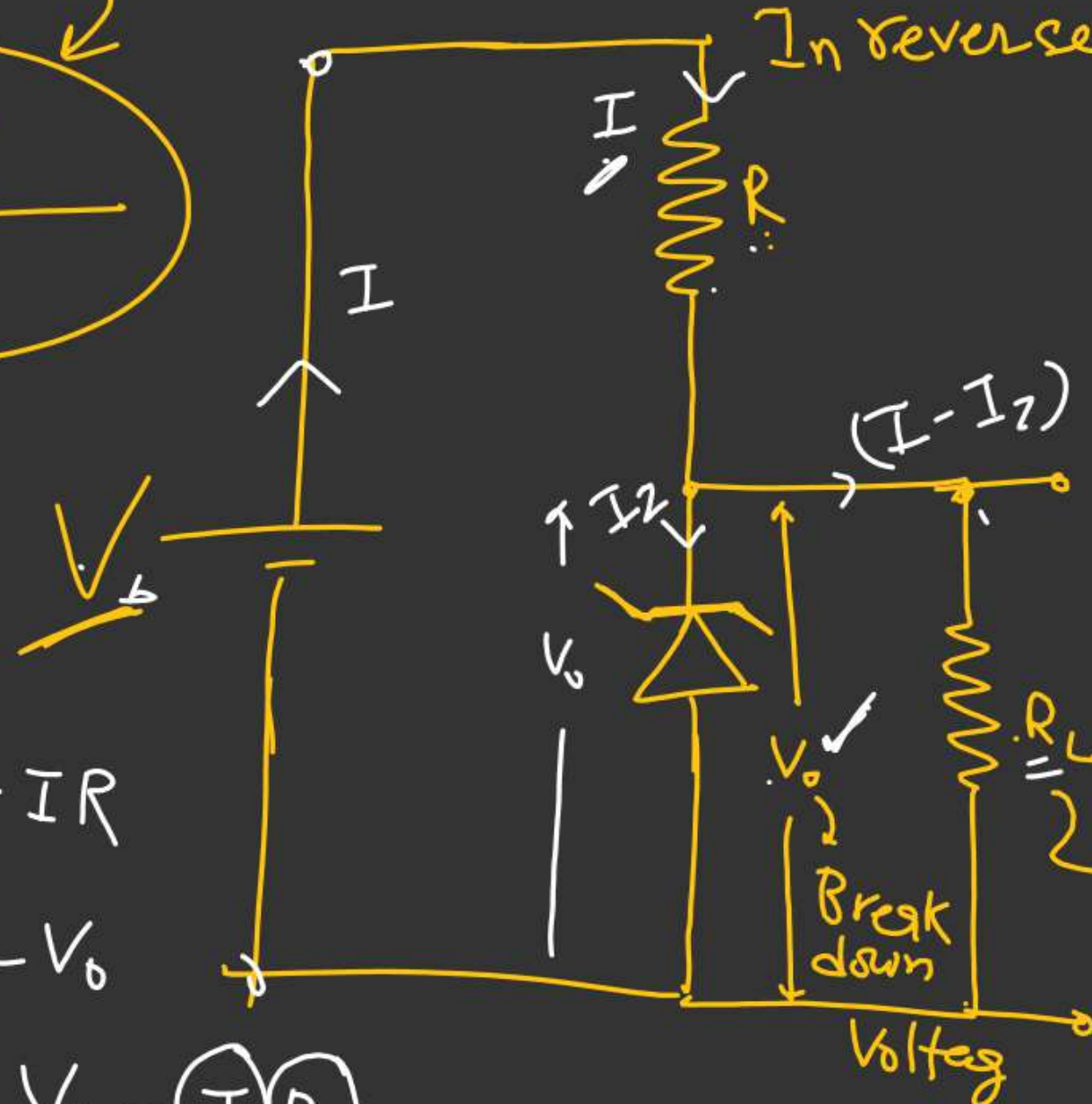

$$V_b = V_o + IR$$

$$IR = V_b - V_o$$

$$\underline{V_o} = \underline{V_b} - \underline{I} \underline{R}$$

Constant

Changy. Changy.

$V_{R_L} = V_o$
Constant output

(Load Resistance) from where we get output

SEMICONDUCTORS

ELECTRICAL CONDUCTIVITY OF A SEMICONDUCTOR

Consider a block of semiconductor of length l , area of cross-section A , and having free electron density n_e and hole density n_h .

suppose a potential difference V is applied across its ends. The electric field setup inside it will be $\left[E = \frac{V}{l}\right]$

Mobility $\rightarrow \mu = \frac{E}{v_d}$

Electrons begin to drift with velocity v_e in the opposite direction of E while holes drift in the direction of E with velocity v_h .

Total current = Electron current + Hole current

$$I = I_e + I_h \rightarrow \text{hole current}$$


$$[\mu_e = \text{Electron mobility}]$$

$$I_e = n_e e A v_e, I_h = n_h e A v_h$$

$$[\mu_h = \text{Hole Mobility}]$$

$$I = eA(n_e v_e + n_h v_h) \checkmark$$

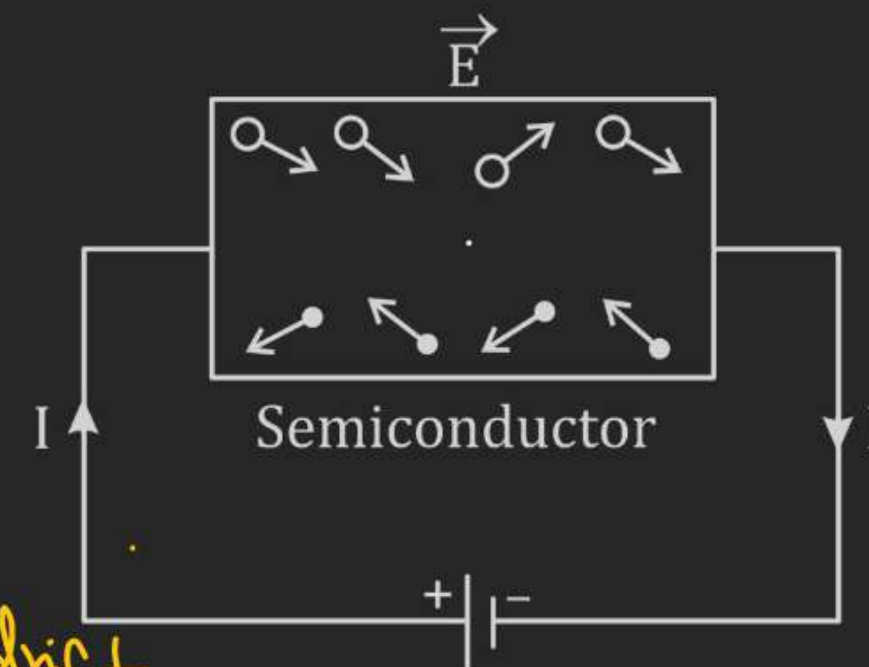$v_e = \text{drift velocity of } e^-$ $I = n_e A v_d$ $v_h = \text{drift velocity of hole}$



SEMICONDUCTORS

↘ If R is the resistance of the semiconductor block and ρ its resistivity $R = \rho \frac{l}{A}$.

If the applied field E is low the Semiconductor obey ohm's law.

$$I = \frac{V}{R} = \frac{El}{\rho l/A} = \frac{EA}{\rho} \Rightarrow I = \frac{EA}{\rho} = eA(n_e v_e + n_h v_h)$$

$$\frac{E}{\rho} = e(n_e v_e + n_h v_h) \left(\mu_e = \frac{v_e}{E}, \mu_h = \frac{v_h}{E} \right)$$

$$\frac{E}{\rho} = e(n_e \mu_e E + n_h \mu_h E) \Rightarrow \frac{1}{\rho} = e(n_e \mu_e + n_h \mu_h) \quad \text{Eq. 9mP.}$$

$$\sigma = \frac{1}{\rho} \Rightarrow \sigma = e(n_e \mu_e + n_h \mu_h) \quad \text{Eq. 9mP.}$$

SEMICONDUCTOR & DIODE


Q.1 Mobilities of electrons and holes for an intrinsic silicon is $0.64 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $0.36 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$ respectively. If the electron and hole densities are equal to $1.6 \times 10^{19} \text{ m}^{-3}$. What is the conductivity of silicon?

SEMICONDUCTOR & DIODE

Q.2 When the voltage drop across a p-n junction is increased from 0.80 V to 0.82 V, the change in the diode current is 20 m A. What is the dynamic resistance of the diode?


SEMICONDUCTOR & DIODE

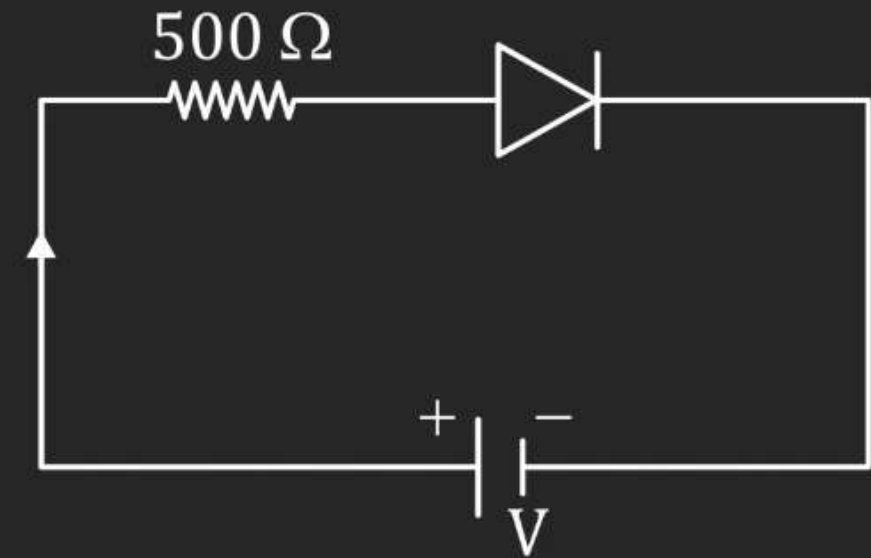Q.3 In the given circuit the voltage drop across the diode is 0.8 V , if the diode can withstand current upto maximum of 30 mA , then find the maximum voltage of the battery




SEMICONDUCTOR & DIODE

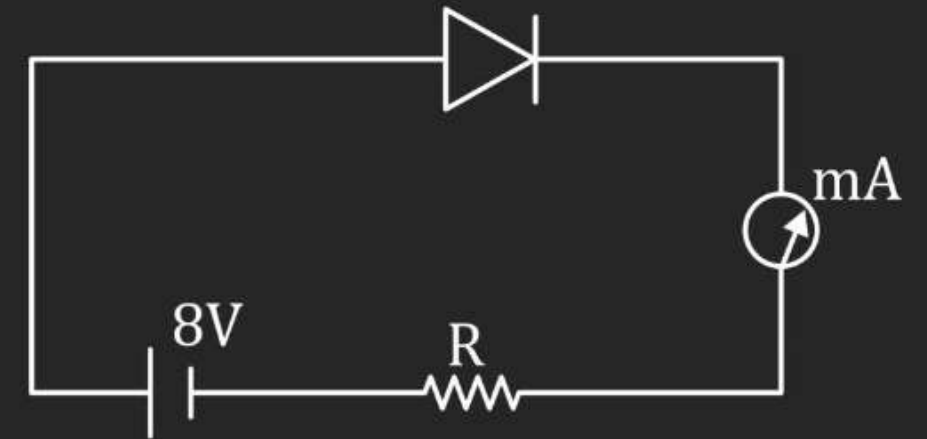Q.4 In the given circuit a silicon diode with knee voltage 0.7V is forward biased with a battery of e.m.f 8V . The current in the circuit is 40mA . Find the power drop at resistor R and diode.



SEMICONDUCTOR & DIODE

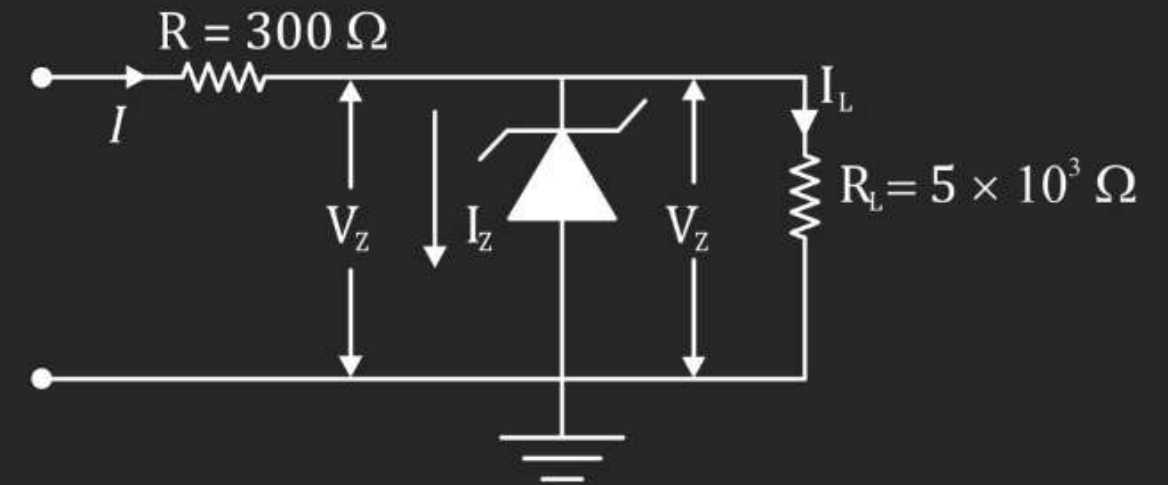
Q.5 In the given figure, what is the voltage needed to maintain 25 V across the load resistance R_L , if Zener diode required a minimum current of 20 mA to work satisfactorily?



SEMICONDUCTOR & DIODE

Q.6 Four equal resistors, each of resistance 10Ω , are connected as shown in the circuit diagram. The equivalent resistance between A and B is


- (A) 5Ω
- (B) 10Ω
- (C) 20Ω
- (D) 40Ω

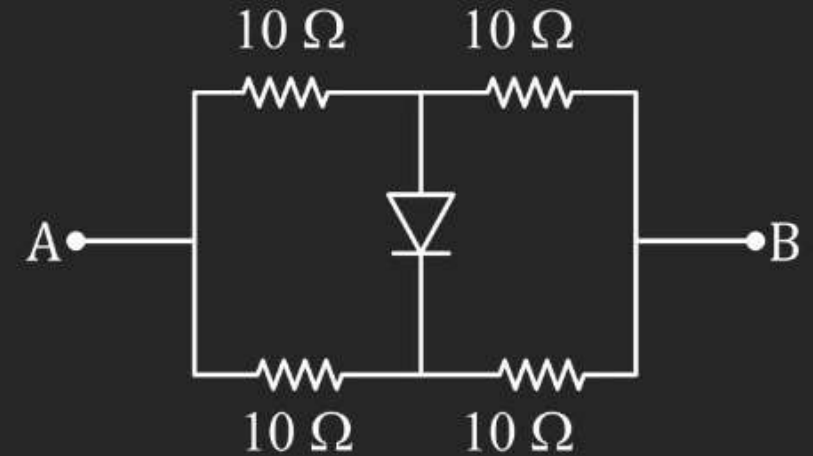

SEMICONDUCTOR & DIODE

Q.7 A full wave rectifier circuit along with the input and output are shown in the figure. The contribution from the diode D_2 is (are)

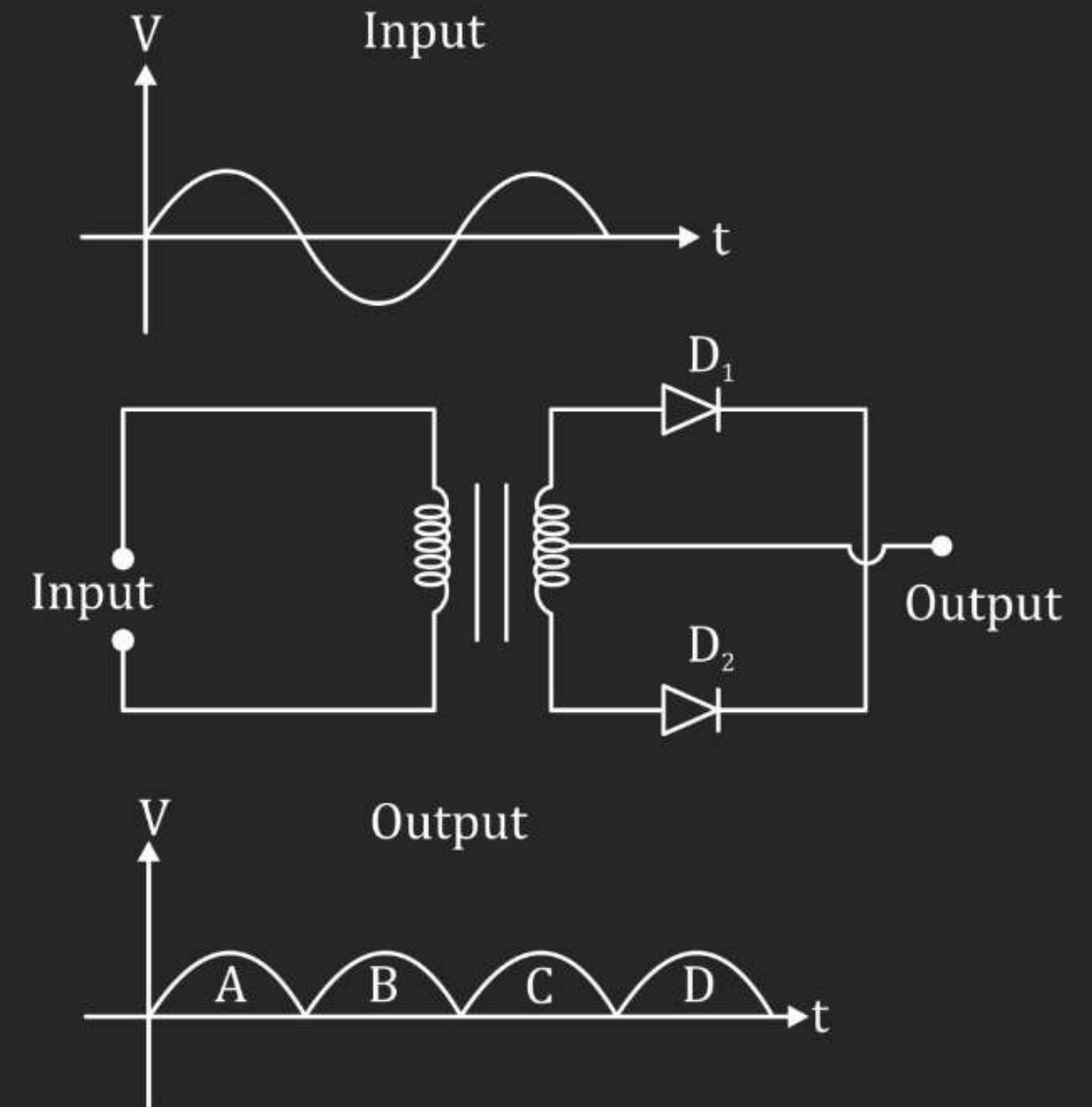- (A) C
- (B) A, C
- (C) B, D
- (D) A, B, C, D




Q.8 In a full wave rectifier circuit operating from 50 Hz mains frequency, the fundamental frequency in the ripple would be

- (A)** 50 Hz
- (B)** 100 Hz
- (C)** 25 Hz
- (D)** 70 Hz


SEMICONDUCTOR & DIODE

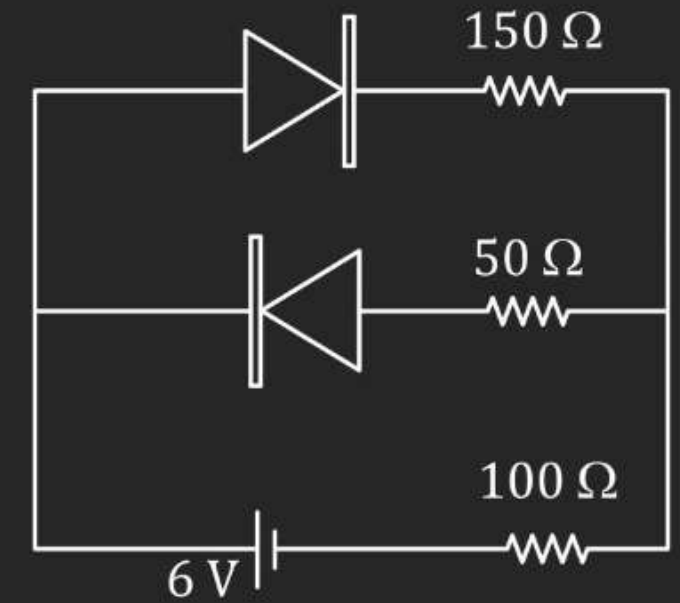Q.9 The circuit contains two diodes each with a forward resistance of 50Ω and with infinite reverse resistance. The current (in A) through 100Ω resistor is




SEMICONDUCTOR & DIODE

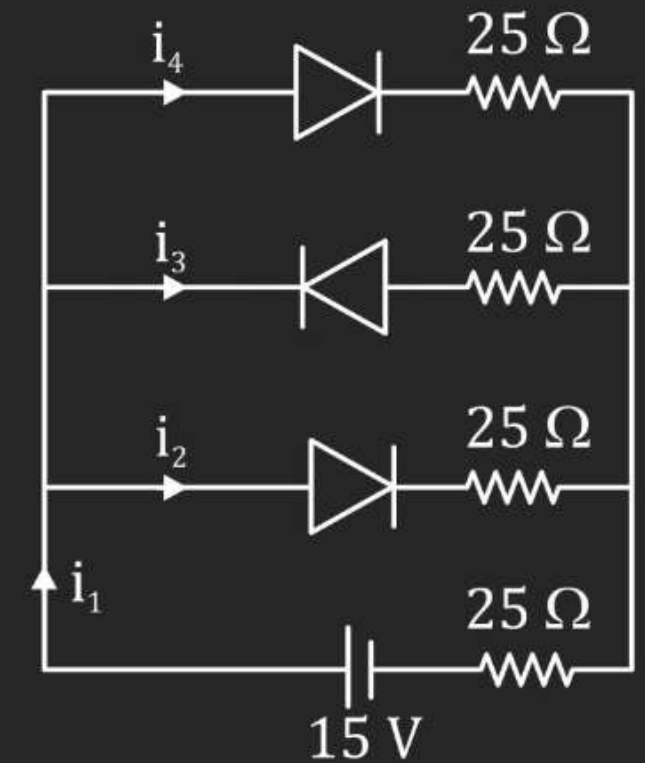Q.10 In the circuit shown, if each diode has a forward biased resistance of 75Ω and infinite resistance in reverse bias, what will be the value of current i_1 (in A)?




SEMICONDUCTOR & DIODE

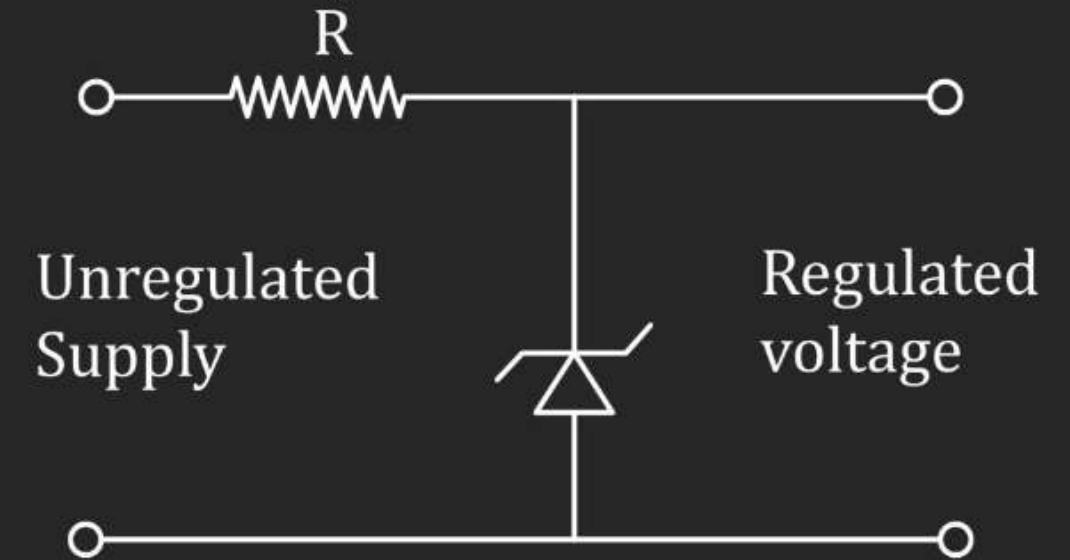Q.11 A Zener diode of power rating 2 W is to be used as a voltage regulator. If Zener has a breakdown of 5 V and it is being fed with voltage fluctuating between 3 V and 7 V, what should be value of R for self operation?



SEMICONDUCTOR & DIODE

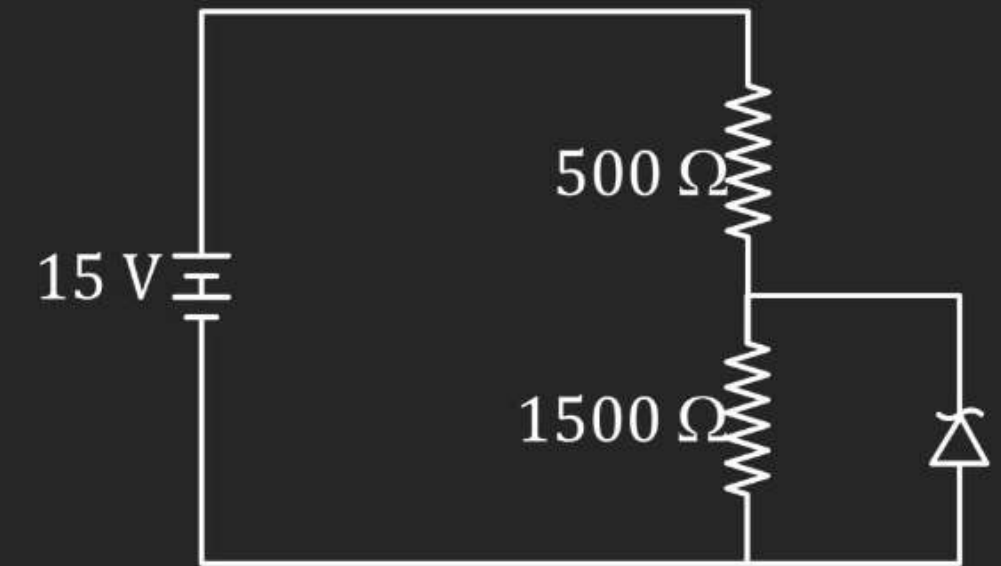Q.12 In the circuit, the current through Zener diode is n mA. Value of n , is (the breakdown voltage is 10 V)



SEMICONDUCTOR & DIODE

- Q.13** Mobility of electrons in a semiconductor is defined as the ratio of their drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is 10^{19} m^{-3} and their mobility is $1.6 \text{ m}^2/(\text{V}\cdot\text{s})$ then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close

[JEE (Main)-2019]

(A) $2\Omega\text{m}$

(B) $0.2\Omega\text{m}$

(C) $0.4\Omega\text{m}$

(D) $4\Omega\text{m}$

$$\frac{1}{\rho} = e(\mu_e n_e + \mu_h n_h)$$

$$\frac{1}{\rho} = e(\mu_e n_e)$$

$n = \text{No of electrons per unit volume}$

✓ check

Q.14 Drift speed of electrons, when 1.5 A of current flows in a copper wire of cross section 5 mm^2 , is v . If the electron density in copper is $9 \times 10^{28} / \text{m}^3$ the value of v in mm/s is close to (Take charge of electron to be $= 1.6 \times 10^{-19} \text{ C}$)

[JEE (Main)-2019]

(A) 0.02

(B) 0.2

(C) 3

(D) 2

SEMICONDUCTOR & DIODE


Q.15 Ge and Si diodes start conducting at 0.3 V and 0.7 V respectively. In the following figure if Ge diode connection are reversed, the value of V_0 changes by (assume that the Ge diode has large breakdown voltage)

(A) 0.2 V

☒ (B) 0.4 V

(C) 0.6 V

(D) 0.8 V

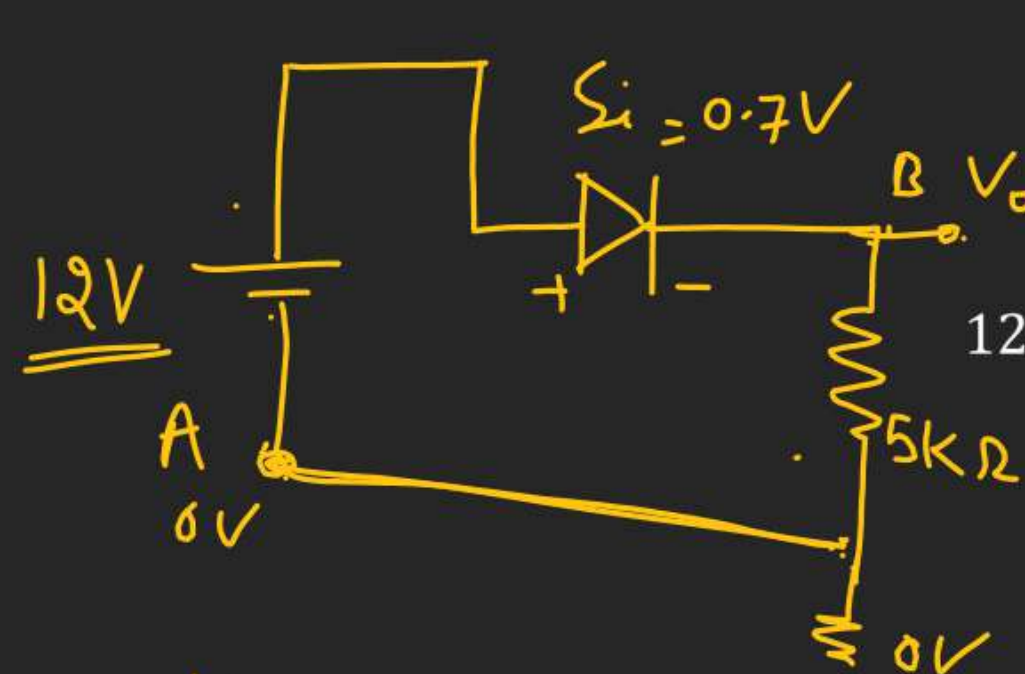

$$12 - 0.3 = (V_0)_i$$

$$11.7 = (V_0)_i$$


$$V_A + 12 - 0.7 = (V_0)_f$$

$$0 + 12 - 0.7 = (V_0)_f$$

$$11.3 = (V_0)_f$$

$$\Delta V = (V_0)_i - (V_0)_f$$

[JEE (Main)-2019]

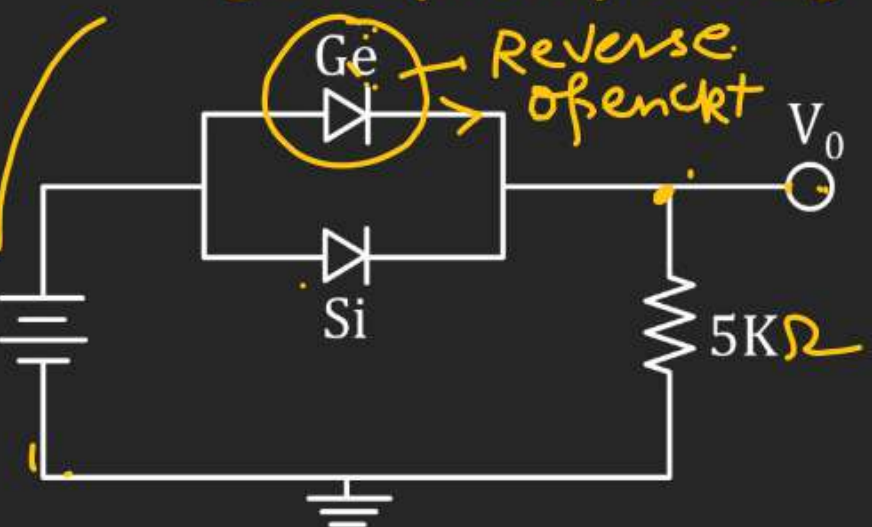

Q.16 To get output ' 1 ' at R, for the given logic gate circuit the input values must be


(A) $X = 1, Y = 1$

(B) $X = 0, Y = 0$

(C) $X = 1, Y = 0$

(D) $X = 0, Y = 1$

[JEE (Main)-2019]

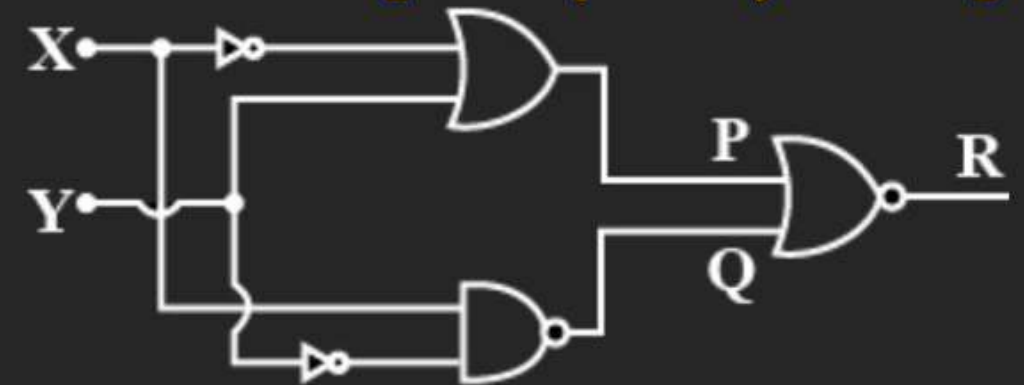

SEMICONDUCTOR & DIODE

Q.17 For the circuit shown below, the current through the Zener diode is

[JEE (Main)-2019]

(A) Zero

(B) 9 mA

(C) 14 mA

(D) 5 mA

$$i = \frac{120 - 50}{5 \times 10^3}$$


$$i = \left(\frac{70}{5 \times 10^3} \right)$$

$$i = 14 \text{ mA}$$

$$i_1 = \frac{50}{10 \times 10^{-3}}$$

$$= 5 \text{ mA}$$
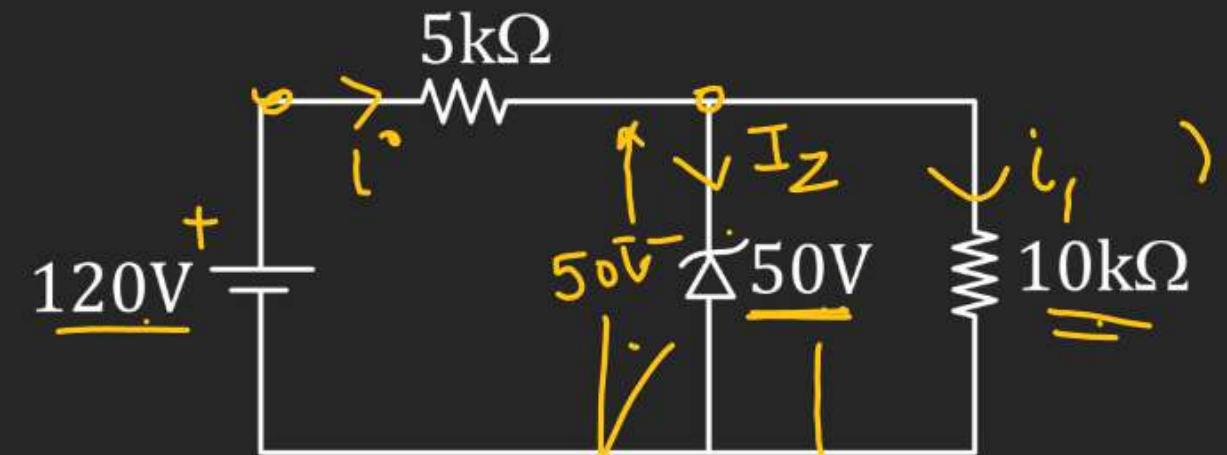
$$\begin{aligned} I_Z &= i - i_1 \\ &= (14 - 5) \text{ mA} \\ &= 9 \text{ mA} \end{aligned}$$



Reverse Biase.
Breakdown voltage



Q.18 In the given circuit the current through Zener Diode is close to


[JEE (Main)-2019]

(A) 6.7 mA

(B) 0.0 mA


(C) 4.0 mA

(D) 6.0 mA

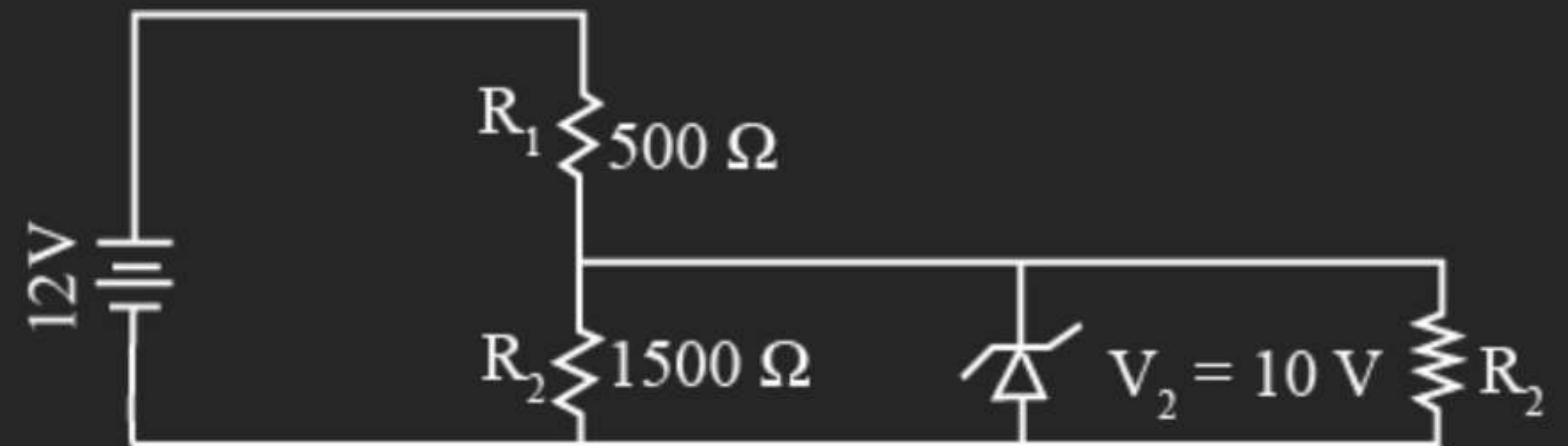

Q.19 The circuit shown below contains two ideal diodes, each with a forward resistance of 50Ω . If the battery voltage is 6 V , the current through the 100Ω resistance (in amperes) is

[JEE (Main)-2019]

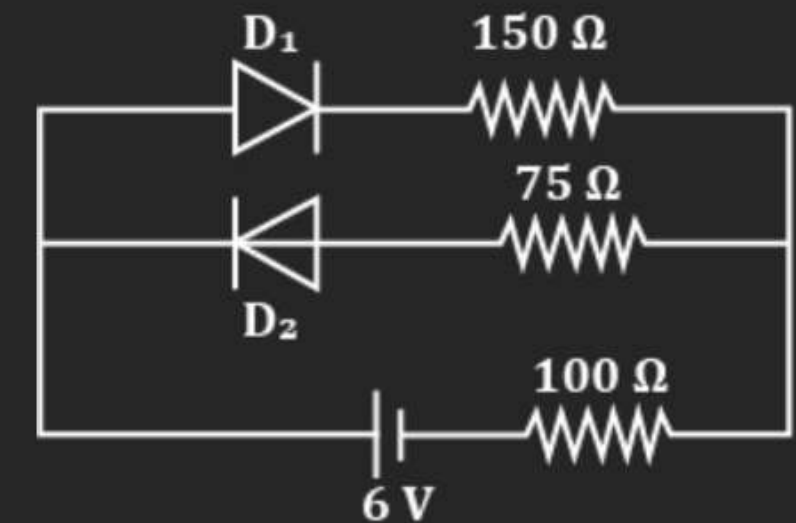

(A) 0.036

(B) 0.020

(C) 0.030

(D) 0.027

Q.20 The output of the given logic circuit is:


(A) $A\bar{B} + \bar{A}B$

(B) $A\bar{B}$

(C) $AB + \overline{AB}$

(D) $\bar{A}B$

[JEE (Main)-2019]

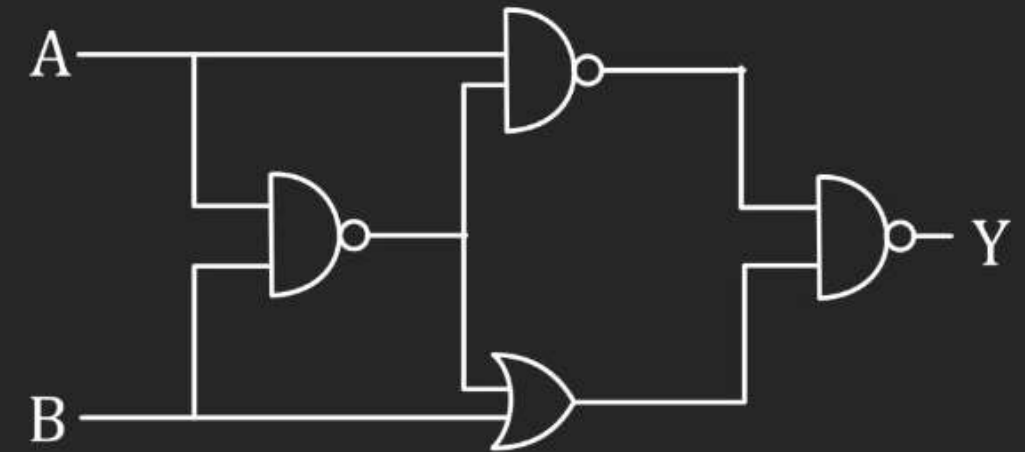

Q.21 The reverse breakdown voltage of a Zener diode is 5.6 V in the given circuit.

The current I_Z through the Zener is


[JEE (Main)-2019]

(A) 15 mA

(B) 7 mA

(C) 10 mA


(D) 17 mA

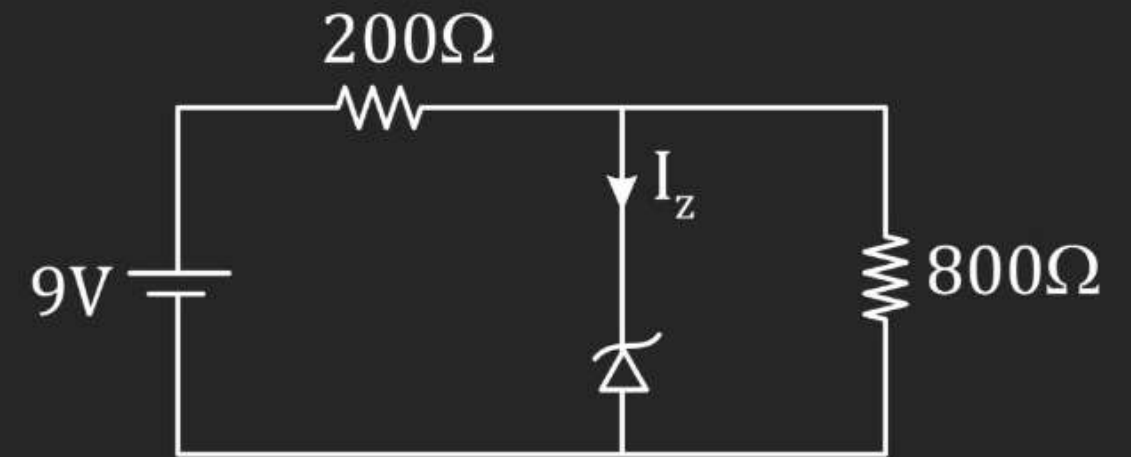

Q.22 The figure represents a voltage regulator circuit using a Zener diode. The breakdown voltage of the Zener diode is 6 V and the load resistance is, $R_L = 4\text{k}\Omega$. The series resistance of the circuit is $R_i = 1\text{k}\Omega$. If the battery voltage V_B varies from 8 V to 16 V, what are the minimum and maximum values of the current through Zener diode?


[JEE (Main)-2019]

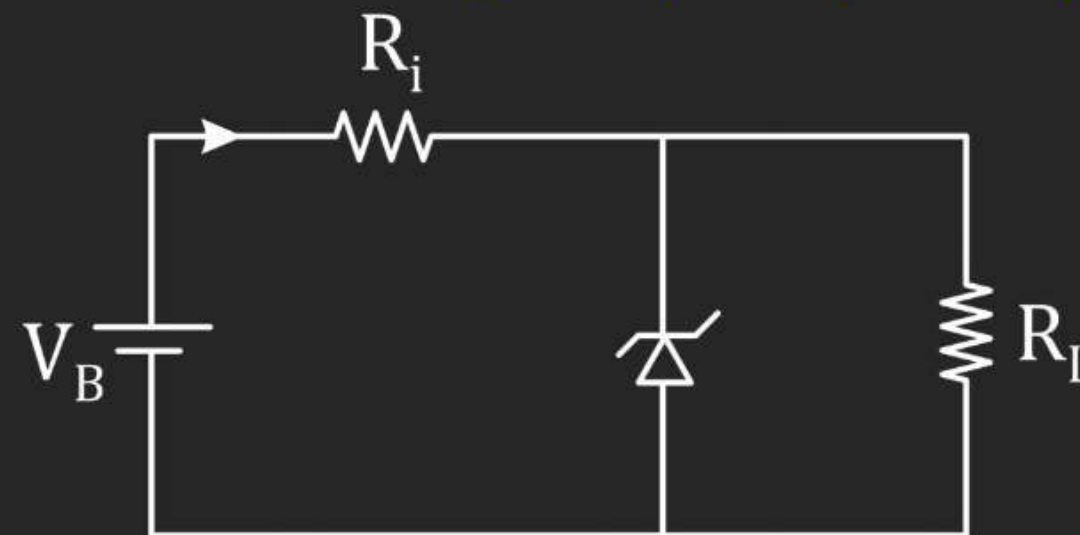- (A) 0.5 mA; 6 mA
- (B) 0.5 mA; 8.5 mA
- (C) 1.5 mA; 8.5 mA
- (D) 1 mA; 8.5 mA



Q.23 Two identical capacitors A and B, charged to the same potential 5 V are connected in two different circuits as shown below at time $t = 0$. If the charge on capacitors A and B at time $t = CR$ is Q_A and Q_B respectively, then (Here e is the base of natural logarithm) **[JEE (Main)-2020]**

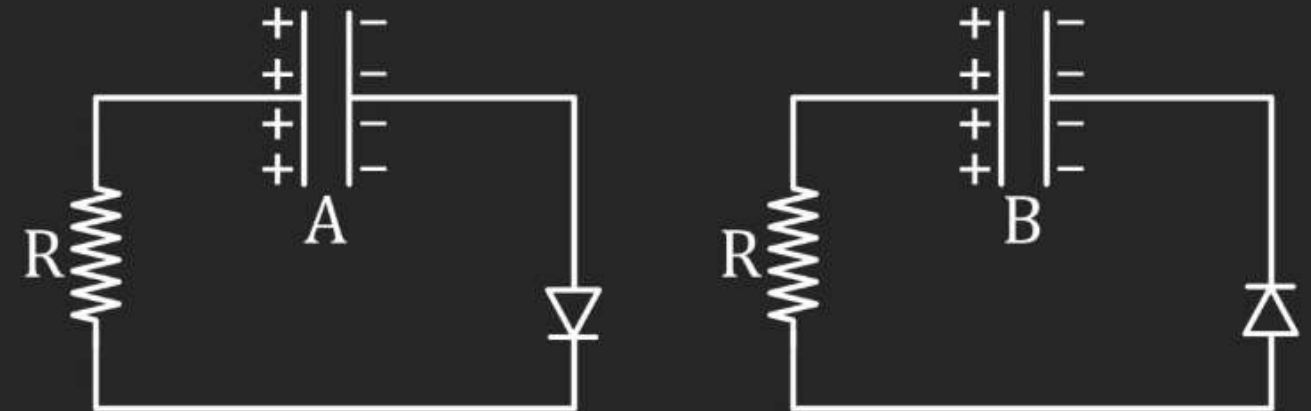
- (A) $Q_A = \frac{CV}{2}, Q_B = \frac{VC}{e}$
(B) $Q_A = VC, Q_B = CV$
(C) $Q_A = \frac{CV}{e}, Q_B = \frac{VC}{2}$
(D) $Q_A = VC, Q_B = \frac{VC}{e}$



Q.24 The current i in the network is

- (A) 0.3 A
- (B) 0.6 A
- (C) 0 A
- (D) 0.2 A

[JEE (Main)-2020]

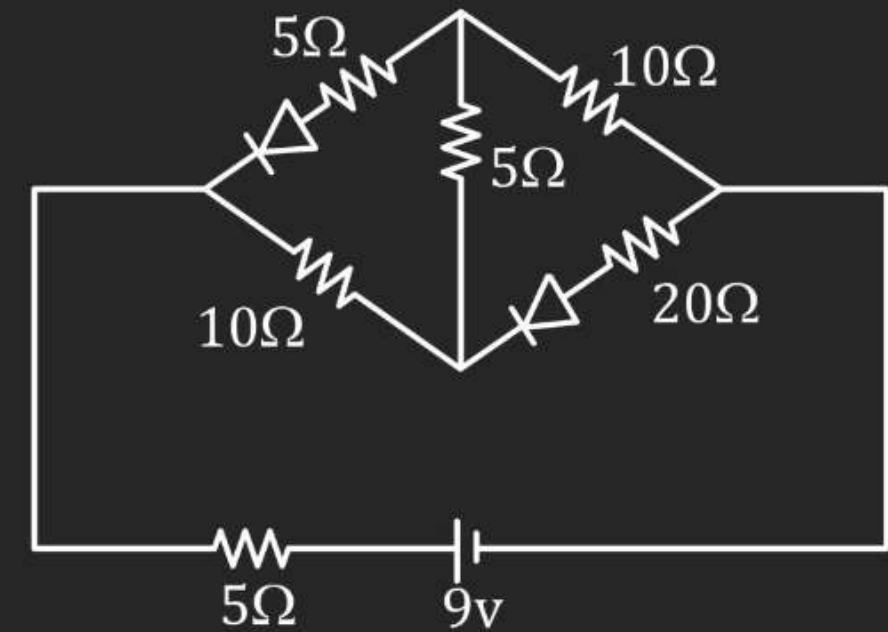


SEMICONDUCTOR & DIODE

Q.25 Two Zener diodes (A and B) having breakdown voltages of 6 V and 4 V respectively, are connected as shown in the circuit below. The output voltage V_0 variation with input voltage linearly increasing with time, is given





by $(V_{\text{input}} = 0 \text{ V at } t = 0)$

(figures are qualitative)

[JEE (Main)-2020]

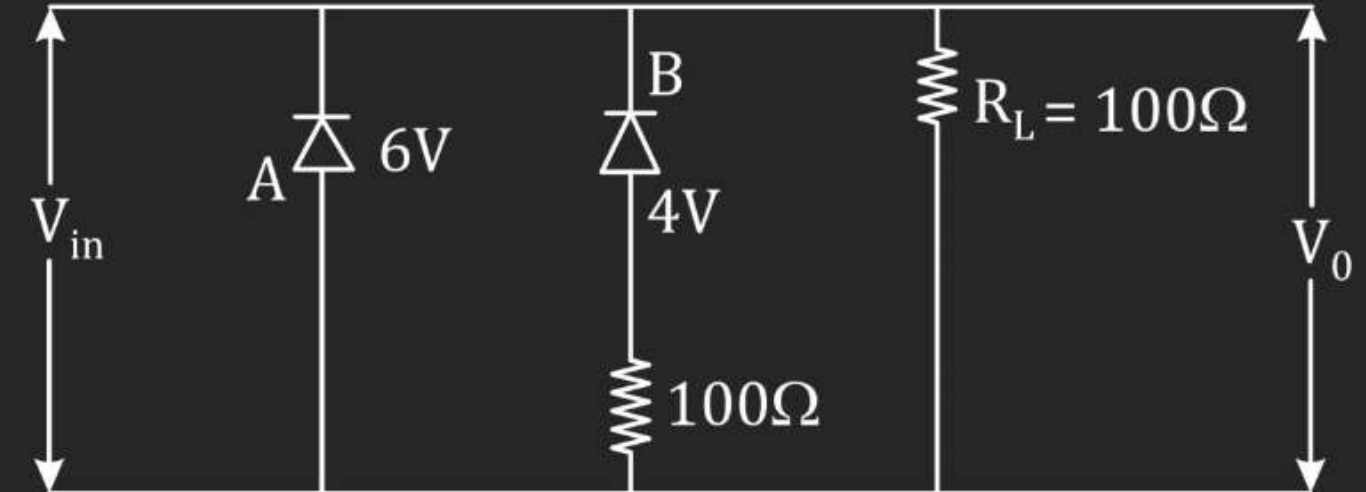


SEMICONDUCTOR & DIODE

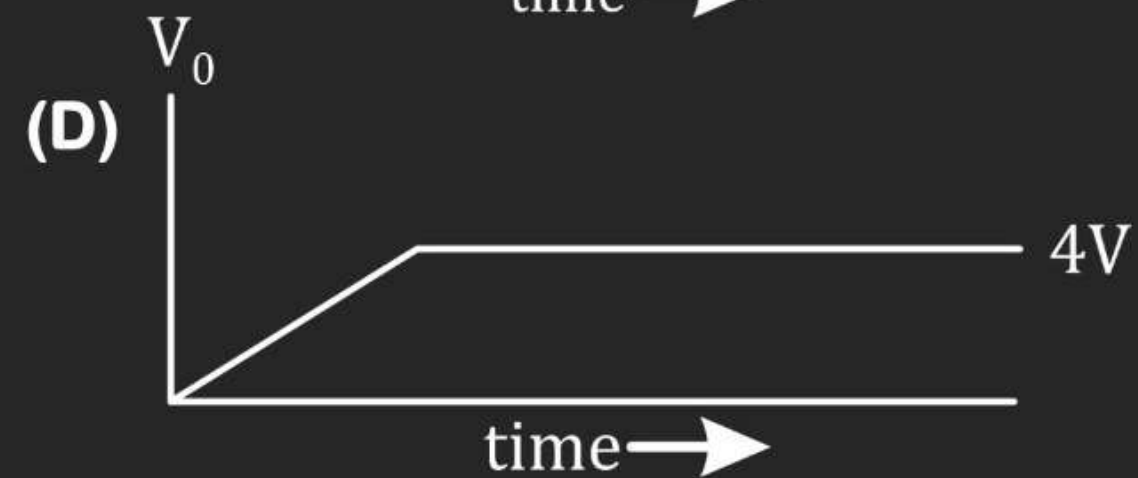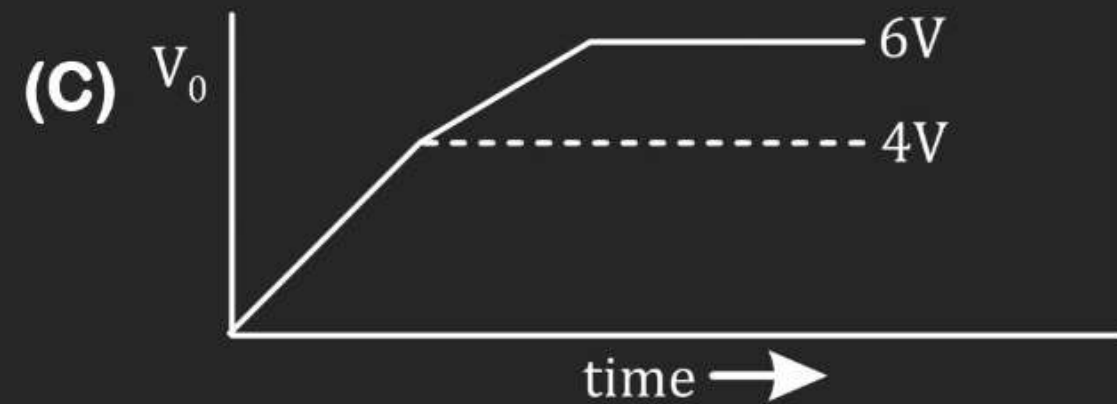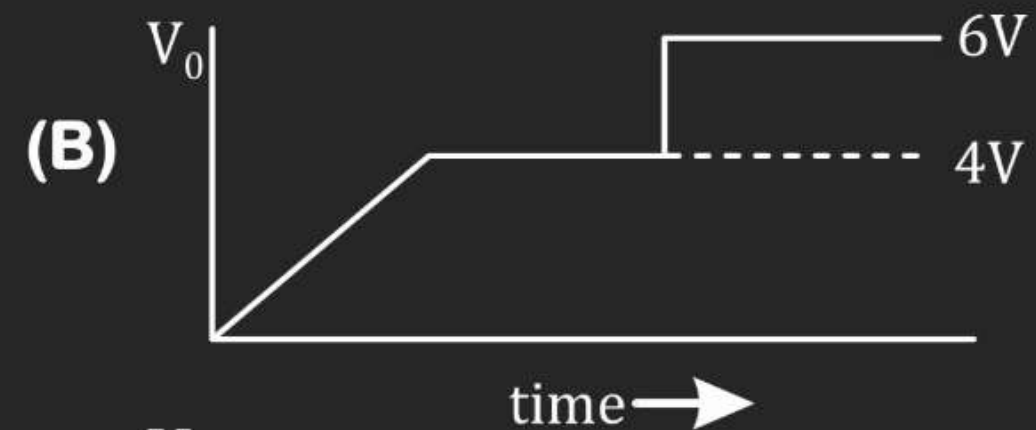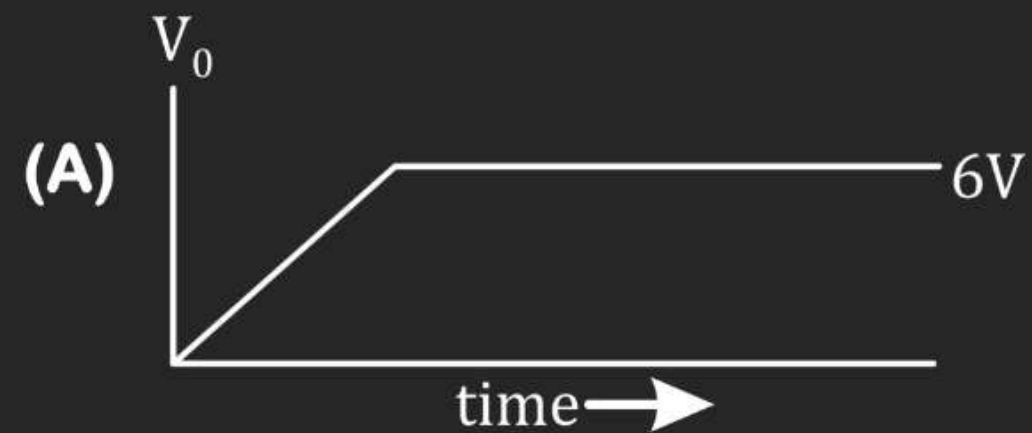

Q.26 A 5 V battery is connected across the points X and Y. Assume D_1 and D_2 to be normal silicon diodes. Find the current supplied by the battery if the +ve terminal of the battery is connected to point X.

[JEE (Main)-2021]

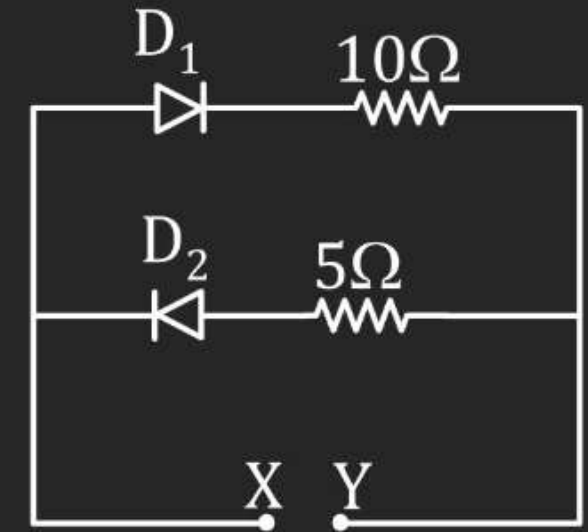- (A) -1.5 A
- (B) $\sim 0.5 \text{ A}$
- (C) $\sim 0.43 \text{ A}$
- (D) $\sim 0.86 \text{ A}$



Q.27 Take the breakdown voltage of the zener diode used in the given circuit as 6 V. For the input voltage shown in figure below, the time variation of the output voltage is (Graphs drawn are schematic and not to scale)

[JEE (Main)-2020]

