

Capacitive Ckt

CAPACITOR

Q.3 Find the charges on the three capacitors shown in figure (a).

K.V.L in the Close-loop ABCEFA

$$6 + 6 - \frac{q}{4} - \frac{q_1}{2} = 0$$

$$\frac{q}{4} + \frac{q_1}{2} = 12$$

$$-q + 2q_1 = 48 \quad \text{--- (i)}$$

K.V.L in the Closed loop ABEFA:

$$+6 + \frac{q - q_1}{5} - \frac{q_1}{2} = 0$$

$$60 + 2(q - q_1) - 5q_1 = 0$$

$$60 + 2q - 2q_1 - 5q_1 = 0$$


$$7q_1 - 2q = 60 \quad \text{--- (ii)}$$

$$\frac{2(i) + (ii)}{2q + 4q_1 = 96 \quad \text{--- (iv)}}$$

$$2q + 4q_1 = 96 \quad \text{--- (iv)}$$

$$11q_1 = 156 \Rightarrow q_1 = \frac{156}{11} \mu C \checkmark$$
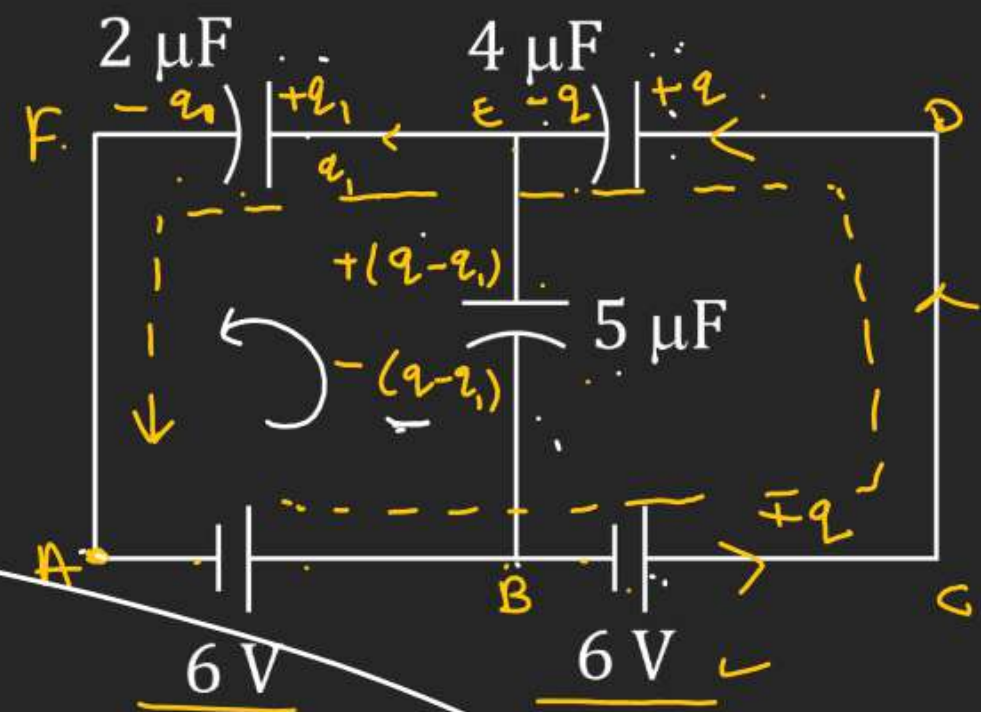
$$\begin{aligned} q &= 48 - 2q_1 \\ &= (48 - 2 \times 156) \\ &= 216 \frac{11}{11} \end{aligned}$$



Capacitive Ckt

CAPACITOR


Q.6 A circuit has a section AB shown in Fig. The emf of the source equals $\varepsilon = 10\text{ V}$, the capacitor capacitances are equal to $C_1 = 1.0\mu\text{F}$ and $C_2 = 20\mu\text{F}$, and the potential difference $V_A - V_B = 5.0\text{ V}$. Find the voltage across each capacitor.

$$V_A - \frac{q}{1} + 10 - \frac{q}{20} = V_B$$

$$(V_A - V_B) + 10 = \left(q + \frac{q}{20}\right)$$

$$15 = \frac{21q}{20}$$
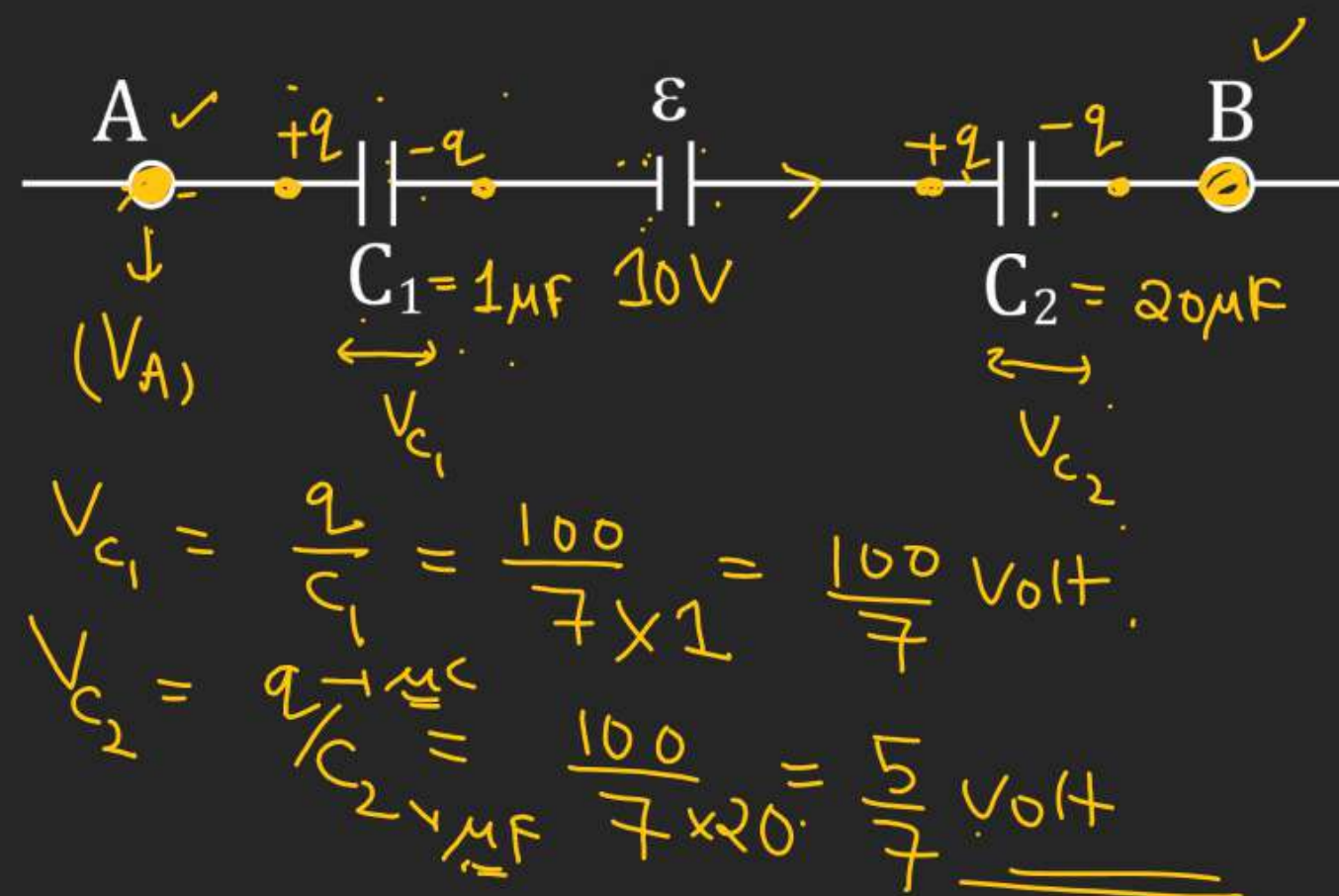
$$q = \left(\frac{15 \times 20}{21}\right) = \frac{100}{7} \mu\text{C}$$




Capacitive Ckt

CAPACITOR

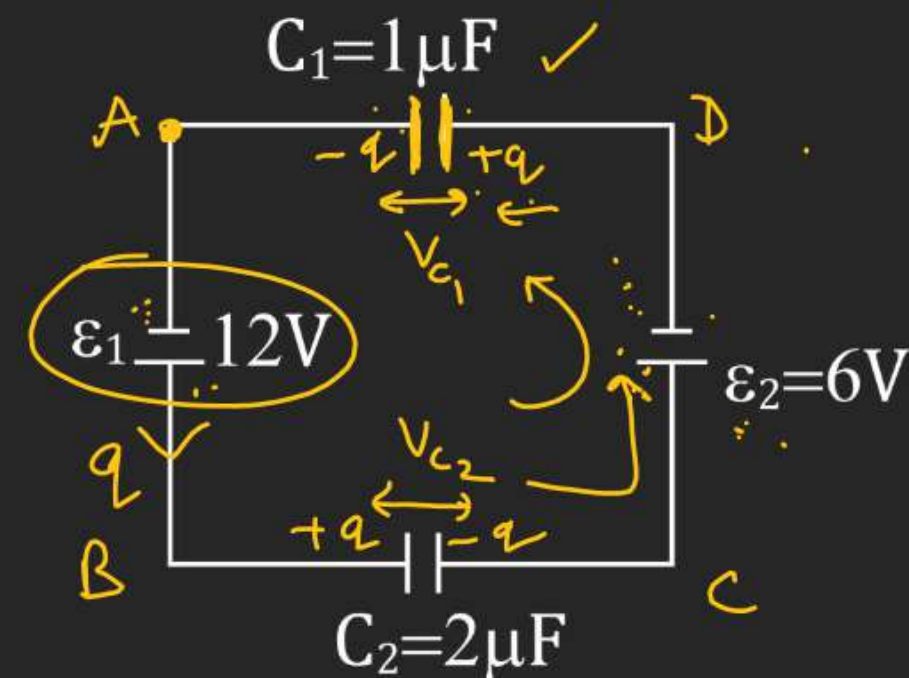Q.7 In a circuit shown in Fig. find the potential difference between the left and right plates of each capacitor.

K.V.L in closed loop.
ABCD A
 $12 - \frac{q}{2} - 6 - \frac{q}{1} = 0$
 $6 = (q + \frac{q}{2}) = \frac{3q}{2}$
 $q = \frac{12}{3} = 4\mu C$



$$V_{C_1} = \frac{4\mu C}{1\mu F} = 4 \text{ Volt}$$


$$V_{C_2} = \frac{q}{2} = \frac{4}{2} = 2 \text{ Volt}$$

Capacitive Ckt

CAPACITOR

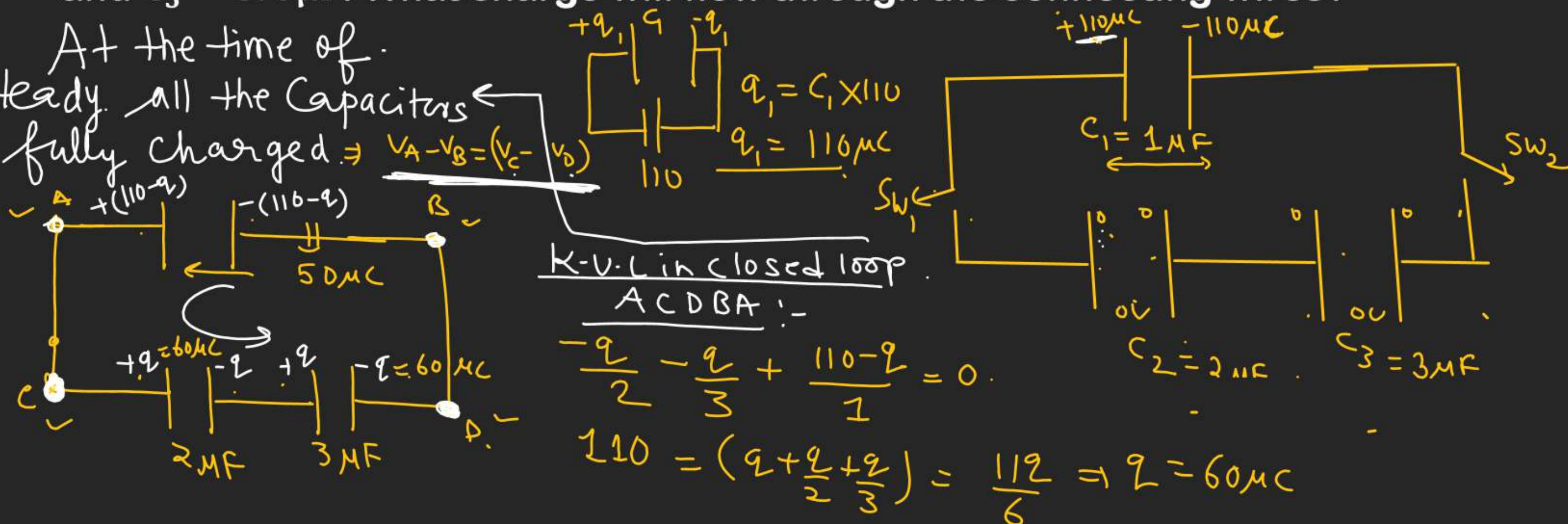Q.8 A capacitor of capacitance $C_1 = 1.0\mu\text{F}$ charged up to a voltage $V = 110\text{ V}$ is connected in parallel to the terminals of a circuit consisting of two uncharged capacitors connected in series and possessing the capacitances $C_2 = 2.0\mu\text{F}$ and $C_3 = 3.0\mu\text{F}$. What charge will flow through the connecting wires?

At the time of
Steady. all the Capacitors
fully charged $\Rightarrow V_A - V_B = (V_C - V_D)$



CAPACITOR

Heat dissipated after switching \rightarrow

$$\text{Heat Energy} = (U_f - U_i)$$


$$U_i = \frac{(110)^2 \times 10^{-12}}{2 \times 1 \times 10^{-6}} = \frac{(110)^2}{2} \mu\text{J} = \left(\frac{12100}{2}\right) \mu\text{J} = \underline{\underline{6050 \mu\text{J}}}$$

$$U_f = \left(\frac{(60)^2}{2 \times 2} + \frac{(60)^2}{3 \times 2} + \frac{(50)^2}{1 \times 2} \right) \mu\text{J} = \checkmark \Rightarrow \underline{\underline{\text{heat}}}$$

CAPACITOR

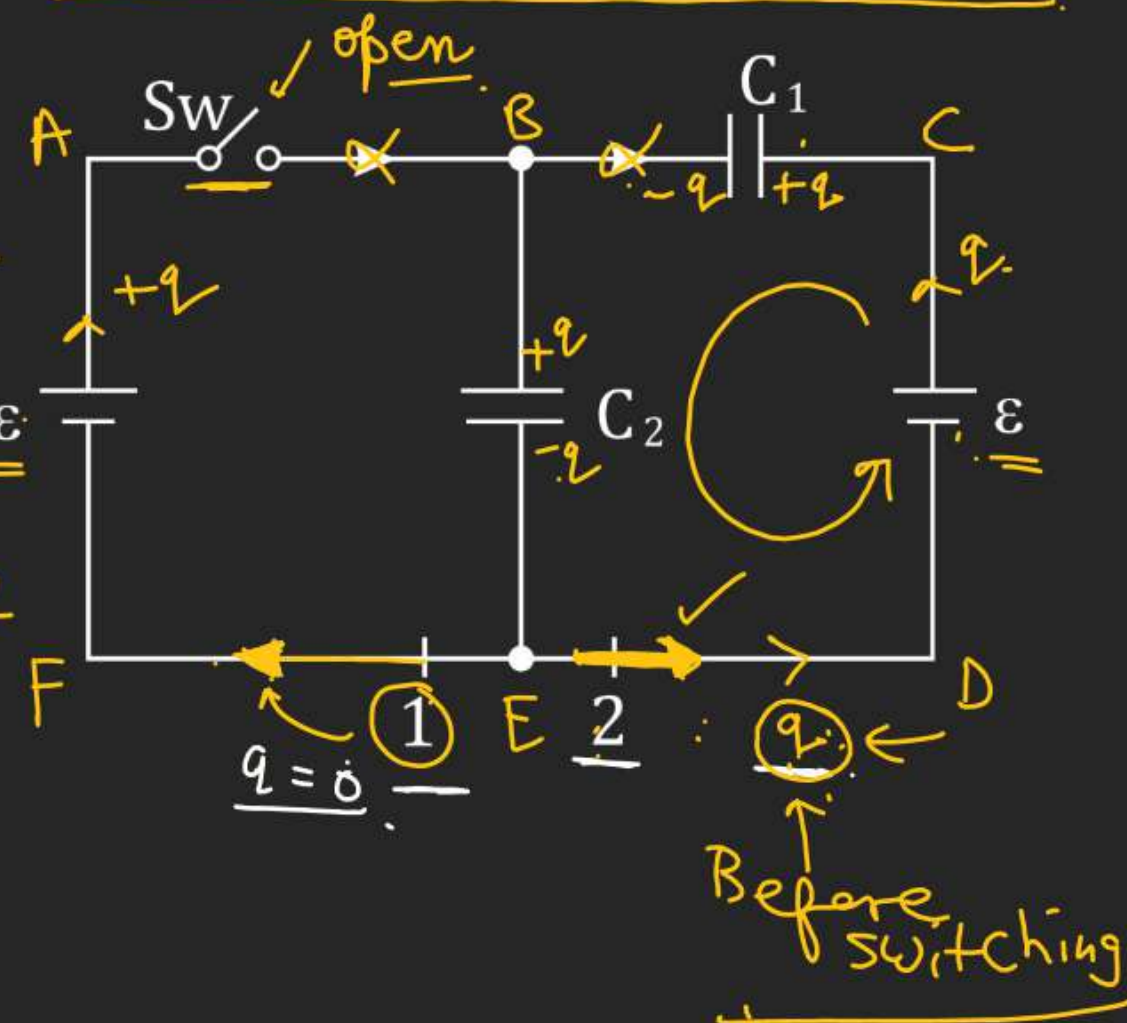Q.9 What charges will flow after the shorting of the switch S_w in the circuit illustrated in Fig. Through sections 1 and 2 in the directions indicated by the arrows?

⇒ Calculate Charges on the Capacitors before S_w is Closed. & after S_w is Closed. the difference in the Charge on the Capacitor flow through the wire



Capacitive Ckt

CAPACITOR

When SW - open

$$q = C_{eq} \cdot \mathcal{E}$$

$$q = \left(\frac{C_1 C_2}{C_1 + C_2} \right) \mathcal{E} \leftarrow$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

For branch-1


$$\text{Charge flow} = q_1 = (C_2 \mathcal{E})$$

For branch-2

$$\text{Charge flow} = (q_f) - (q_i)$$

$$= - (q_1 - q_2) - q$$

$$= 0 - q = - \frac{C_1 C_2 \mathcal{E}}{C_1 + C_2}$$

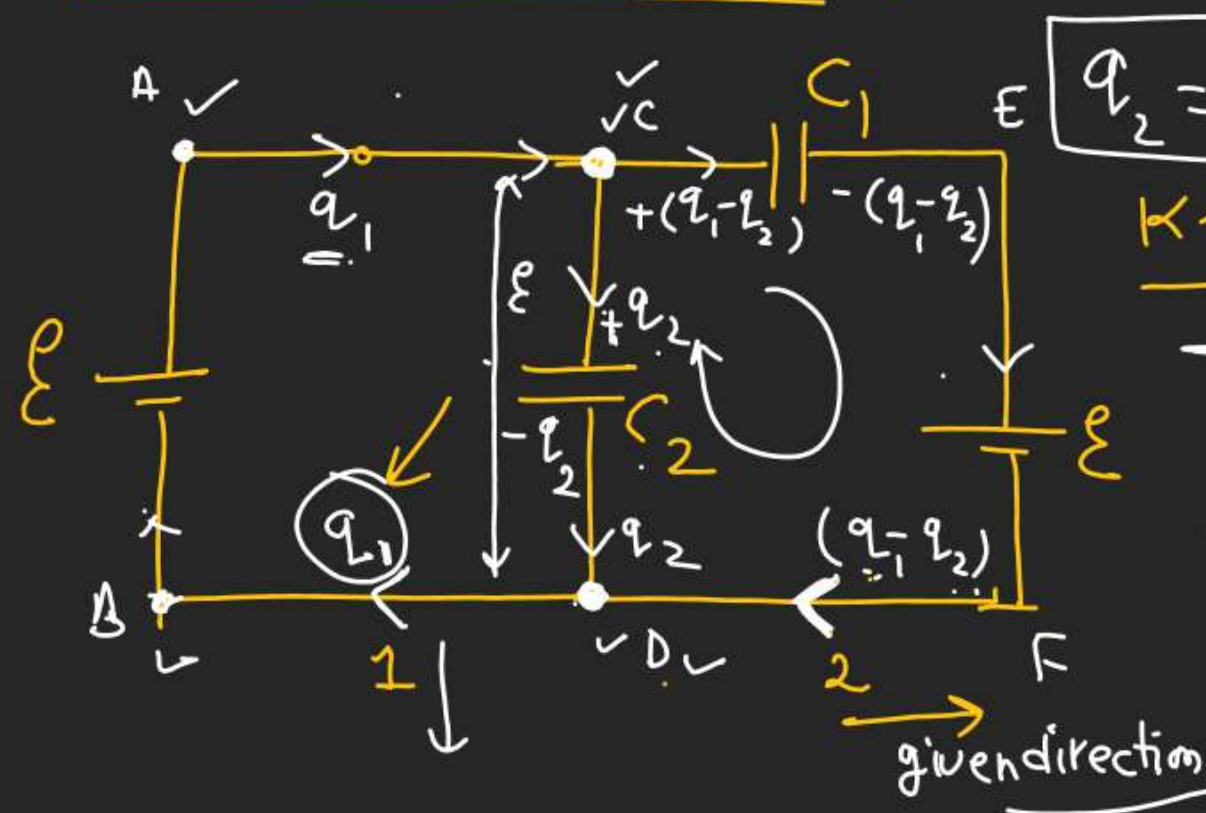When SW closed

$$q_2 = C_2 \mathcal{E} \checkmark$$

K.V.L in closed loop C E F D

$$- \left(\frac{q_1 - q_2}{C_1} \right) - \mathcal{E} + \frac{q_2}{C_2} = 0$$

$$- \frac{q_1}{C_1} + \frac{q_2}{C_1} + \frac{q_2}{C_2} = \mathcal{E}$$

$$- \frac{q_1}{C_1} + \frac{C_2 \mathcal{E}}{C_1} + \frac{\mathcal{E}}{2} = \mathcal{E}$$

$$q_1 = C_2 \mathcal{E}$$

(*) Concept of balance (wheat stone bridge) →

From ① & ②

$$\frac{C_1}{C_2} = \frac{C_3}{C_4} \quad (**)$$

(*) A wheat stone bridge is said to be balance when

($V_B = V_D$) i.e. charge on Capacitor C_5 is zero.

$$V_A - V_B = \frac{q_1}{C_1} \quad (V_B = V_D)$$


$$V_A - V_D = \frac{q_2}{C_2}$$

$$V_A - V_D = \frac{q_2}{C_2}$$

$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \quad \text{--- ①}$$

$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \quad \text{--- ①}$$
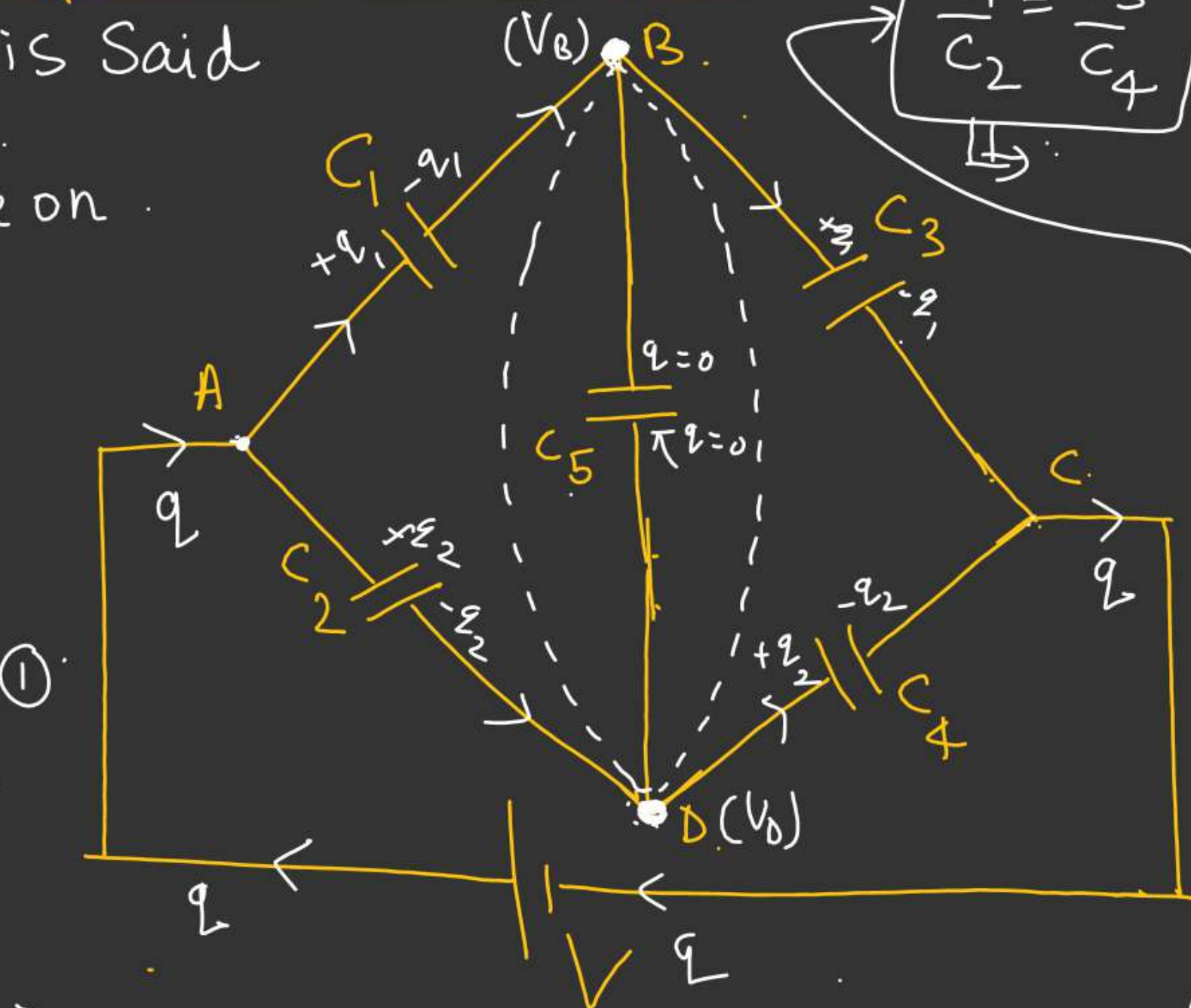
$$\frac{q_1}{C_1} = \frac{q_2}{C_2} \quad \text{--- ①}$$



Capacitive Ckt *H.W.*

CAPACITOR

Q.10 In the circuit shown in Fig. the emf of each battery is equal to $V = 60\text{ V}$, and the capacitor capacitances are equal to $C_1 = 20\mu\text{F}$ and $C_2 = 3.0\mu\text{F}$. Find the charges which will flow after the shorting of the switch S_w through the section 1, 2 and 3 in the directions indicated by the arrows.

